

# EECS 16B    Designing Information Devices and Systems II

## Spring 2021    Discussion Worksheet

# Discussion 1B

## 1 KVL/KCL Review

Kirchhoff's Circuit Laws are two important laws used for analyzing circuits. Kirchhoff's Current Law (KCL) says that the sum of all currents entering a node must equal 0. For example, in Figure 1, the sum of all currents entering node 1 is  $I_1 - I_2 - I_3 = 0$ . Assuming that  $I_1$  and  $I_3$  are known, we can easily obtain a solvable equation for  $V_x$  by applying Ohm's law:  $I_1 - \frac{V_x}{R_1} - I_3 = 0$ .

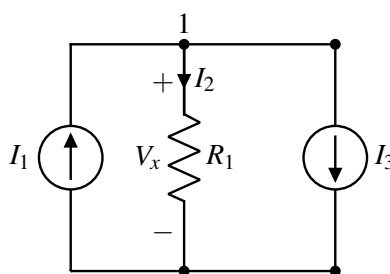


Figure 1: KCL Circuit

Kirchhoff's Voltage Law (KVL) states that the sum of all voltages in a circuit loop must equal 0. To apply KVL to the circuit shown in Figure 2, we can add up voltages in the loop in the counterclockwise direction, which yields  $-V_1 + V_x + V_y = 0$ . Using the relationships  $V_x = i \cdot R_1$  and  $i = I_1$ , we can solve for all unknowns in this circuit. You can use these two laws to solve any circuit that is planar and linear.

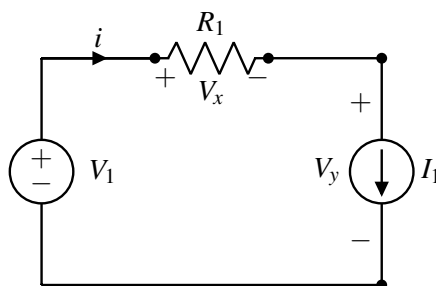


Figure 2: KVL Circuit

If you would like to review these concepts more in-depth, you can check out [the EECS16A Fall 2020 course notes](#).

## 2 Op-amp Review

Figure 3 shows the equivalent model of an op-amp. It is important to note that this is the general model of an op-amp, so our op-amp golden rules cannot be applied to this unless certain conditions are met.

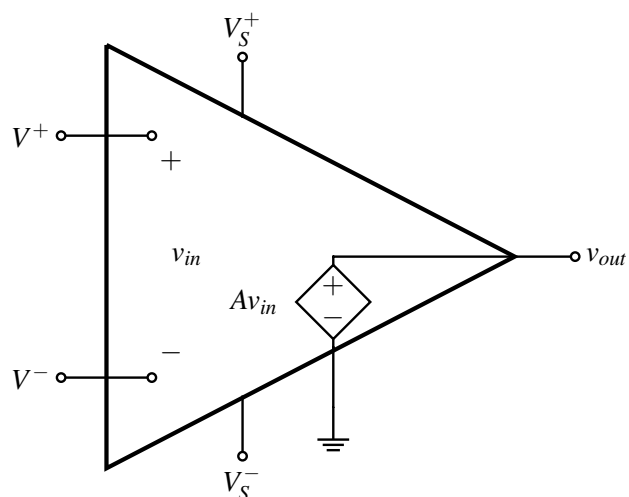


Figure 3: General Op-Amp Model

### Conditions Required for the Golden Rules:

- (a)  $R_{in} \rightarrow \infty$
- (b)  $R_{out} \rightarrow 0$
- (c)  $A \rightarrow \infty$
- (d) The op-amp must be operated in negative feedback.

When conditions (a)-(c) are met, the op-amp is considered ideal. Figure 4 shows an ideal op-amp in negative feedback, which can be analyzed using the Golden Rules.

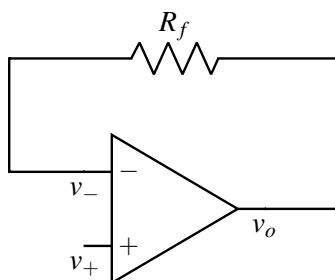


Figure 4: Ideal Op-Amp in Negative Feedback

### Golden Rules of ideal op-amps in negative feedback:

- (a) No current can flow into the input terminals ( $I_- = 0$  and  $I_+ = 0$ ). (This property follows from condition (a) and does not require negative feedback.)
- (b) The (+) and (-) terminals are at the same voltage ( $V_+ = V_-$ ).

If you would like to review these concepts more in-depth, you can check out [op-amp introduction](#) and [op-amp negative feedback](#) from the EECS16A course notes.

## 1. KVL/KCL Review

Use Kirchhoff's Laws on the circuit below to find  $V_x$  in terms of  $V_{in}, R_1, R_2, R_3$ .

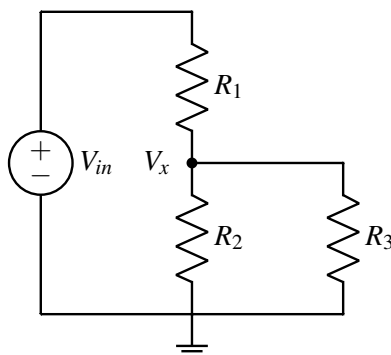


Figure 5: Example Circuit

- (a) What is  $V_x$ ?
- (b) As  $R_3 \rightarrow \infty$ , what is  $V_x$ ? What is the name we used for this type of circuit?

## 2. Op-Amp Summer

Consider the following circuit (assume the op-amp is ideal):

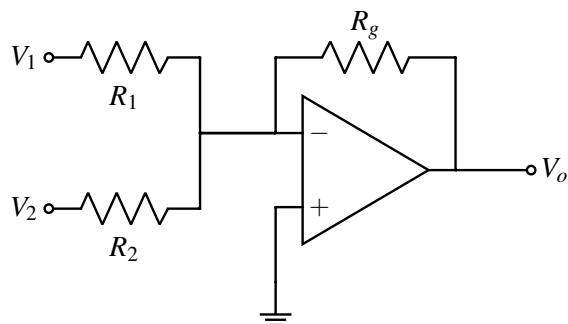


Figure 6: Op-amp Summer


What is the output  $V_o$  in terms of  $V_1$  and  $V_2$ ? You may assume that  $R_1, R_2$ , and  $R_g$  are known.

### 3. Current Sources And Capacitors (The following problem has been adapted from EECS16A Fall 20 Disc 9A.)

Recall charge has units of Coulombs (C), and capacitance is measured in Farads (F) =  $\frac{\text{Coulomb}}{\text{Volt}}$ .

It may also help to note metric prefix examples:  $3\mu\text{F} = 3 \times 10^{-6}\text{F}$ .

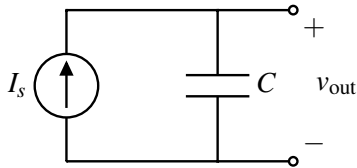
Given the circuit below, find an expression for  $v_{\text{out}}(t)$  in terms of  $I_s$ ,  $C$ ,  $V_0$ , and  $t$ , where  $V_0$  is the initial voltage across the capacitor at  $t = 0$ .



Then plot the function  $v_{\text{out}}(t)$  over time on the graph below for the following conditions detailed below. Use the values  $I_s = 1\text{mA}$  and  $C = 2\mu\text{F}$ .

- Capacitor is initially uncharged  $V_0 = 0$  at  $t = 0$ .
- Capacitor has been charged with  $V_0 = +1.5\text{V}$  at  $t = 0$ .
- Practice:** Swap this capacitor for one with half the capacitance  $C = 1\mu\text{F}$ , which is initially uncharged  $V_0 = 0$  at  $t = 0$ .

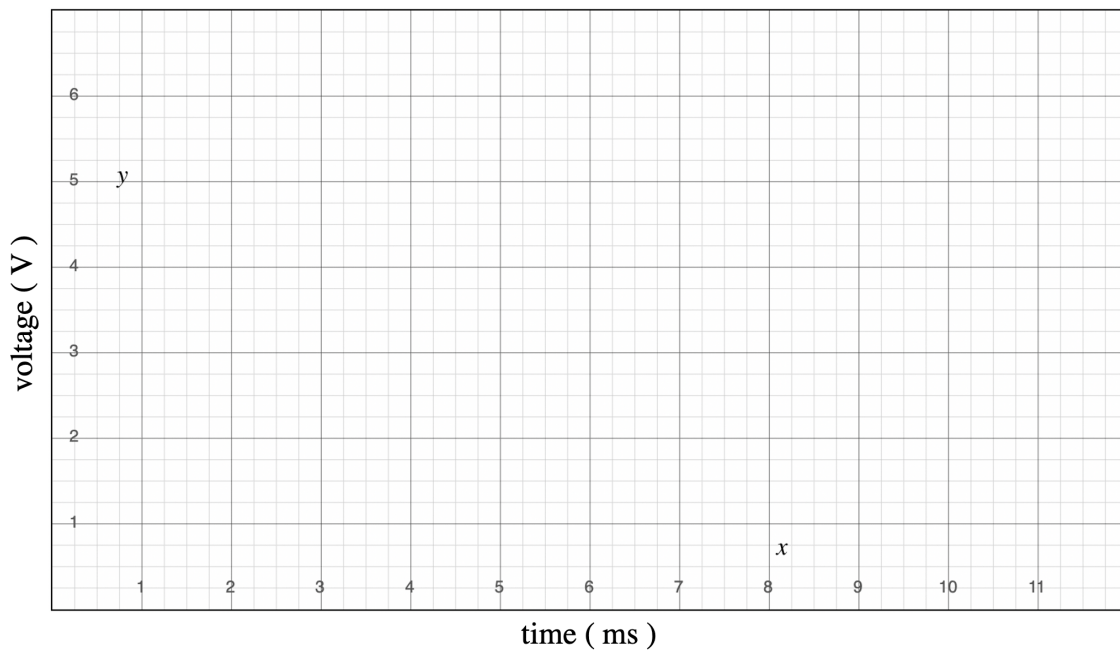HINT: Recall the calculus identity  $\int_a^b f'(x)dx = f(b) - f(a)$ , where  $f'(x) = \frac{df}{dx}$ .



#### 4. Linear Algebra Review

For the following matrices, find the following properties:

- i. What is the column space of the matrix?
- ii. What is the null space of the matrix?
- iii. What are the eigenvalues and corresponding eigenspaces for the matrix?

(a)  $\begin{bmatrix} 2 & 4 \\ 0 & 3 \end{bmatrix}$

(b)  $\begin{bmatrix} 1 & -2 \\ 2 & -4 \end{bmatrix}$

(c)  $\begin{bmatrix} 2 & 0 & 0 \\ 0 & 0.5 & 0.5 \\ 0 & 0.5 & 0.5 \end{bmatrix}$

For this matrix you are told that the eigenvalues are: 2, 1, and 0.