

# EECS 16B    Designing Information Devices and Systems II


## Fall 2021    Discussion Worksheet

# Discussion 1A

For this discussion, [Note 1](#) is helpful for background in transistors and RC circuits.

### 1. NAND Circuit

Let us consider a NAND logic gate. This circuit implements the boolean function  $\overline{(A \cdot B)}$ . The  $\cdot$  stands for the AND operation, and the  $\overline{\quad}$  stands for NOT; combining them, we get NAND!

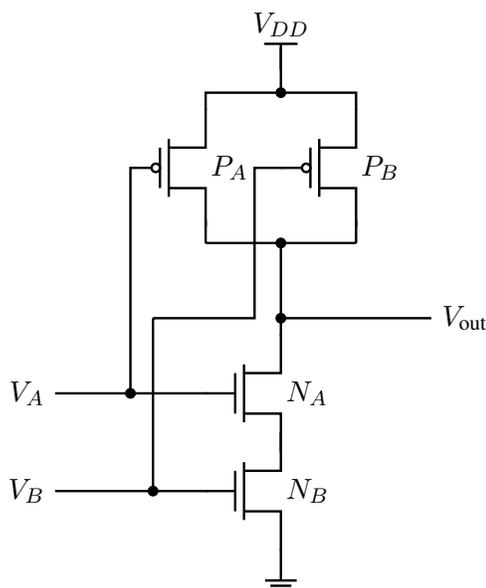

**Figure 1:** NAND gate transistor-level implementation.

$V_{tn}$  and  $V_{tp}$  are the threshold voltages for the NMOS and PMOS transistors, respectively. Assume that  $V_{DD} > V_{tn}$  and  $|V_{tp}| > 0$ .

- (a) Label the gate, source, and drain nodes for the NMOS and PMOS transistors above.

**Solution:** In an NMOS, the terminal at the higher potential is always the drain, and the terminal at the lower potential is always the source. Therefore, the drains are at the top of  $N_A$  (connected to  $V_{out}$ ) and the top of  $N_B$  (connected to  $N_A$ ). The sources are at the bottom of  $N_A$  (connected to  $N_B$ ) and the bottom of  $N_B$  (connected to ground). The gate terminal of  $N_A$  is connected to  $V_A$ ; the gate of  $N_B$  is connected to  $V_B$ .

In a PMOS, the terminal at the higher potential is always the source, and the terminal at the lower potential is always the drain. Therefore, the source is at the top of  $P_A$  and  $P_B$  (connected to  $V_{DD}$ ). The drain is at the bottom of  $P_A$  and  $P_B$  (connected to  $V_{out}$ ). The gate terminal of  $P_A$  is connected to  $V_A$ ; the gate of  $P_B$  is connected to  $V_B$ .

- (b) If  $V_A = V_{DD}$  and  $V_B = V_{DD}$ , which transistors act like open switches? Which transistors act like closed switches? What is  $V_{out}$ ?

**Solution:**  $P_A$  and  $P_B$  are off (open switches).  $N_B$  and  $N_A$  are on (closed switches).  $V_{\text{out}} = 0V$  because it is connected to ground through a closed circuit consisting of  $P_A$  and  $P_B$  (and detached from  $V_{DD}$ ).

(c) If  $V_A = 0V$  and  $V_B = V_{DD}$ , what is  $V_{\text{out}}$ ?

**Solution:**  $P_B$  and  $N_A$  are off (open switches).  $P_A$  and  $N_B$  are on (closed switches).  $V_{\text{out}} = V_{DD}$  because it is connected to  $V_{DD}$  through a closed circuit consisting of  $P_A$  (and detached from ground, since *both*  $N_A$  and  $N_B$  must be closed for  $V_{\text{out}}$  to be connected to ground).

(d) If  $V_A = V_{DD}$  and  $V_B = 0V$ , what is  $V_{\text{out}}$ ?

**Solution:**  $P_A$  and  $N_B$  are off (open switches).  $P_B$  and  $N_A$  are on (closed switches). But, since  $N_B$  is open,  $N_A$  being closed doesn't connect  $V_{\text{out}}$  to ground. So,  $V_{\text{out}} = V_{DD}$  because it is connected to  $V_{DD}$  through a closed switch.

Note that with the simplest transistor model, one cannot determine  $V_{GS}$  for  $N_A$ , since we don't know the source voltage for that transistor.  $V_{\text{out}}$  is still high, because regardless of whether  $N_A$  is on, there is an open (or very high resistance) between  $V_{\text{out}}$  and ground while there is a short to  $V_{DD}$ .

(e) If  $V_A = 0V$  and  $V_B = 0V$ , what is  $V_{\text{out}}$ ?

**Solution:**  $N_B$  is off, creating an open circuit.  $P_A$  and  $P_B$  are on, creating a closed circuit.  $V_{\text{out}} = V_{DD}$  because it is connected by closed circuit to  $V_{DD}$ .

Like above, the source of  $N_A$  has an ambiguous value and we cannot determine whether  $N_A$  is on or off. However, this doesn't affect the output because the path to ground is an open (since  $N_B$  is definitely off,  $V_{GS,N_A} = 0 \leq V_{tn}$ ).

(f) Write out the truth table for this circuit.

$V_A$	$V_B$	$V_{\text{out}}$
0	0	
0	$V_{DD}$	
$V_{DD}$	0	
$V_{DD}$	$V_{DD}$	

**Solution:**

$V_A$	$V_B$	$V_{\text{out}}$
0	0	$V_{DD}$
0	$V_{DD}$	$V_{DD}$
$V_{DD}$	0	$V_{DD}$
$V_{DD}$	$V_{DD}$	0

## 2. RC Circuits - Part I

In this problem, we will find the voltage across a capacitor over time in an RC circuit. In this part, we set up our problem by first defining four functions over time:  $I(t)$  is the current at time  $t$ ,  $V(t)$  is the voltage across the circuit at time  $t$ ,  $V_R(t)$  is the voltage across the resistor at time  $t$ , and  $V_C(t)$  is the voltage across the capacitor at time  $t$ .

Recall from 16A that the voltage across a resistor is defined as  $V_R = RI_R$  where  $I_R$  is the current across the resistor. Also, recall that the voltage across a capacitor is defined as  $V_C = \frac{Q}{C}$  where  $Q$  is the charge across the capacitor.

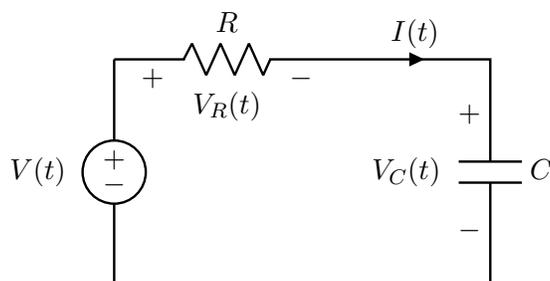


Figure 2: Example Circuit

- (a) First, find an equation that relates the current across the capacitor  $I(t)$  with the voltage across the capacitor  $V_C(t)$ .

**Solution:** We start from the  $Q$ - $V$  relationship of the capacitor:

$$Q(t) = CV_C(t).$$

Differentiating  $V_C(t) = \frac{Q(t)}{C}$  in terms of  $t$ , we get

$$\frac{dV_C(t)}{dt} = \frac{dQ(t)}{dt} \frac{1}{C}.$$

By definition, the change in charge is the current across the capacitor, so

$$\frac{d}{dt} V_C(t) = I(t) \frac{1}{C} \quad (1)$$

- (b) Write a system of equations that relates the functions  $I(t)$ ,  $V_C(t)$ , and  $V(t)$ .

**Solution:** From KCL, we have

$$\begin{aligned} \frac{V(t) - V_C(t)}{R} - I(t) &= 0 \\ RI(t) + V_C(t) &= V(t) \end{aligned} \quad (2)$$

- (c) So far, we have two relations between  $I(t)$  and  $V_C(t)$ . To solve this system of equations, we can remove  $I(t)$  from the equation using what we found in part (a). Rewrite the previous equation in part (b) in the form of a differential equation.

**Solution:**

From part (a), we have

$$I(t) = \frac{dV_C(t)}{dt} C$$

Substituting this into Equation 2 gives us

$$RC \frac{dV_C(t)}{dt} + V_C(t) = V(t)$$

### Contributors:

- Kumar Krishna Agrawal.
- Lev Tauz.
- Varun Mishra.
- Regina Eckert.