

Homework 4

This homework is due on Friday, September 23, 2022 at 11:59PM. Self-grades and HW Resubmissions are due the following Friday, September 30, 2022 at 11:59PM.

1. Hambley P5.46

Find the phasors for the voltage and the currents of the circuit shown in Figure 1. Construct a phasor diagram showing I_s , V , I_R , and I_L . What is the phase relationship between V and I_s ?

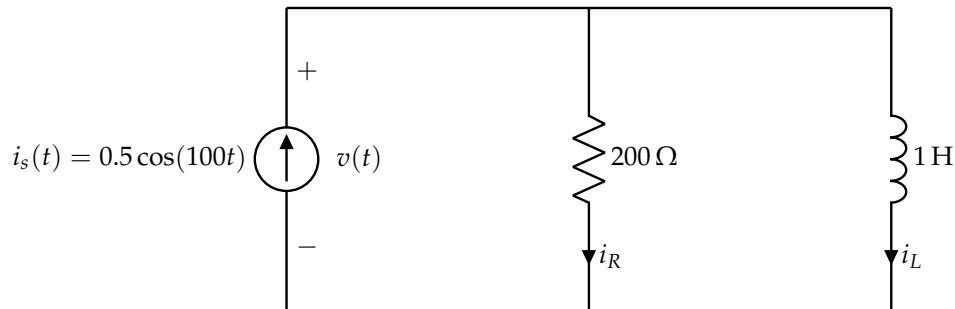


Figure 1: P5.46

Solution: We have that $I_s = 0.5\angle 0^\circ$. The impedance of the resistor is 200 and the impedance of the inductor is $j100$. Hence, the combined, equivalent impedance is $\frac{1}{\frac{1}{200} - \frac{j}{100}}$. The angle is $-\arctan\left(\frac{-\frac{1}{100}}{\frac{1}{200}}\right) = 63.44^\circ$ and the magnitude is $\frac{1}{\sqrt{(\frac{1}{200})^2 + (\frac{1}{100})^2}} = 89.44$. Hence,

$$V = I_s \frac{1}{\frac{1}{200} - \frac{j}{100}} = 44.72\angle 63.44^\circ \quad (1)$$

Using Ohm's law, we have


$$I_R = \frac{V}{R} = 0.2236\angle 63.44^\circ \quad (2)$$

and

$$I_L = \frac{V}{j\omega L} \quad (3)$$

$$= 0.4472\angle(63.44 - 90)^\circ = 0.4472\angle -26.56^\circ \quad (4)$$

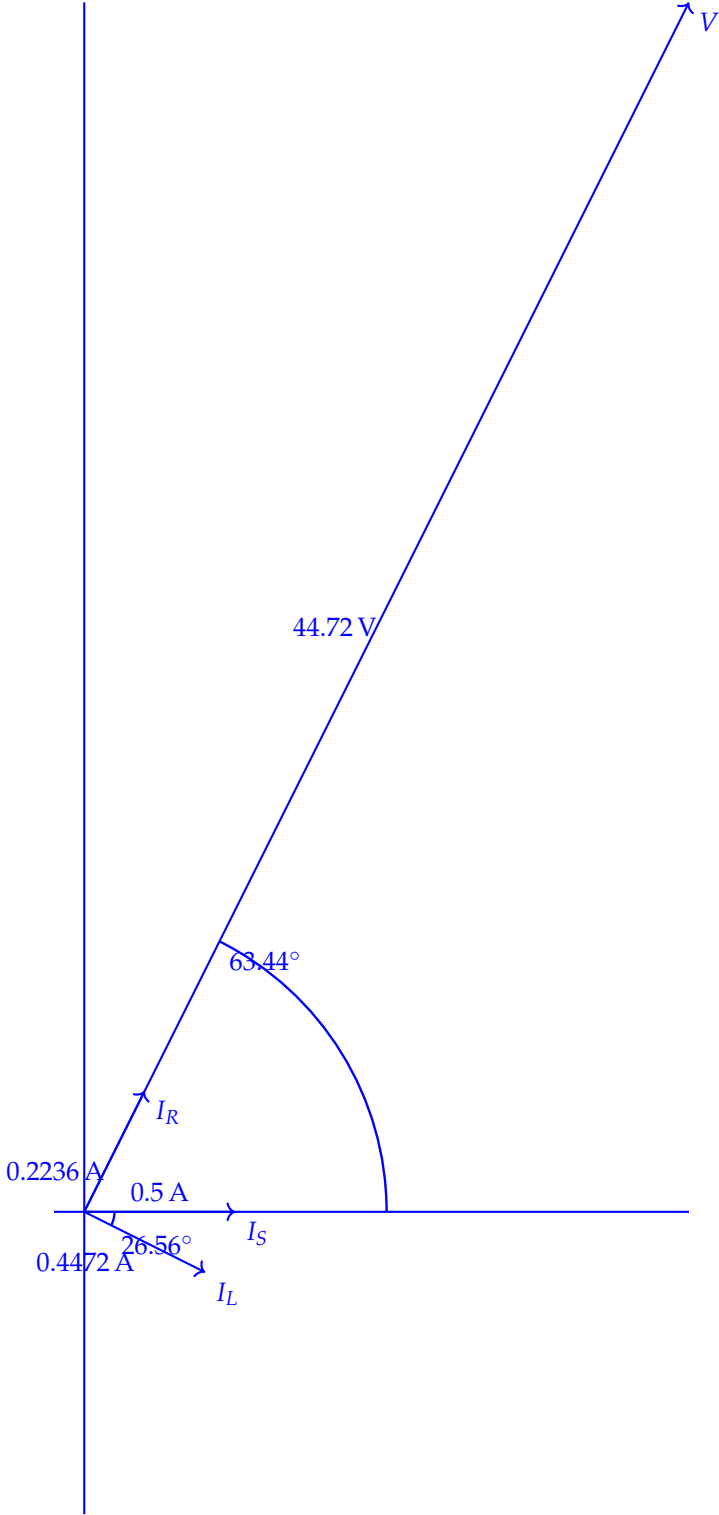Hence, V leads I_s by 63.44° . A phase diagram is shown below:



2. Hambley P5.65

Consider a load that has an impedance given by $Z = 100 - j50\Omega$. The current flowing through the load is $I = 15\sqrt{2}\angle 30^\circ\text{A}$. Is the load inductive or capacitive? Determine the power factor, power, reactive power, and apparent power delivered to the load.

Solution: This is a capacitive load because the reactance (imaginary part of the impedance) is negative. The RMS current is $I_{\text{RMS}} = \frac{I}{\sqrt{2}} = 15$. The power is

$$P = I_{\text{RMS}}^2 R = (15^2)(100) = 22.5 \text{ kW} \quad (5)$$

and the reactive power is

$$Q = I_{\text{RMS}}^2 X = (15^2)(-50) = -11.25 \text{ kV A} \quad (6)$$

The angle between the two is $\theta = \arctan\left(\frac{Q}{P}\right) = -26.57^\circ$, so the power factor is $\cos(\theta) = 89.44\%$ and the apparent power is $\sqrt{P^2 + Q^2} = 25.16 \text{ kV A}$

3. Hambley P5.83

(a) Find the Thevenin and Norton equivalent circuits for the circuit shown in Figure 2.



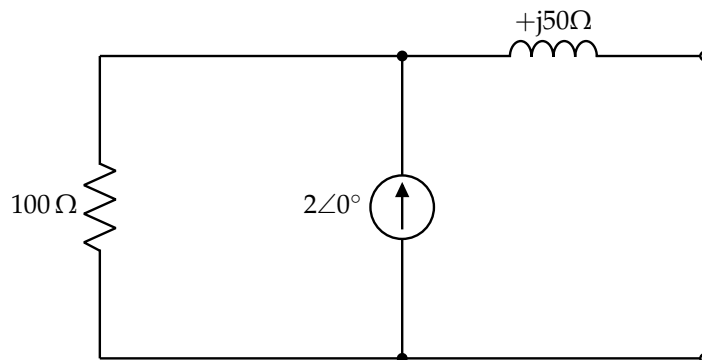



Figure 2: P5.83

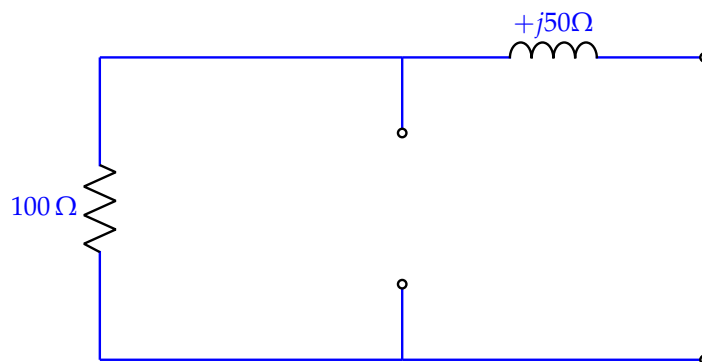Solution: Zeroing the current source, we have



Thus, the Thevenin impedance is $Z_t = 100 + j50 = 111.8\angle 26.57^\circ$. Under open circuit conditions, there is zero voltage across the inductance, since the current flows through the resistance. Hence, the Thevenin voltage is $V_t = (2\angle 0^\circ)(100) = 200\angle 0^\circ$. From this, the Norton current is $I_n = \frac{V_t}{Z_t} = 1.789\angle -26.57^\circ$. The Thevenin and Norton equivalent circuits are shown below respectively:

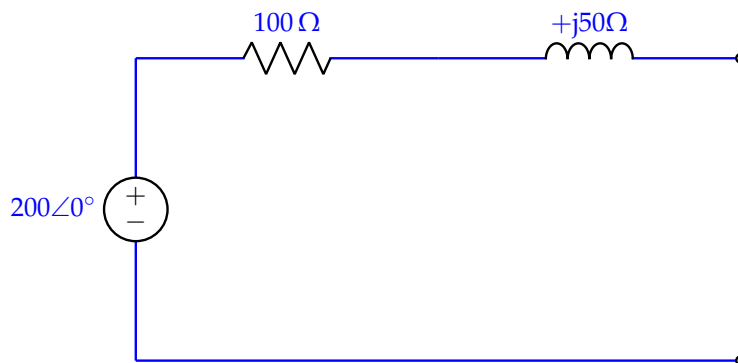

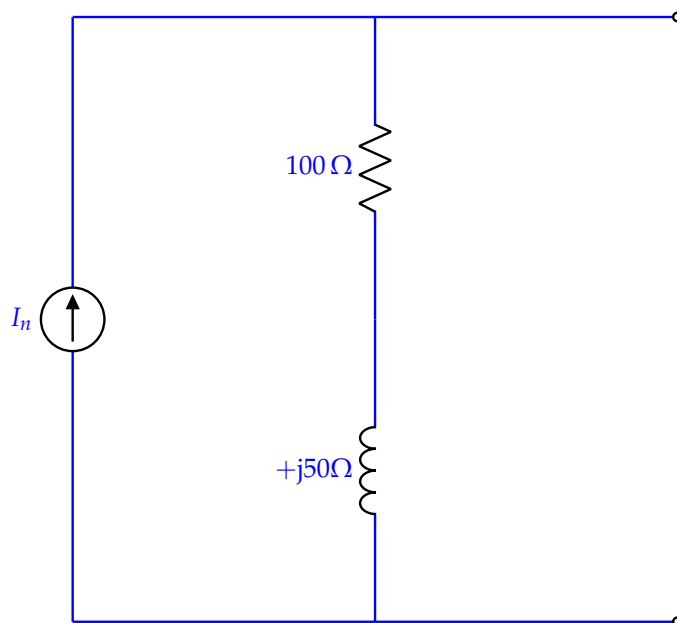

- (b) Find the maximum power that this circuit can deliver to a load if the load can have any complex impedance.

Solution: The load that would maximize power is $Z_{\text{load}} = (Z_t)^* = 100 - j50$. Using the Thevenin equivalent circuit, the current in this circuit would then be

$$I_{\text{load}} = \frac{V_t}{Z_t + Z_{\text{load}}} = \frac{200}{100 + j50 + 100 - j50} = 1 \quad (7)$$

so $I_{\text{load-RMS}} = \frac{1}{\sqrt{2}}$. Finally, the power would be $P_{\text{load}} = R_{\text{load}}(I_{\text{load-RMS}})^2 = 100\left(\frac{1}{\sqrt{2}}\right)^2 = 50\ \text{W}$.

- (c) Repeat the previous part, but this time the load is purely resistive.

Solution: The purely resistive load that would maximize power is $Z_{\text{load}} = |Z_t| = 111.8$. Again, using the Thevenin equivalent circuit, we find that

$$I_{\text{load}} = \frac{V_t}{Z_t + Z_{\text{load}}} = \frac{200}{100 + j50 + 111.8} = 0.9190 \angle -13.28^\circ \quad (8)$$

so $I_{\text{load-RMS}} = \frac{0.9190}{\sqrt{2}}$. Finally, the power would be $P_{\text{load}} = R_{\text{load}}(I_{\text{load-RMS}})^2 = 100\left(\frac{0.9190}{\sqrt{2}}\right)^2 = 47.21\ \text{W}$.

4. Hambley P6.27

The input signal of a first-order lowpass filter with the transfer function given by Equation 6.9 on page 288 of the text and a half-power frequency of 400 Hz is

$$v_{\text{in}}(t) = 1 + 2 \cos(800\pi t + 30^\circ) + 3 \cos(20 \times 10^3 \pi t) \quad (9)$$

Find an expression for the output voltage.

Solution: The transfer function is given by Equation 6.9 in the text:

$$H(f) = \frac{1}{1 + j \frac{f}{f_B}} \quad (10)$$

The given input signal is

$$v_{\text{in}}(t) = 1 + 2 \cos(800\pi t + 30^\circ) + 3 \cos(20 \times 10^3 \pi t) \quad (11)$$

which has components with frequencies of 0, 400, and 10000 Hz. Evaluating the transfer function for these frequencies yields

$$H(0) = \frac{1}{1 + j \frac{0}{400}} = 1 \quad (12)$$

$$H(400) = 0.7071 \angle -45^\circ \quad (13)$$

$$H(10 \times 10^3) = 0.04 \angle -87.71^\circ \quad (14)$$

Applying the appropriate value of the transfer function to each component of the input signal yields the output:

$$v_{\text{out}}(t) = 1 + 1.4142 \cos(800\pi t - 15^\circ) + 0.12 \cos(20 \times 10^3 \pi t - 87.71^\circ) \quad (15)$$

5. Hambley P6.30

Sketch the magnitude of the transfer function $H(f) = \frac{V_{\text{out}}}{V_{\text{in}}}$ to scale versus frequency for the circuit shown in Figure 3. What is the value of the half-power frequency? (HINT: Start by finding the Thevenin equivalent circuit seen by the capacitance.)


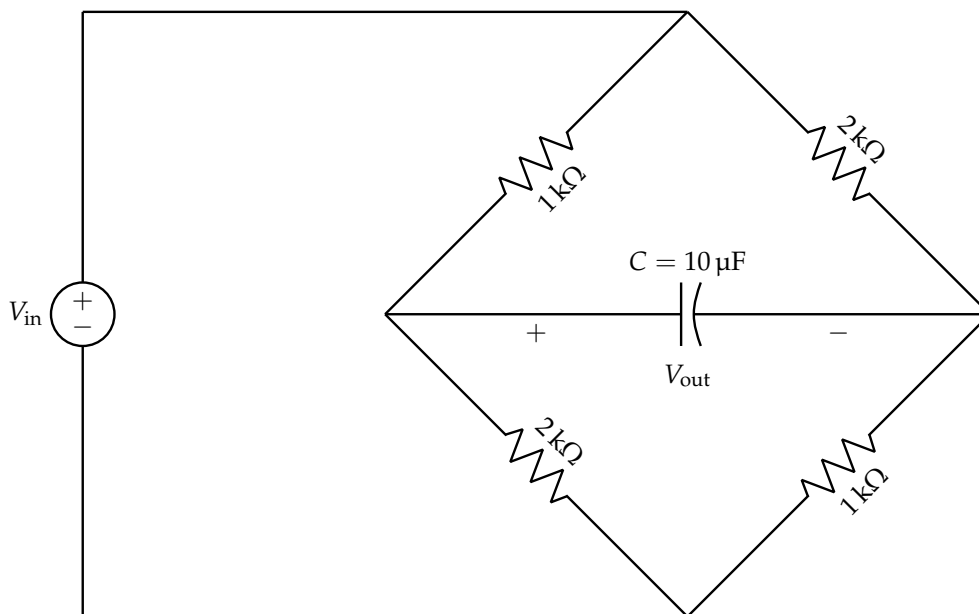


Figure 3: P6.30

Solution:

The circuit seen by the capacitance is

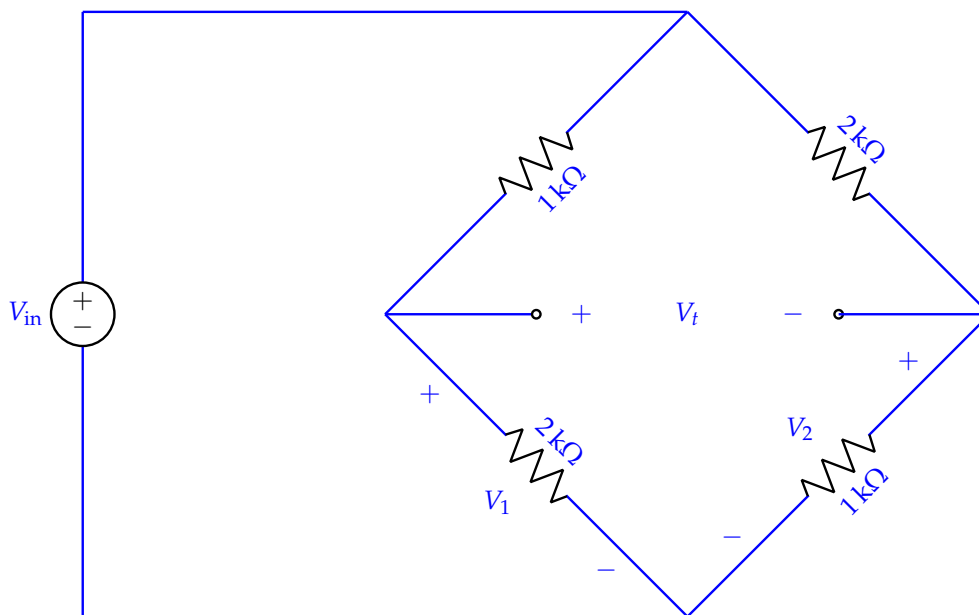


The open-circuit or Thevenin voltage is

$$V_t = V_1 - V_2 \quad (16)$$

$$= V_{in} \frac{2000}{2000 + 1000} - V_{in} \frac{1000}{1000 + 2000} \quad (17)$$

$$= \frac{1}{3} V_{in} \quad (18)$$

Zeroing the source, we have

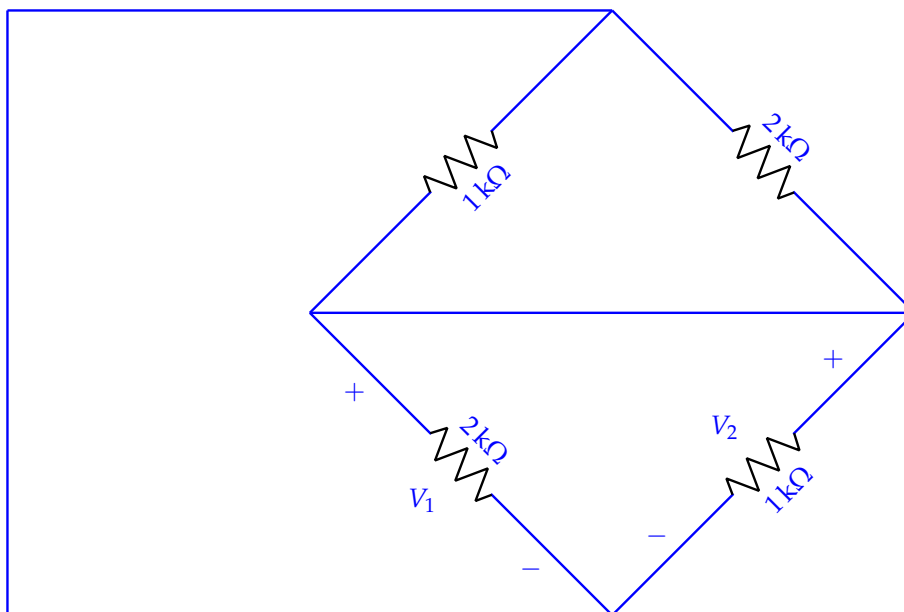


The Thevenin resistance is

$$R_t = \frac{1}{\frac{1}{1000} + \frac{1}{2000}} + \frac{1}{\frac{1}{2000} + \frac{1}{1000}} \quad (19)$$

$$= 1333 \Omega \quad (20)$$

Thus, the equivalent circuit is

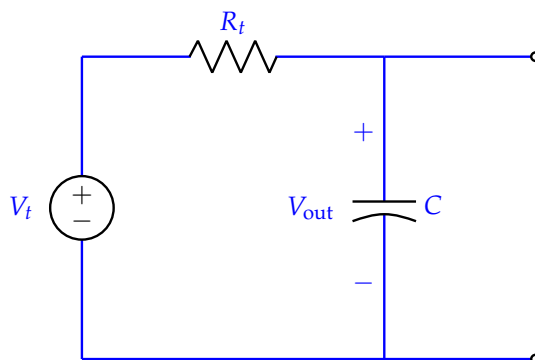


As in the text, this circuit has the transfer function

$$\frac{V_{out}}{V_t} = \frac{1}{1 + j\frac{f}{f_B}} \quad (21)$$

where $f_B = \frac{1}{2\pi R_t C} = \frac{1}{2\pi(1333)\times 10^{-5}} = 11.94 \text{ Hz}$. Using eq. (18) to substitute for V_t in eq. (21) and rearranging, we have

$$\frac{V_{\text{out}}}{V_t} = \frac{\frac{1}{3}}{1 + j\frac{f}{f_B}} \quad (22)$$

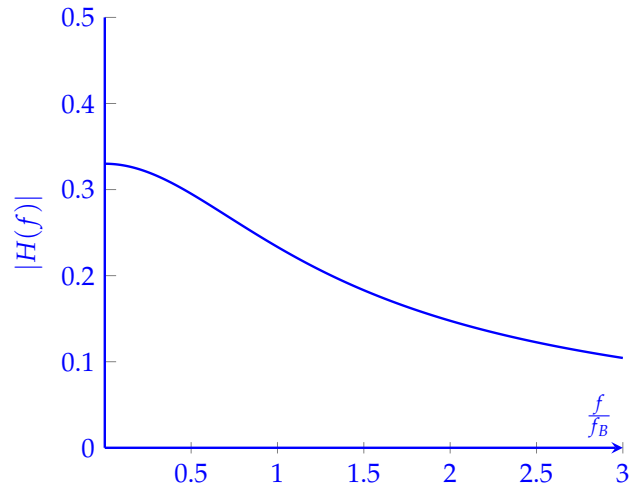A sketch of the transfer function magnitude is shown below:



6. Hambley P6.33

Consider the circuit shown in Figure 4. This circuit consists of a source having an internal resistance of R_s , an RC lowpass filter, and a load resistance of R_l .

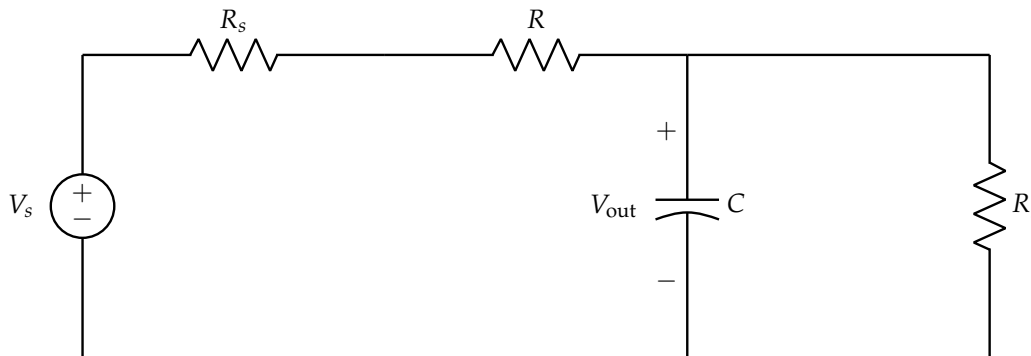


Figure 4: P6.33(a)

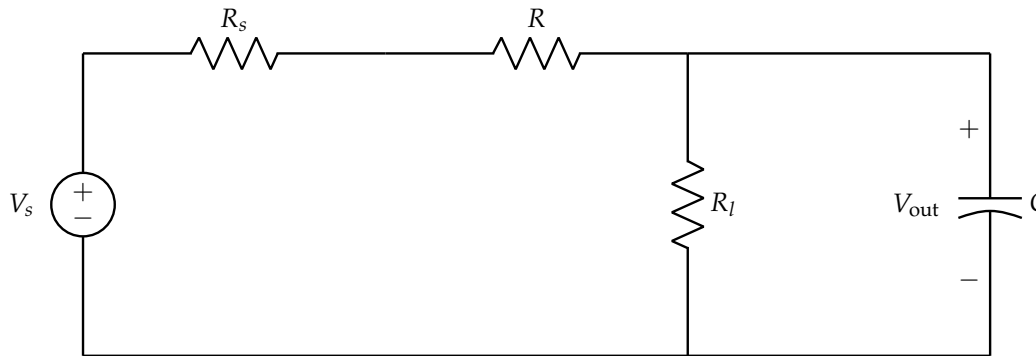



Figure 5: P6.33(b)

(a) Show that the transfer function of this circuit is given by

$$H(f) = \frac{V_{\text{out}}}{V_s} = \frac{R_l}{R_s + R + R_l} \times \frac{1}{1 + j \frac{f}{f_B}} \quad (23)$$

in which the half-power frequency f_B is given by $f_B = \frac{1}{2\pi R_t C}$ where $R_t = \frac{R_l(R_s+R)}{R_l+R_s+R}$. Notice that R_t is the parallel combination of R_l and $(R_s + R)$. (HINT: One way to make this problem easier is to rearrange the circuit as shown in Figure 5 and then to find the Thevenin equivalent for the source and resistances.)

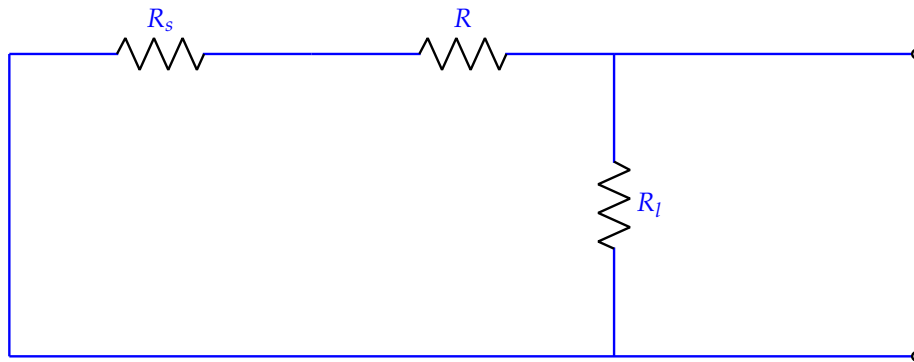Solution: First, we find the Thevenin equivalent for the source and resistances.




The open-circuit voltage is given by

$$v_t(t) = v_s(t) \frac{R_l}{R_s + R + R_l} \quad (24)$$

In terms of phasors, this becomes


$$V_t = V_s \frac{R_l}{R_s + R + R_l} \quad (25)$$

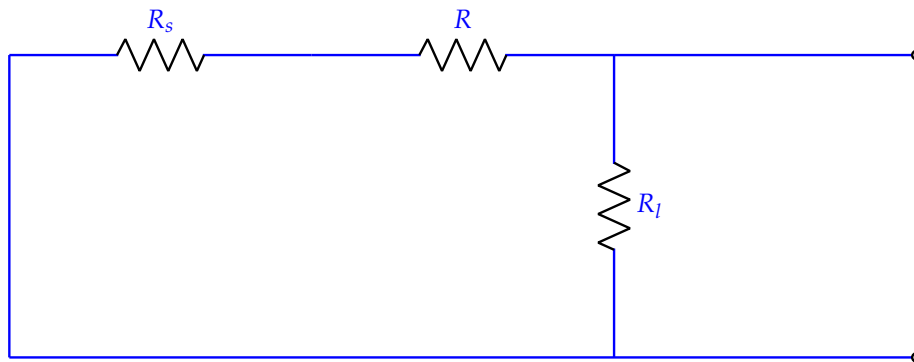Zeroing the source, we find the Thevenin resistance:



$$R_t = \frac{1}{\frac{1}{R_l} + \frac{1}{R+R_s}} \quad (26)$$

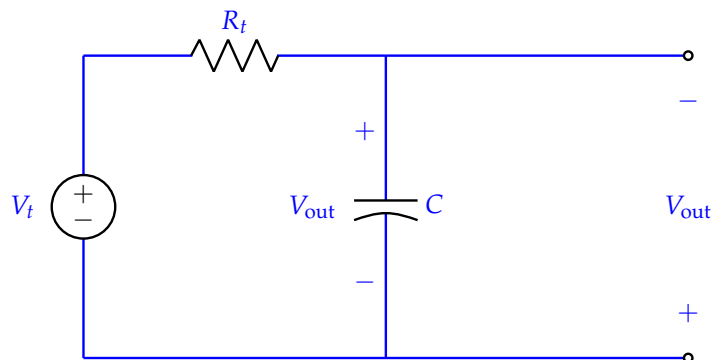Thus, the original circuit has the equivalent:



The transfer function for this circuit is

$$\frac{V_{\text{out}}}{V_t} = \frac{1}{1 + j\frac{f}{f_B}} \quad (27)$$

where $f_B = \frac{1}{2\pi R_t C}$. Using eq. (25) to substitute for V_t in eq. (27) and rearranging, we have

$$H(f) = \frac{V_{\text{out}}}{V_s} = \frac{R_t}{R_s + R + R_t} \times \frac{1}{1 + j\frac{f}{f_B}} \quad (28)$$

- (b) Given that $C = 0.2 \mu\text{F}$, $R_s = 2 \text{ k}\Omega$, $R = 47 \text{ k}\Omega$, and $R_t = 1 \text{ k}\Omega$, sketch the magnitude of $H(f)$ to scale versus $\frac{f}{f_B}$ from 0 to 3.


Solution: Evaluating for the circuit components given, we have

$$R_t = 980 \Omega \quad (29)$$

$$f_B = 812 \text{ Hz} \quad (30)$$

$$H(f) = \frac{0.02}{1 + j\frac{f}{f_B}} \quad (31)$$

The resulting plot is

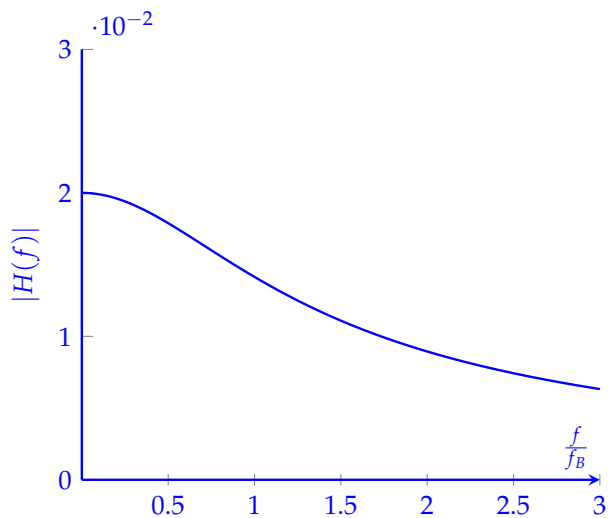

7. Hambley P6.53

A transfer function is given by


$$H(f) = \frac{100}{1 + j\frac{f}{1000}} \quad (32)$$

Sketch the asymptotic magnitude and phase Bode plots to scale. What is the value of the half-power frequency?

Solution: We have that

$$|H(f)| = \frac{100}{\sqrt{1 + \left(\frac{f}{1000}\right)^2}} \quad (33)$$

so $|H(f)|_{\text{dB}} = 20 \log(100) - 20 \log\left(\sqrt{1 + \left(\frac{f}{1000}\right)^2}\right) = 40 - 20 \log\left(\sqrt{1 + \left(\frac{f}{1000}\right)^2}\right)$. This is similar to the transfer function treated in Section 6.4 in the text except for the additional 40 dB constant. The half-power frequency is $f_B = 1000$. The asymptotic Bode plots are:

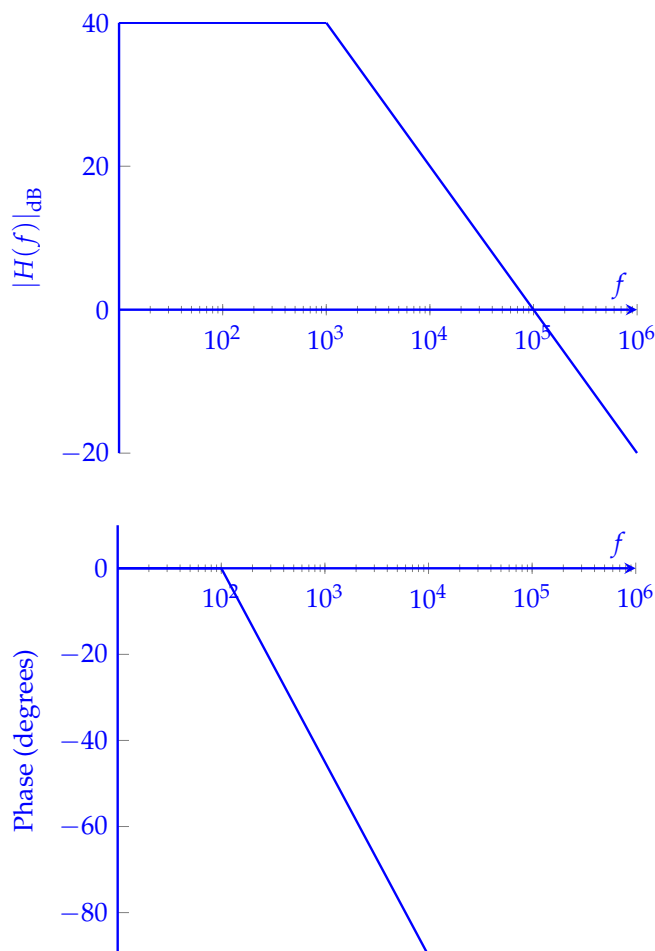

8. Hambley P6.55

Sketch the asymptotic magnitude and phase Bode plots to scale for the transfer function

$$H(f) = 10 \frac{1 - j\frac{f}{100}}{1 + j\frac{f}{100}} \quad (34)$$

Solution: We have that

$$|H(f)| = 10 \frac{\sqrt{1 + \left(\frac{f}{100}\right)^2}}{\sqrt{1 + \left(\frac{f}{100}\right)^2}} = 10 \quad (35)$$

so $|H(f)|_{\text{dB}} = 20 \log(10) = 20$. The phase is $-2 \arctan\left(\frac{f}{100}\right)$. The asymptotic Bode plots are:

