


EE16B
Designing Information
Devices and Systems II

Lecture 1B
Transient RC Circuit, Diff EQ



Announcements

- Last time:
 - Intro
 - Review of EECS16A
- Announcements:
 - Pre-Lab 0 & 1 are posted and due Monday
(Junha says: no longer than 30min for both)

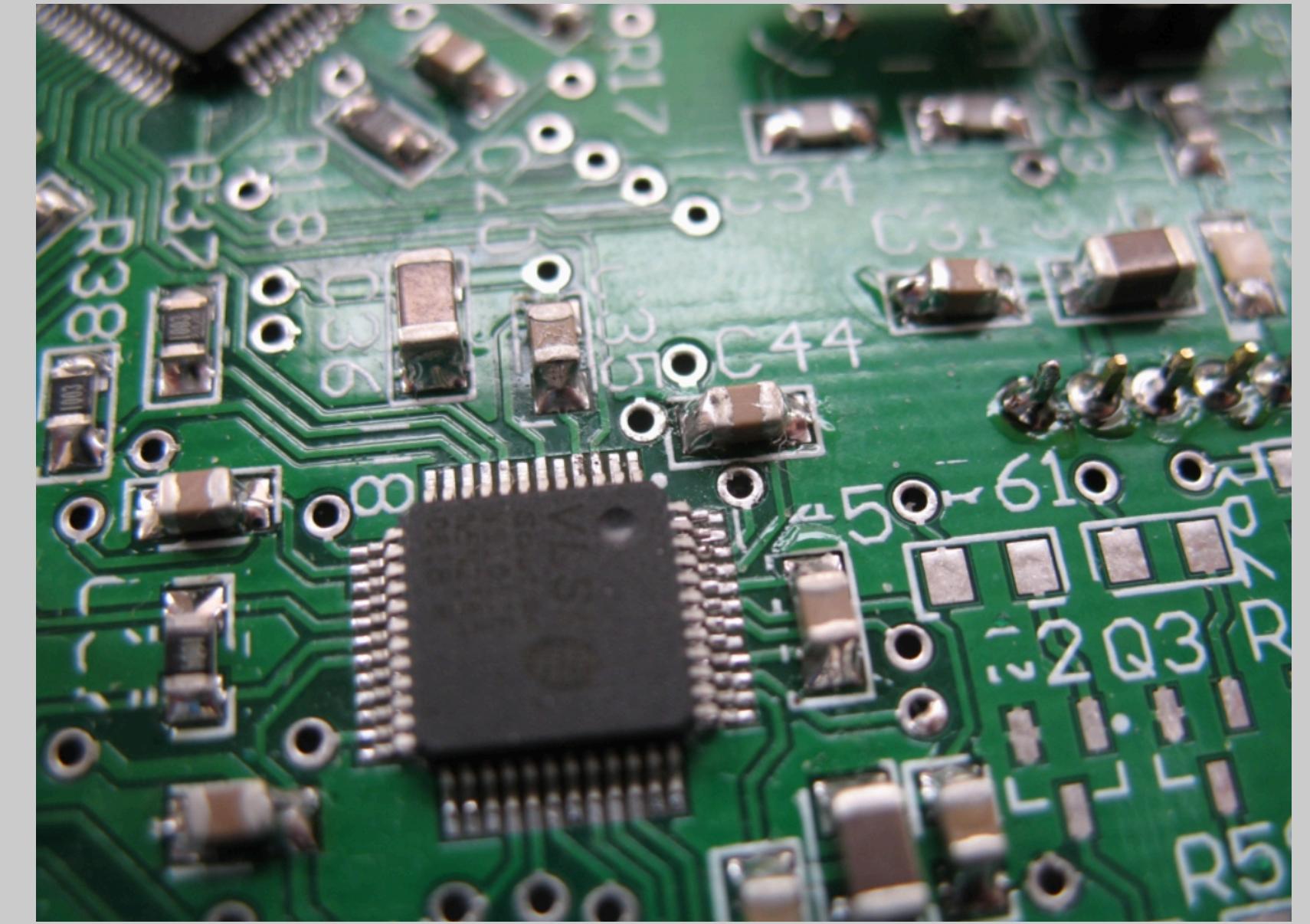
- Intentional capacitors:
 - Essential components in modern electronics
 - Energy storage, filtering, memory



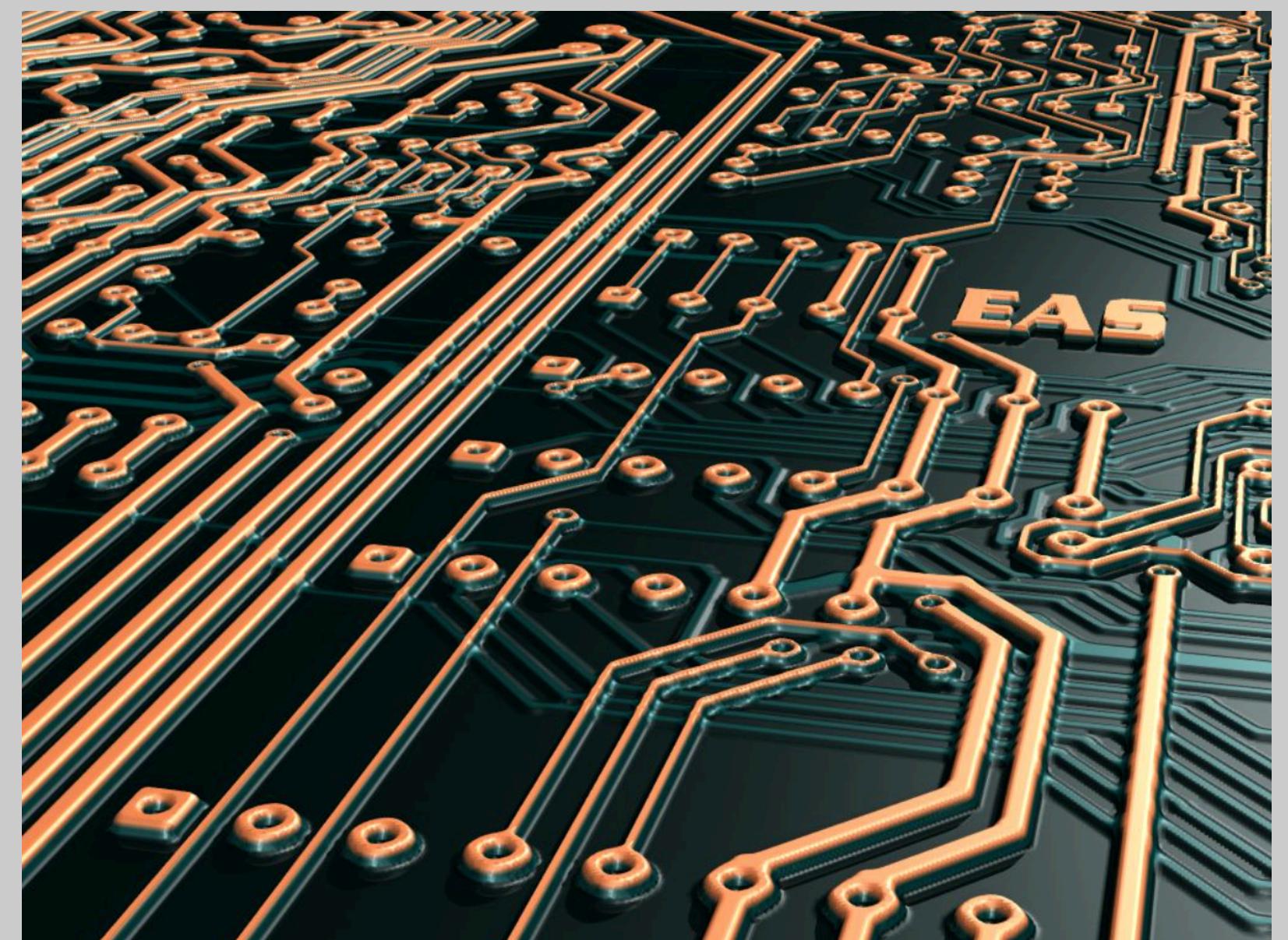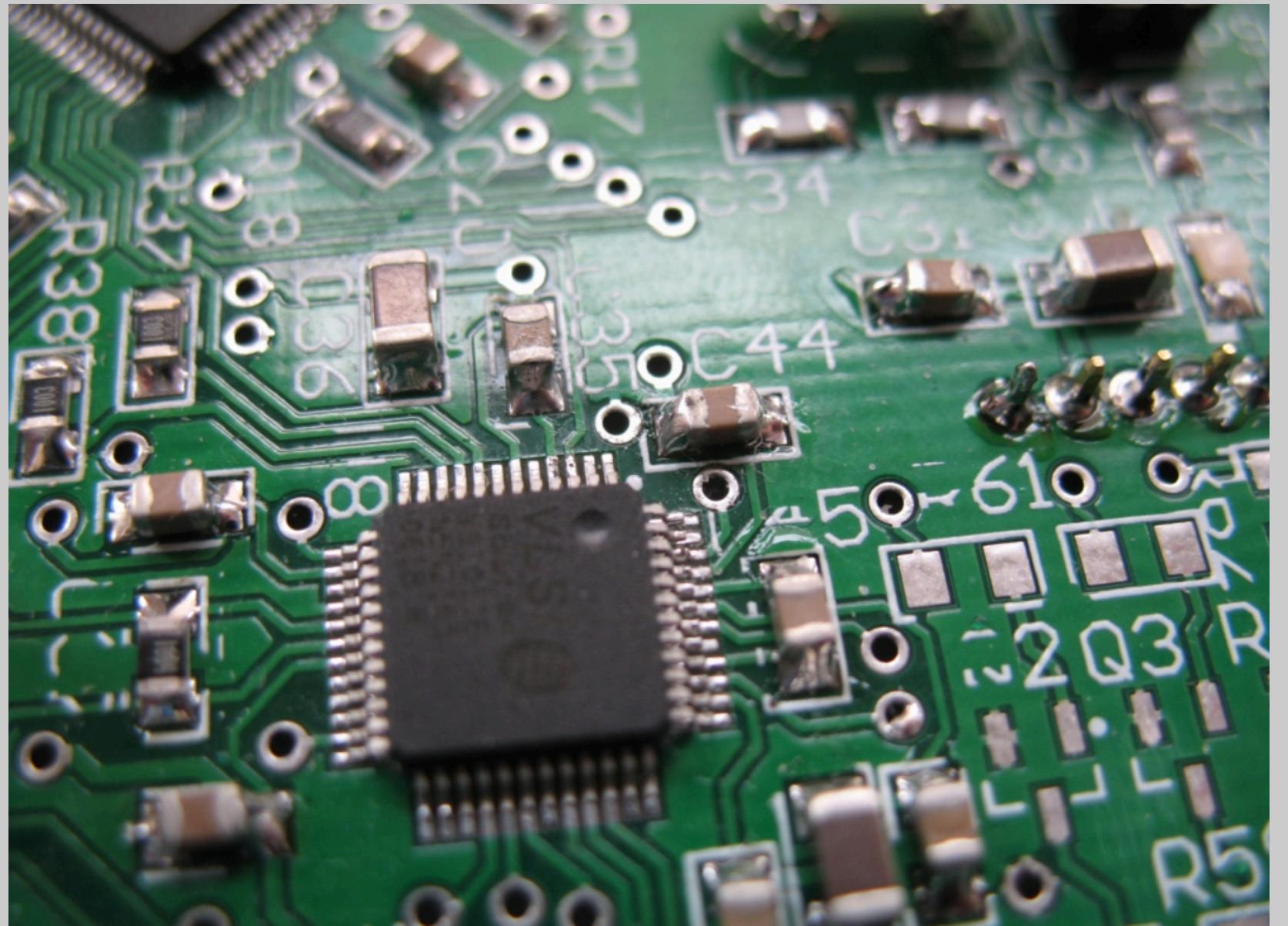
- Intentional capacitors:
 - Essential components in modern electronics
 - Energy storage, filtering, memory
- Unintentional (parasitic)
 - Any close traces with dielectric between becomes a cap!



Parallel Capacitors:

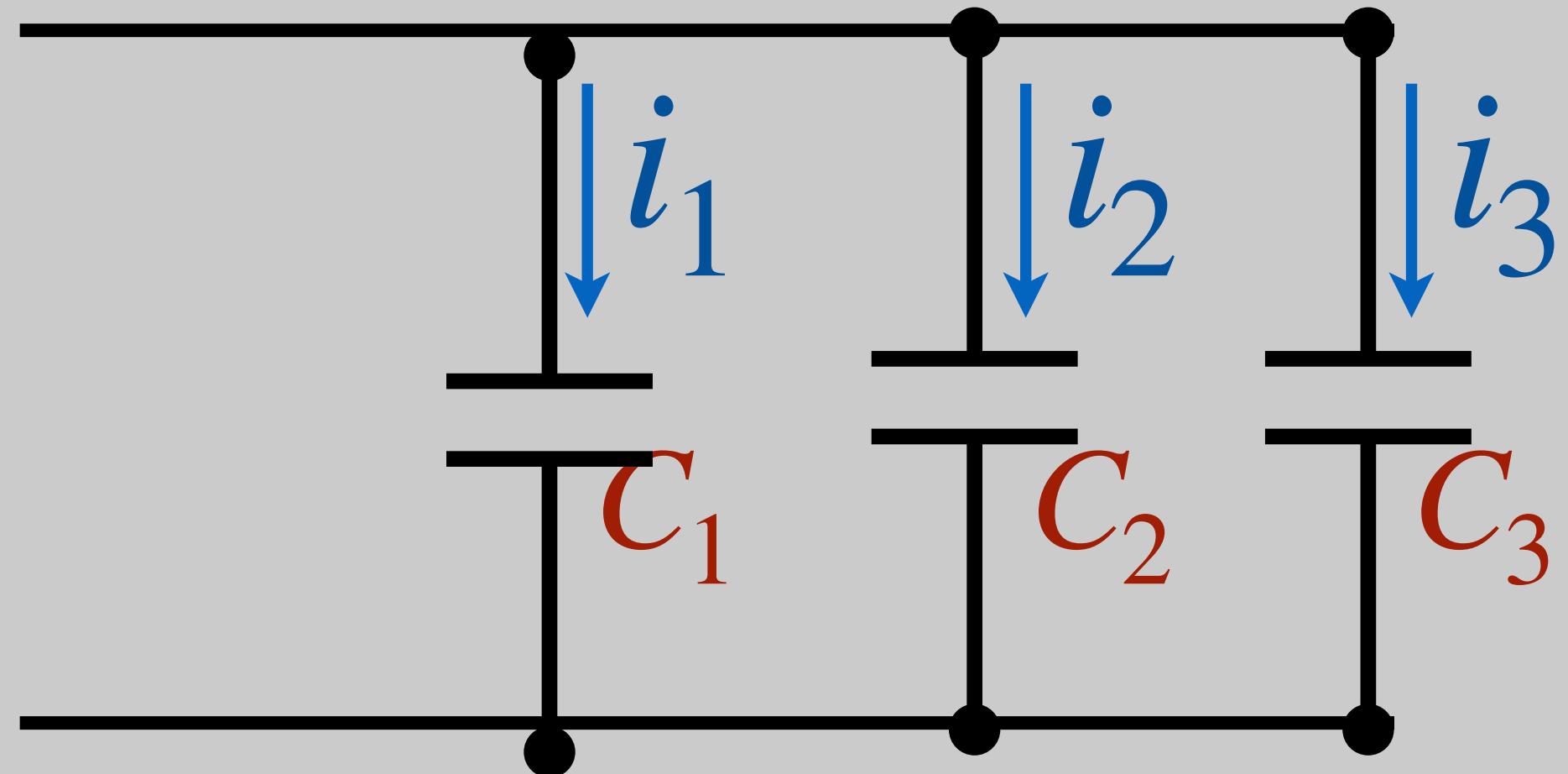

Parallel Capacitors:

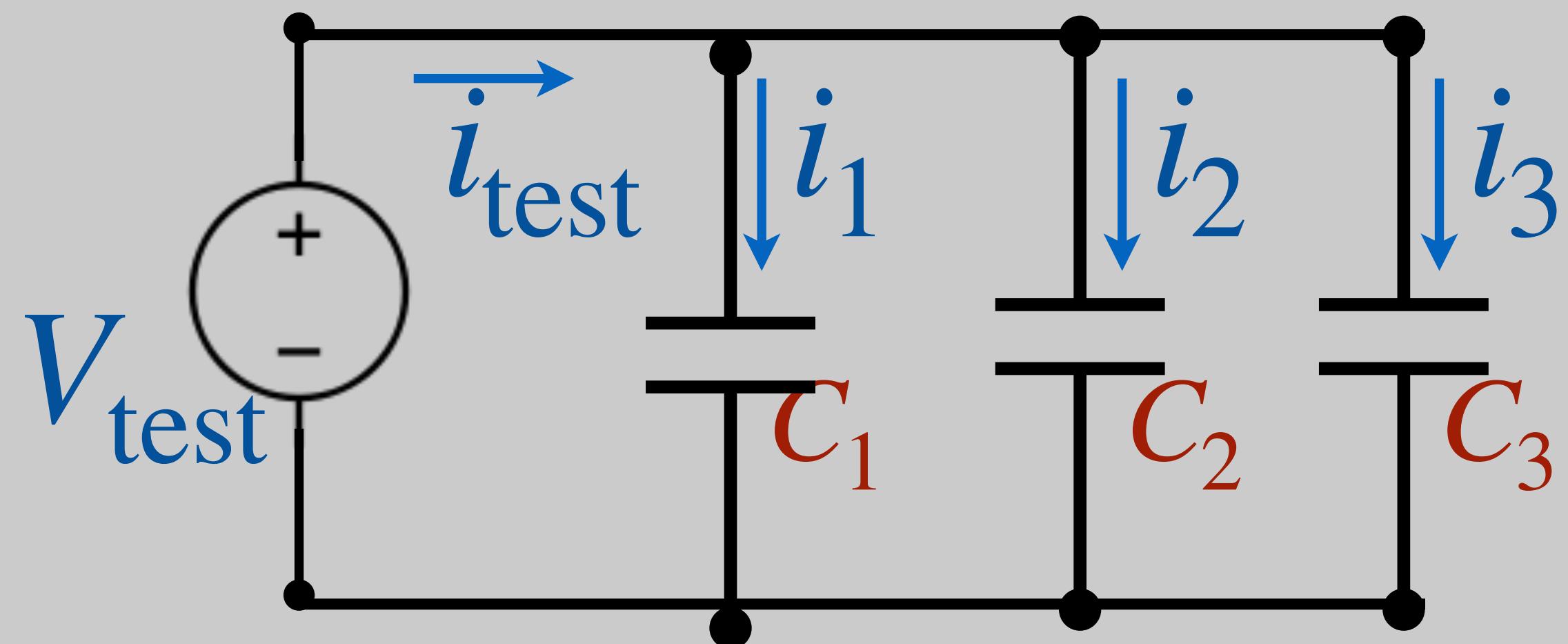


$$\dot{i}_{\text{test}} = i_1 + i_2 + i_3$$

$$C_{\text{eq}} \frac{dV_{\text{test}}}{dt} = C_1 \frac{dV_{\text{test}}}{dt} + C_2 \frac{dV_{\text{test}}}{dt} + C_3 \frac{dV_{\text{test}}}{dt}$$

$$C_{\text{eq}} = C_1 + C_2 + C_3$$

Parallel Capacitors:

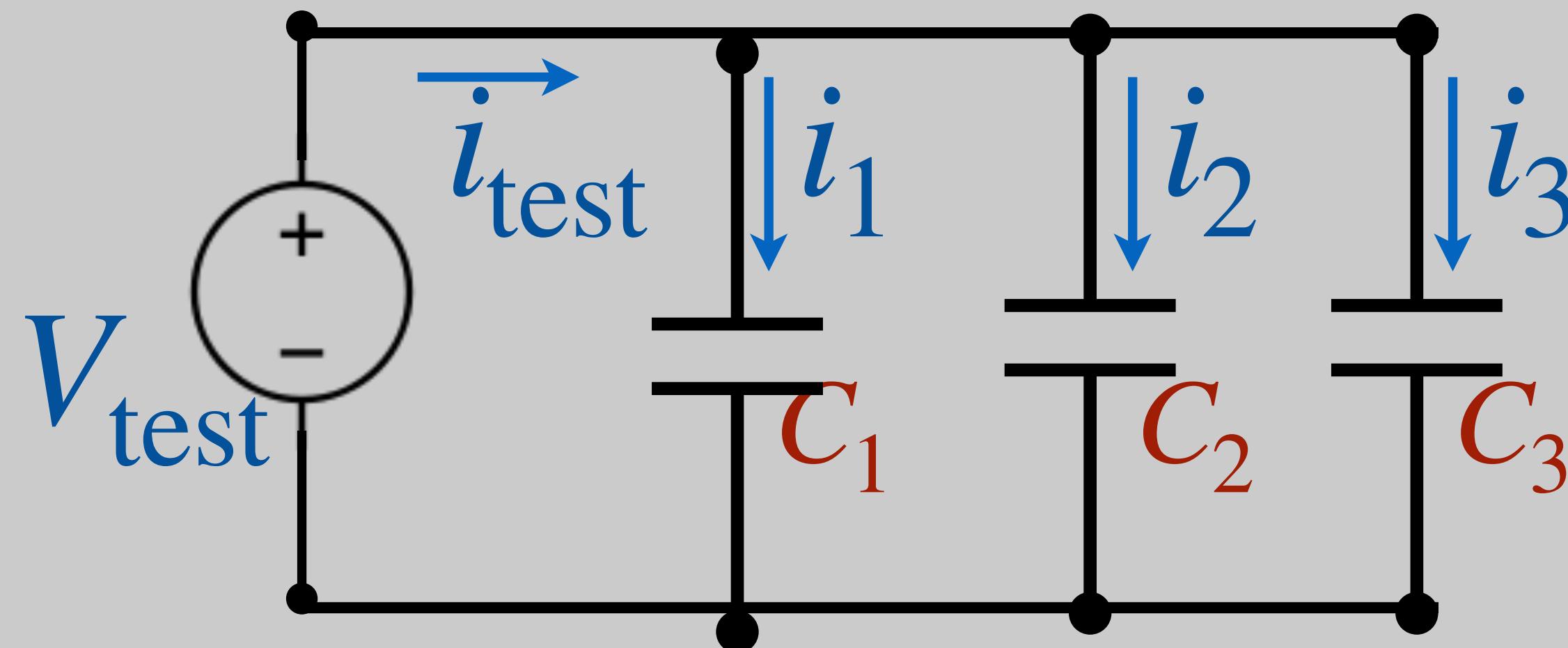


$$\dot{i}_{\text{test}} = i_1 + i_2 + i_3$$


$$C_{\text{eq}} \frac{dV_{\text{test}}}{dt} = C_1 \frac{dV_{\text{test}}}{dt} + C_2 \frac{dV_{\text{test}}}{dt} + C_3 \frac{dV_{\text{test}}}{dt}$$

$$C_{\text{eq}} = C_1 + C_2 + C_3$$

Series Capacitors:

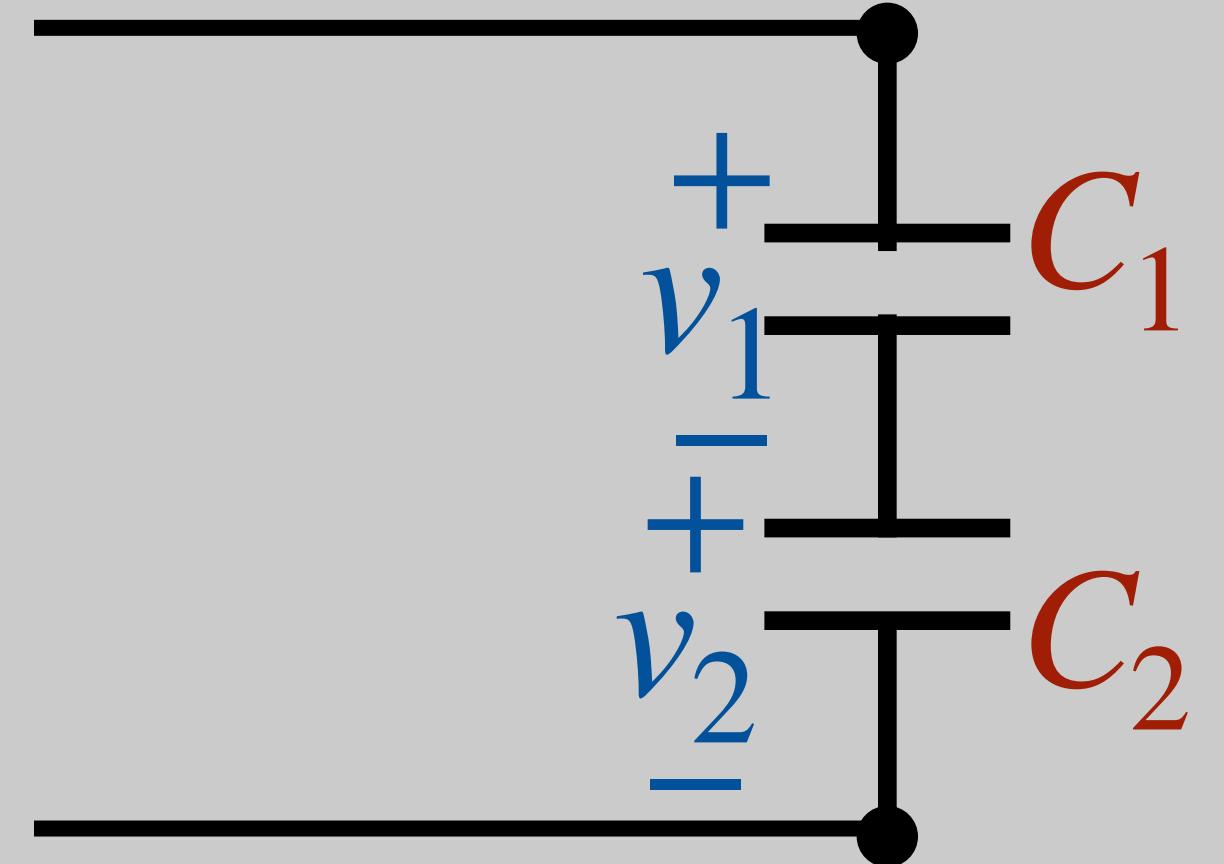

Parallel Capacitors:

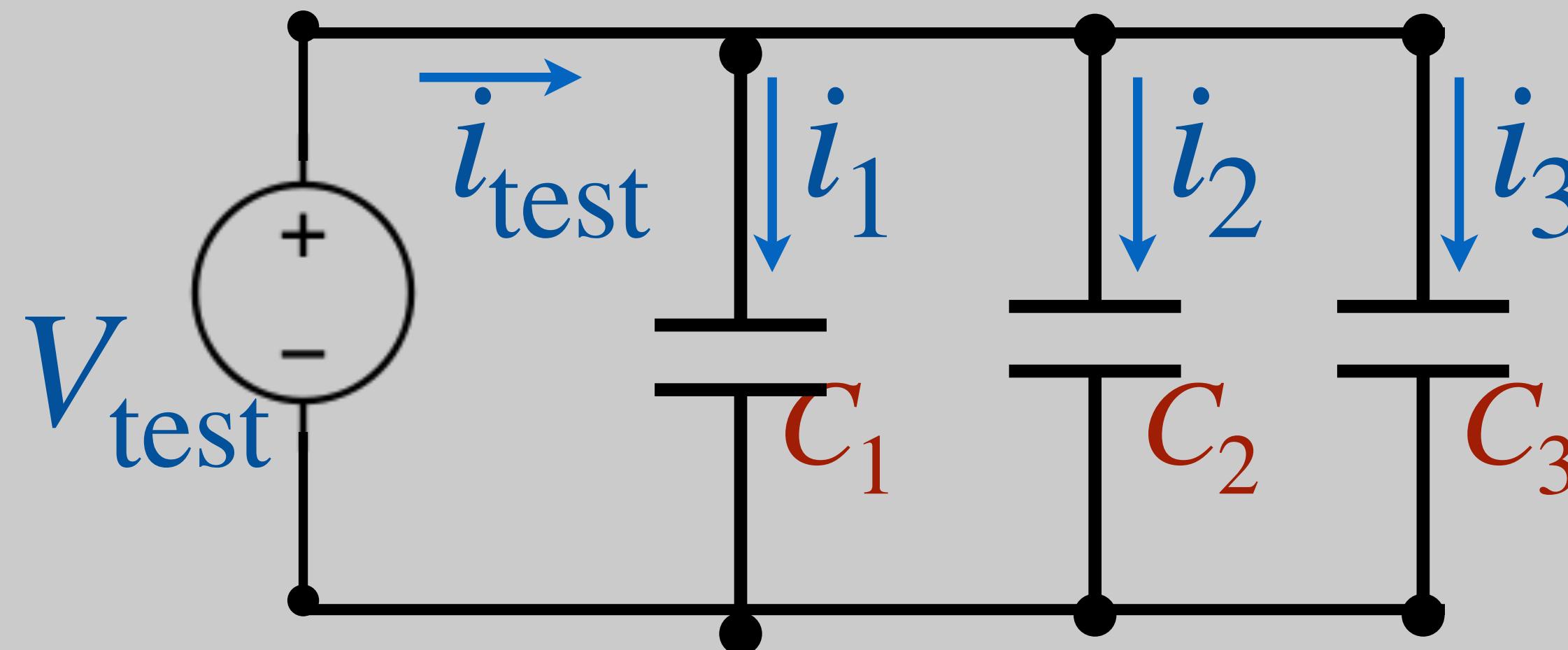


$$i_{\text{test}} = i_1 + i_2 + i_3$$

$$C_{\text{eq}} \frac{dV_{\text{test}}}{dt} = C_1 \frac{dV_{\text{test}}}{dt} + C_2 \frac{dV_{\text{test}}}{dt} + C_3 \frac{dV_{\text{test}}}{dt}$$

$$C_{\text{eq}} = C_1 + C_2 + C_3$$

Series Capacitors:




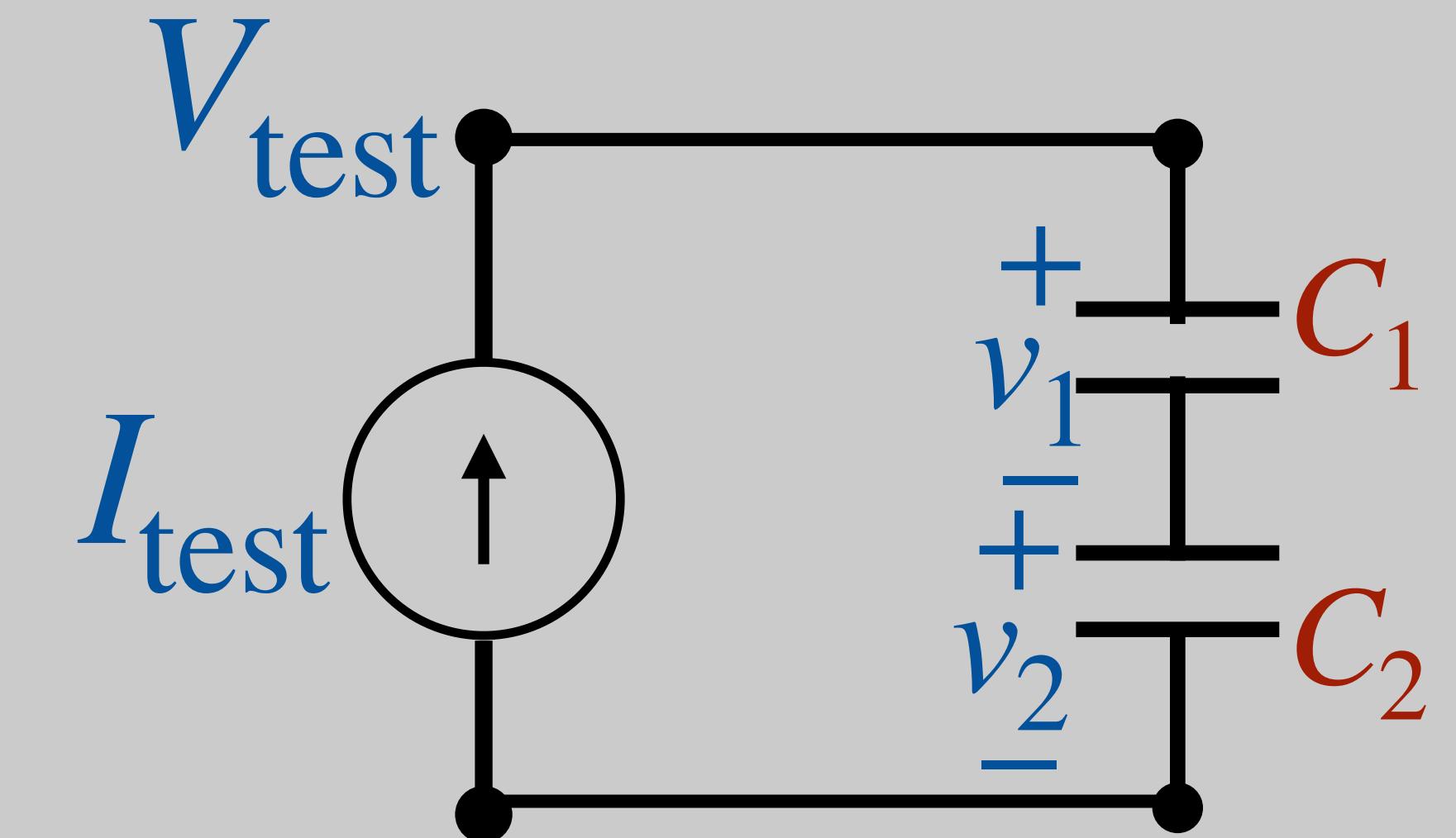


$$i_{\text{test}} = C_{\text{eq}} \frac{dV_{\text{test}}}{dt} = C_{\text{eq}} \frac{dV_1}{dt} + C_{\text{eq}} \frac{dV_2}{dt}$$


$$i_{\text{test}} = C_{\text{eq}} \frac{i_{\text{test}}}{C_1} + C_{\text{eq}} \frac{i_{\text{test}}}{C_2}$$

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2}$$



EECS16A Review

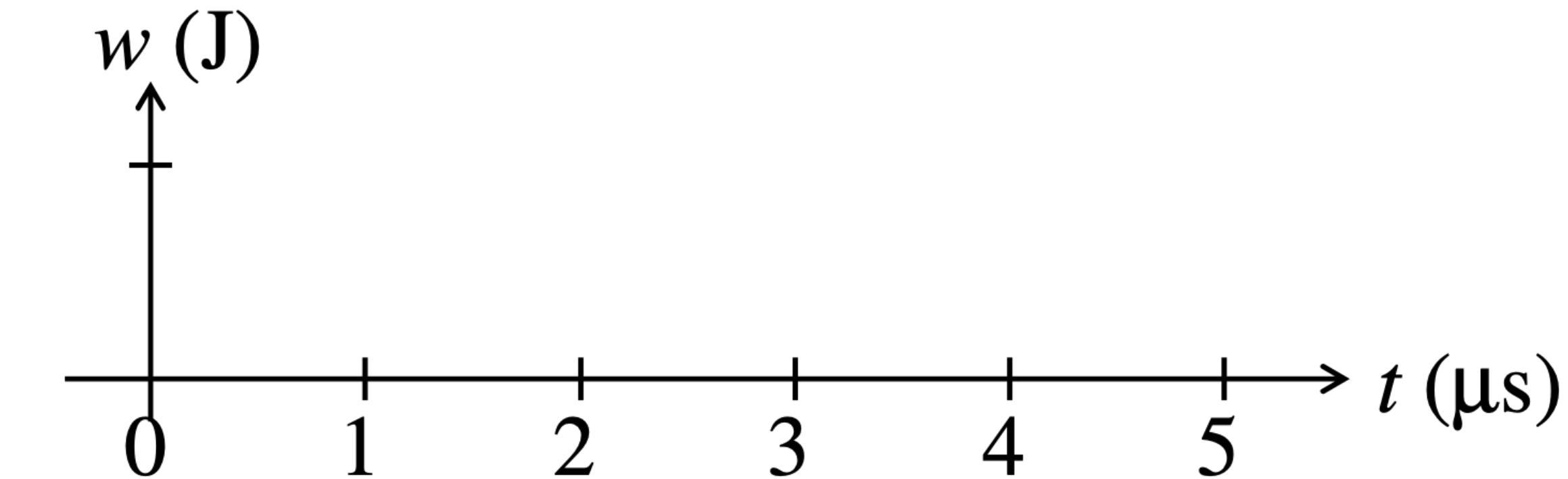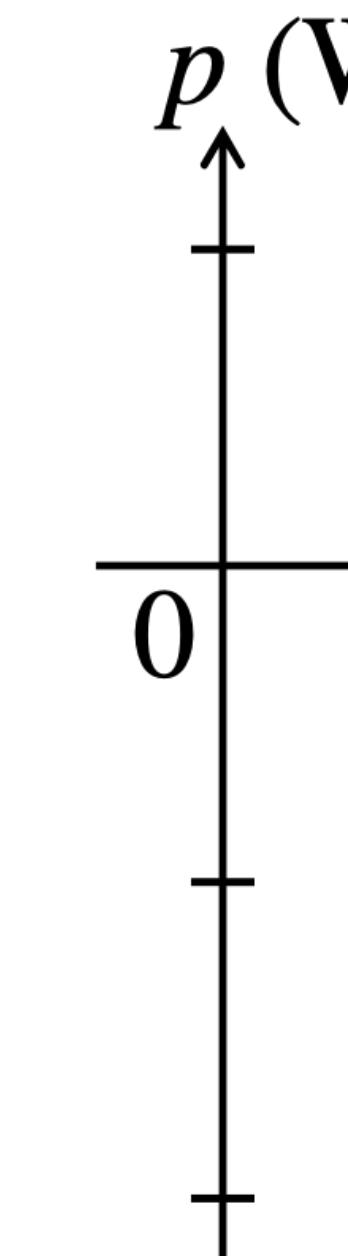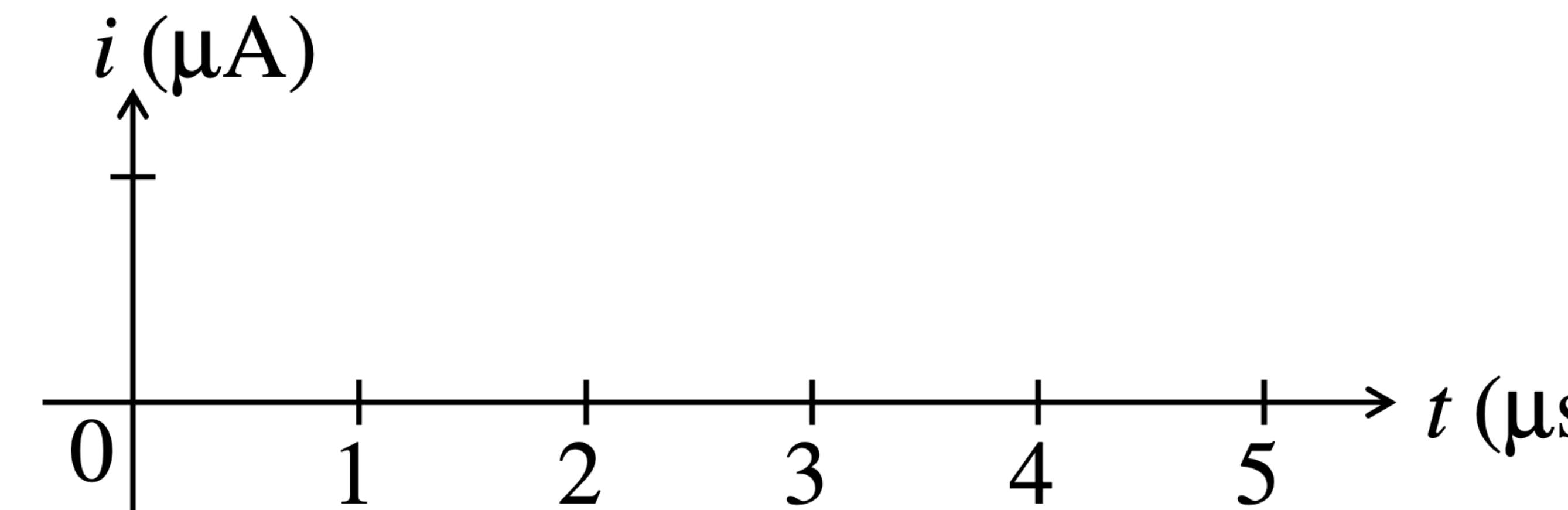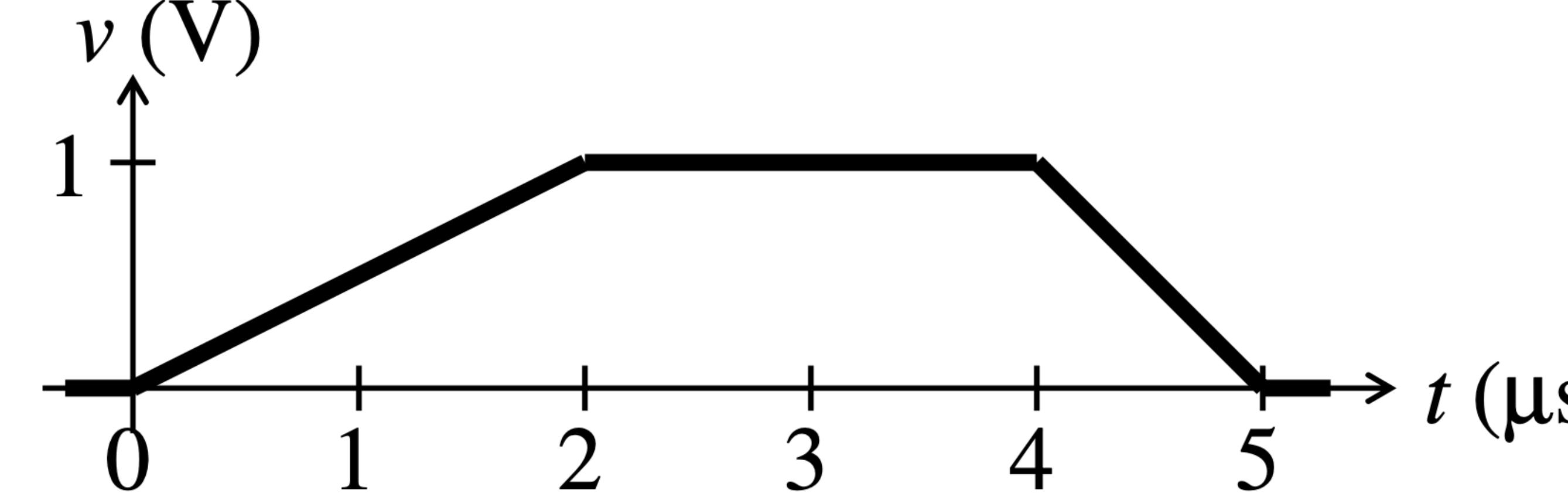



$$i = C \frac{dv}{dt}$$

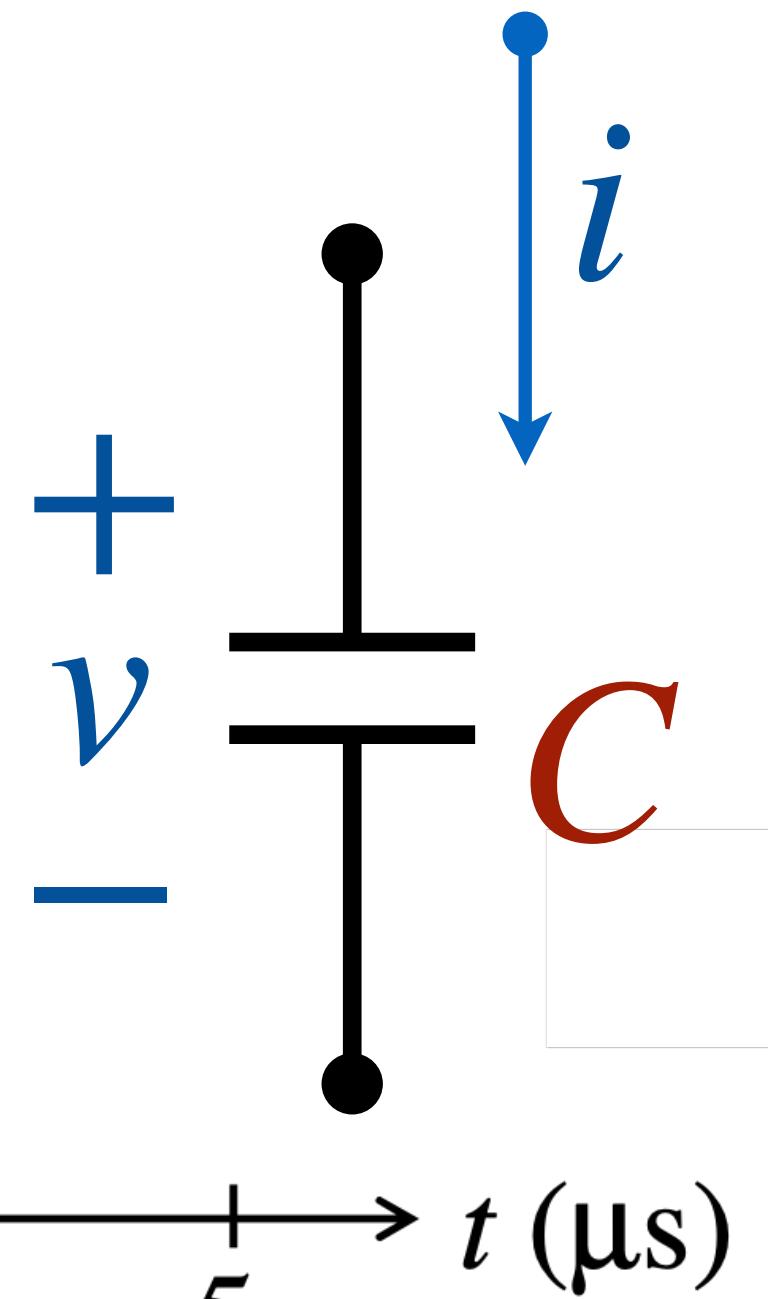



EECS16A Review

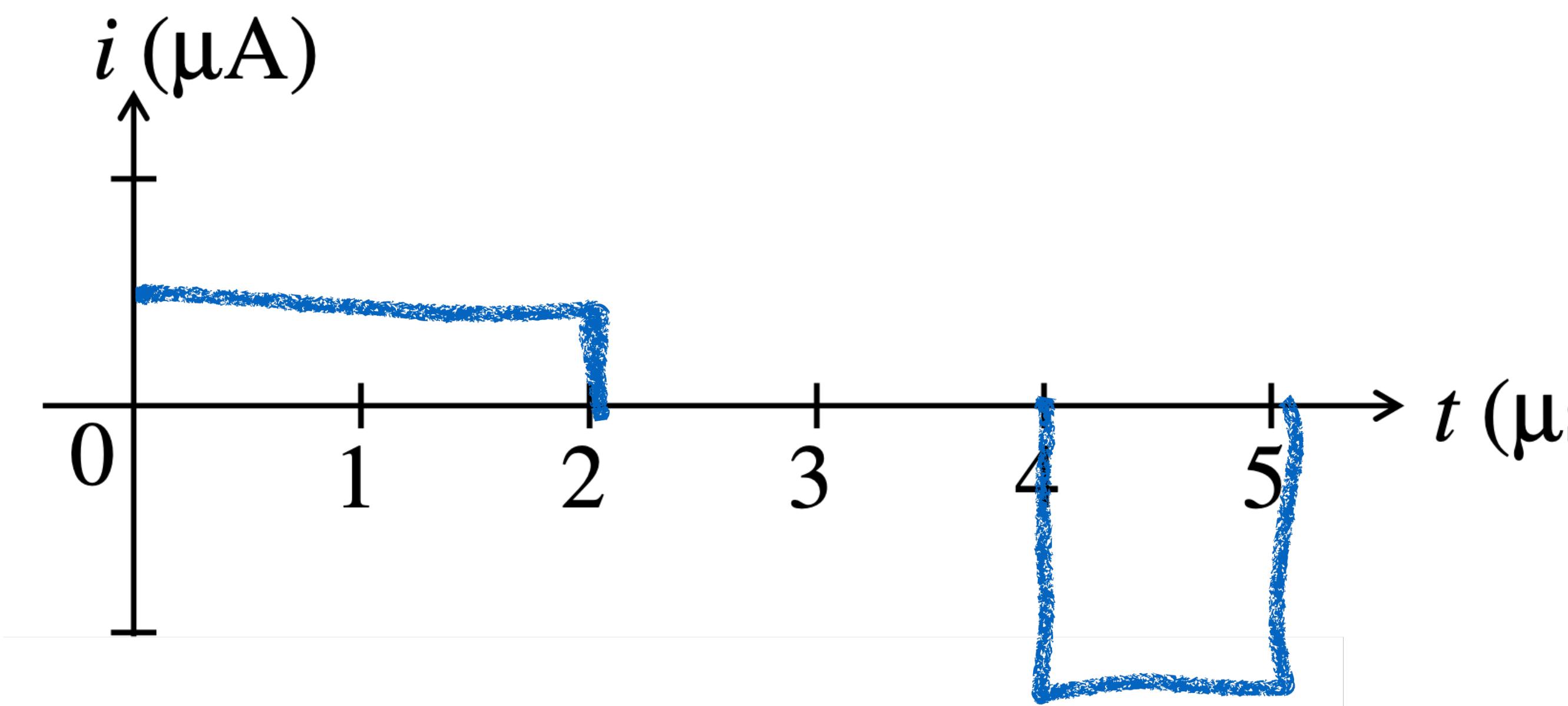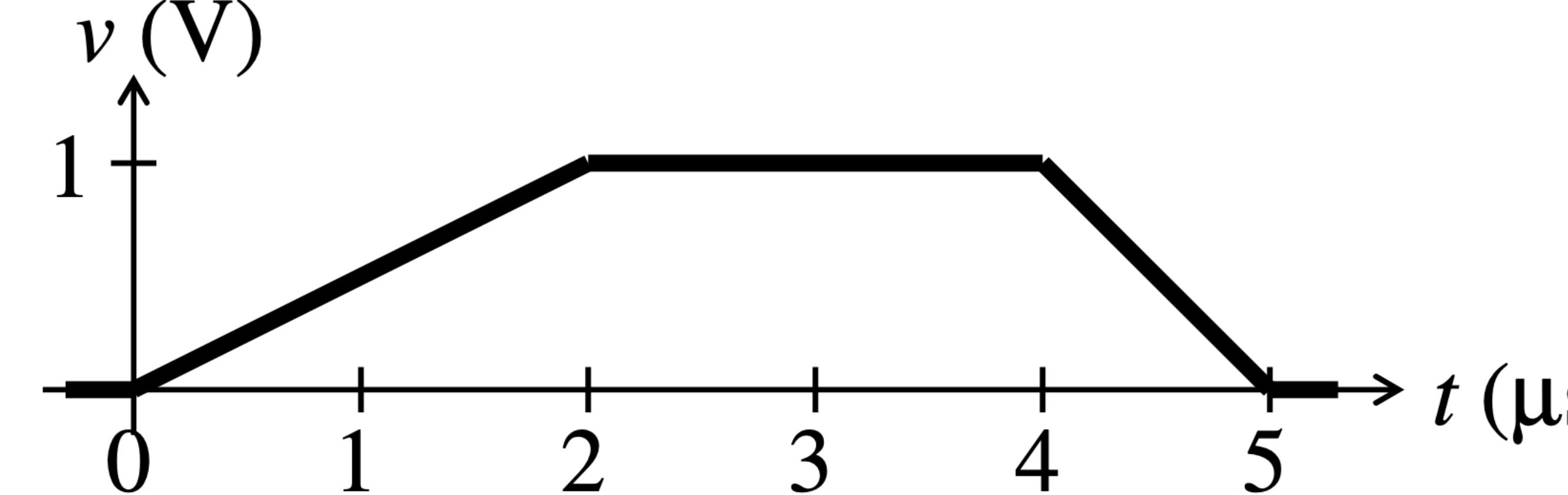




$$i = C \frac{dv}{dt}$$

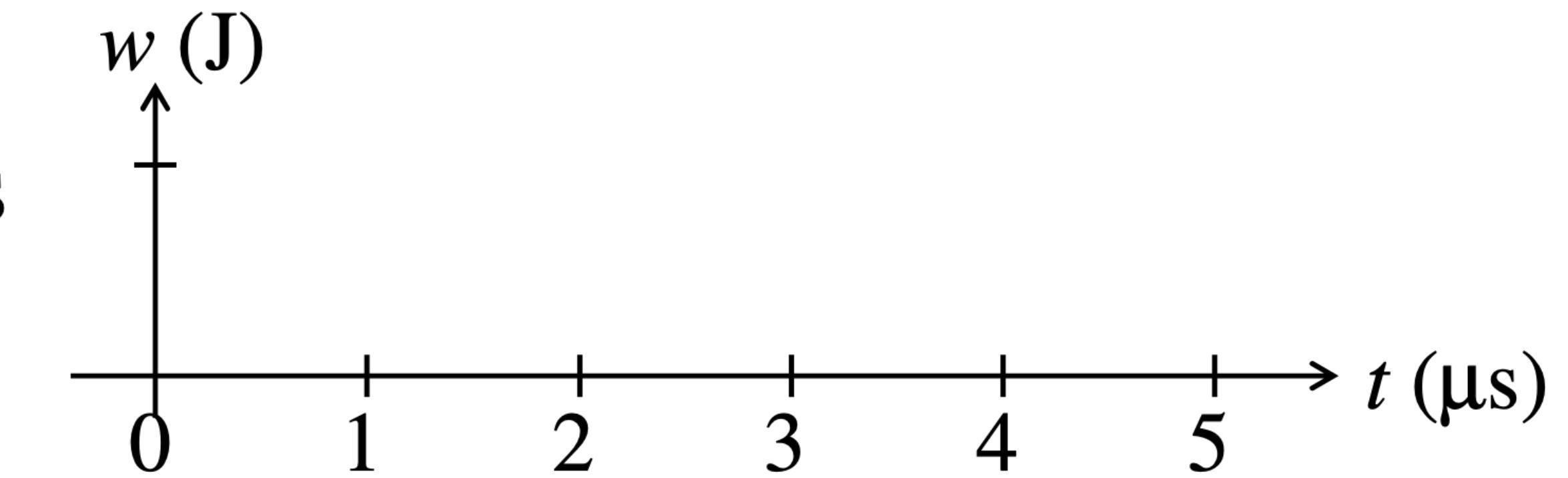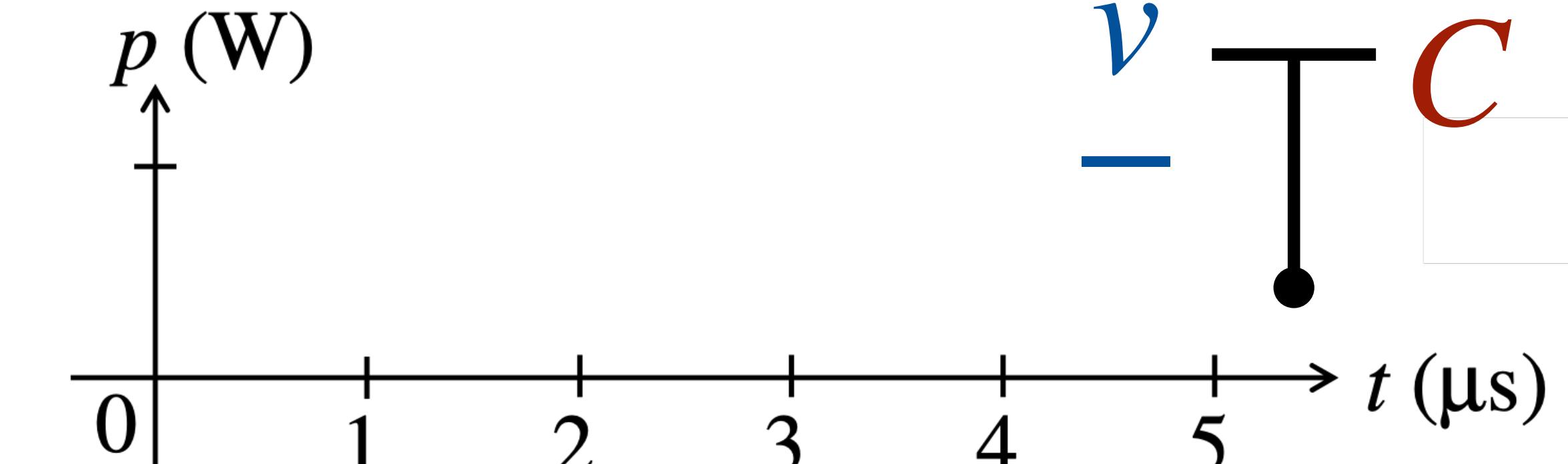



EECS16A Review

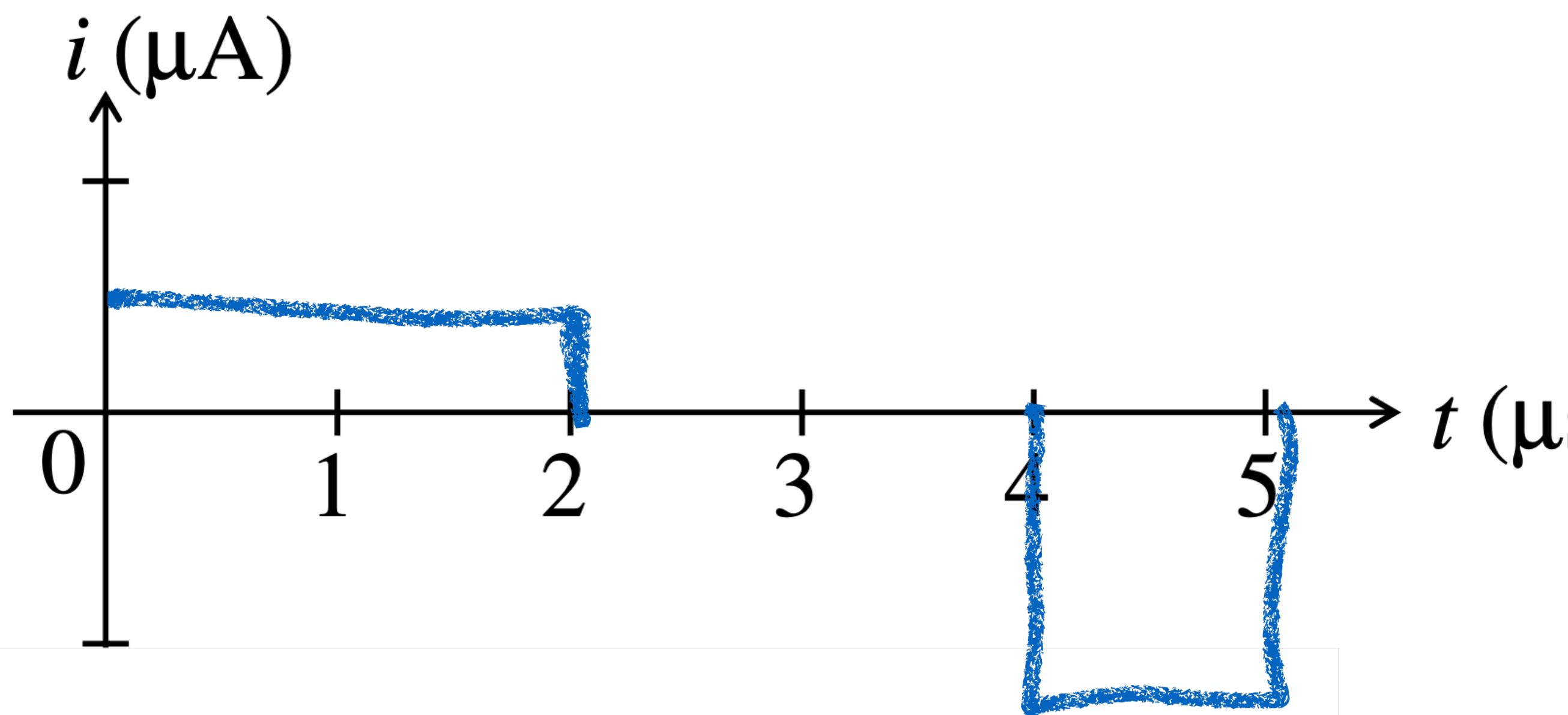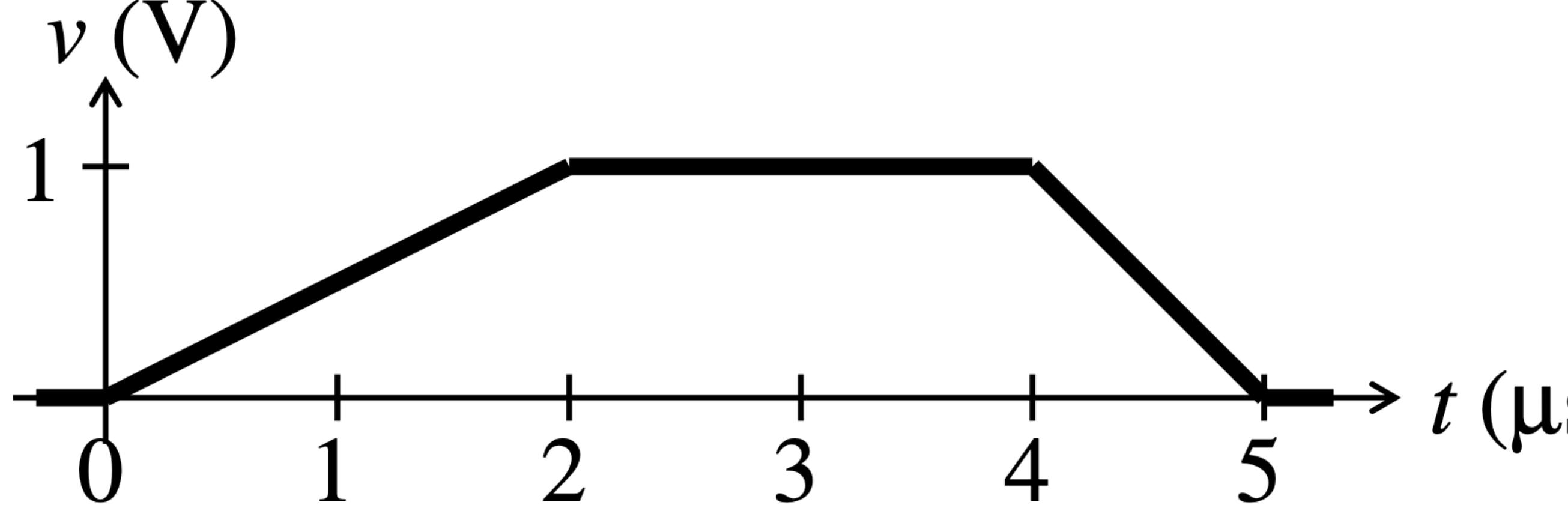

$$i = C \frac{dv}{dt}$$

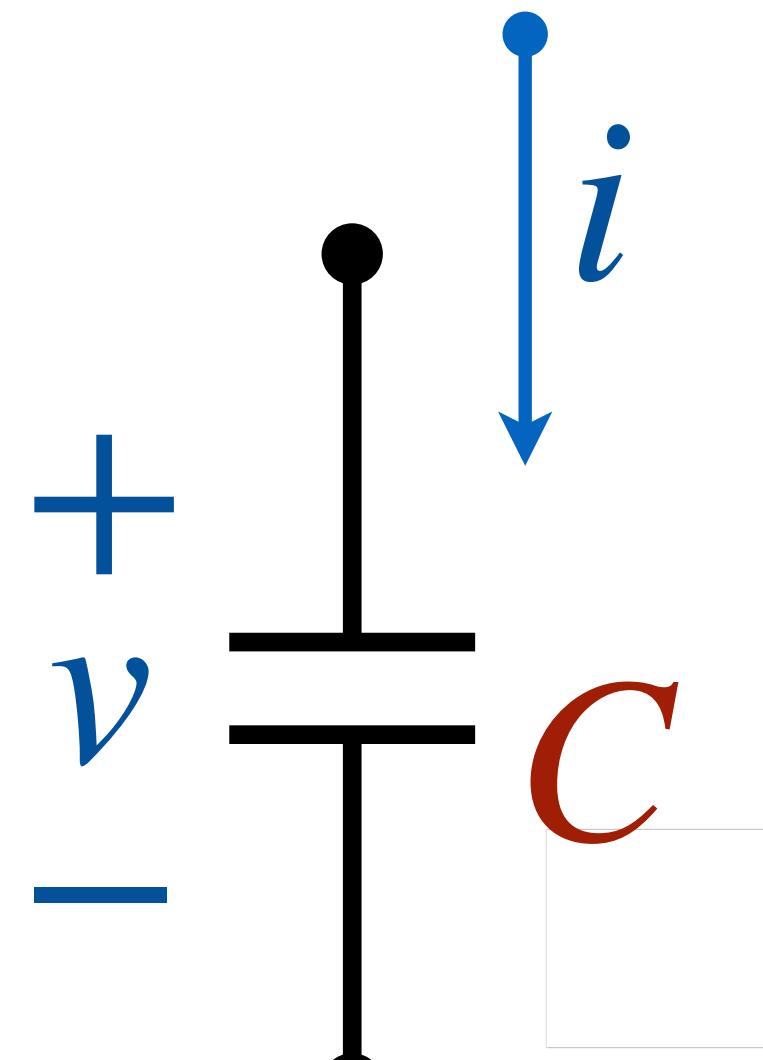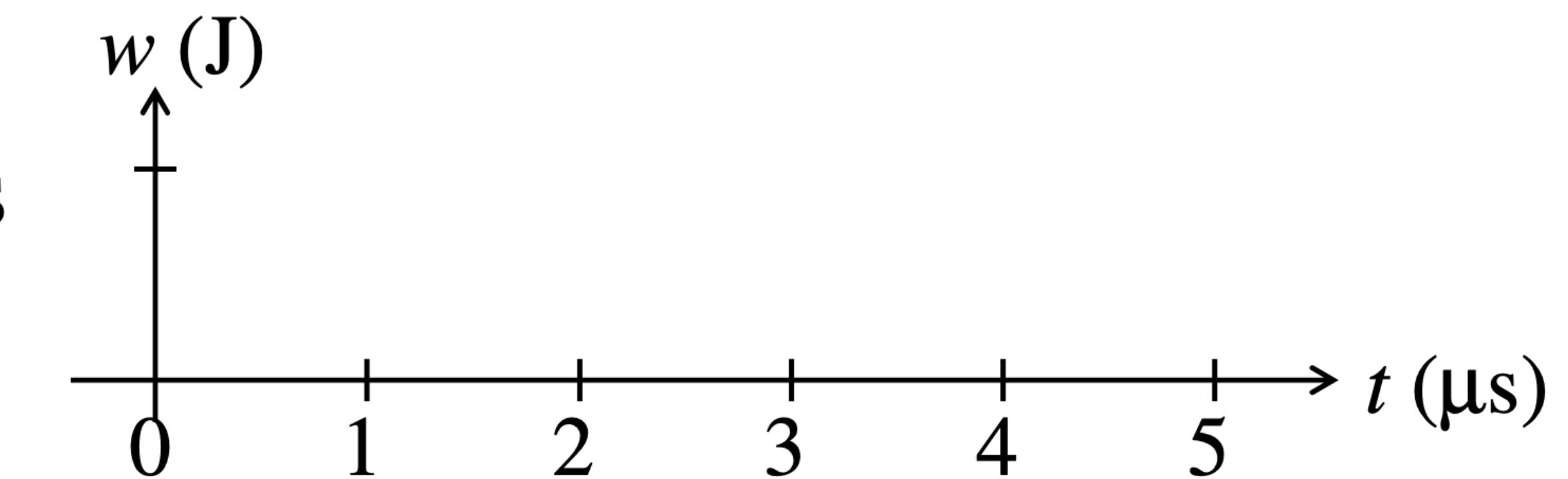
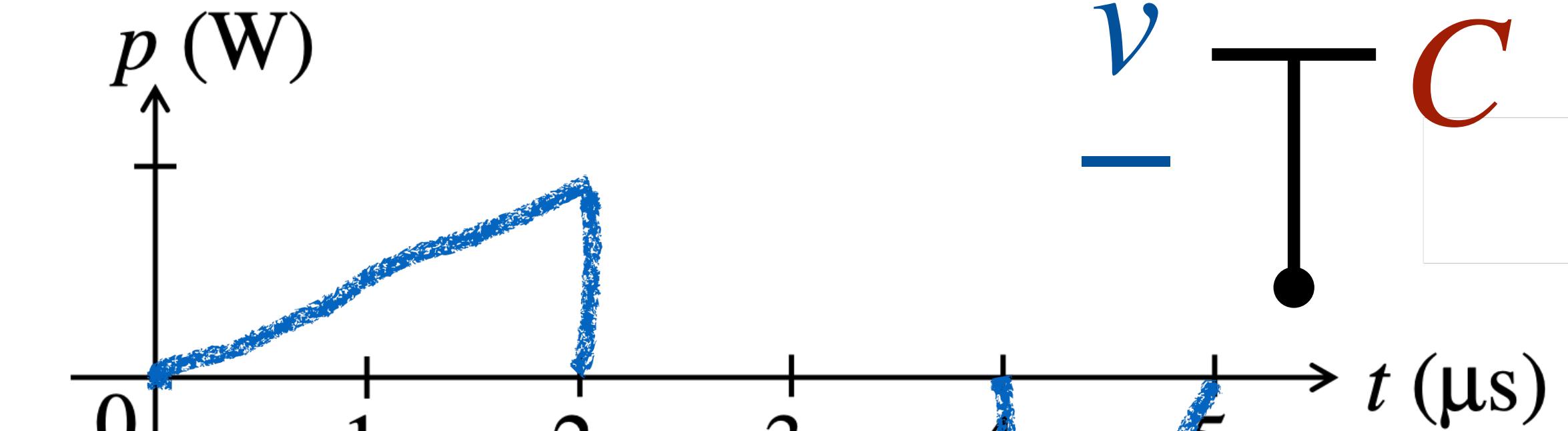


EECS16A Review

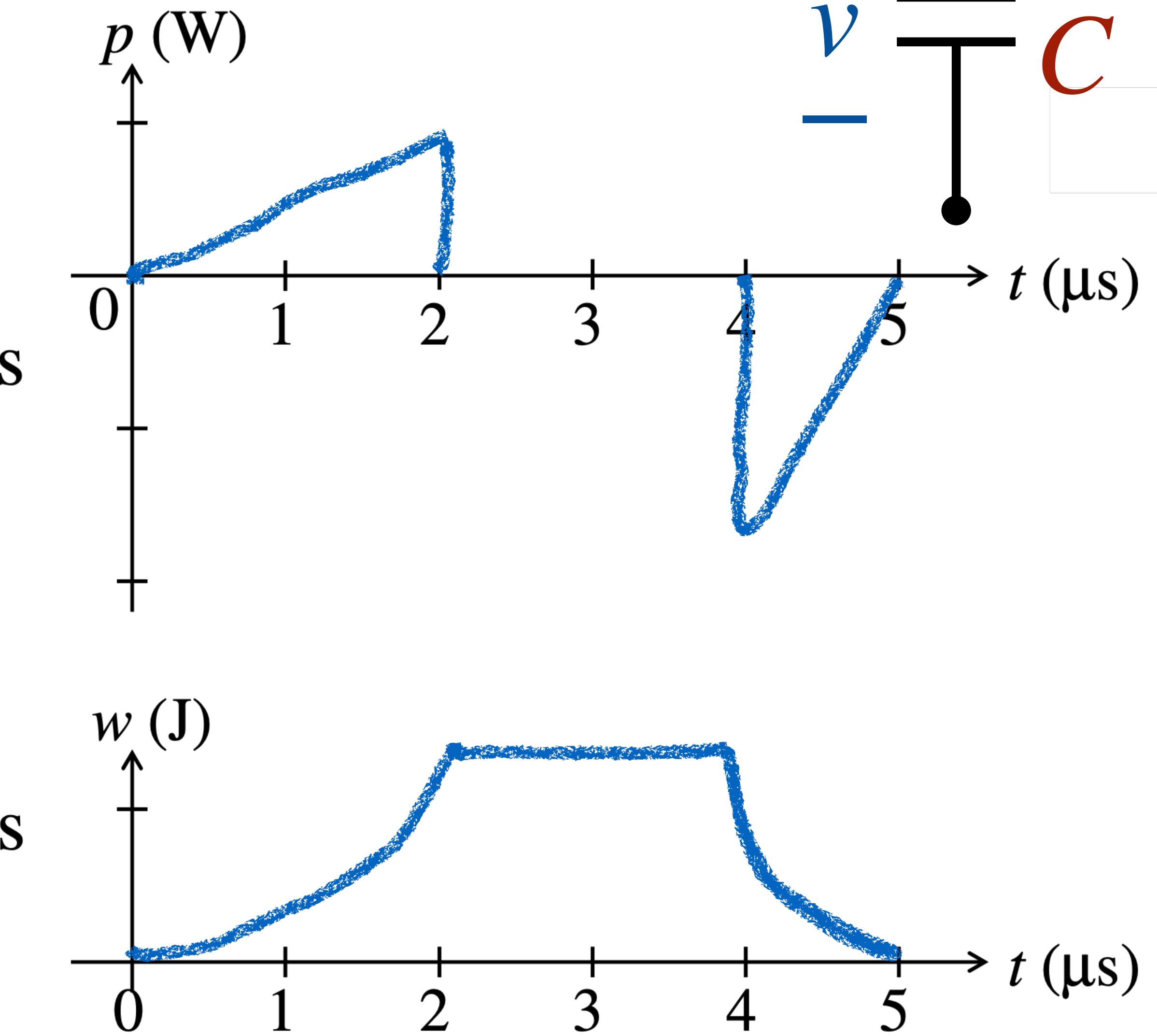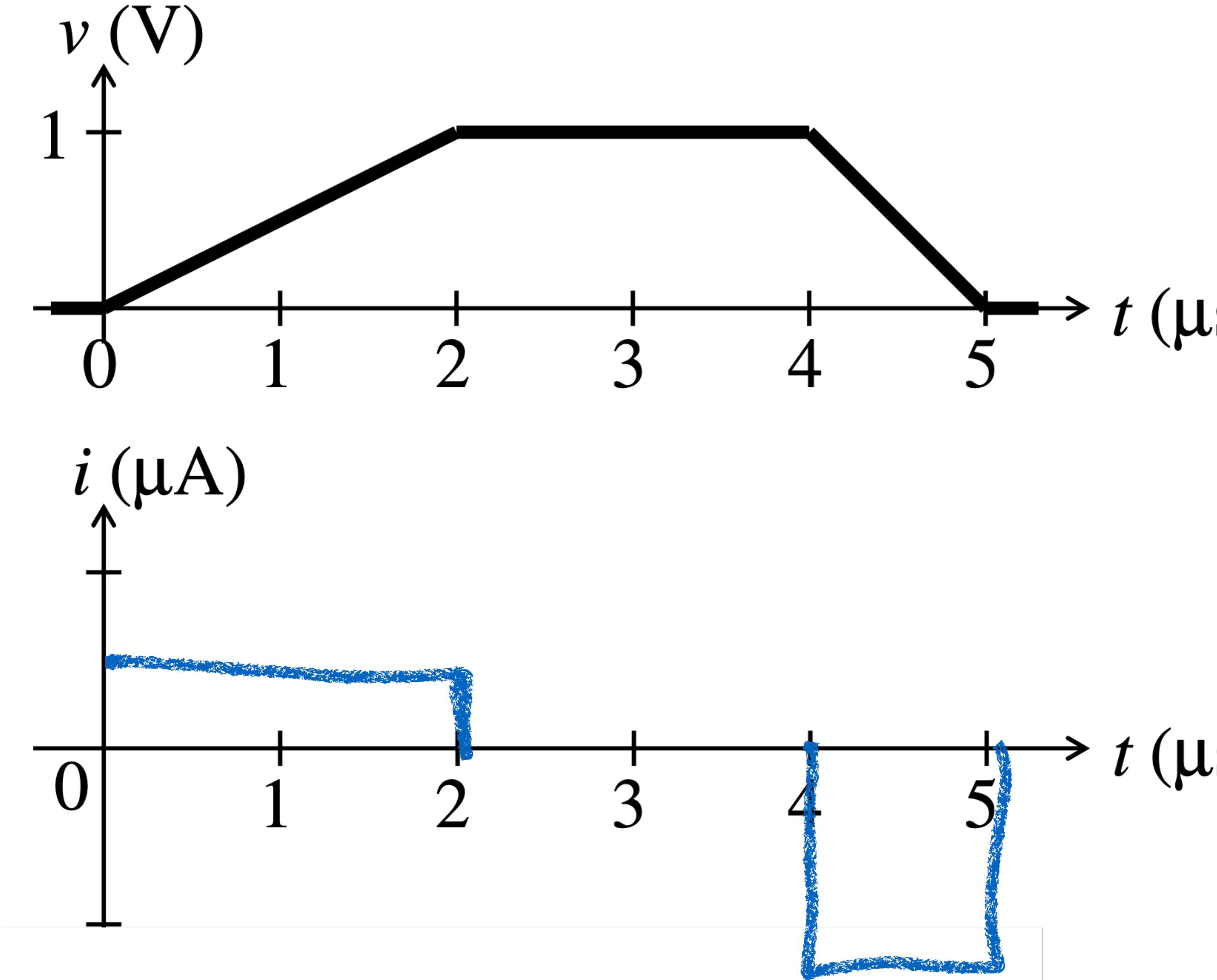


$$i = C \frac{dv}{dt}$$

Transient Response

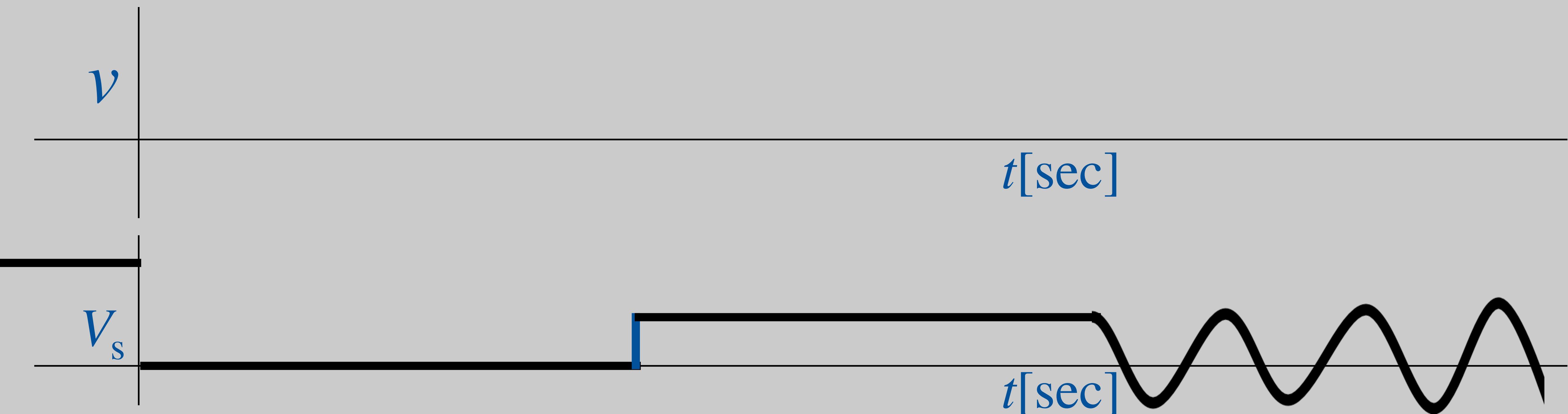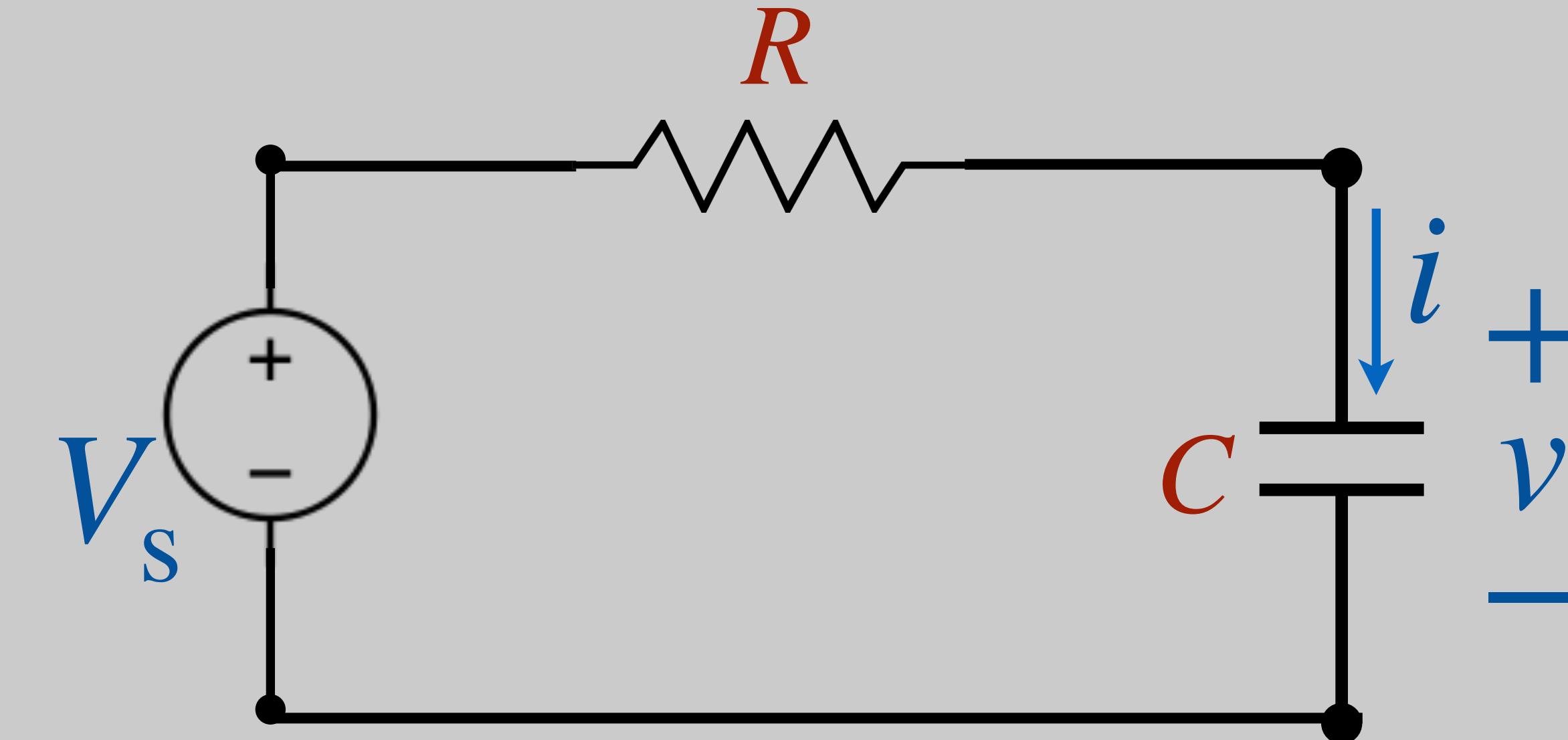

RC Circuits

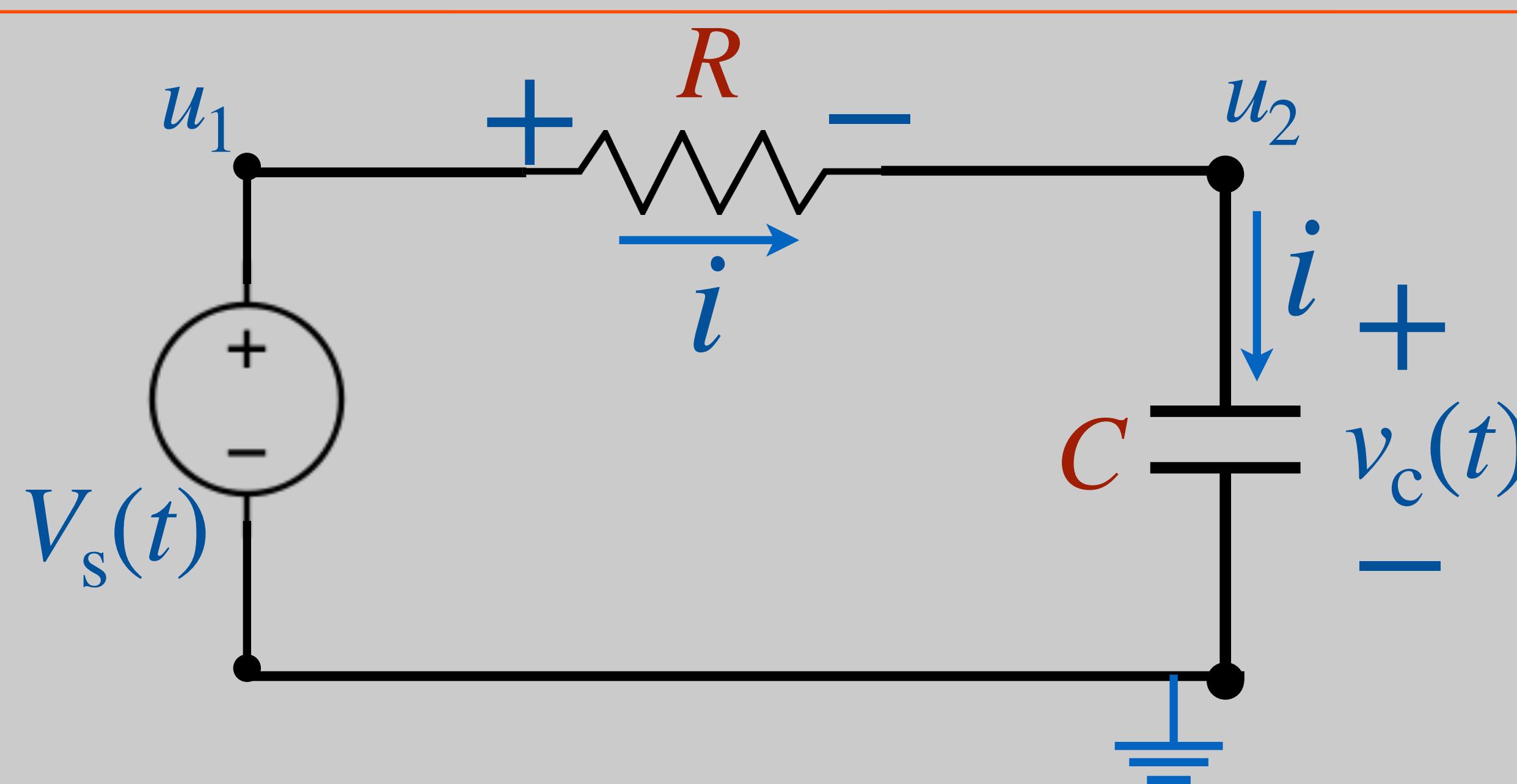

$$V_s - v_c = C \frac{dv_c}{dt} R$$

$$v_c + RC \frac{dv_c}{dt} = V_s \Rightarrow \frac{dv_c}{dt} + \frac{1}{RC} v_c = \frac{1}{RC} V_s$$


$$u_1 = V_s$$

$$u_2 = v_c$$

$$V_s - v_c = iR$$

$$i = C \frac{dv_c}{dt}$$

RC Circuits

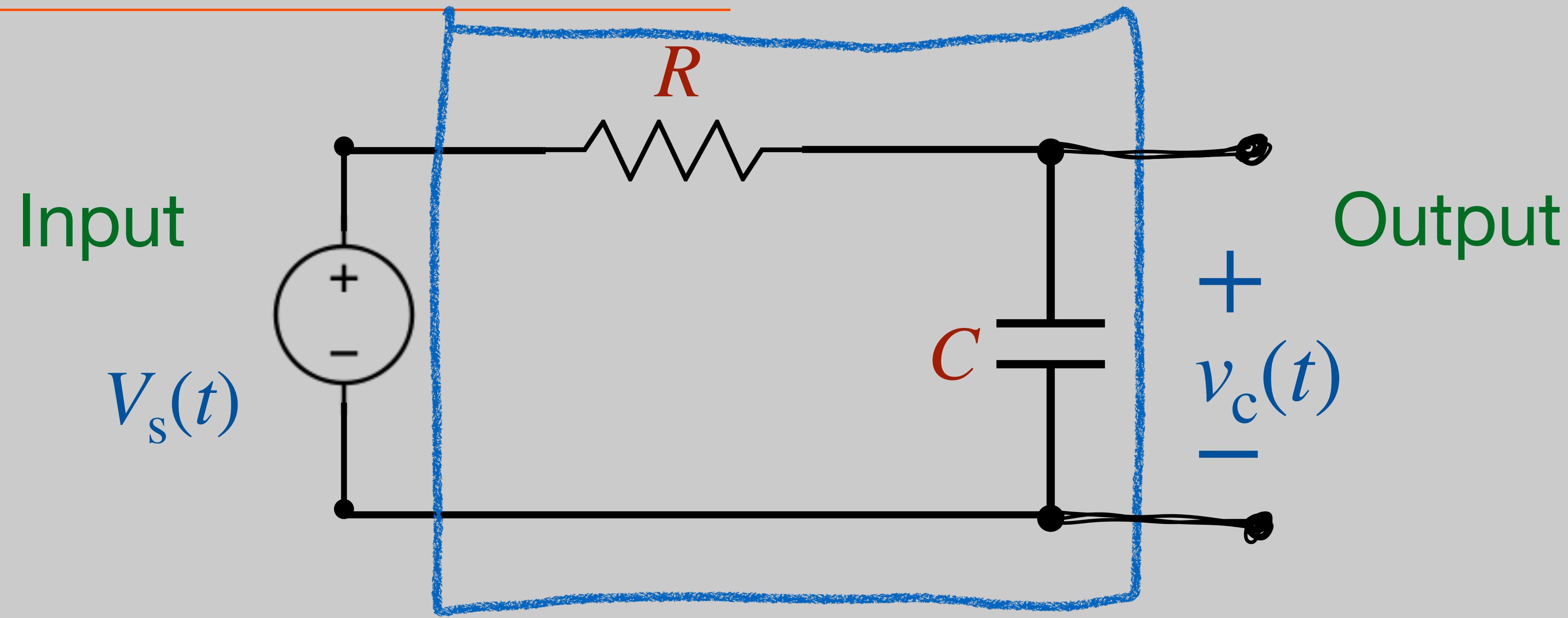


$$RC \frac{dv_c}{dt} + v_c = V_s$$

Constant coefficients
1st order diff. Eq.

$$\frac{dv_c(t)}{dt} + \frac{1}{RC}v_c(t) = \frac{1}{RC}V_s(t)$$

RC Circuits - Steady State

$$\frac{dv_c(t)}{dt} + \frac{1}{RC}v_c(t) = \frac{1}{RC}V_s(t)$$

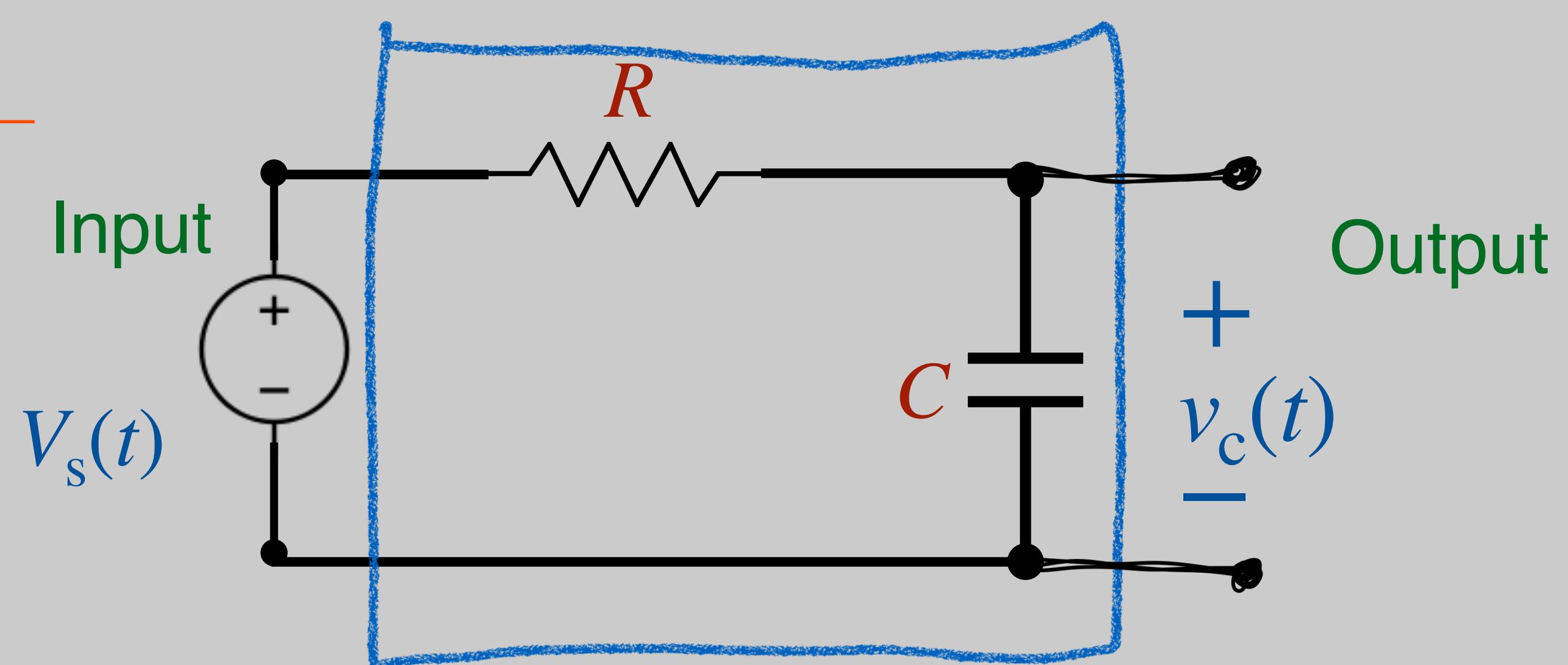

Example 1: Steady state


Set $V_s(t) = V_0$

$$\frac{dv_c}{dt} = 0$$


$$0 + \frac{1}{RC}v_c(t) = \frac{1}{RC}V_0 \Rightarrow v_c(t) = V_0$$

Natural Response of RC circuits

$$\frac{dv_c(t)}{dt} + \frac{1}{RC}v_c(t) = \frac{1}{RC}V_s(t)$$

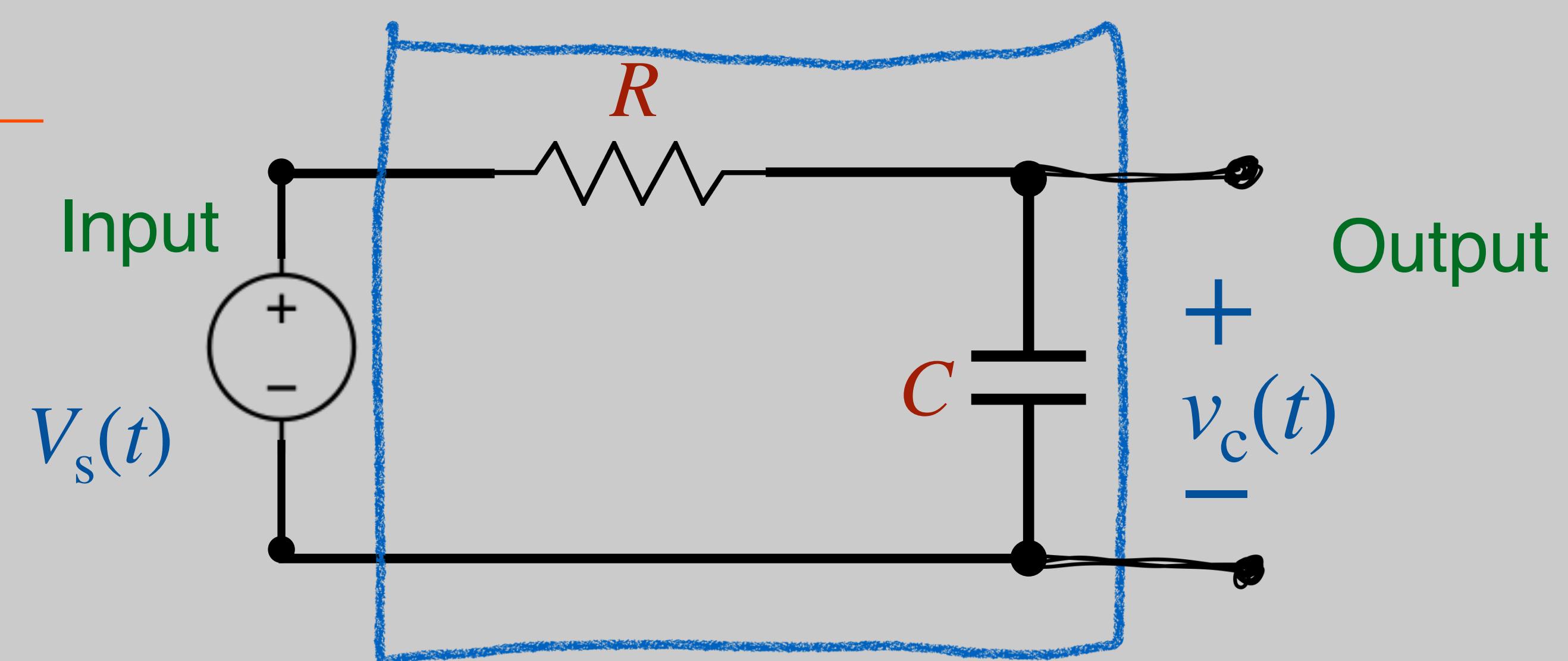

Example 2: Step-down

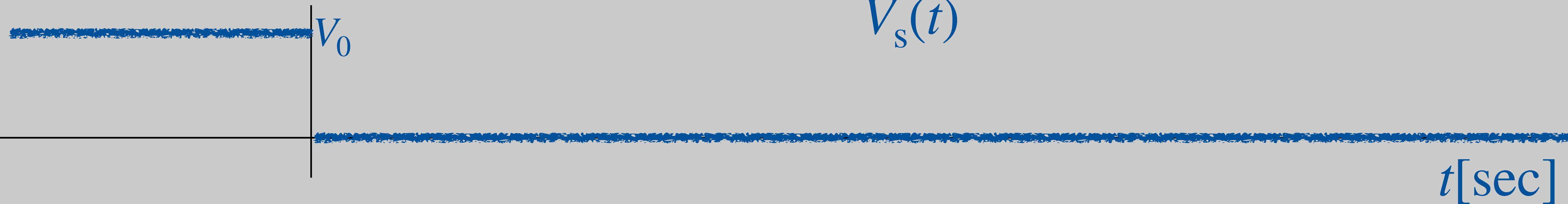

$$V_s(t) = 0 \quad | t > 0$$

$$v_c(0) = V_0$$

$$\Rightarrow \frac{dv_c(t)}{dt} + \frac{1}{RC}v_c(t) = 0$$


Natural Response of RC circuits

Homogeneous differential equation

$$V_s(t) = 0 \quad | t > 0$$

$$v_c(0) = V_0$$
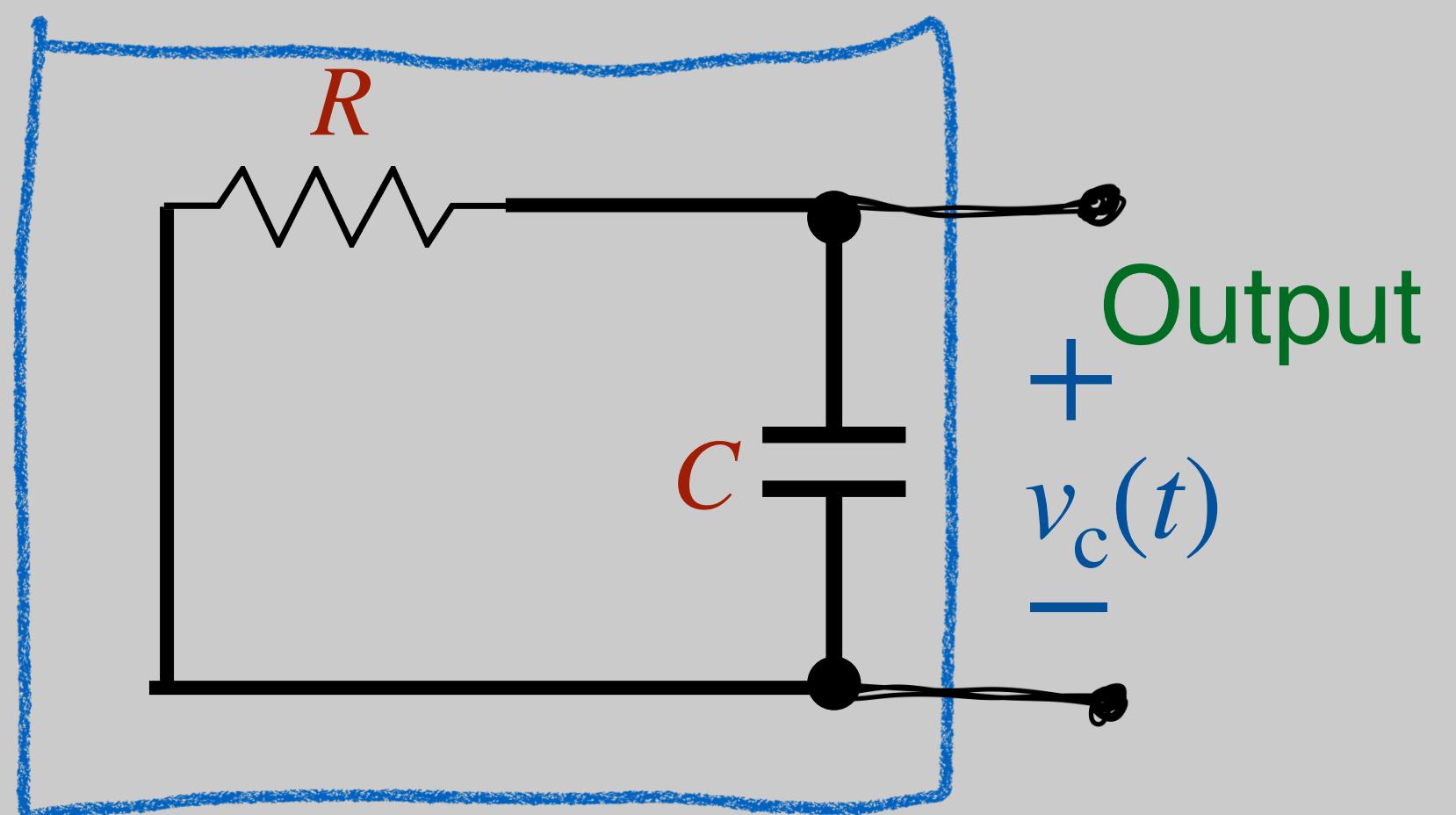
$$\frac{dv_c(t)}{dt} + \frac{1}{RC} v_c(t) = 0$$



Approach:

Guess a solution:

$$\cancel{A \cdot b e^{bt}} + \frac{1}{RC} \cancel{A e^{bt}} = 0 \quad \Rightarrow b = -\frac{1}{RC}$$

Find coeff from initial conditions:

$$v_c(0) = A e^0 = A = V_0 \quad \Rightarrow A = V_0$$


Natural Response of RC circuits

Homogeneous differential equation


$$V_s(t) = 0 \quad | t > 0$$

$$v_c(0) = V_0$$
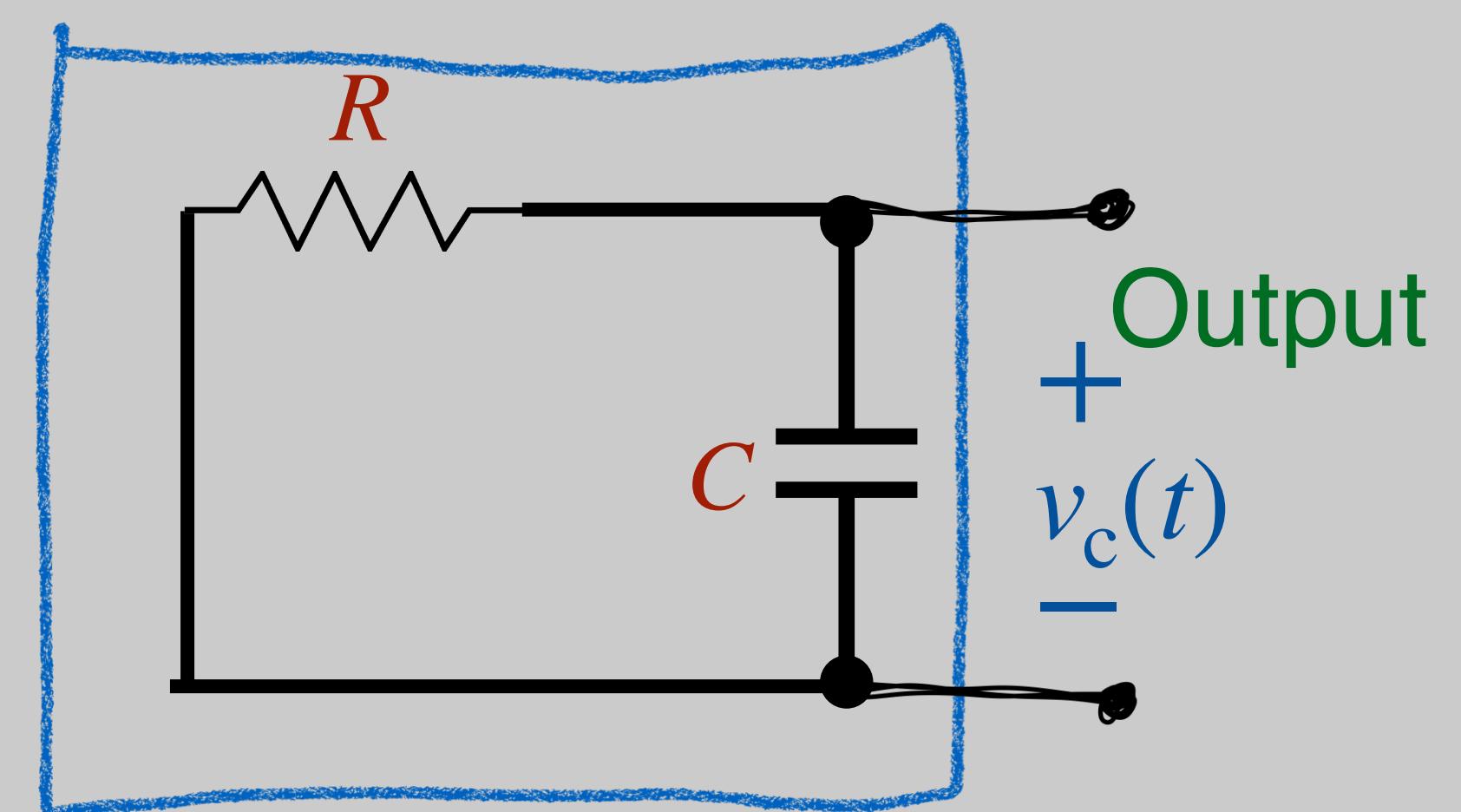
$$\frac{dv_c(t)}{dt} + \frac{1}{RC} v_c(t) = 0$$



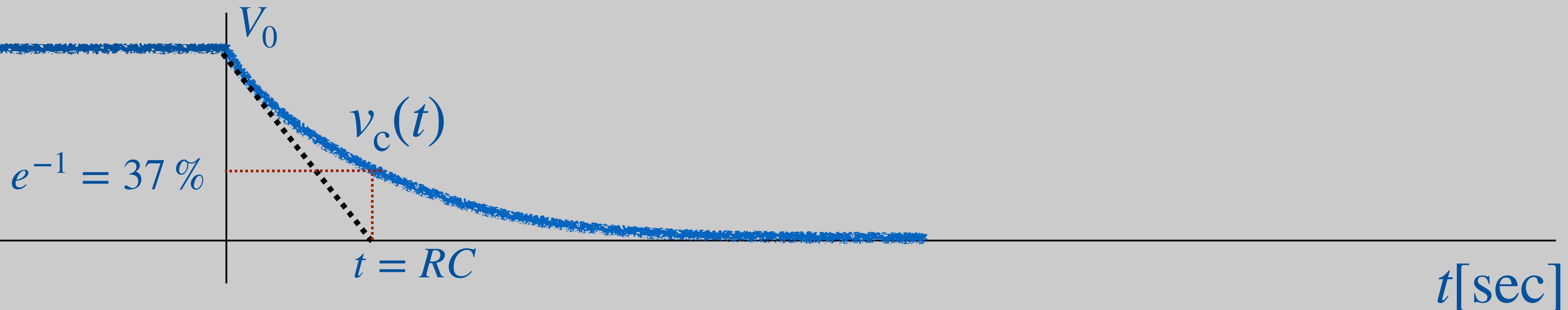Solution: $v_c(t) = V_0 e^{-\frac{t}{RC}}$




$$RC \rightarrow [\Omega][F] = \frac{[V]}{[A]} \frac{[C]}{[V]} = \frac{[C]}{[A]} = \frac{[C]}{[C]/[s]} = [s]$$


RC is discharge time-constant!

Step Response of RC circuits

$$\frac{dv_c(t)}{dt} + \frac{1}{RC}v_c(t) = \frac{1}{RC}V_s(t)$$

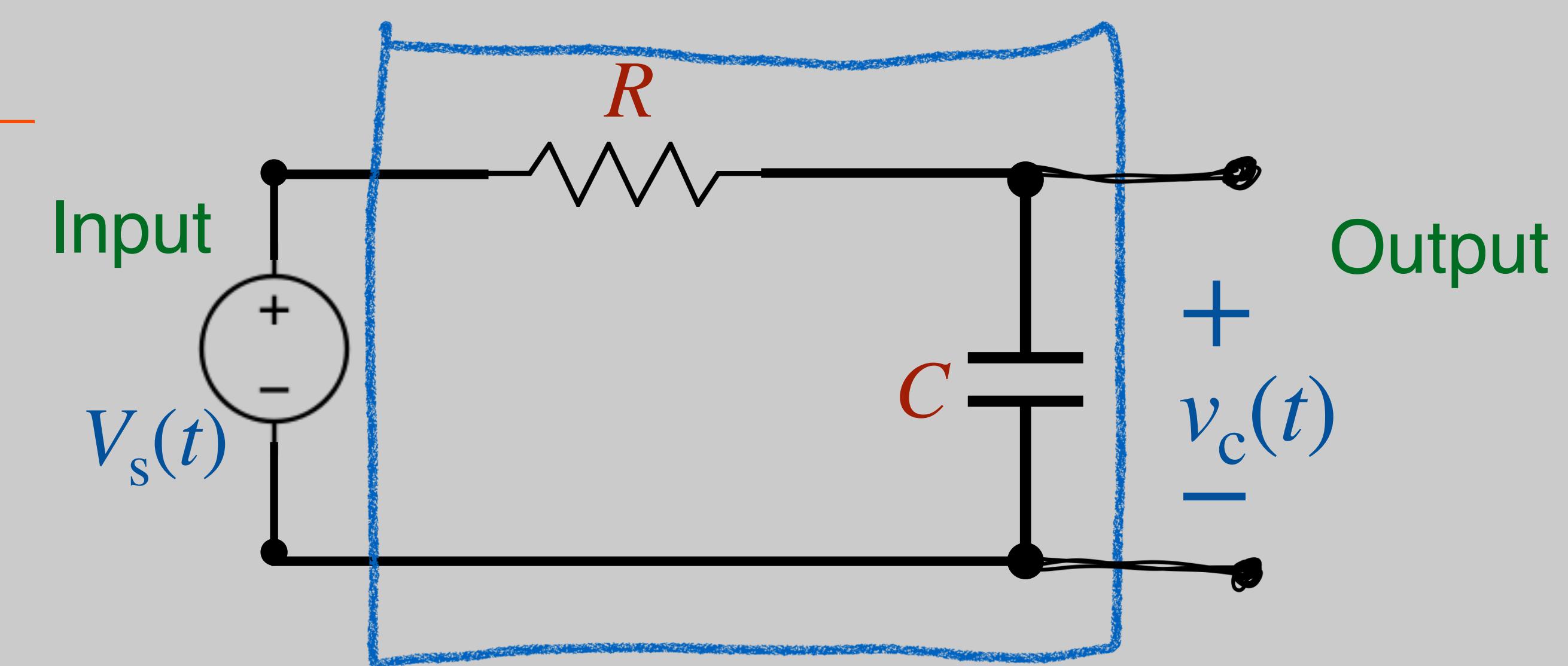

Example 3: Step-Response

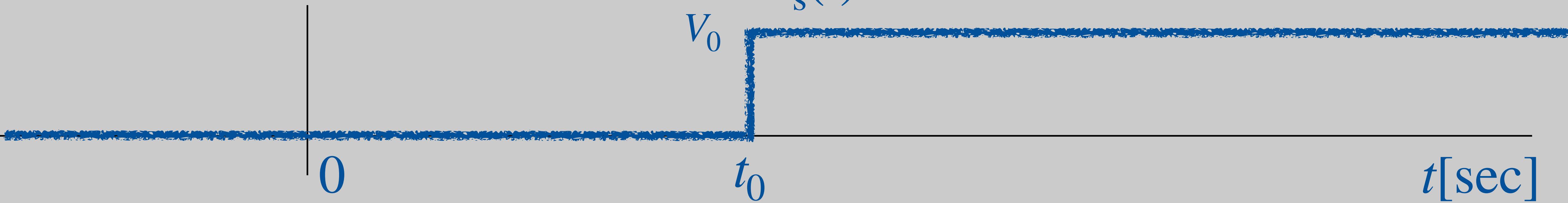

$$V_s(t) = V_0 \quad |t > t_0$$

$$v_c(t_0) = 0$$

$$\Rightarrow \frac{dv_c(t)}{dt} + \frac{1}{RC}v_c(t) = \frac{1}{RC}V_0$$

Step Response of RC circuits

Non-homogeneous Diff. Eq.

$$V_s(t) = V_0 \quad | t > t_0$$

$$v_c(t_0) = 0$$


$$\frac{dv_c(t)}{dt} + \frac{1}{RC} v_c(t) = \frac{1}{RC} V_0$$

Approach:

From Note 1: $v_c(t) = v_h(t) + v_p(t)$

Homogeneous \rightarrow Particular

Guess: $v_c = K e^{-\frac{t}{RC}} + B$

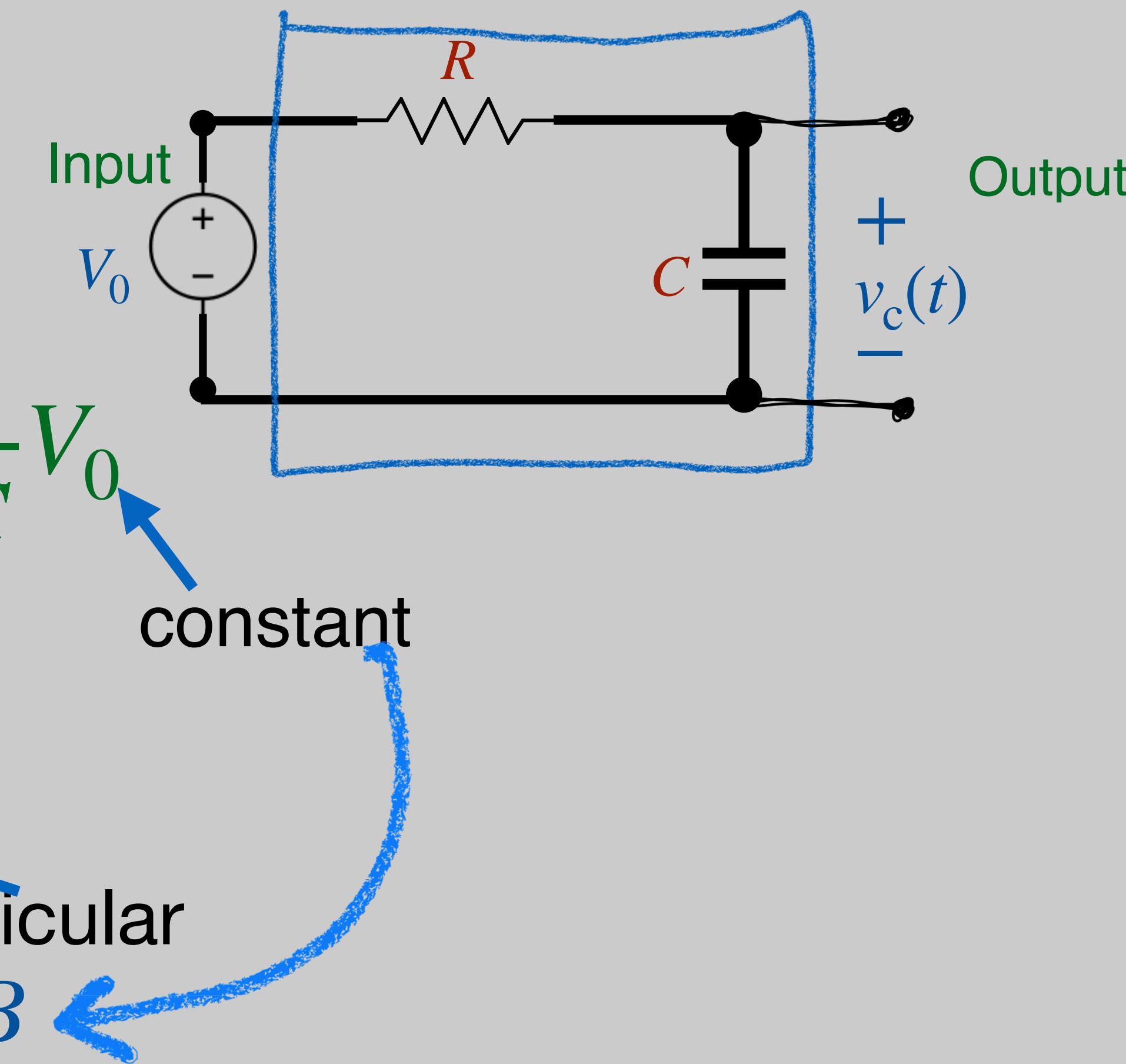


Step Response of RC circuits

Non-homogeneous Diff. Eq.

$$V_s(t) = V_0 \quad | t > t_0$$

$$v_c(t_0) = 0$$
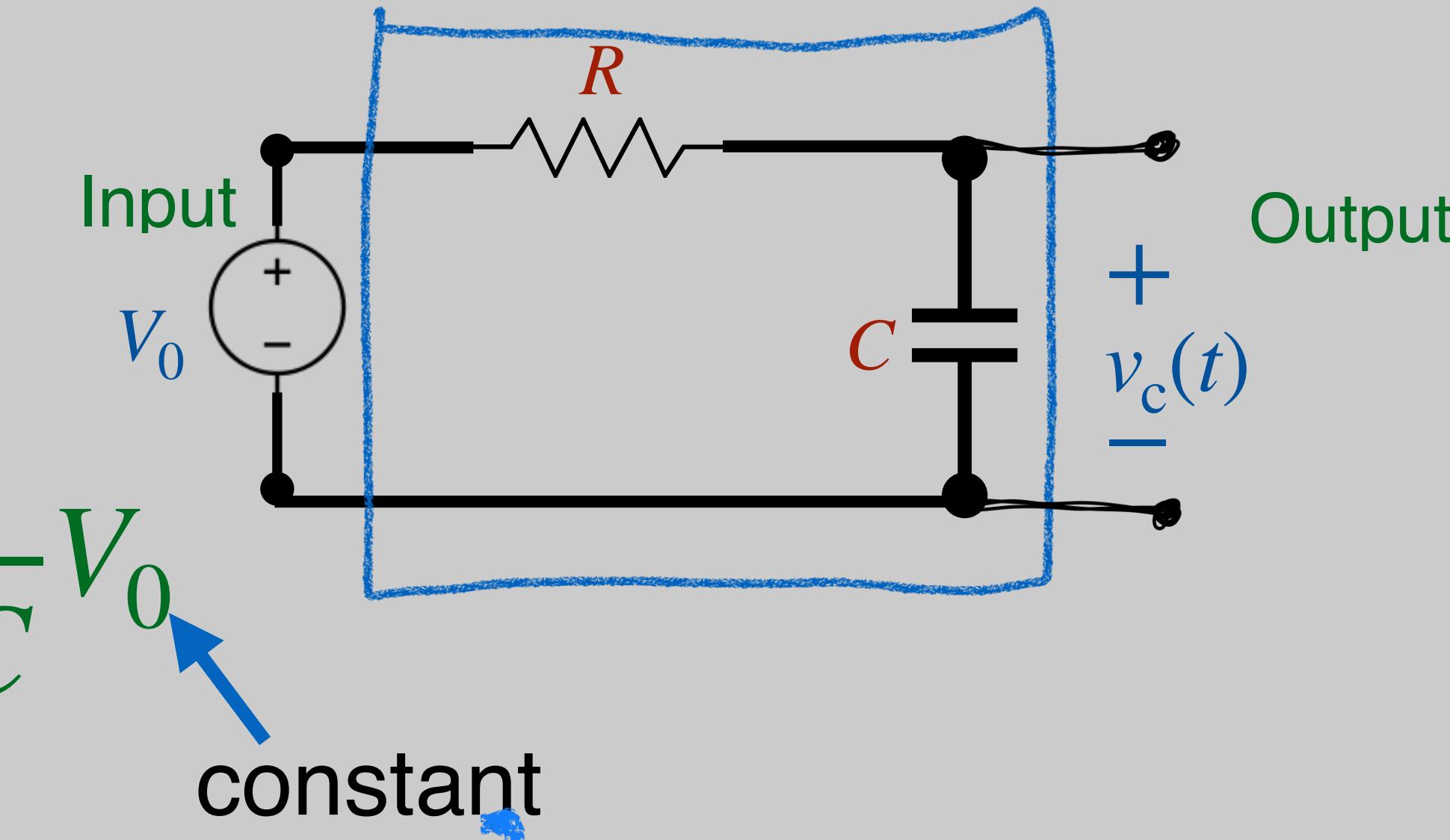
$$\frac{dv_c(t)}{dt} + \frac{1}{RC} v_c(t) = \frac{1}{RC} V_0$$



Approach:

From Note 1: $v_c(t) = v_h(t) + v_p(t)$

Homogeneous \rightarrow Particular

Guess: $v_c = K e^{-\frac{t}{RC}} + B$

Plug in: $\frac{d}{dt}(v_h(t) + v_p(t)) + \frac{1}{RC}(v_h(t) + v_p(t)) = \frac{1}{RC} V_0$

$$-\frac{1}{RC} K e^{-\frac{t}{RC}} + \frac{1}{RC} K e^{-\frac{t}{RC}} + \frac{1}{RC} B = \frac{1}{RC} V_0 \Rightarrow B = V_0$$


Step Response of RC circuits

Non-homogeneous Diff. Eq.

$$V_s(t) = V_0 \quad | t > t_0$$

$$v_c(t_0) = 0$$
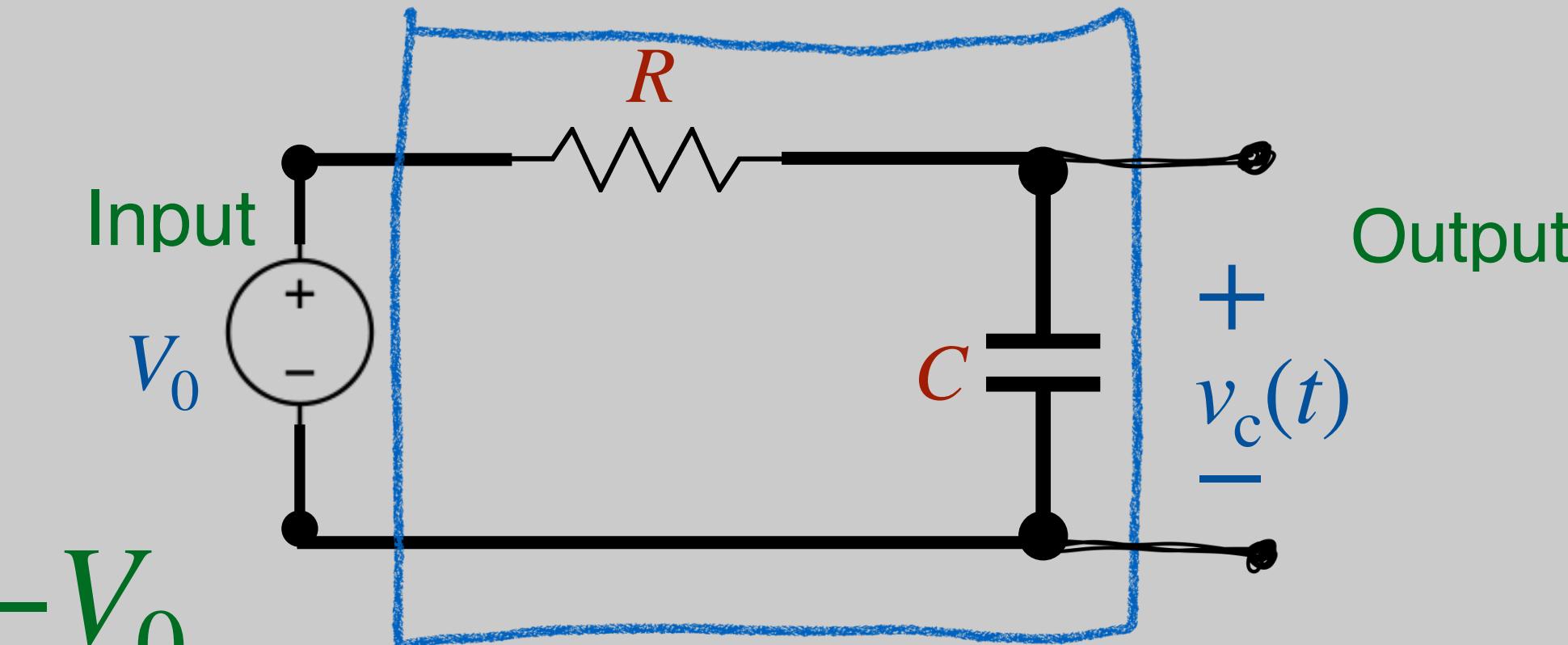
$$\frac{dv_c(t)}{dt} + \frac{1}{RC} v_c(t) = \frac{1}{RC} V_0$$



Initial conditions:

$$v_c = K e^{-\frac{t}{RC}} + V_0$$

$$v_c(t_0) = K e^{-\frac{t_0}{RC}} + V_0 = 0 \quad \Rightarrow K = -V_0 \cdot e^{\frac{t_0}{RC}}$$

$$v_c = -V_0 \cdot e^{\frac{t_0}{RC}} \cdot e^{-\frac{t}{RC}} + V_0 = -V_0 \cdot e^{-\frac{t-t_0}{RC}} + V_0$$

$$= V_0 \left(1 - e^{-\frac{t-t_0}{RC}} \right)$$


Step Response of RC circuits

Non-homogeneous Diff. Eq.

$$V_s(t) = V_0 \quad | t > t_0$$


$$v_c(t_0) = 0$$
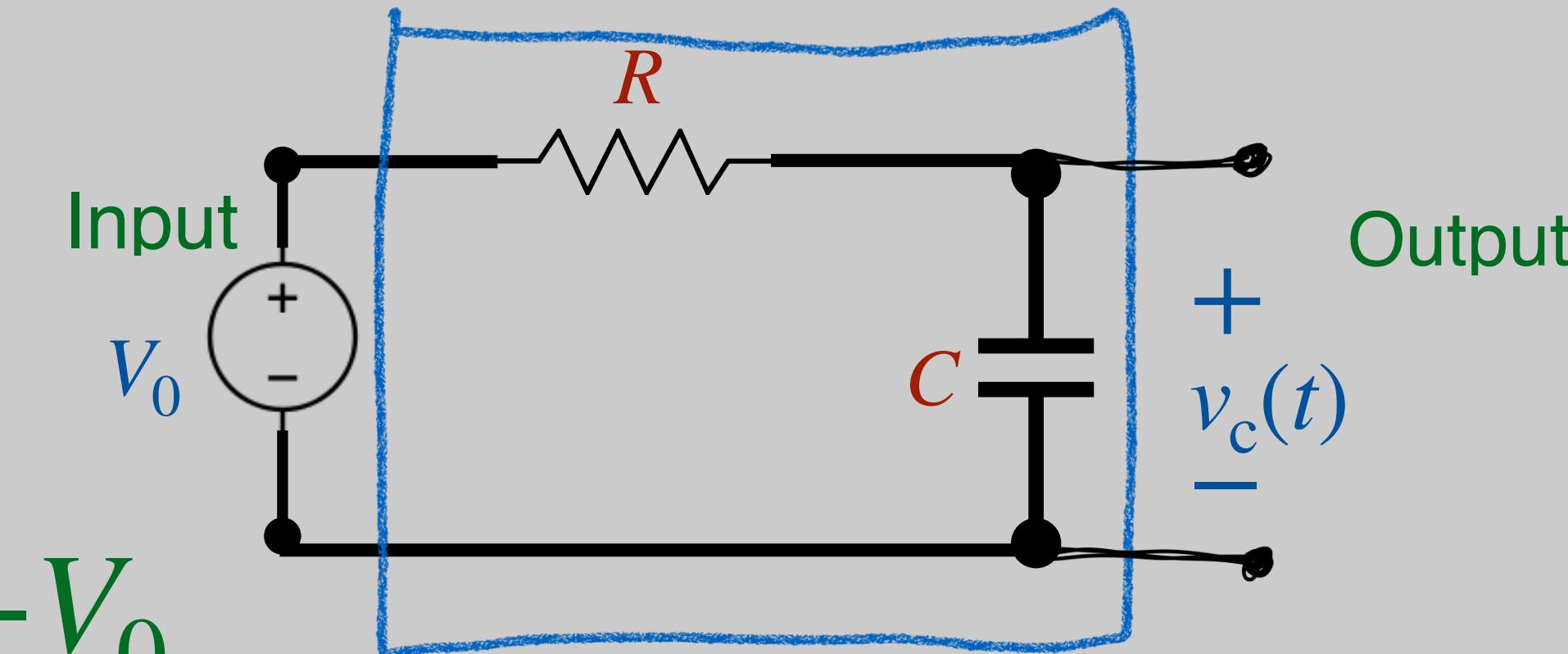
$$\frac{dv_c(t)}{dt} + \frac{1}{RC} v_c(t) = \frac{1}{RC} V_0$$



Solution:


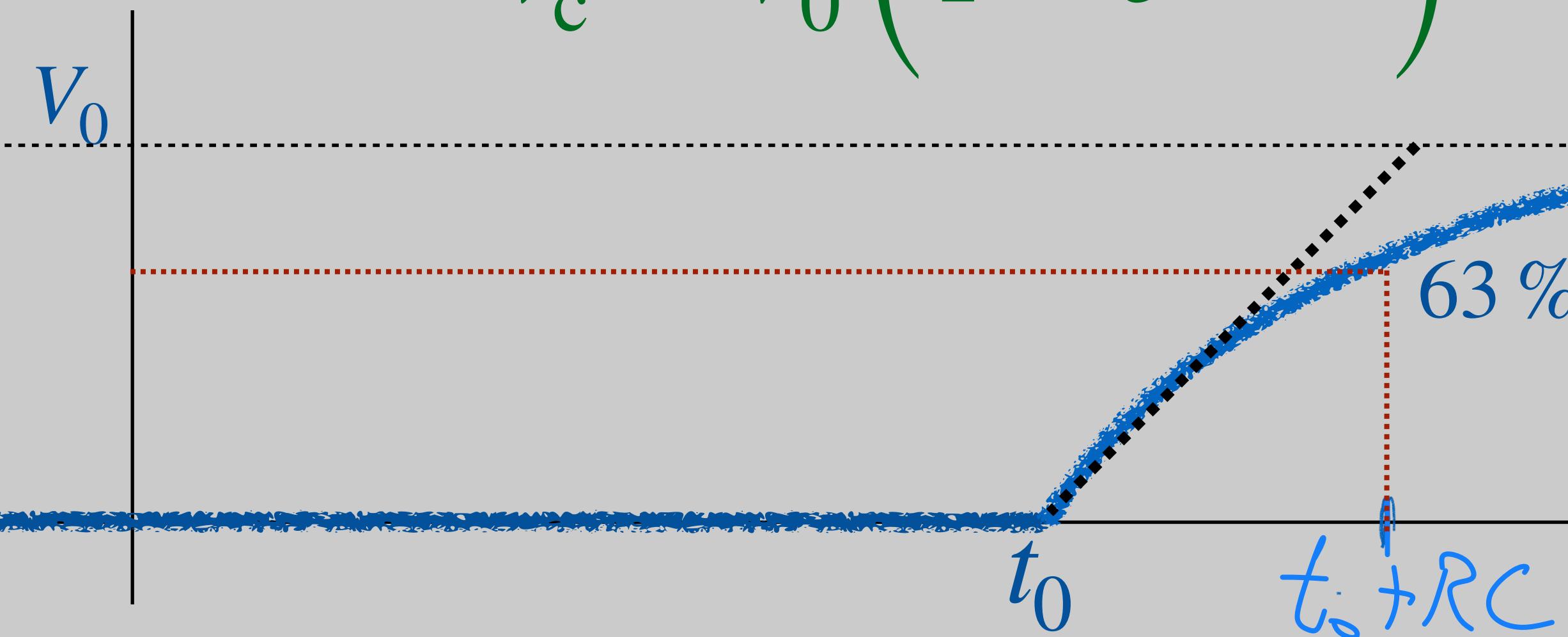
$$v_c = V_0 \left(1 - e^{-\frac{t-t_0}{RC}} \right)$$




Pulse Response of RC circuits

Example 4: Pulse Response:

$$V_s(t) = p(t)$$

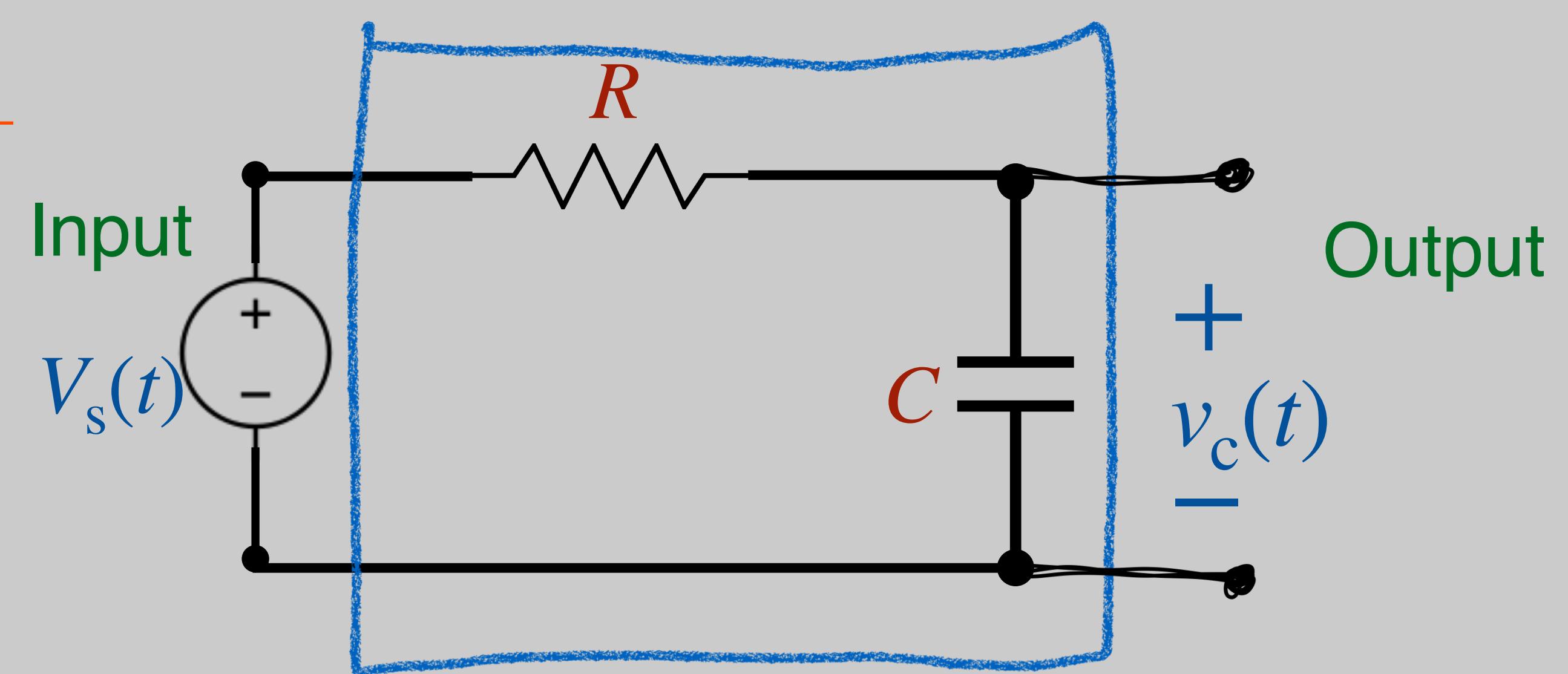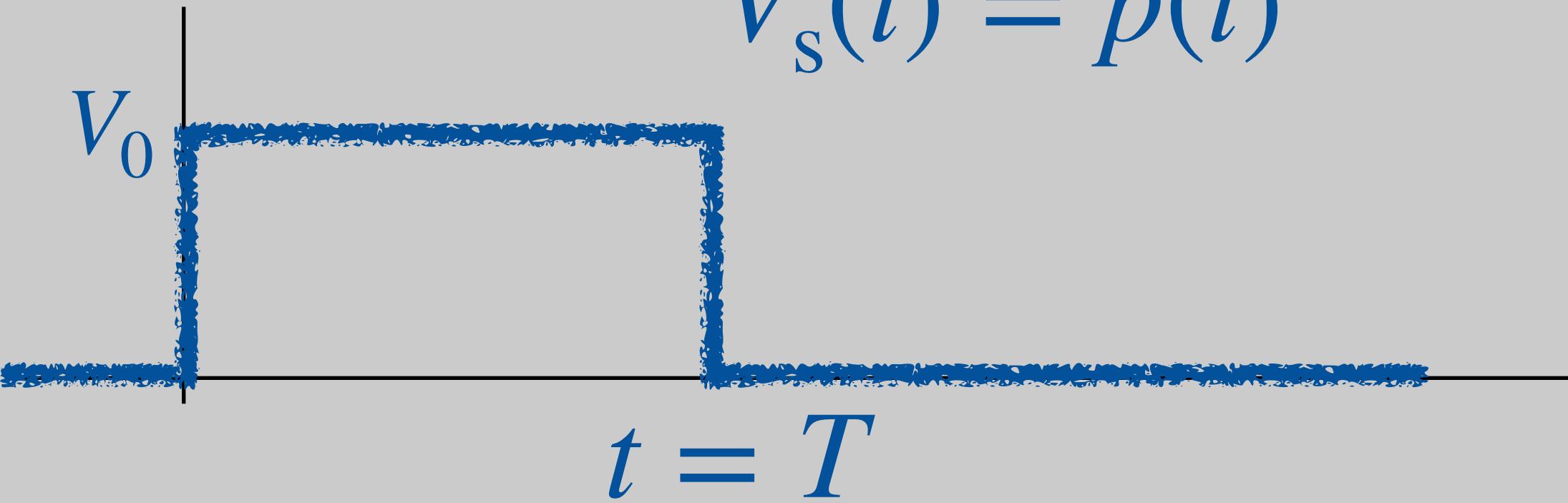



Q: approach? A: Super-position!

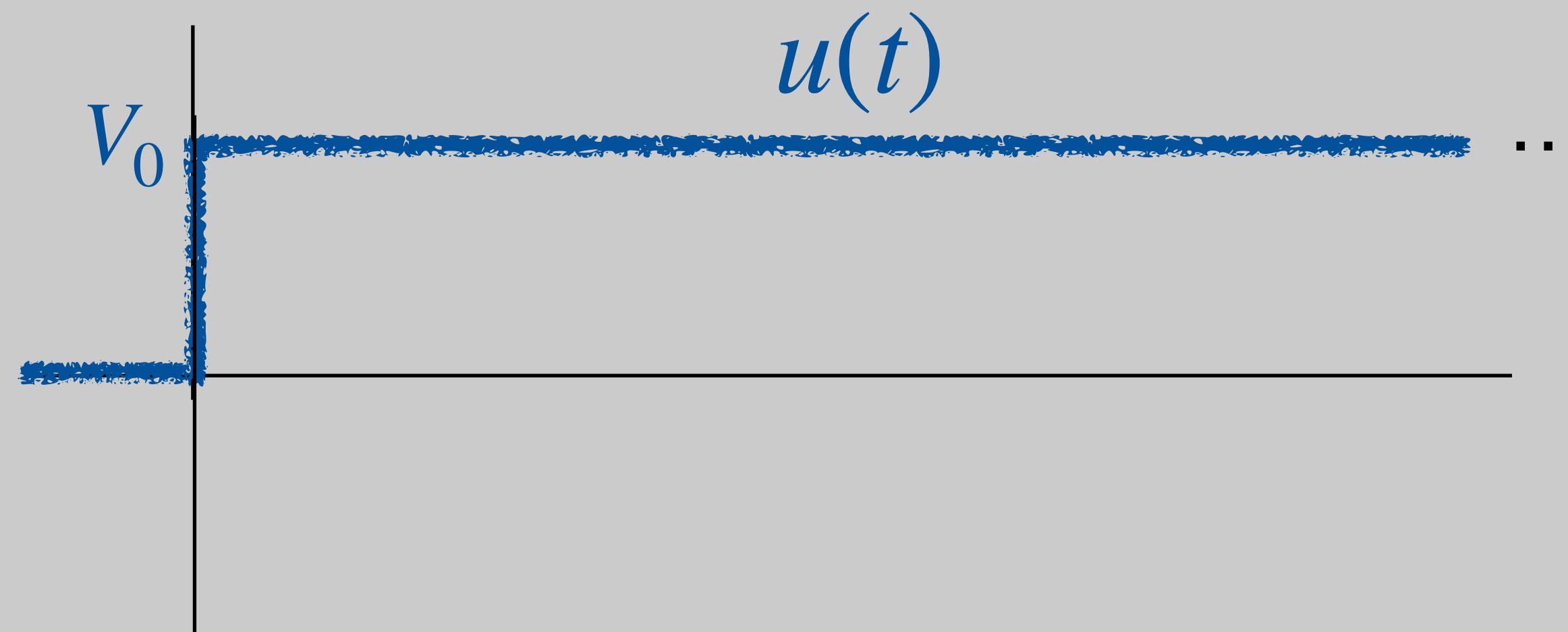


Pulse Response of RC circuits

Example 4: Pulse Response:

$$V_s(t) = p(t)$$

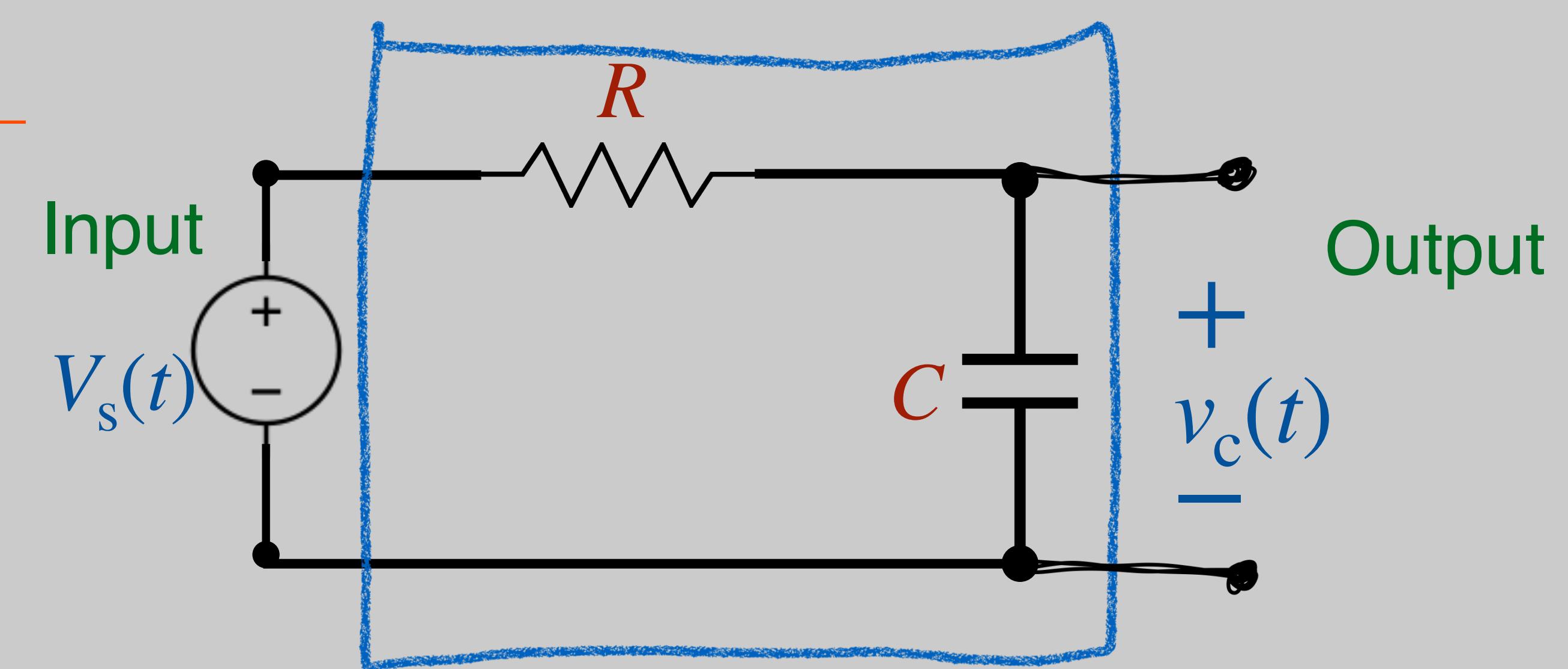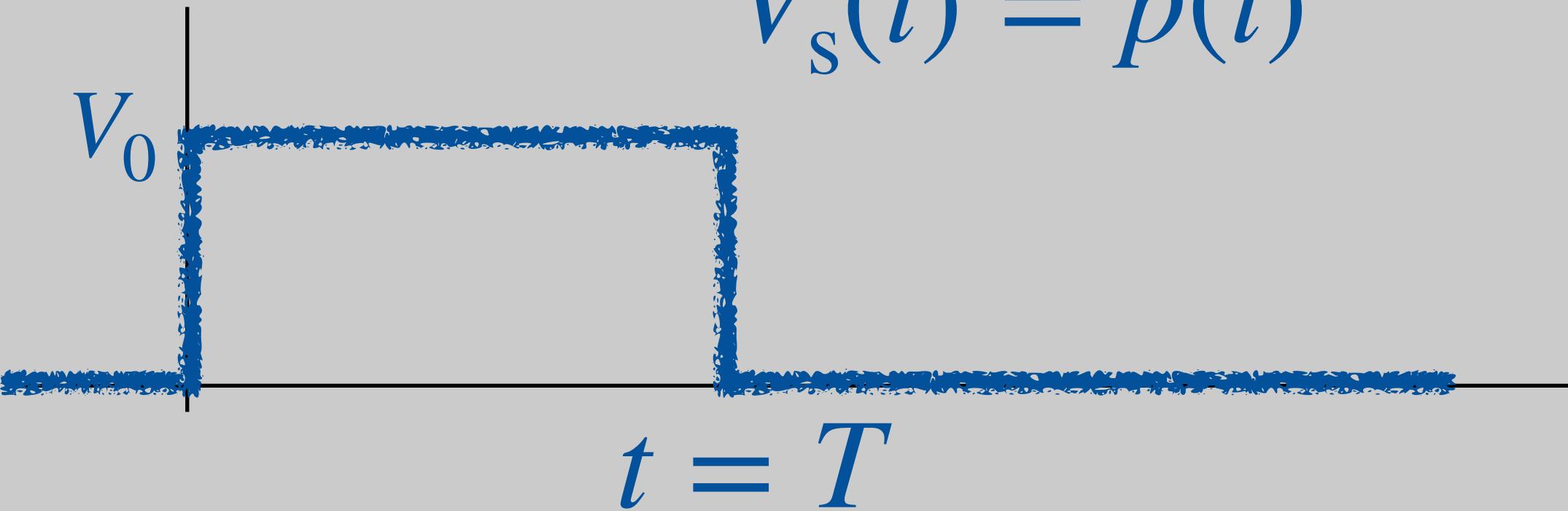


Q: approach? A: Super-position!

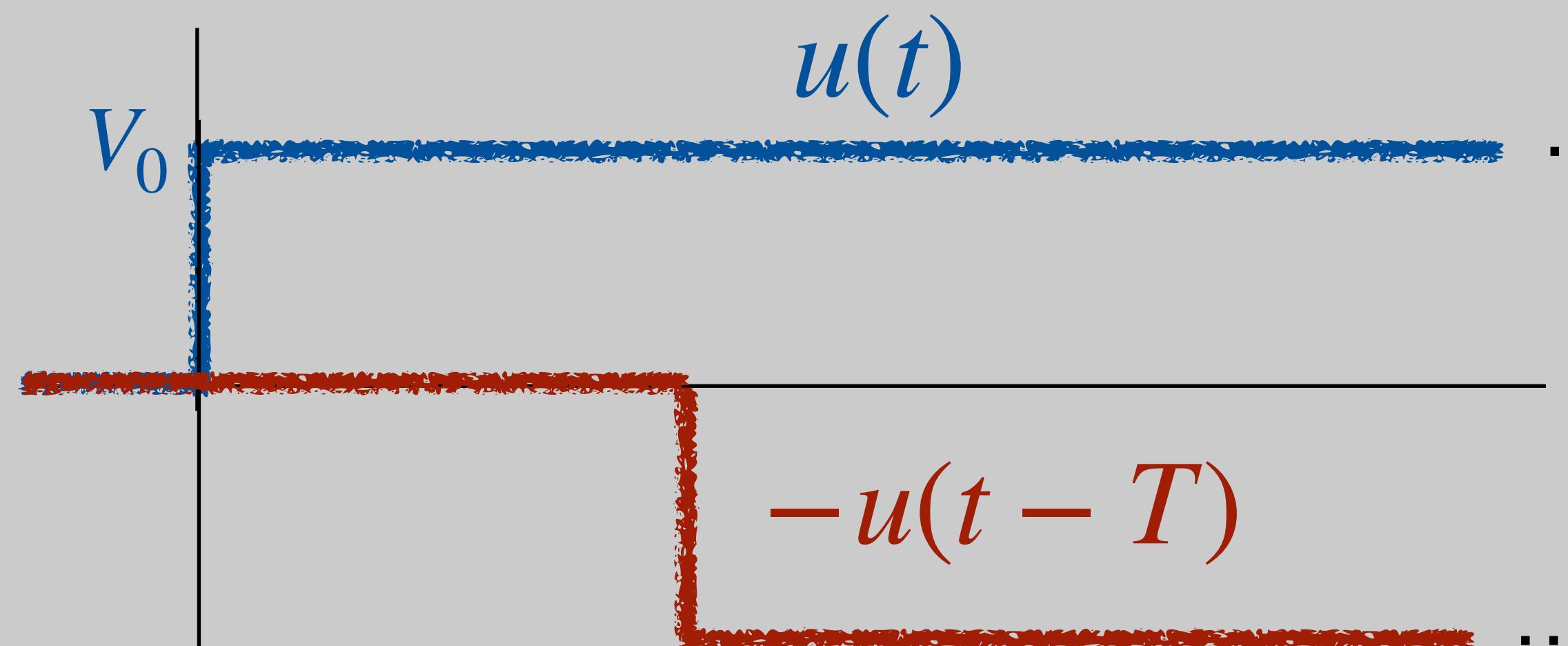


$$p(t) = u(t) - u(t - T)$$

Solve for $u(t)$, solve for $-u(t - T)$
add the results!

Pulse Response of RC circuits

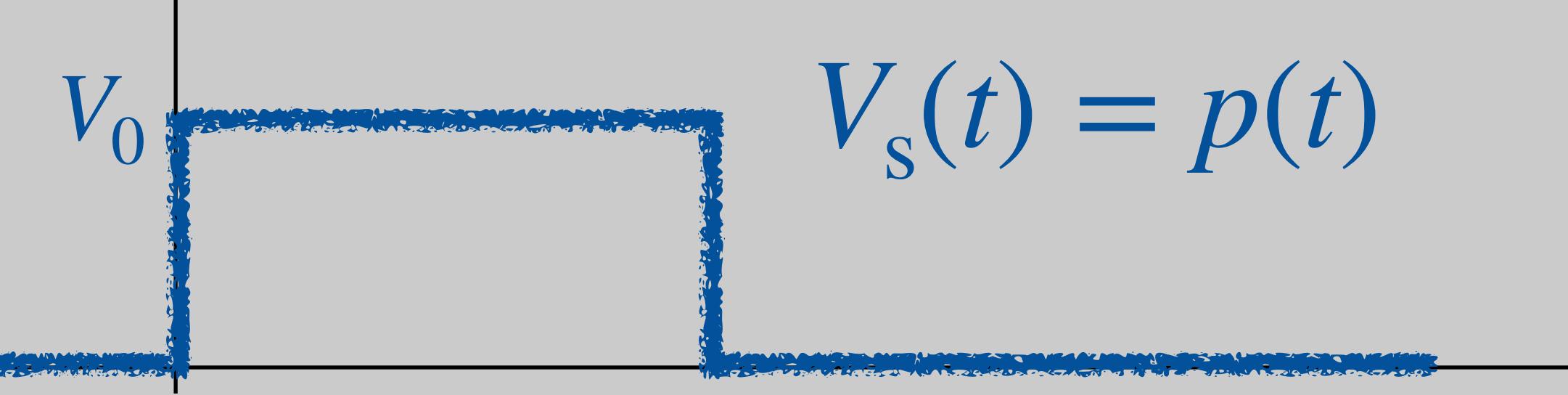


$$p(t) = u(t) - u(t - T)$$

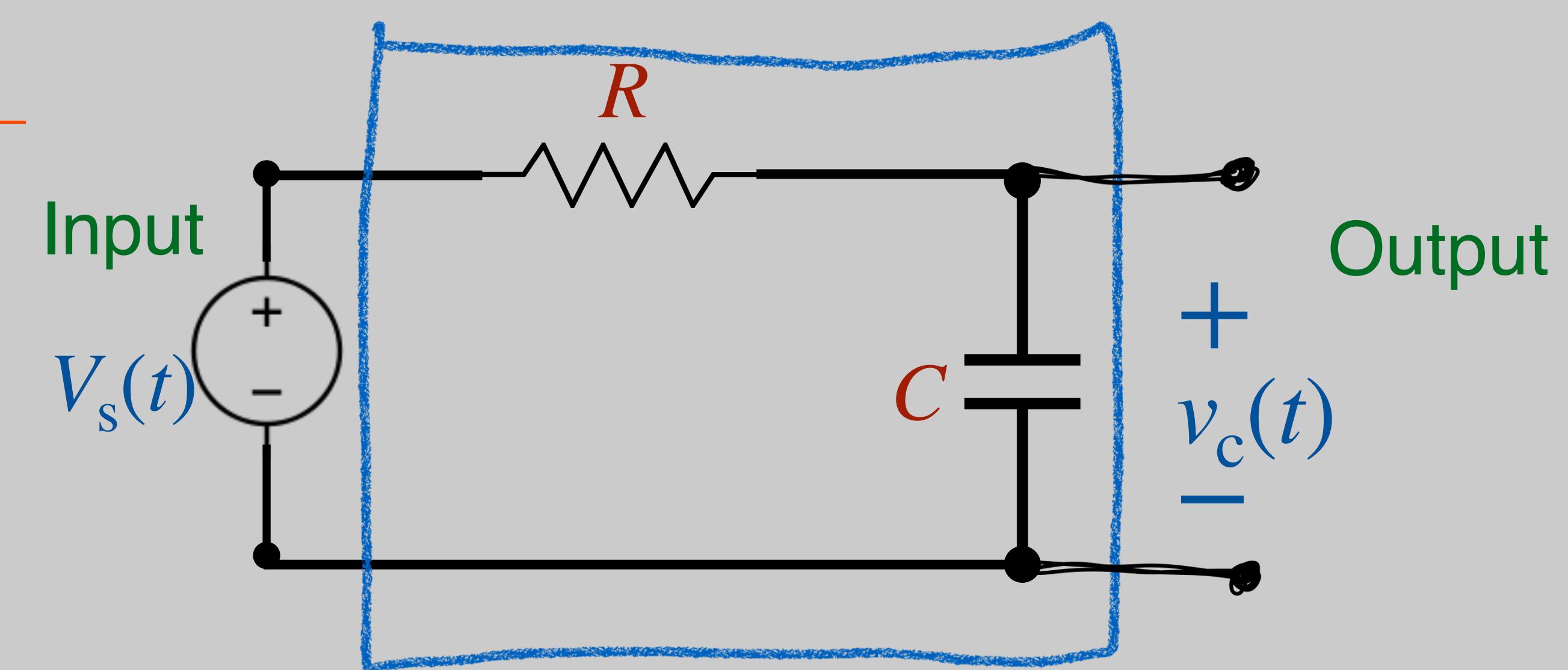


From example 3:


$$V_s(t) = u(t) \Rightarrow v_c = V_0 \left(1 - e^{-\frac{t}{RC}} \right) \quad | t > 0$$

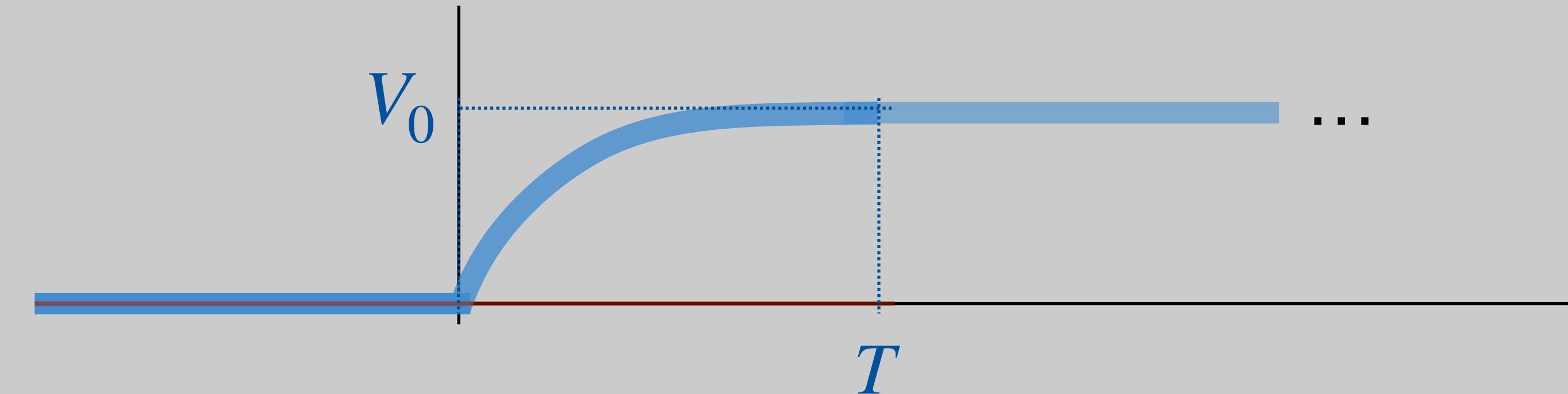

Pulse Response of RC circuits

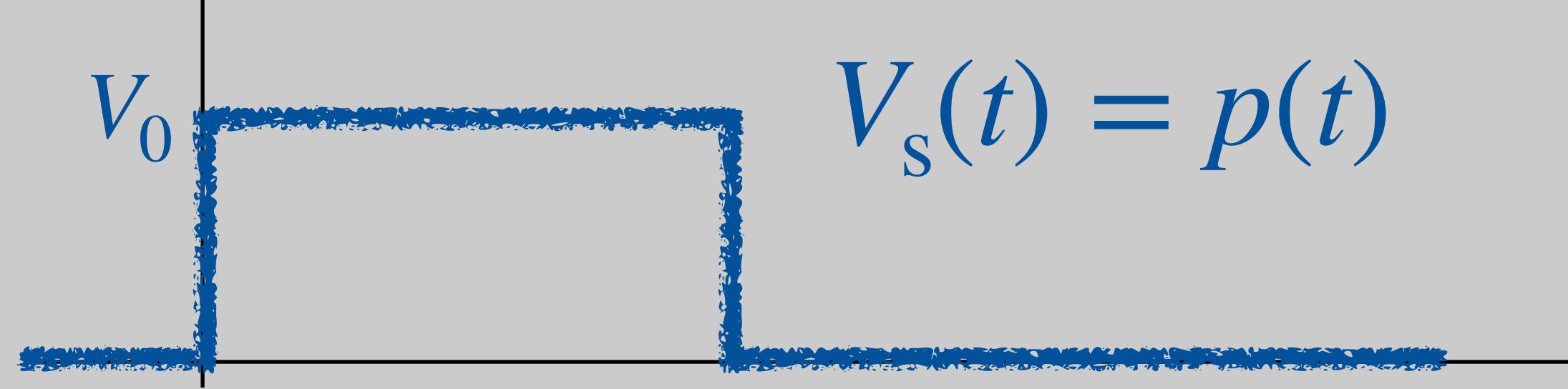


$$p(t) = u(t) - u(t - T)$$

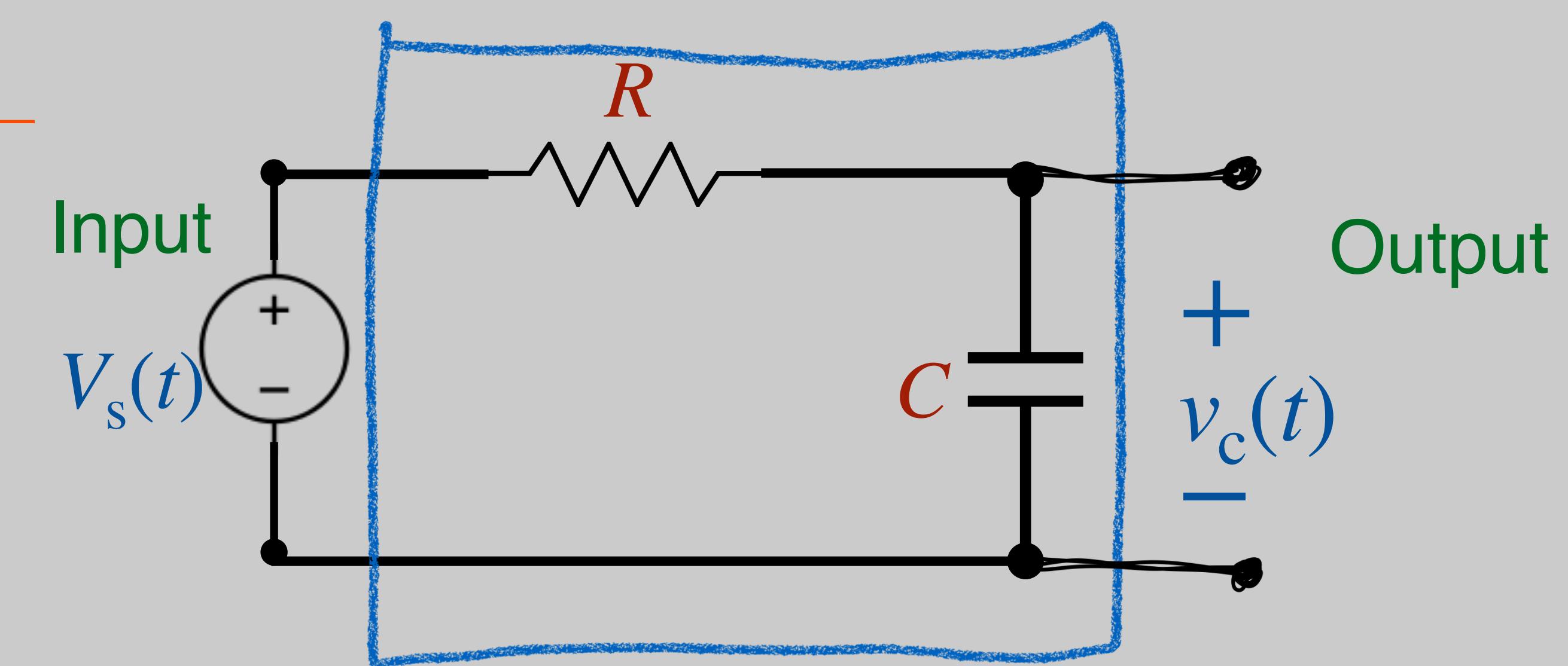


From example 3:

$$V_s(t) = u(t) \Rightarrow v_c = V_0 \left(1 - e^{-\frac{t}{RC}} \right) \quad | t > 0$$


$$V_s(t) = u(t - T) \Rightarrow v_c = V_0 \left(1 - e^{-\frac{t-T}{RC}} \right) \quad | t > T$$

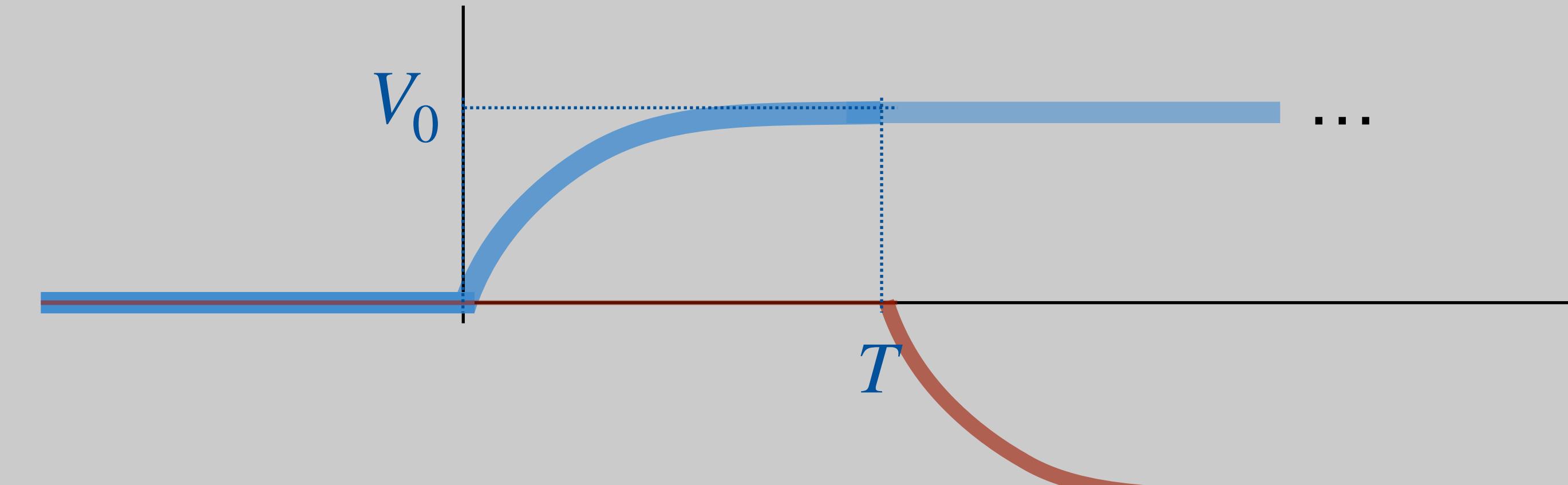

Pulse Response of RC circuits

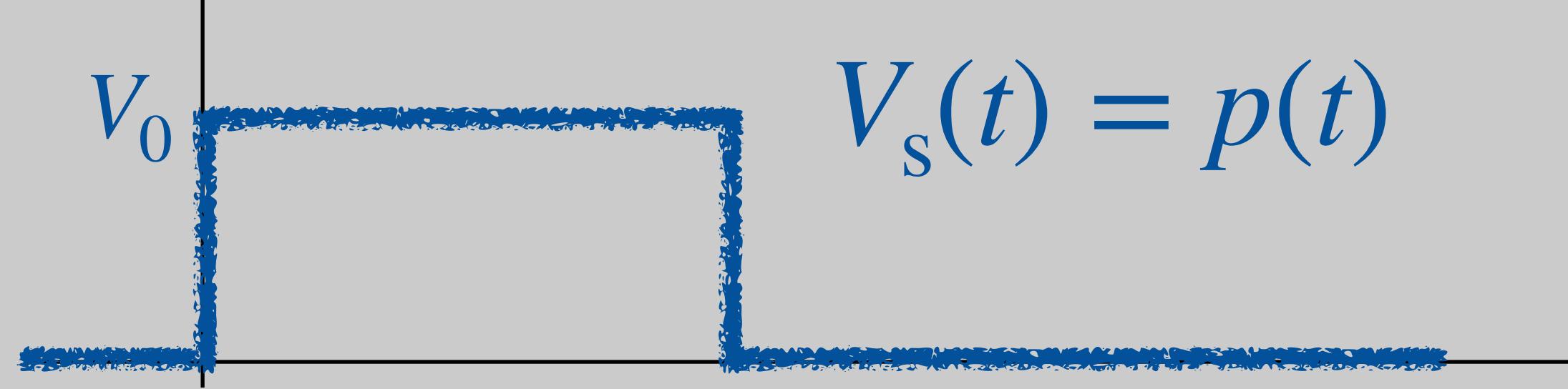

$$p(t) = u(t) - u(t - T)$$

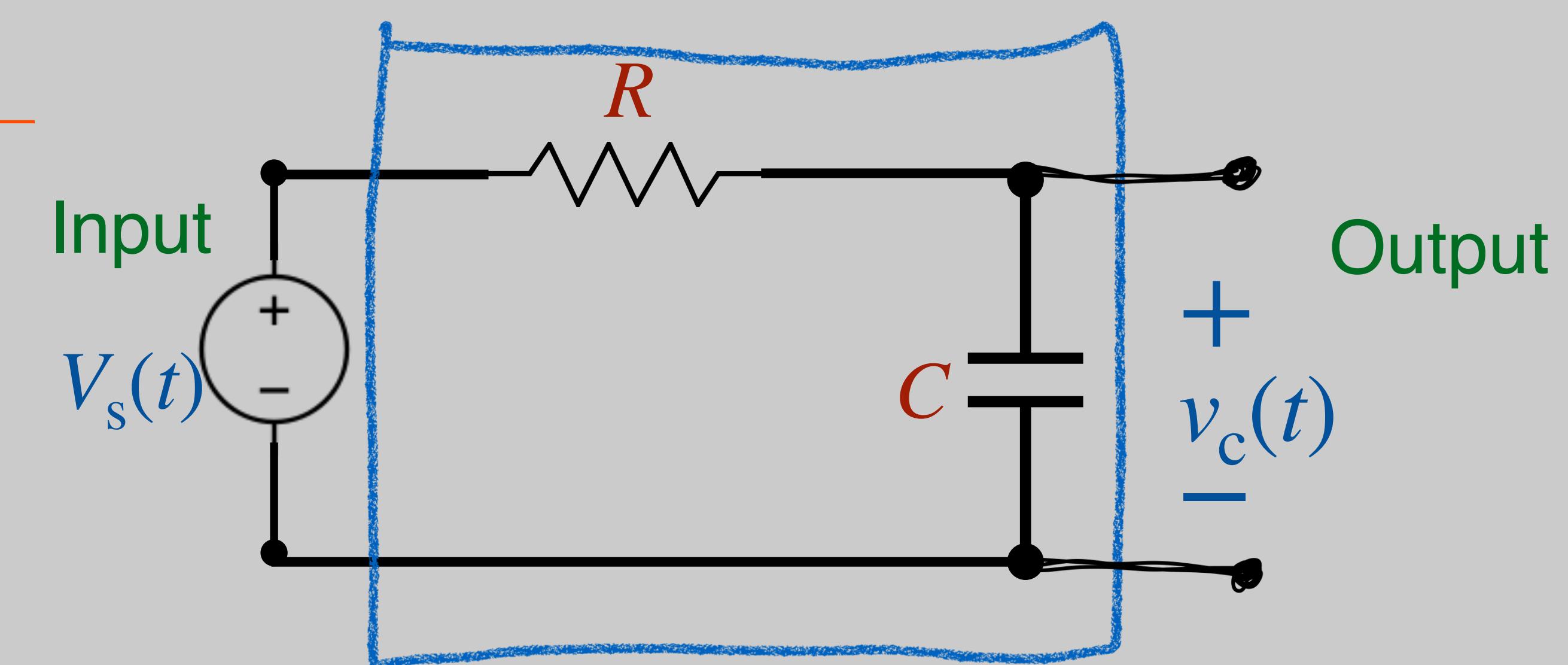


From example 3:

$$V_s(t) = u(t) \Rightarrow v_c = V_0 \left(1 - e^{-\frac{t}{RC}} \right) \quad | t > 0$$

$$V_s(t) = u(t - T) \Rightarrow v_c = V_0 \left(1 - e^{-\frac{t-T}{RC}} \right) \quad | t > T$$

$$V_s(t) = p(t)$$

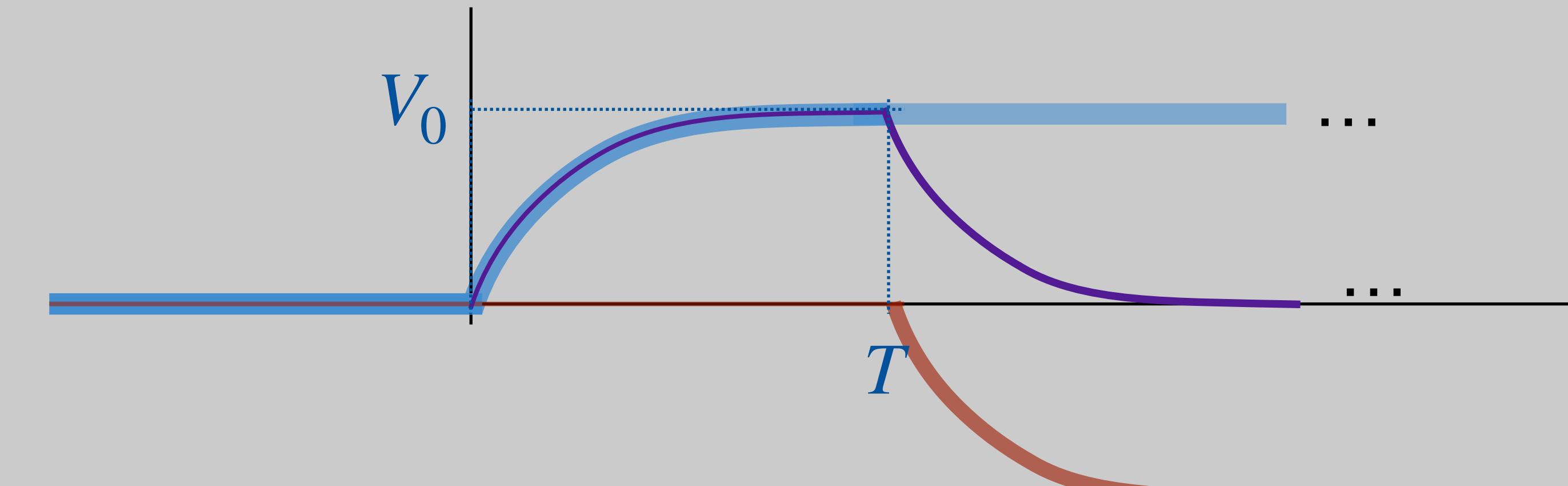


Pulse Response of RC circuits

$$V_s(t) = u(t) \Rightarrow v_c = V_0 \left(1 - e^{-\frac{t}{RC}} \right) \quad | t > 0$$


$$V_s(t) = u(t - T) \Rightarrow v_c = V_0 \left(1 - e^{-\frac{t-T}{RC}} \right) \quad | t > T$$

$$V_s(t) = p(t)$$

“Fast” Circuit $T \gg RC$


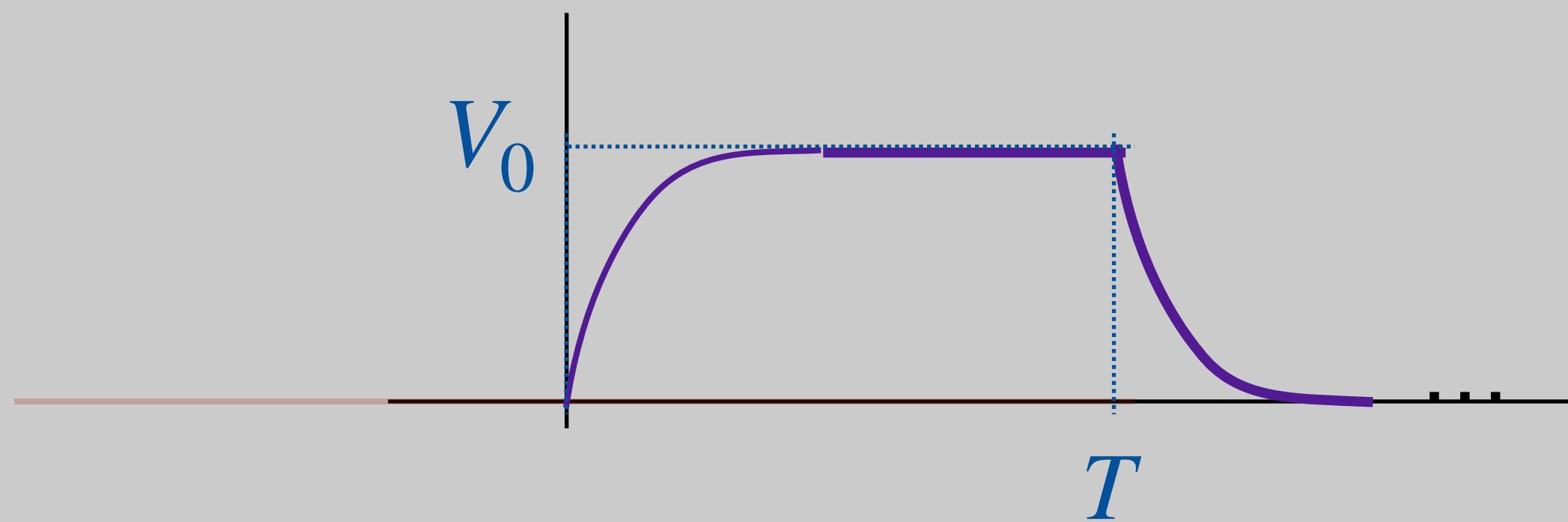


Slow Circuit $T \ll RC$

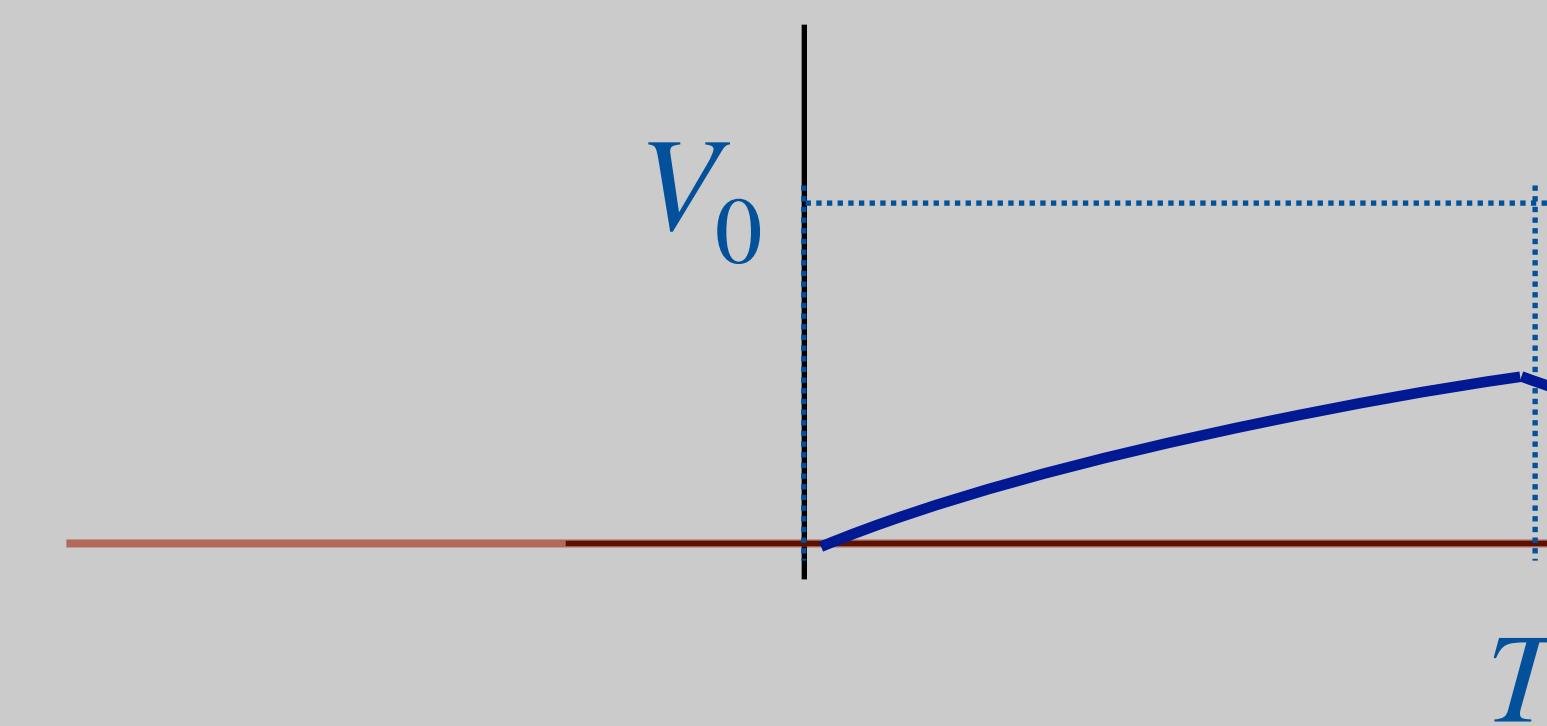


Pulse Response of RC circuits

Pulse train Response:

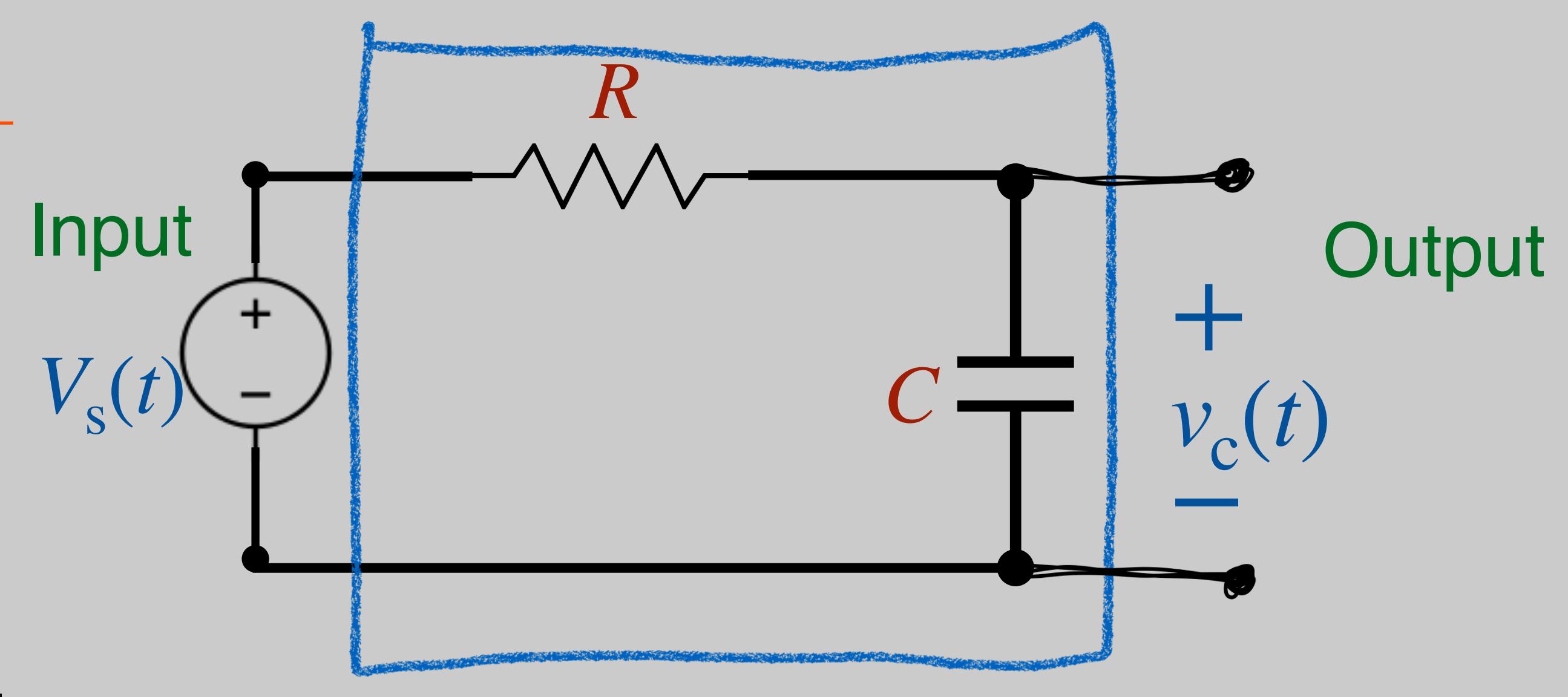
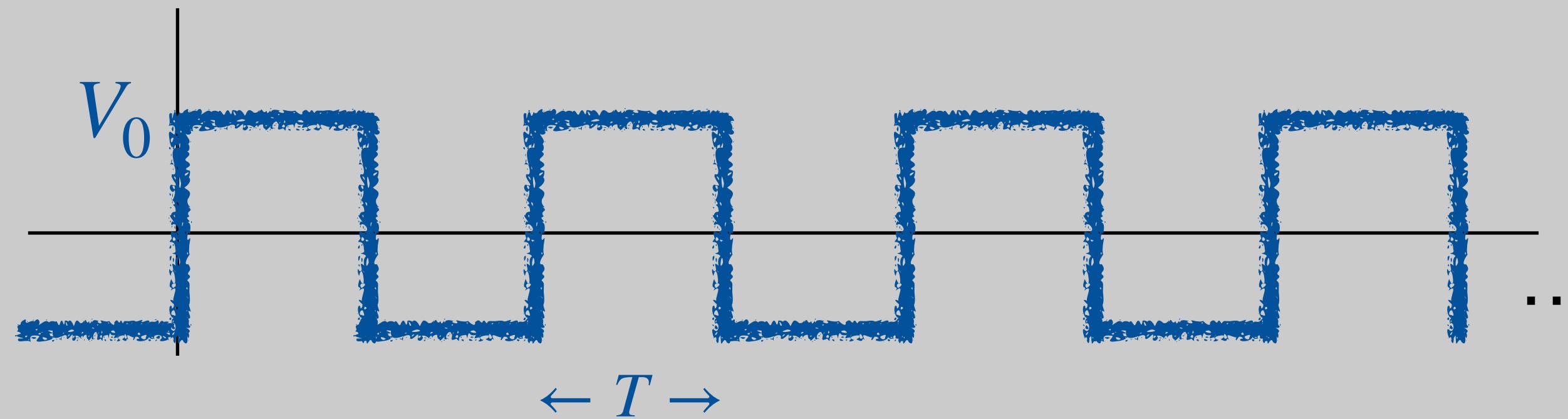


Slow switching - high magnitude

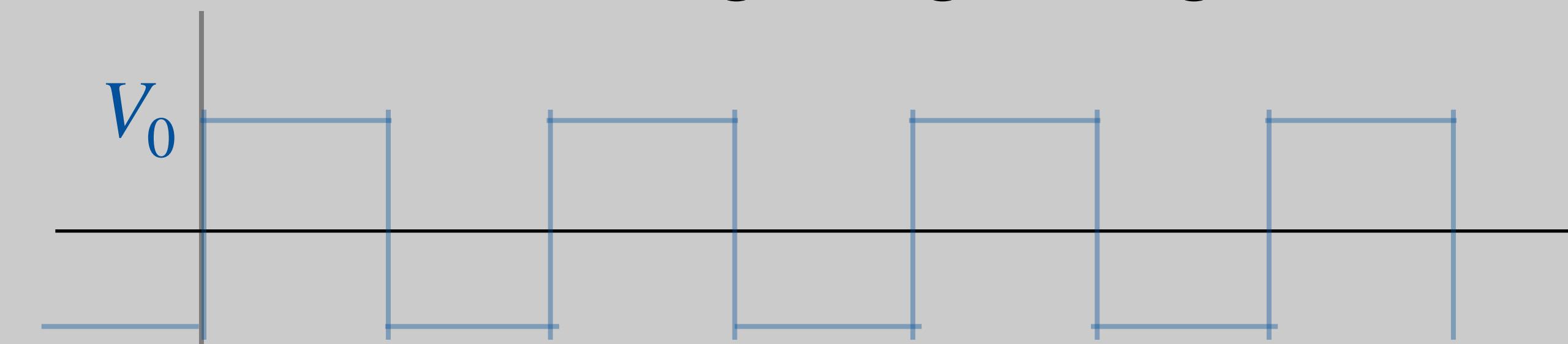


Pulse Response of RC circuits

Pulse train Response:

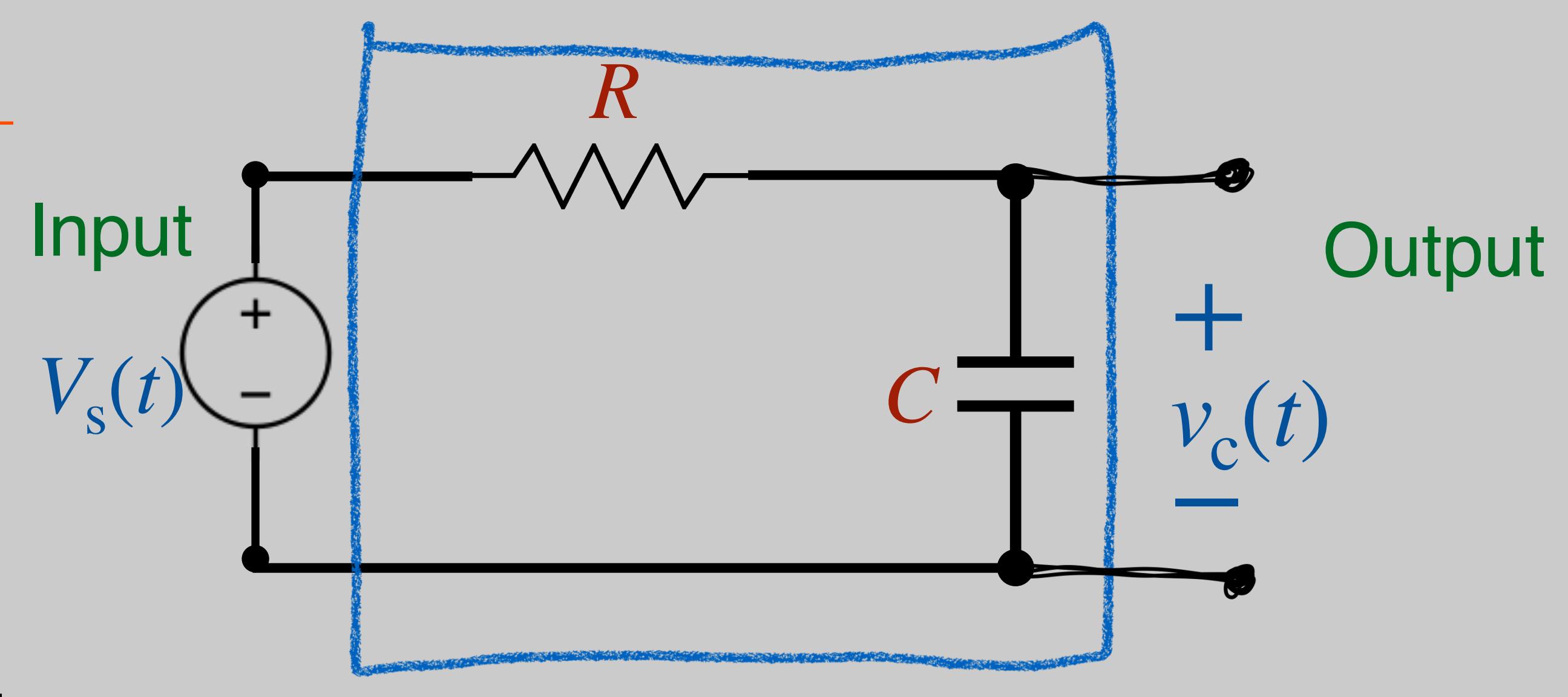
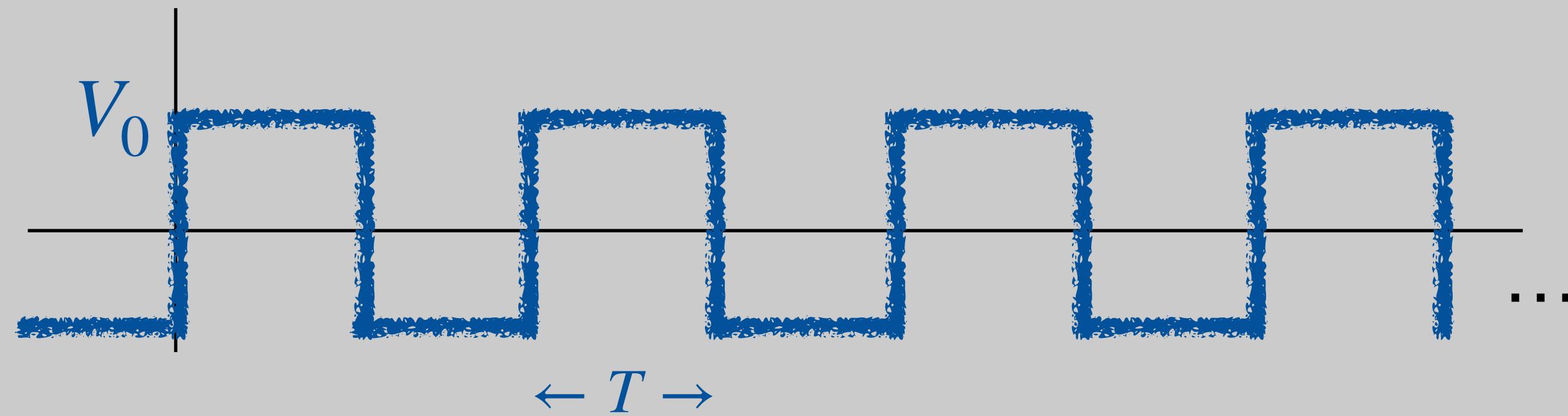


Slow switching - high magnitude

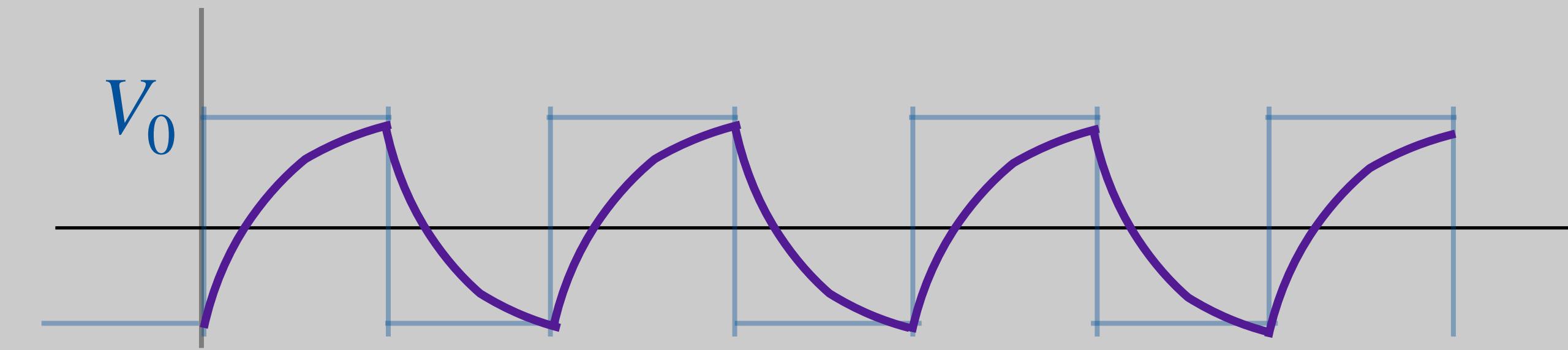


Pulse Response of RC circuits


Pulse train Response:

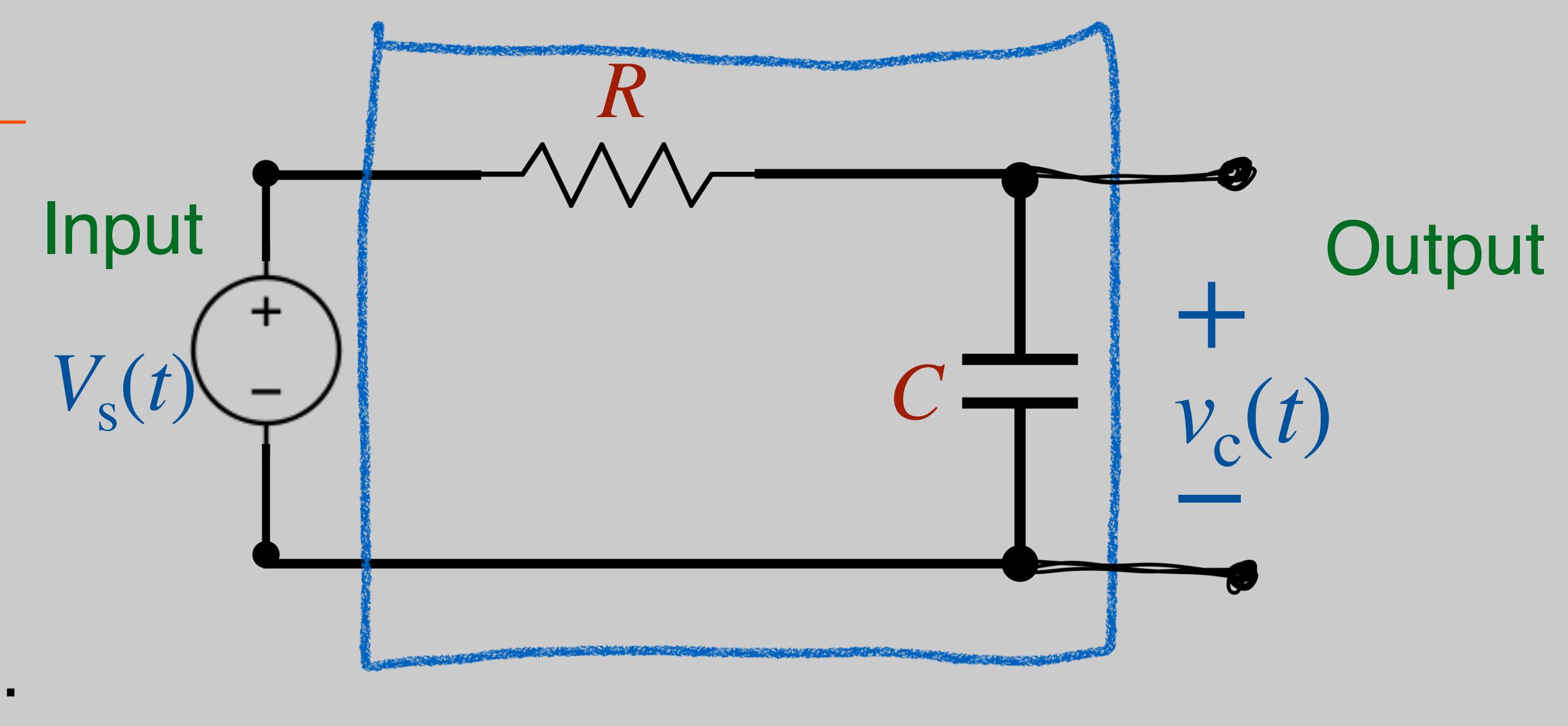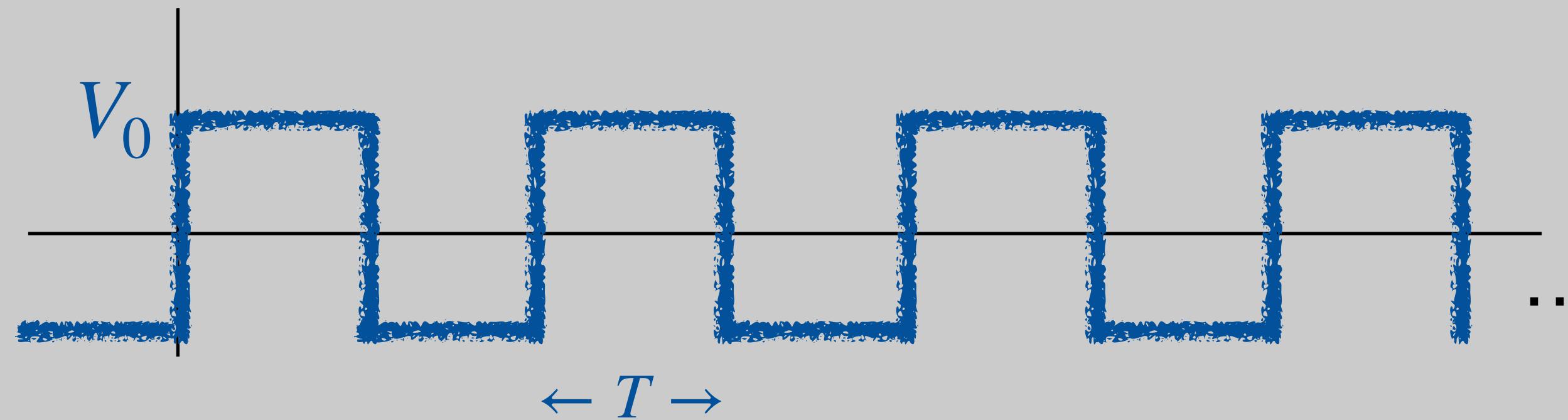

Slow switching - high magnitude


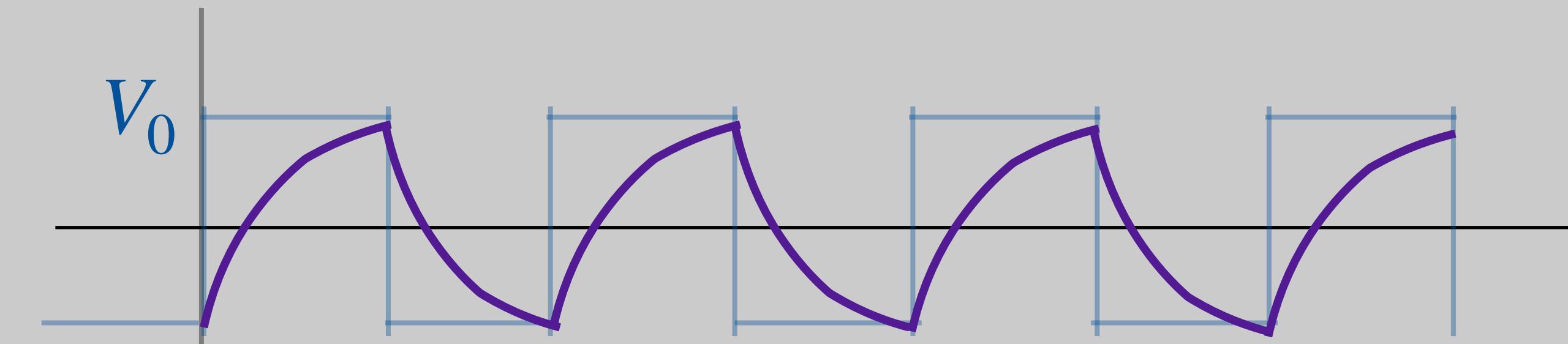


Fast switching - low magnitude

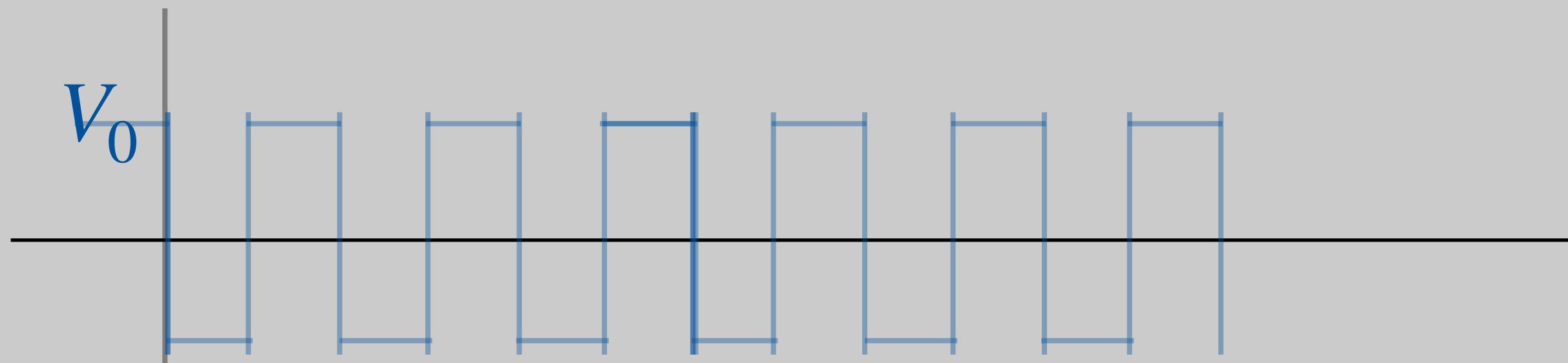


Pulse Response of RC circuits


Pulse train Response:

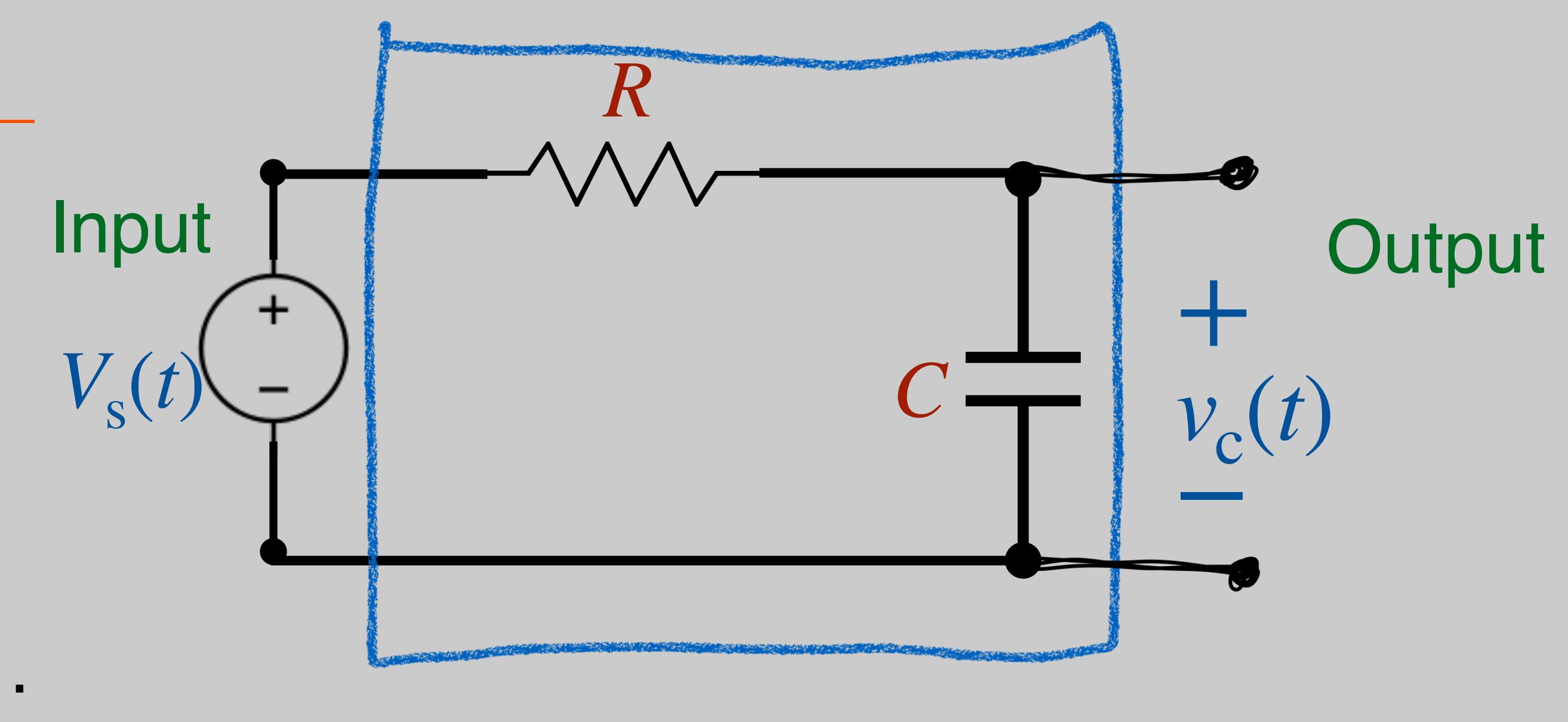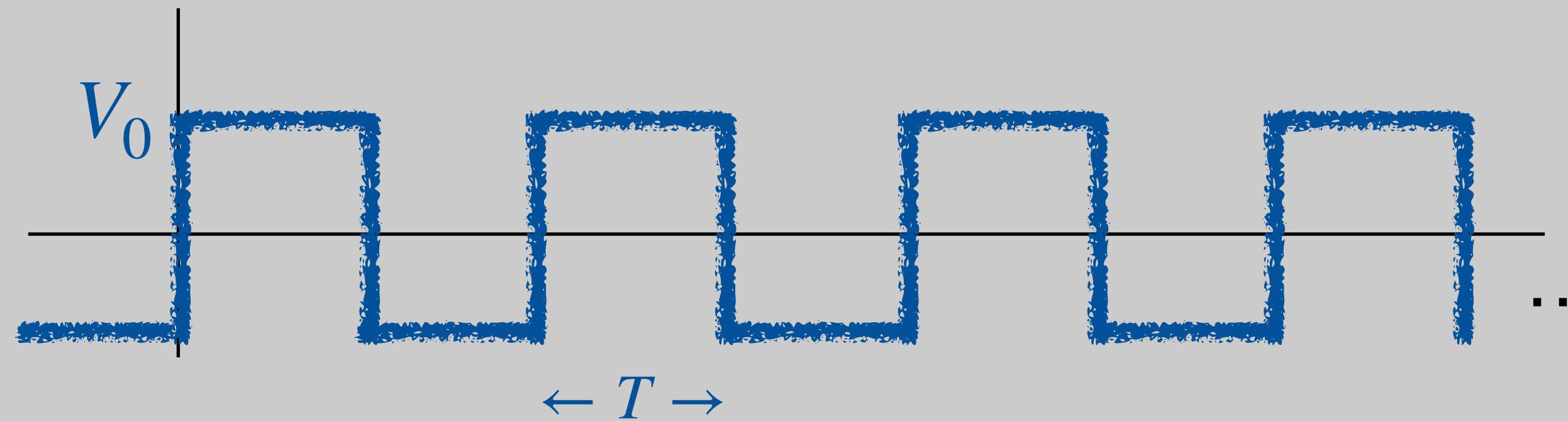

Slow switching - high magnitude

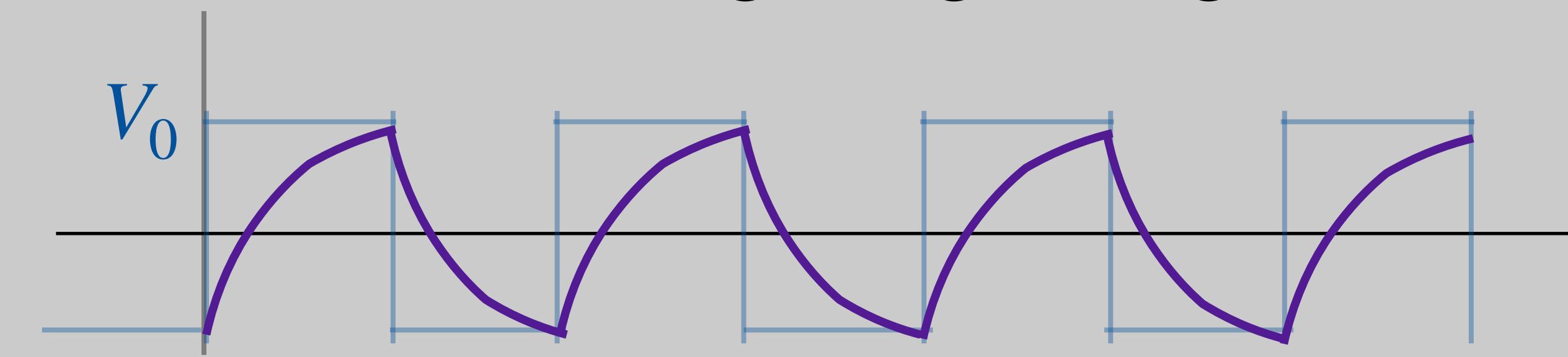

Fast switching - low magnitude

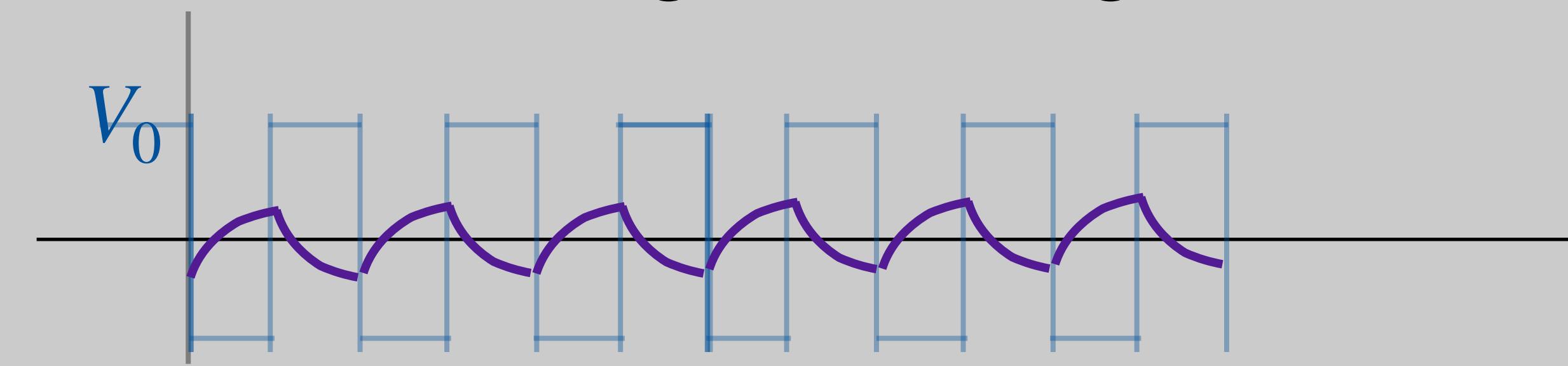

Low-Pass Filter!