

EE16B
Designing Information
Devices and Systems II

Lecture 2A
Inductors and RL Circuit



Announcements

- Last time:
 - Transient behavior of RC circuits
 - Solving 1st Order Diff. Eq.
 - Homogenous - exponential decay
 - Inhomogenous - asymptotic exponential recovery
 - Step response
 - Pulse response
- Today:
 - Inductance, inductors, transformers
 - Solving diff. EQ for arbitrary inputs

Natural Response of RC circuits


$$\frac{dv_c(t)}{dt} + \frac{1}{RC}v_c(t) = \frac{1}{RC}V_s(t)$$
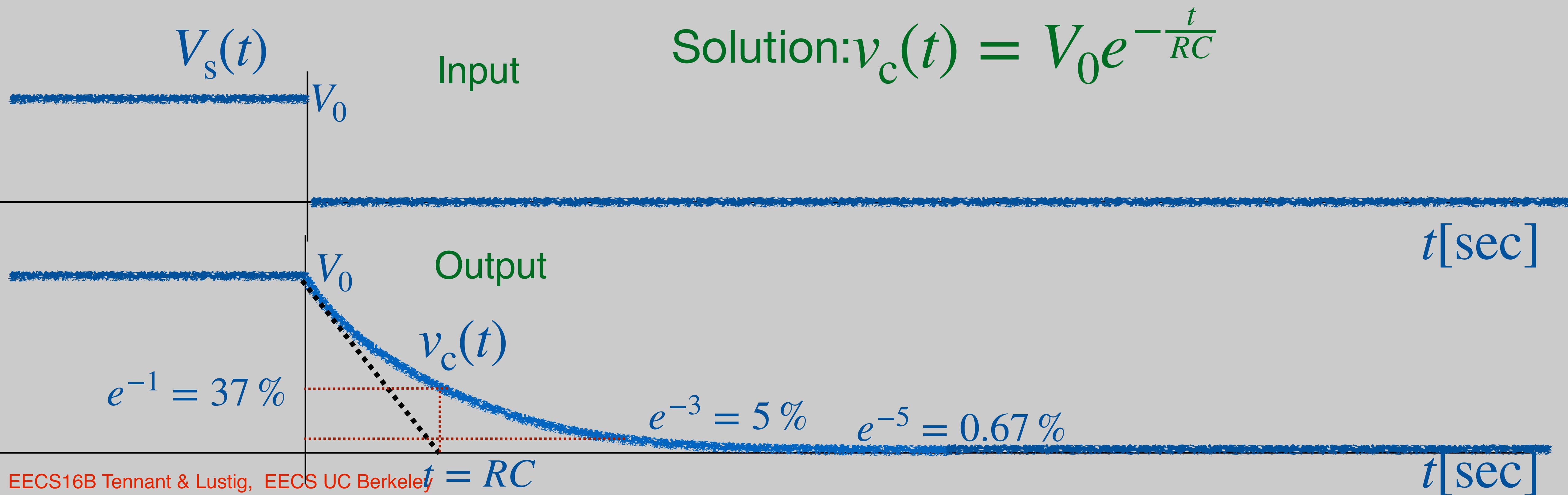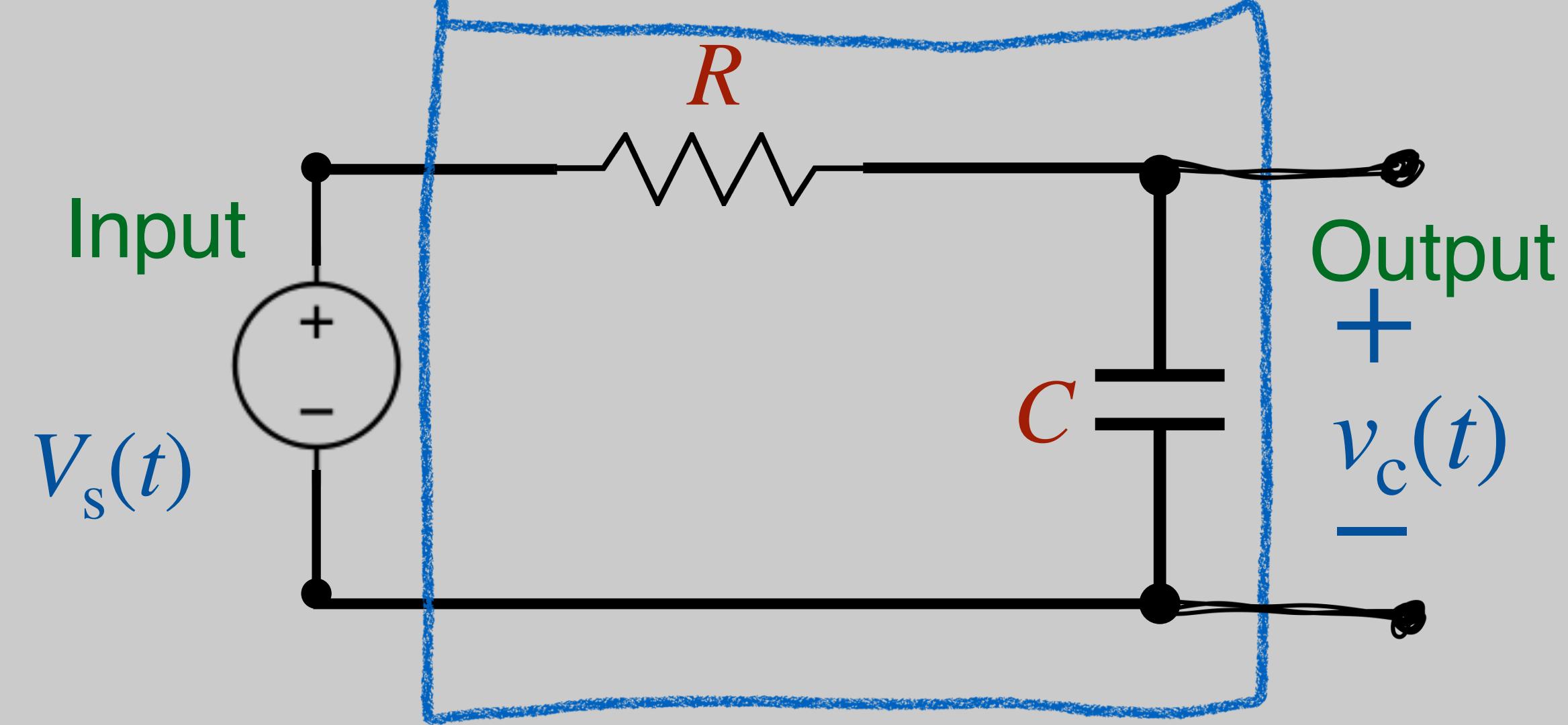
$$\Rightarrow \frac{dv_c(t)}{dt} + \frac{1}{RC}v_c(t) = 0$$




$$\frac{dv_c(t)}{dt} + \frac{1}{RC}v_c(t) = \frac{1}{RC}V_s(t)$$


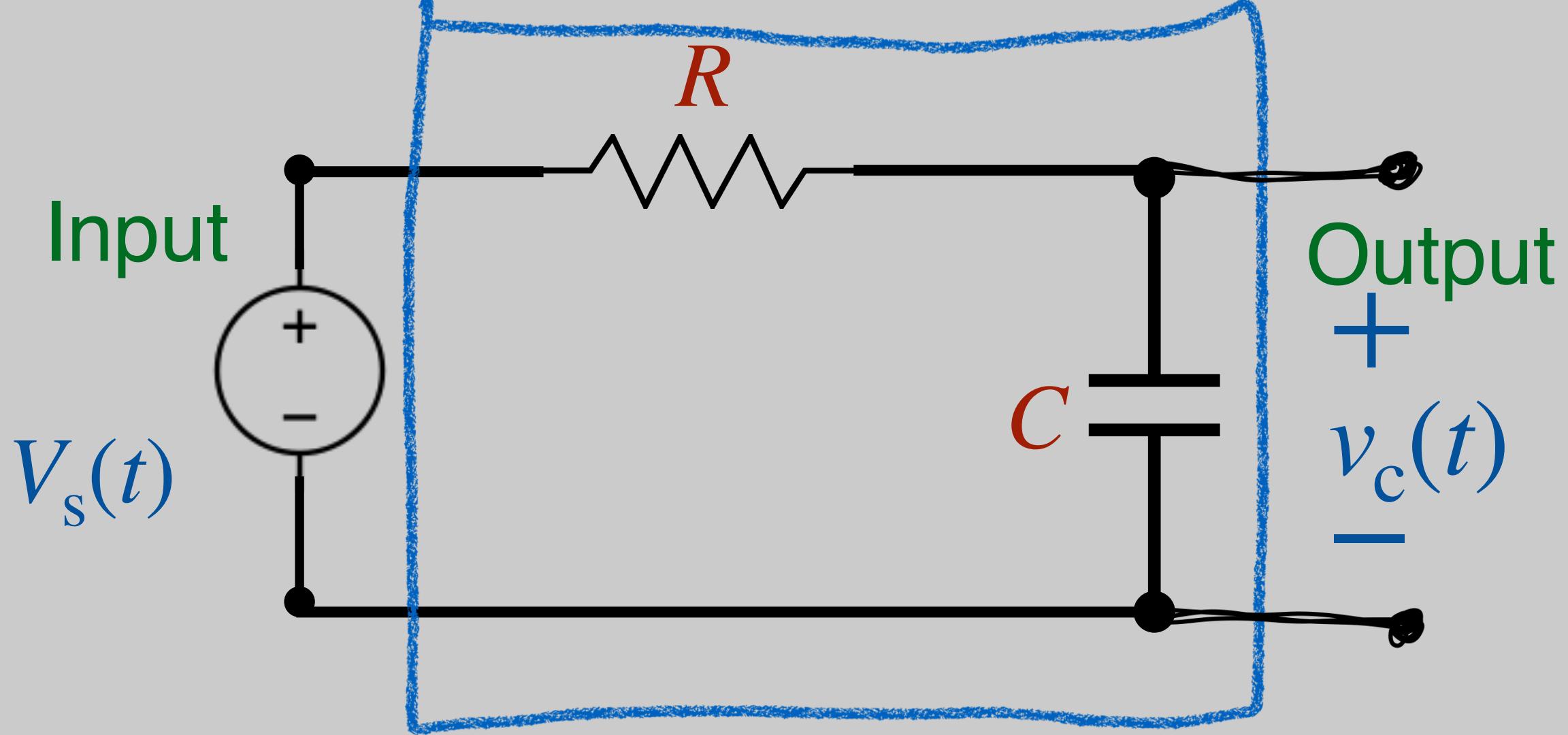
$$\Rightarrow \frac{dv_c(t)}{dt} + \frac{1}{RC}v_c(t) = \frac{1}{RC}V_0$$



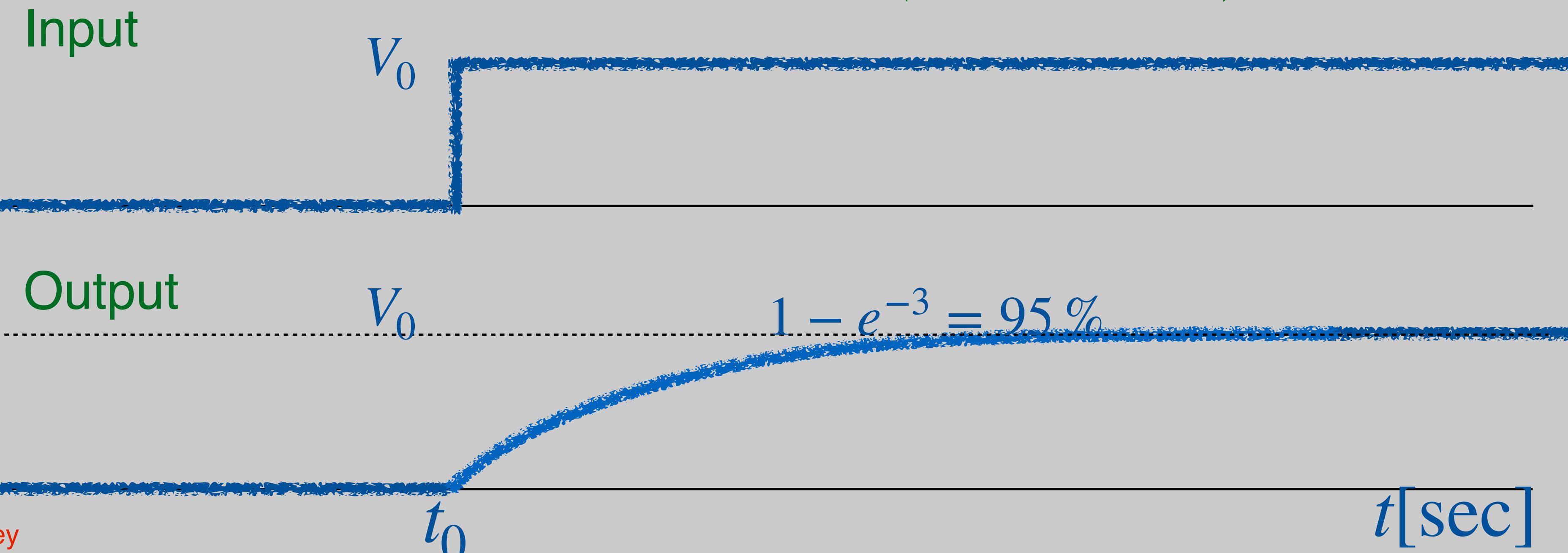
Solution: $v_c = V_0 \left(1 - e^{-\frac{t-t_0}{RC}} \right)$




Pulse Response of RC circuits

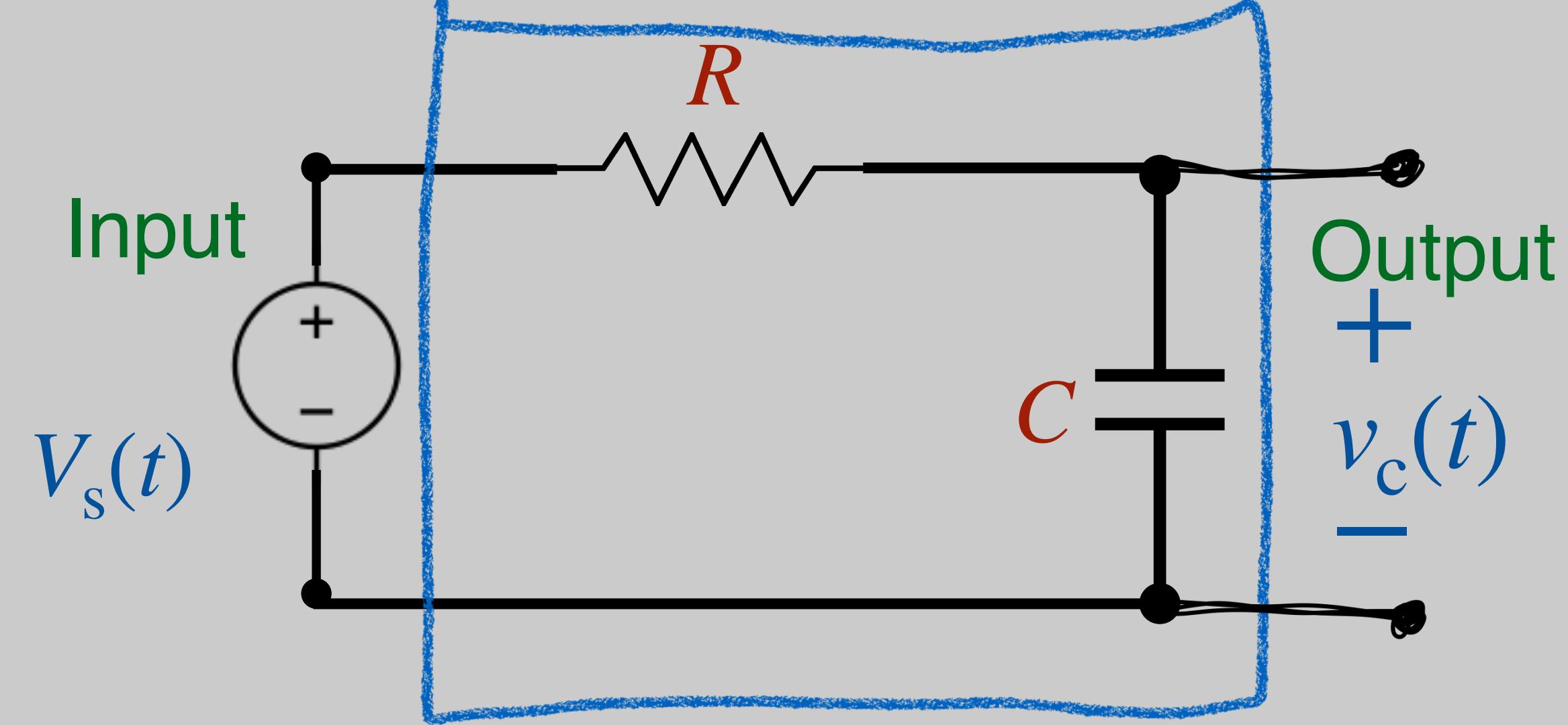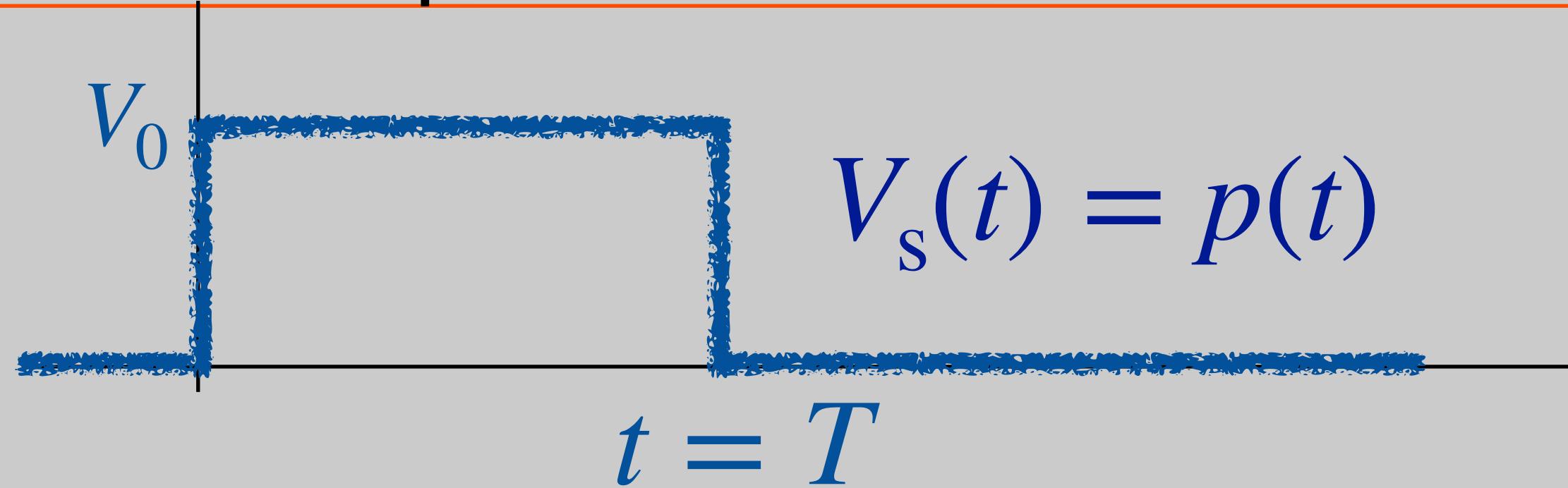


“Fast” Circuit $T \gg RC$

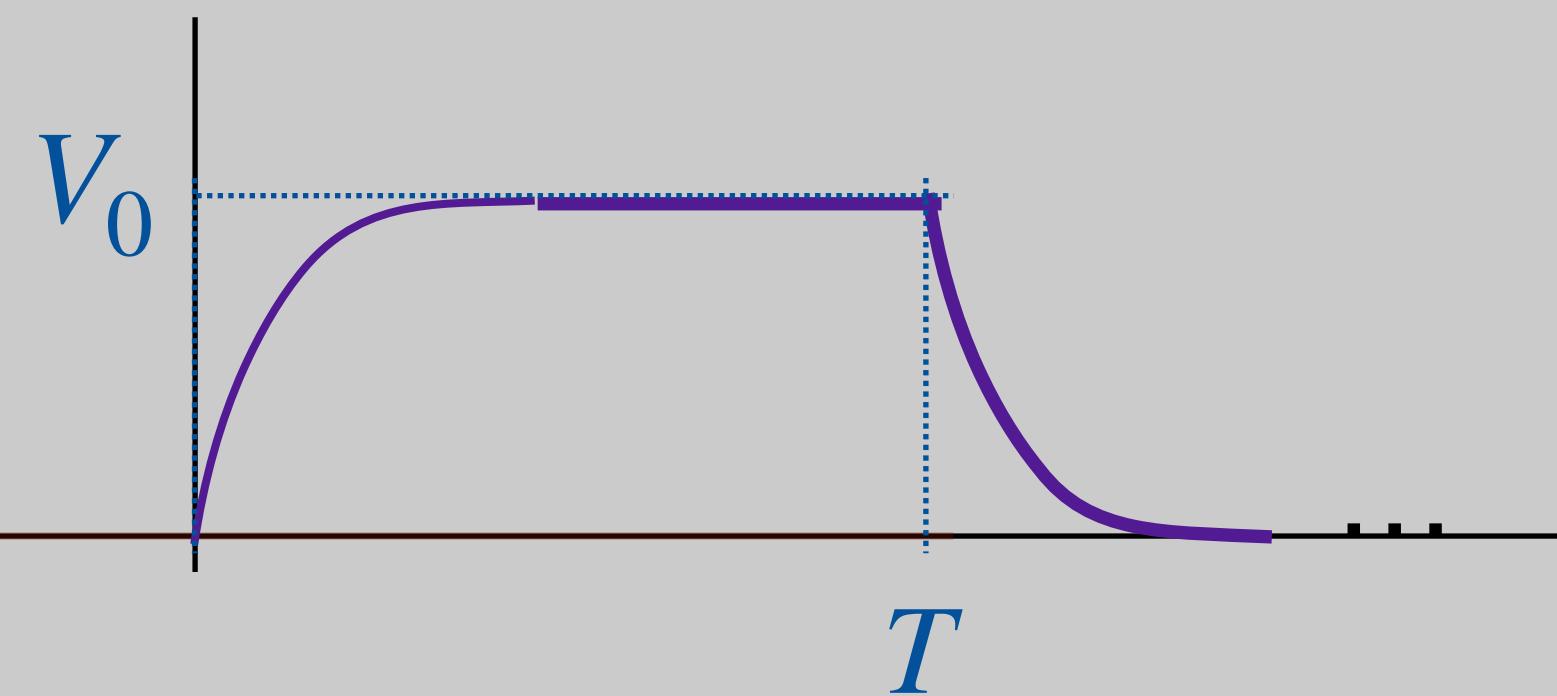

Slow Circuit $T \ll RC$

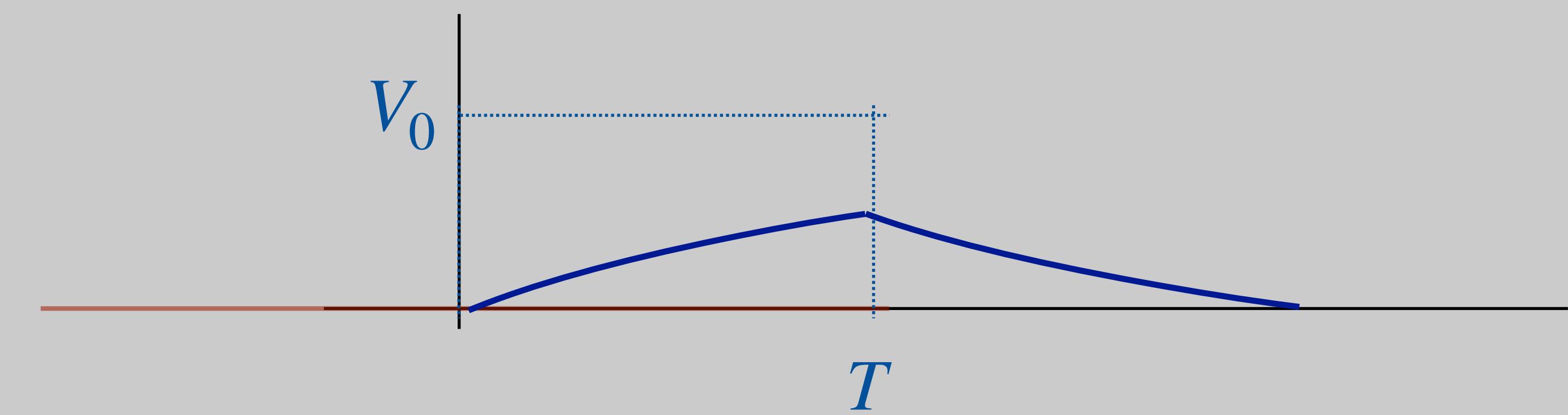


Pulse Response of RC circuits

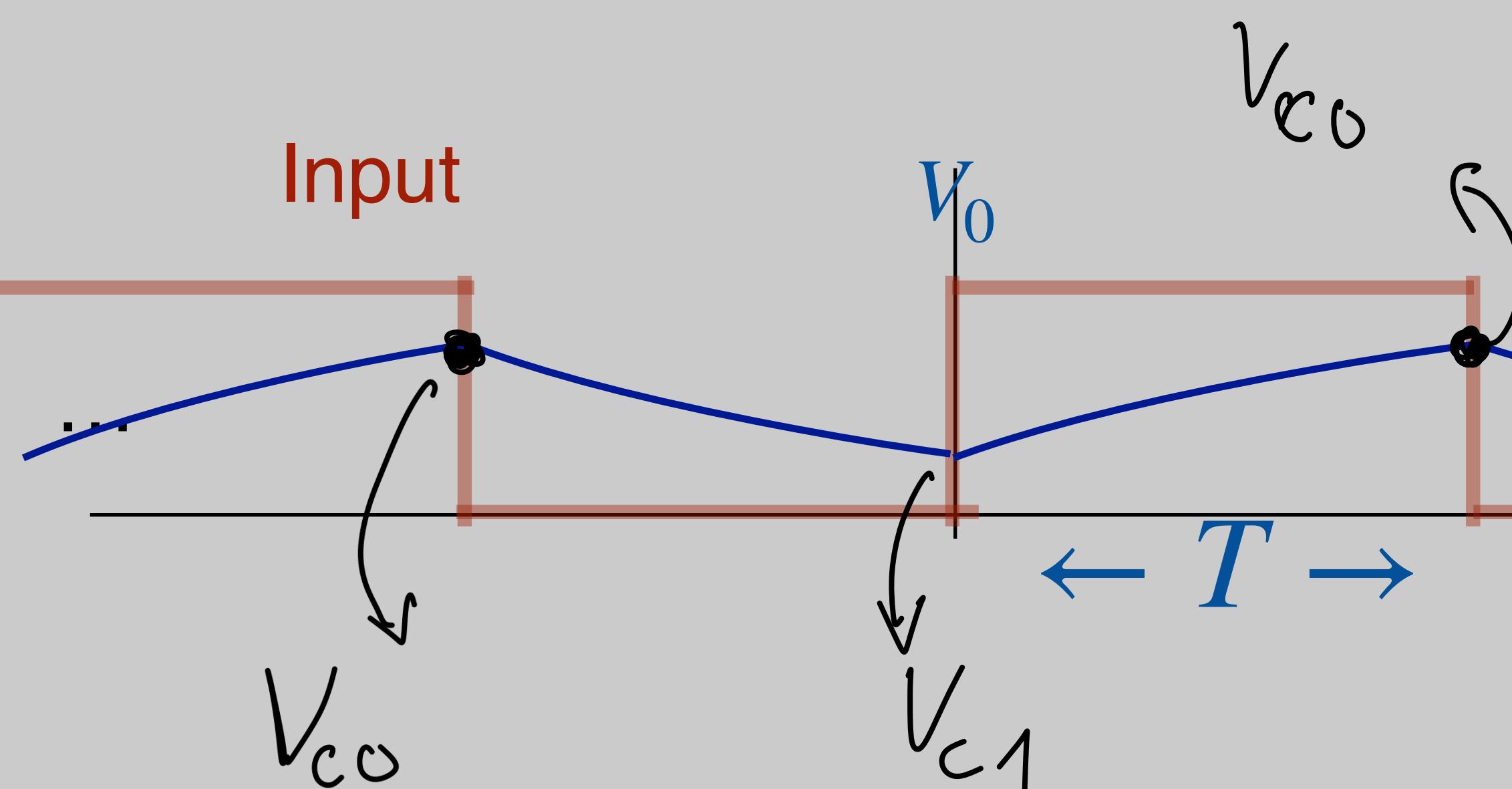


$$\textcircled{1} \quad V_{c1} = V_{c0} e^{-\frac{T}{RC}}$$
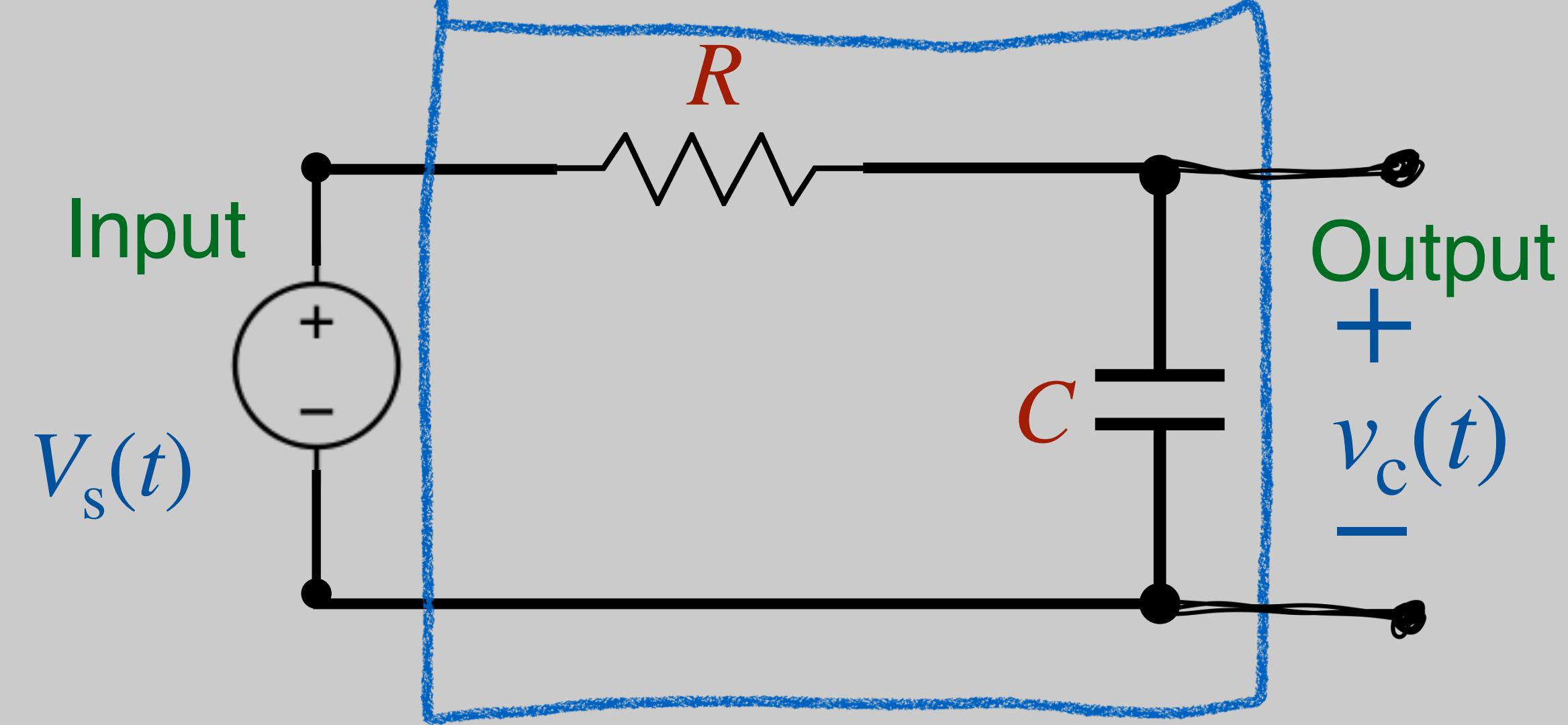
$$\textcircled{2} \quad V_{c0} = V_{c1} e^{-\frac{T}{RC}} + V_0 (1 - e^{-\frac{T}{RC}})$$



Pulse Response of RC circuits

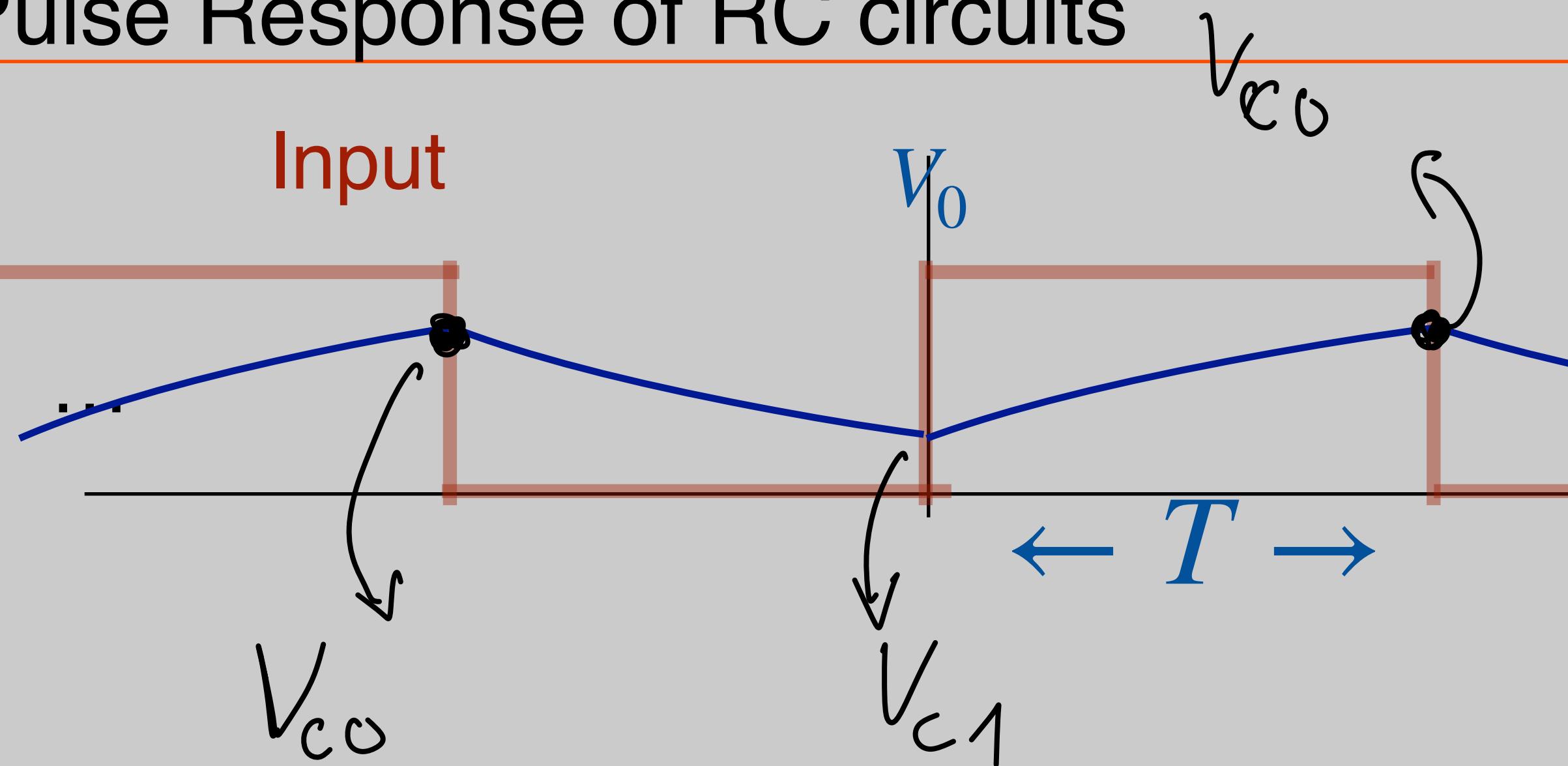


$$\textcircled{1} \quad V_{C1} = V_{C0} e^{-\frac{T}{RC}}$$

$$\textcircled{2} \quad V_{C0} = V_{C1} e^{-\frac{T}{RC}} + V_0 (1 - e^{-\frac{T}{RC}})$$

$$V_{C0} = V_{C0} e^{-\frac{2T}{RC}} + V_0 (1 - e^{-\frac{2T}{RC}})$$

$$V_{C0} = V_0 \frac{(1 - e^{-\frac{T}{RC}})}{(1 - e^{-\frac{2T}{RC}})}$$

Pulse Response of RC circuits

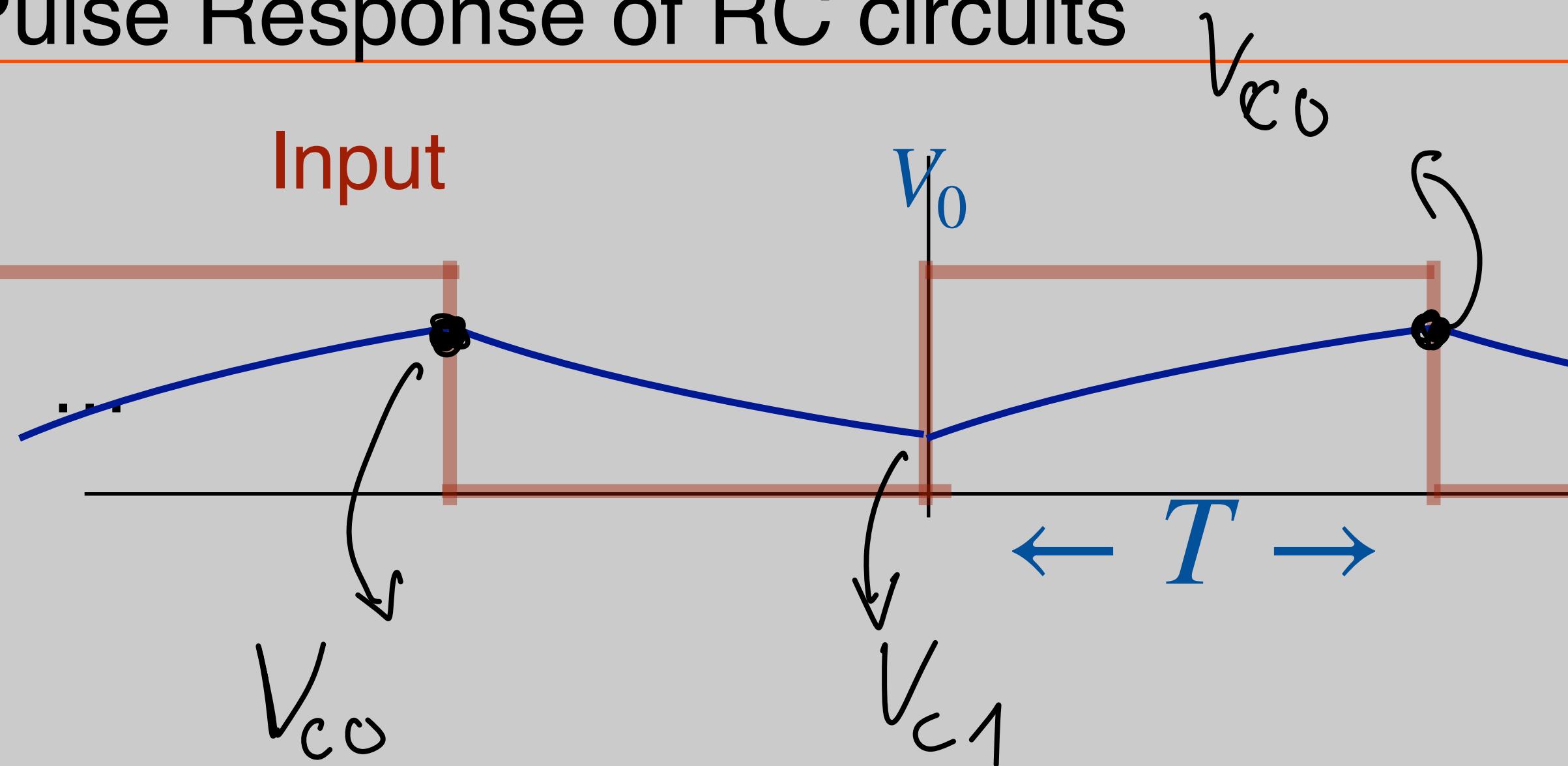

$$\textcircled{1} \quad V_{C1} = V_{C0} e^{-\frac{T}{RC}}$$

$$\textcircled{2} \quad V_{C0} = V_{C1} e^{-\frac{T}{RC}} + V_0 (1 - e^{-\frac{T}{RC}})$$




$$V_{C0} = V_{C0} e^{-\frac{2T}{RC}} + V_0 (1 - e^{-\frac{2T}{RC}})$$

$$V_{C0} = V_0 \frac{(1 - e^{-\frac{T}{RC}})}{(1 - e^{-\frac{2T}{RC}})}$$





$$\lim_{\frac{T}{RC} \rightarrow 0} V_{C0} = \frac{V_0}{2}$$

$$\Delta \Rightarrow V_{C0} - V_{C1} = V_0 (1 - e^{-\frac{T}{RC}})$$





EECS16A Lab1

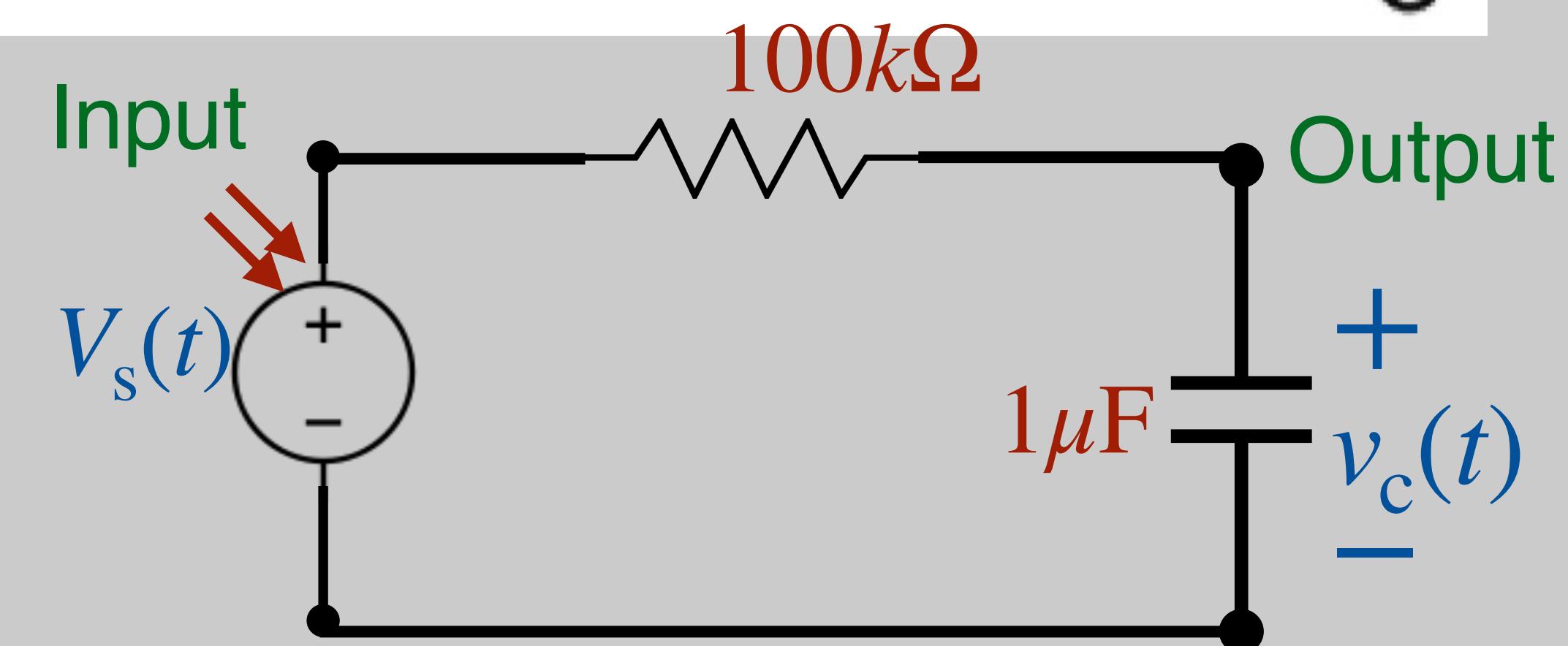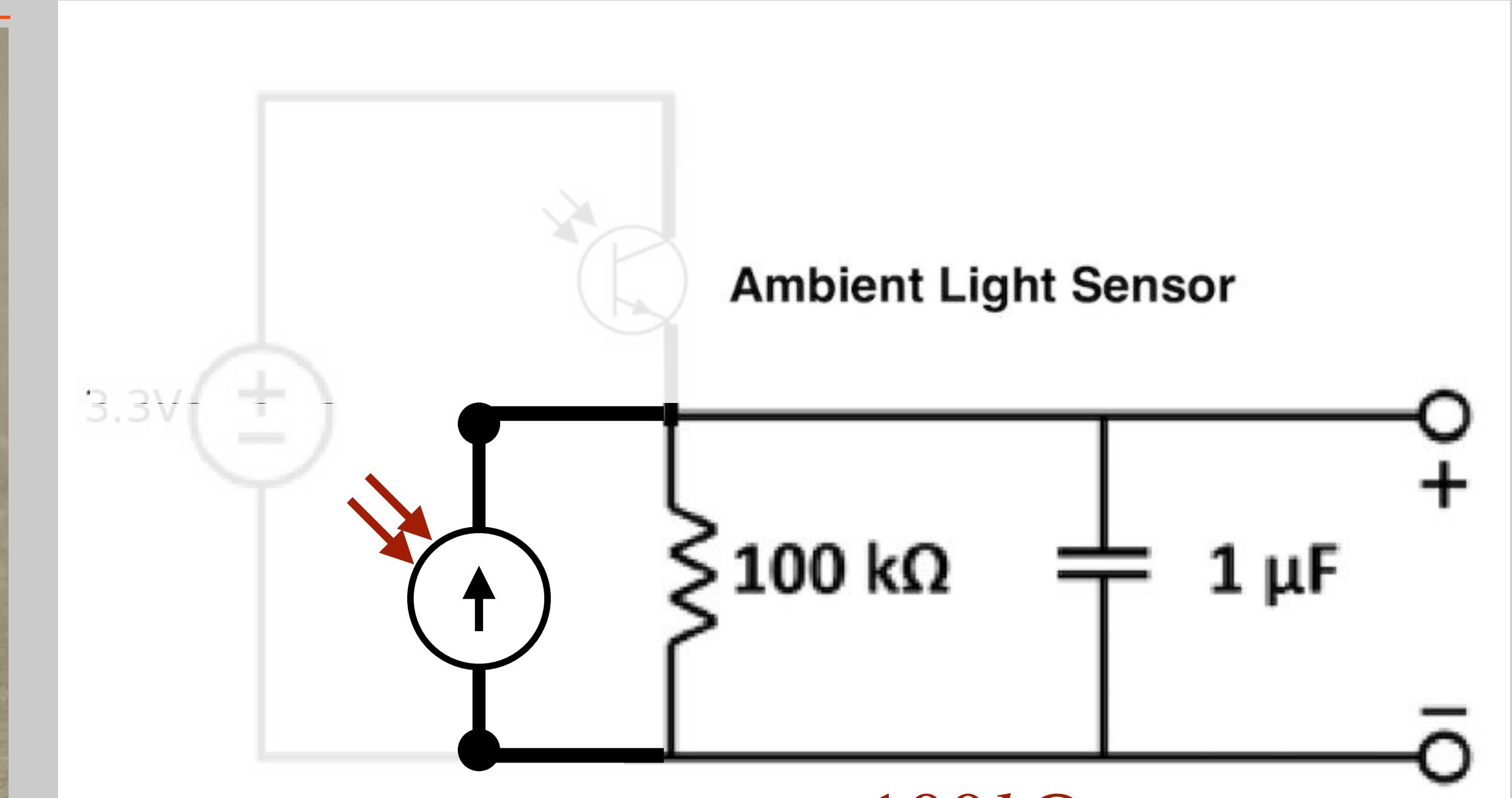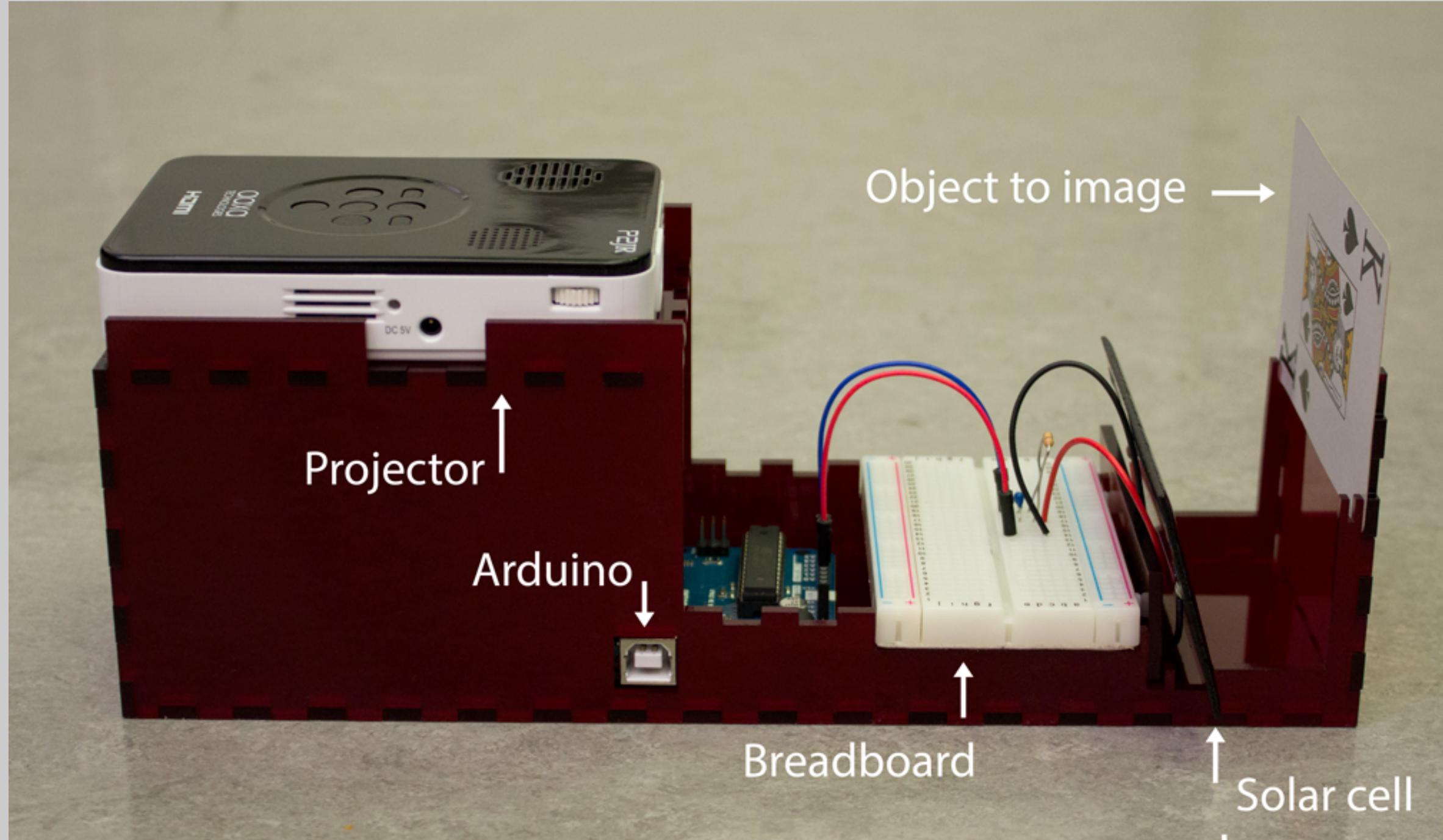





EECS16A Lab1

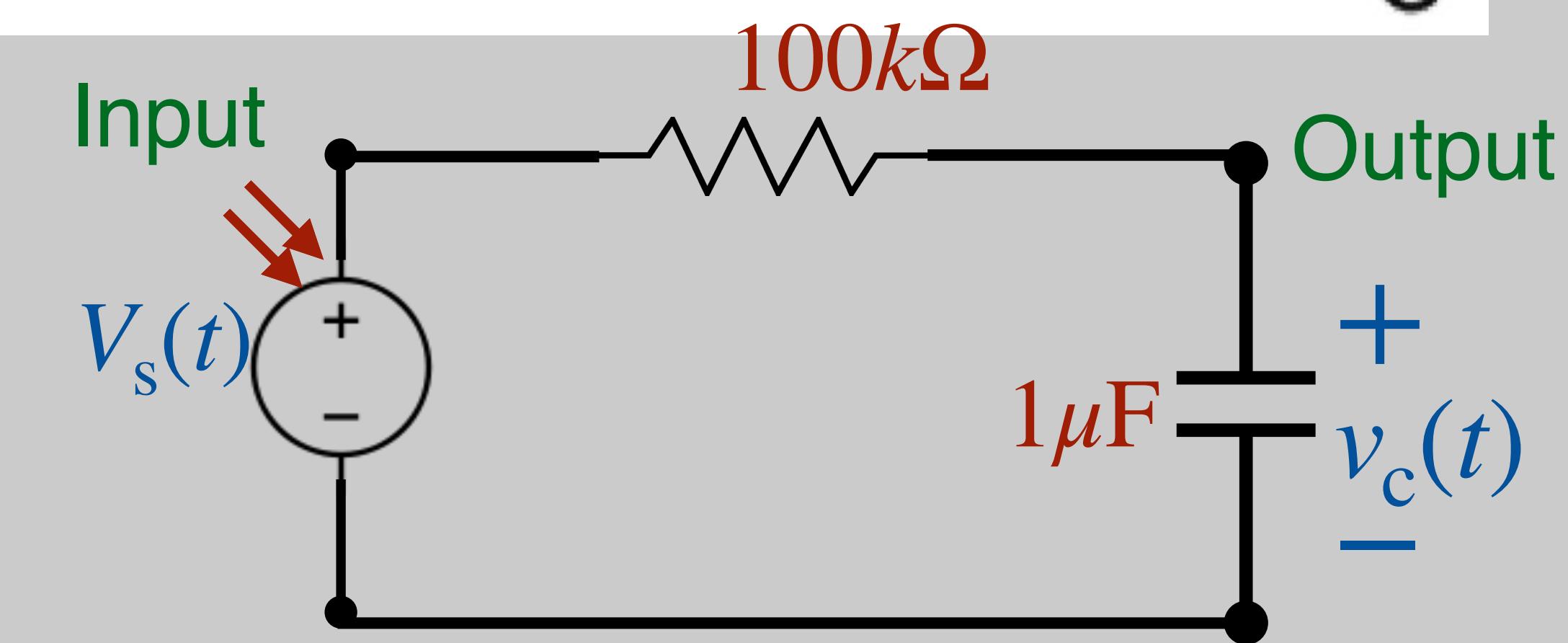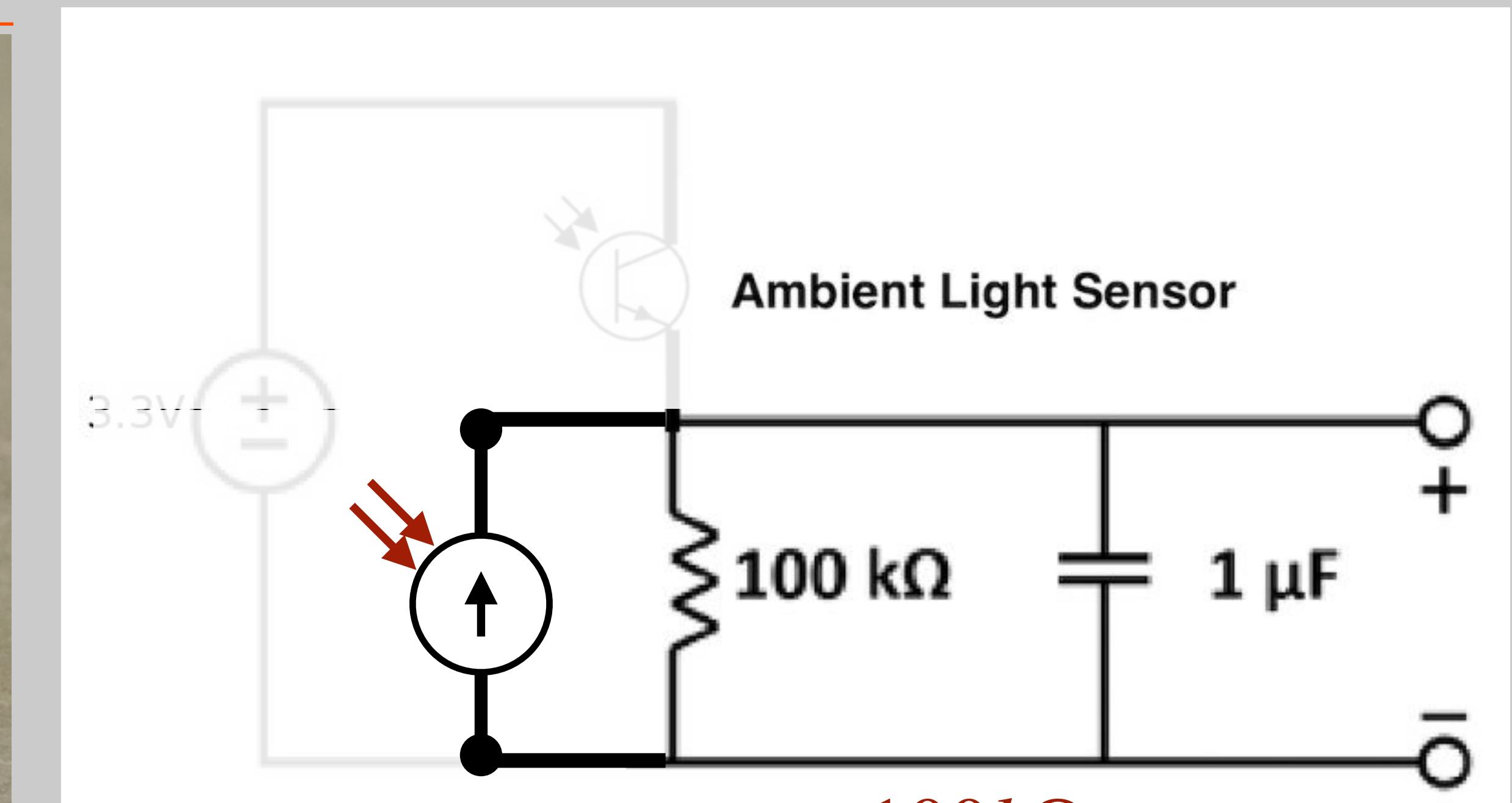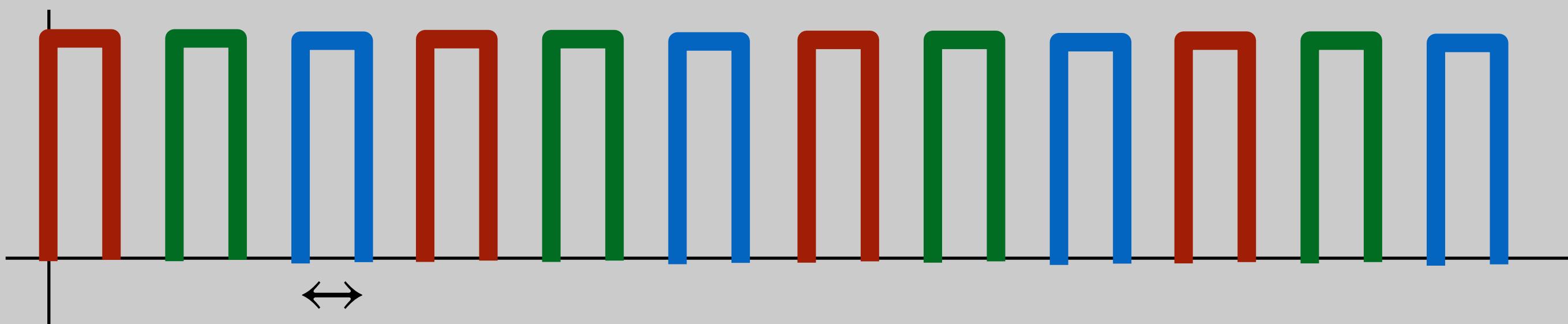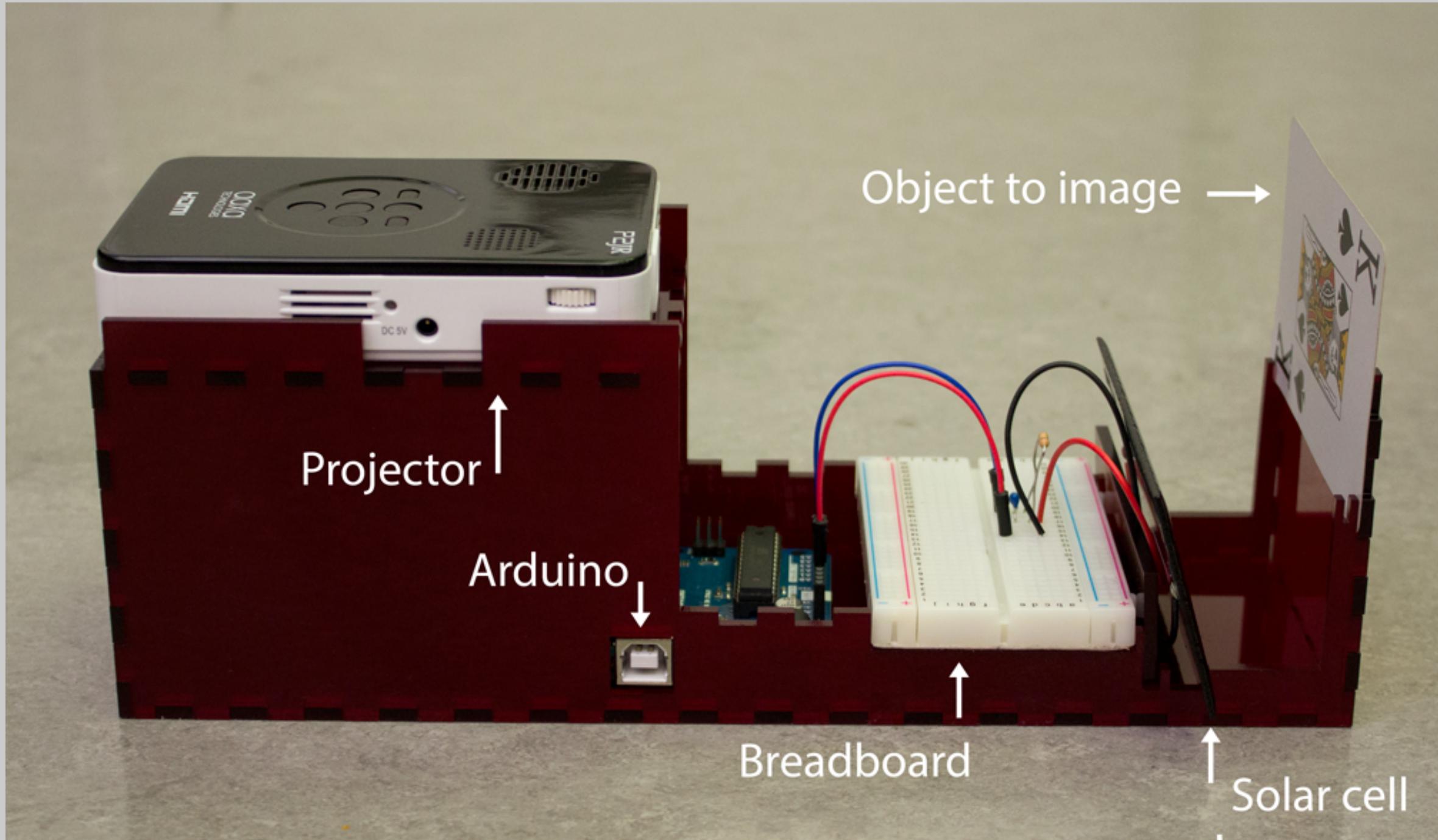

EECS16A Lab1

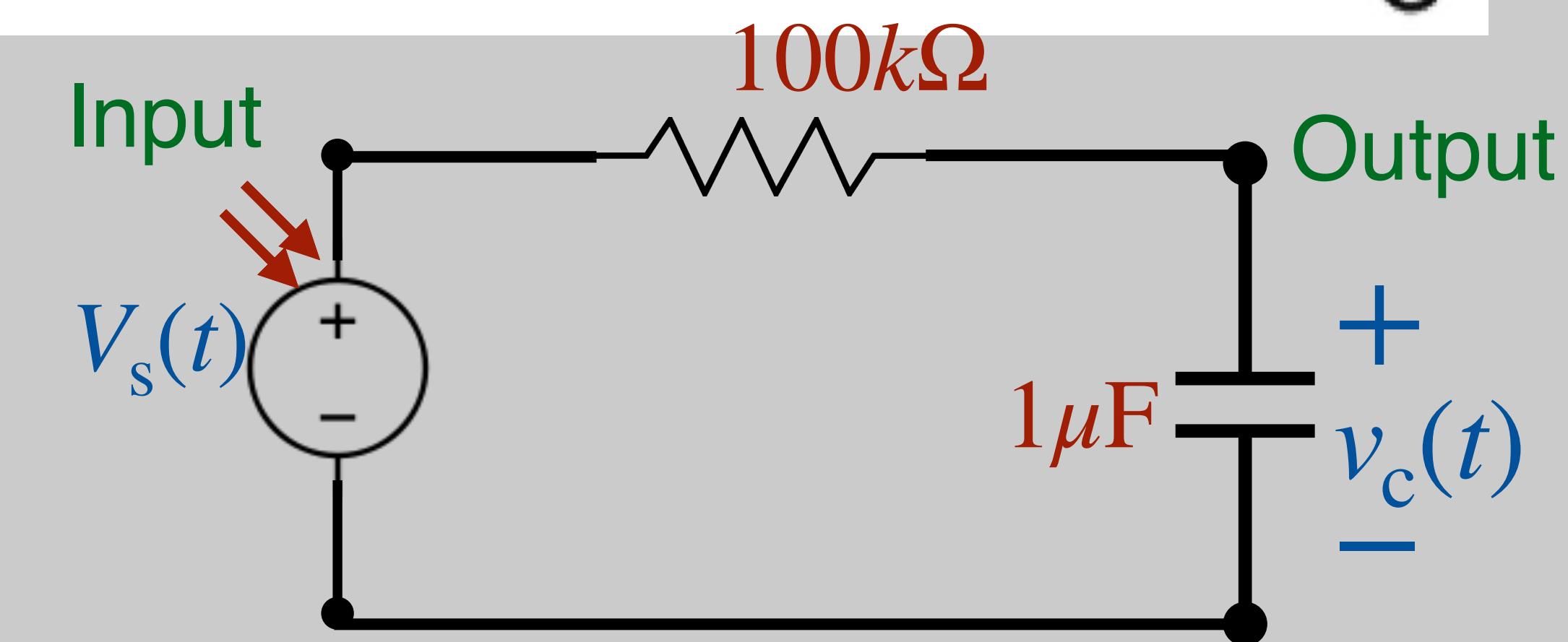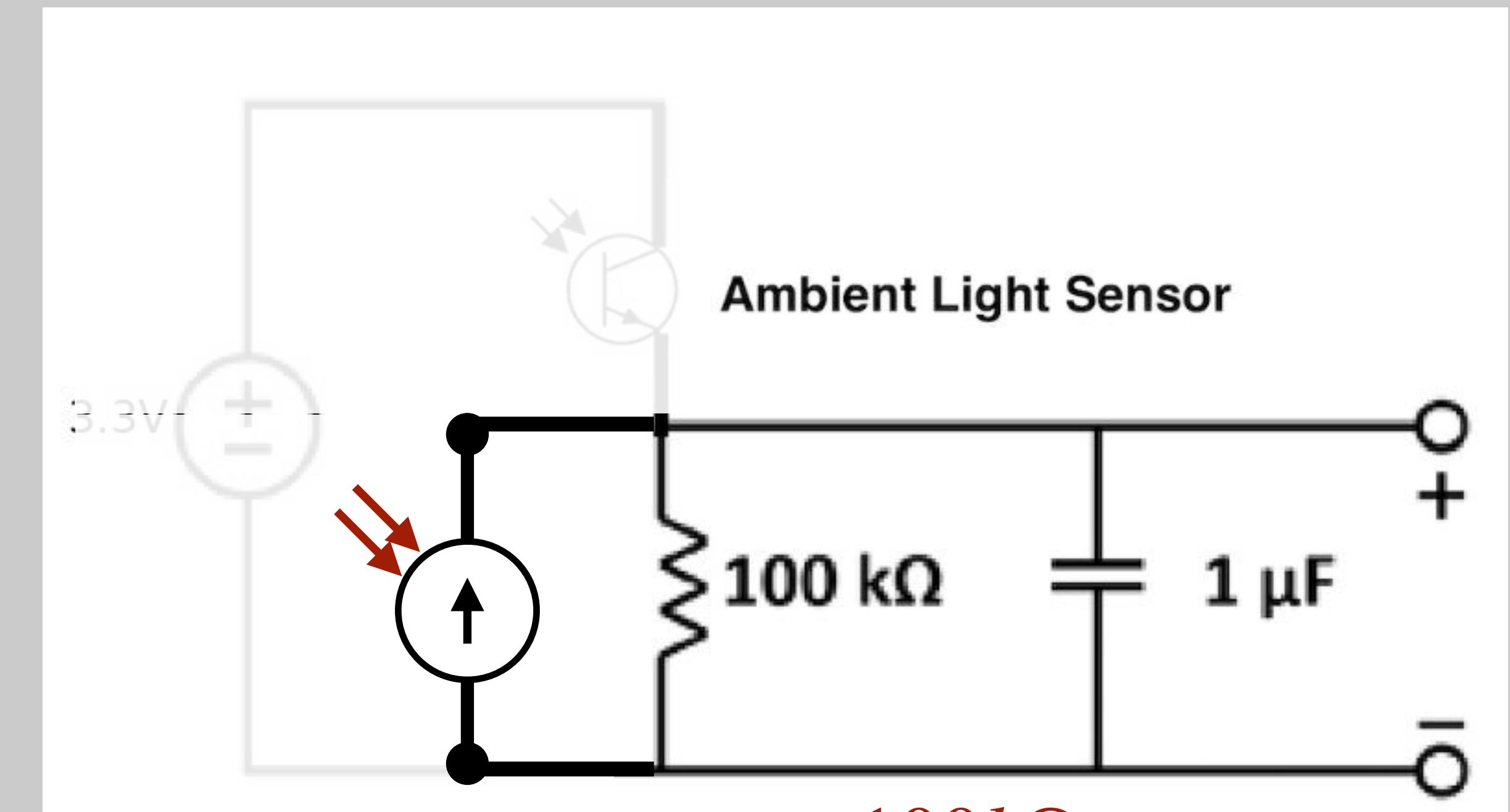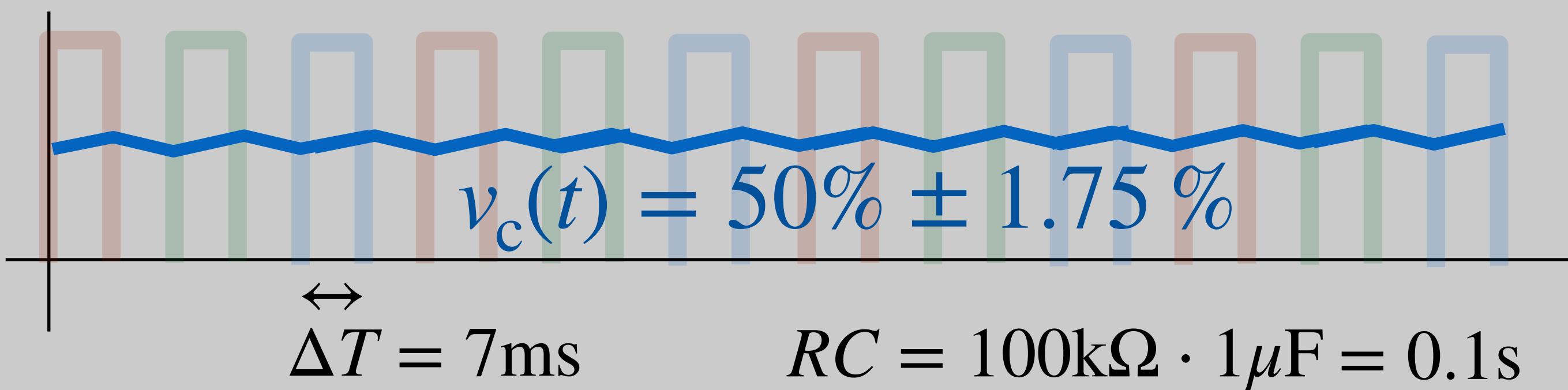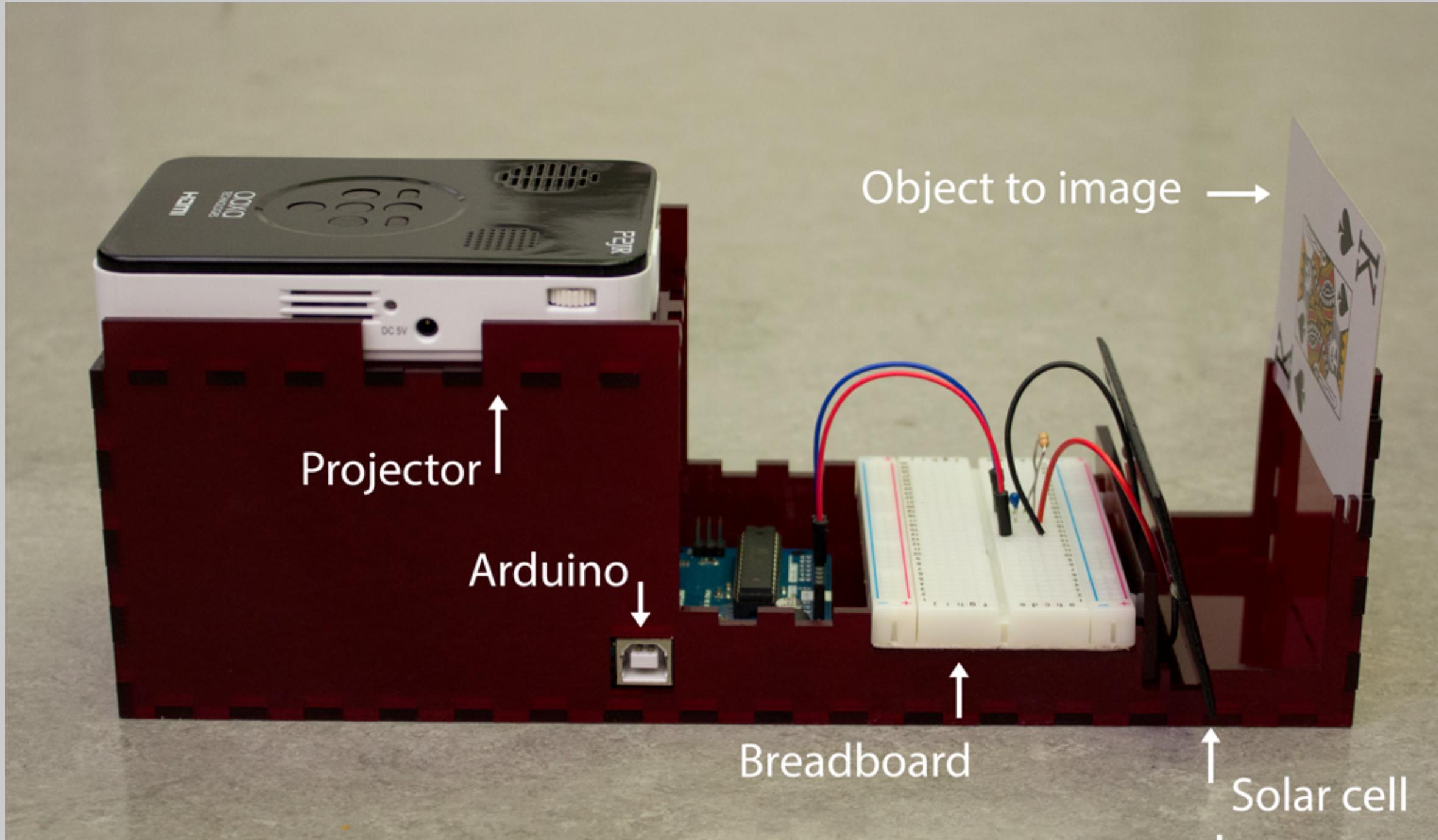

EECS16A Lab1

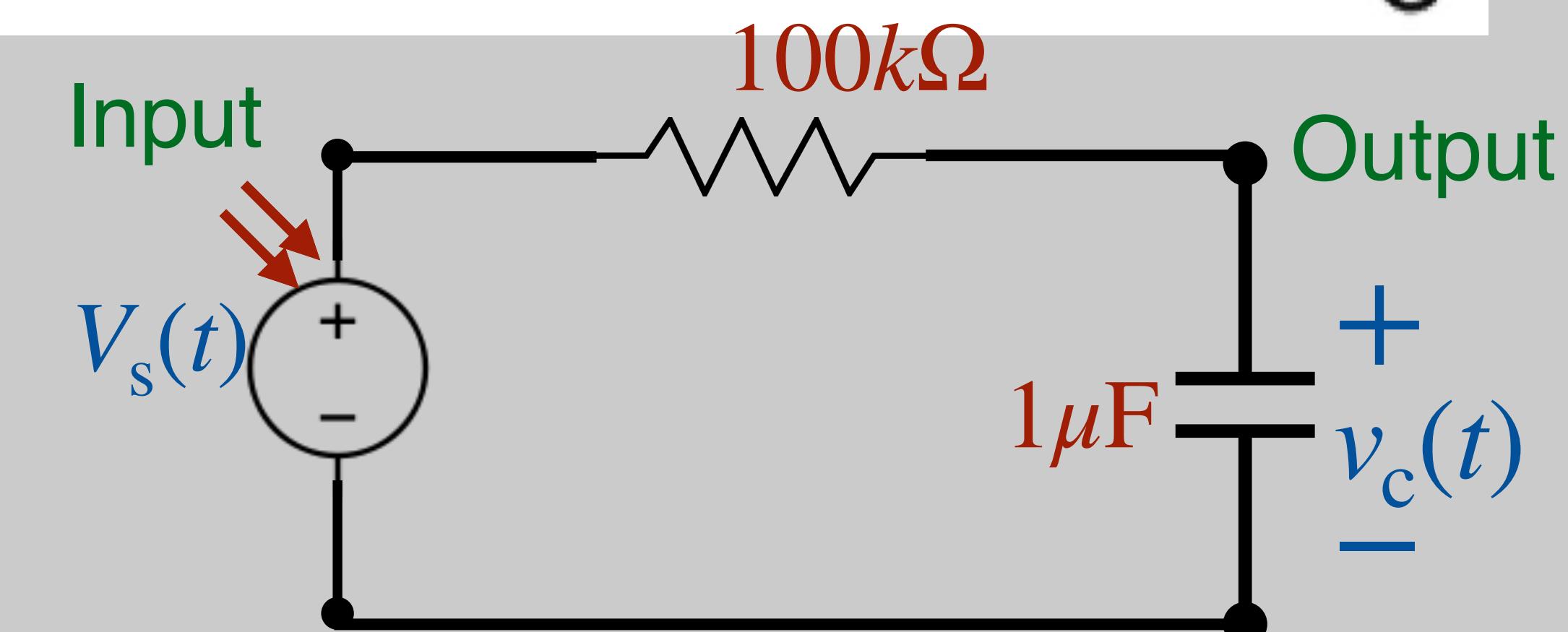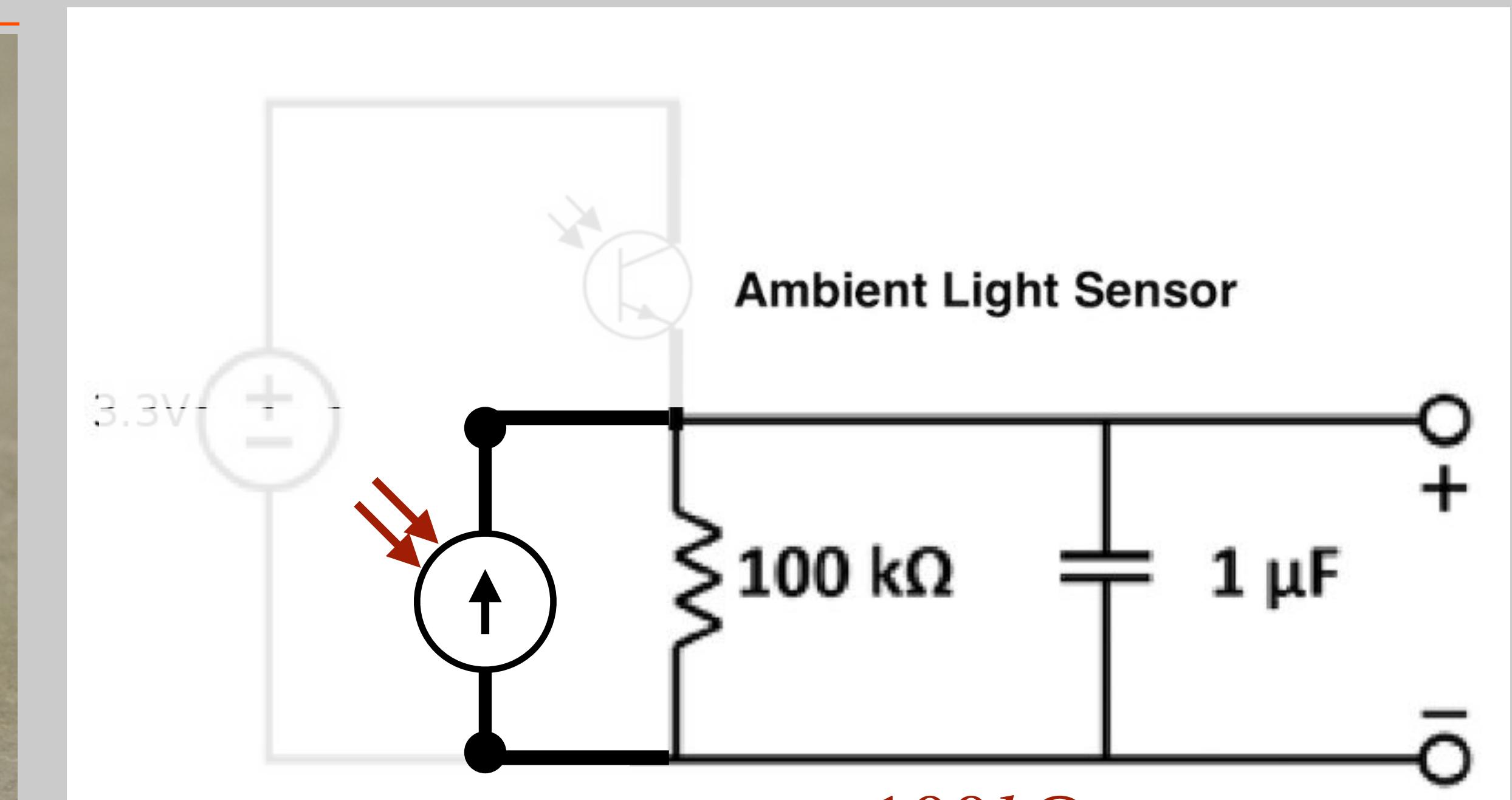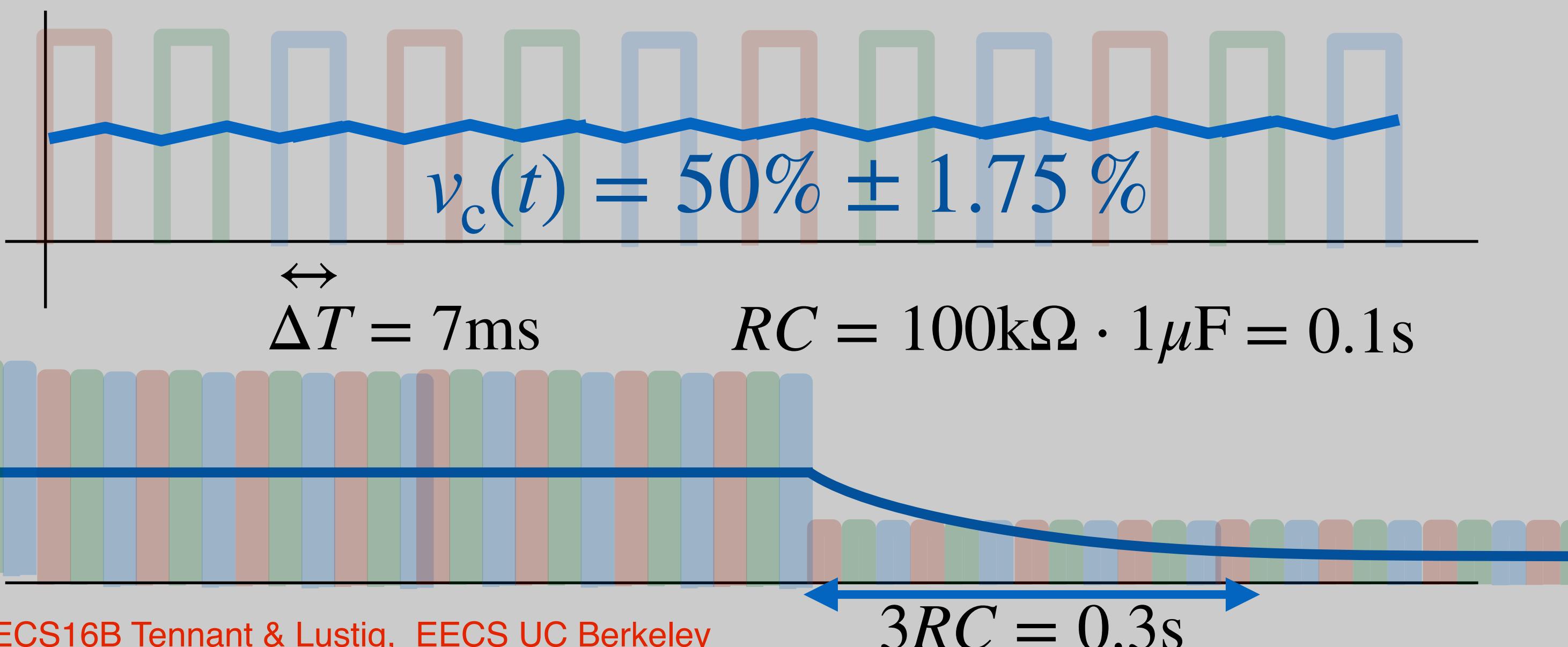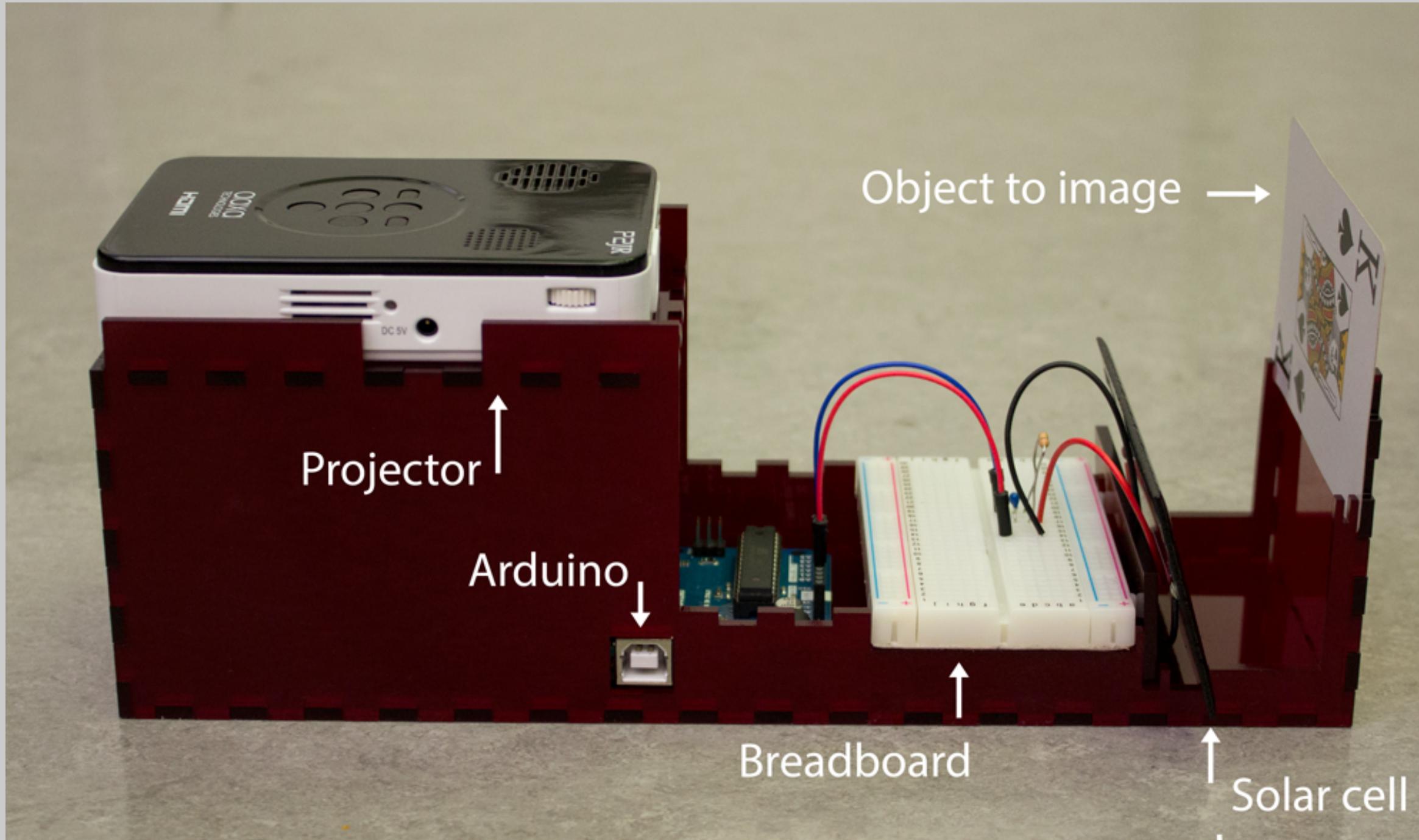

Inductance

- Capacity to store energy in a magnetic field
- Units: Henry [H]
- Components nH (10^{-9}), uH (10^{-6}), mH (10^{-3})
- Magnets, power transformers > 1H




Inductors

- Many designs and uses
- Current produces a magnetic flux:

$$\Phi_B = Li$$

- Change in flux induces voltage
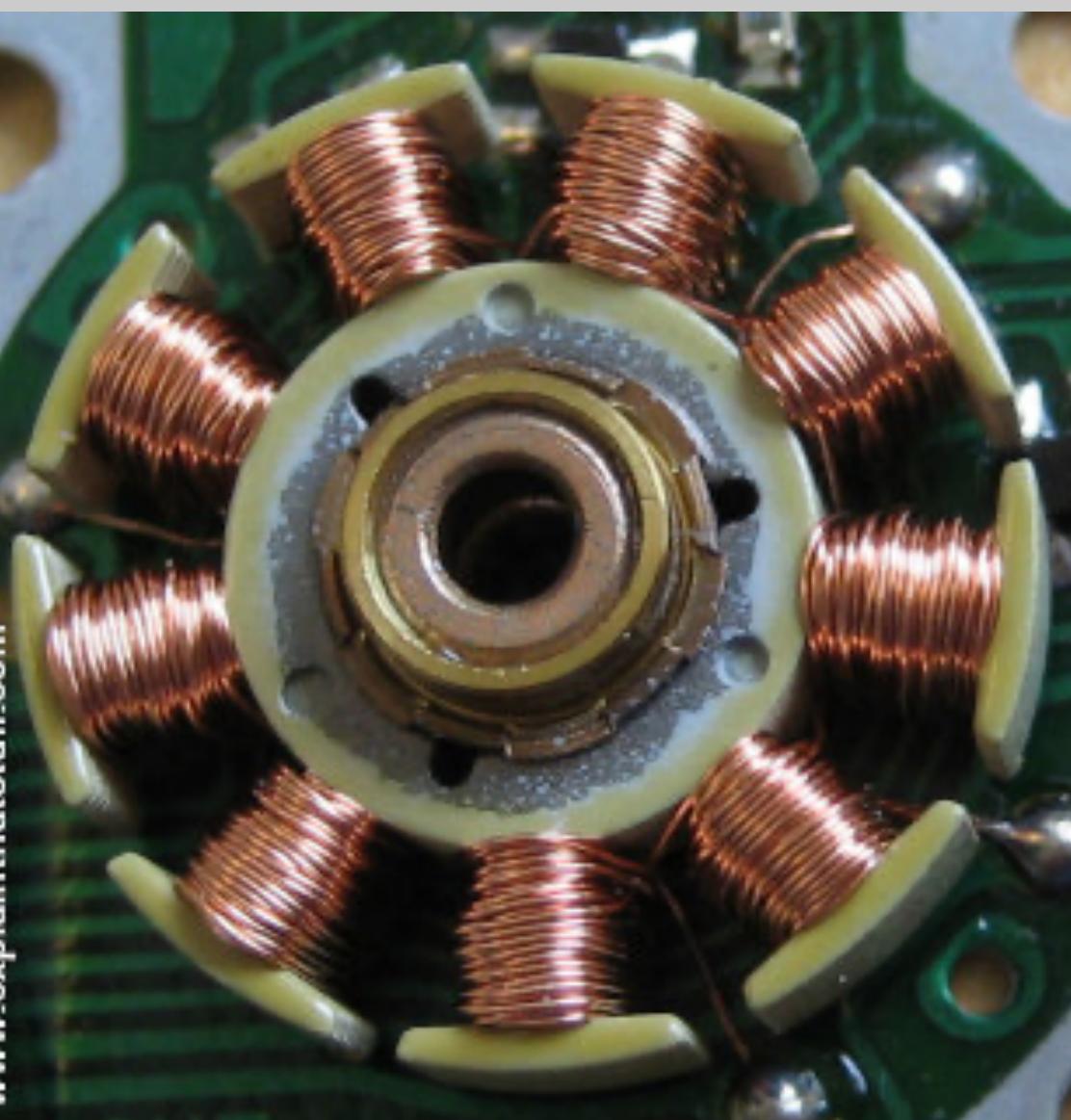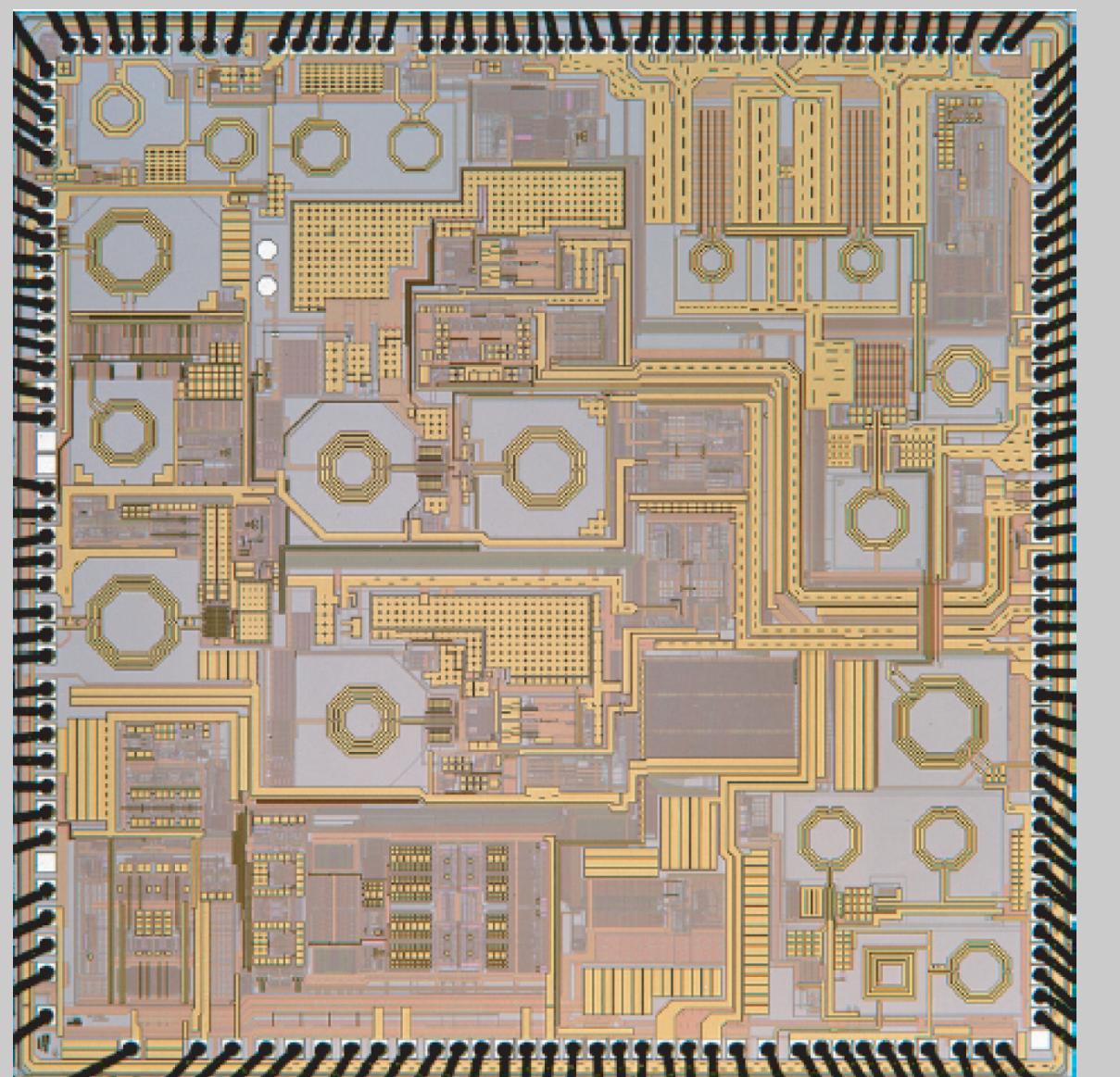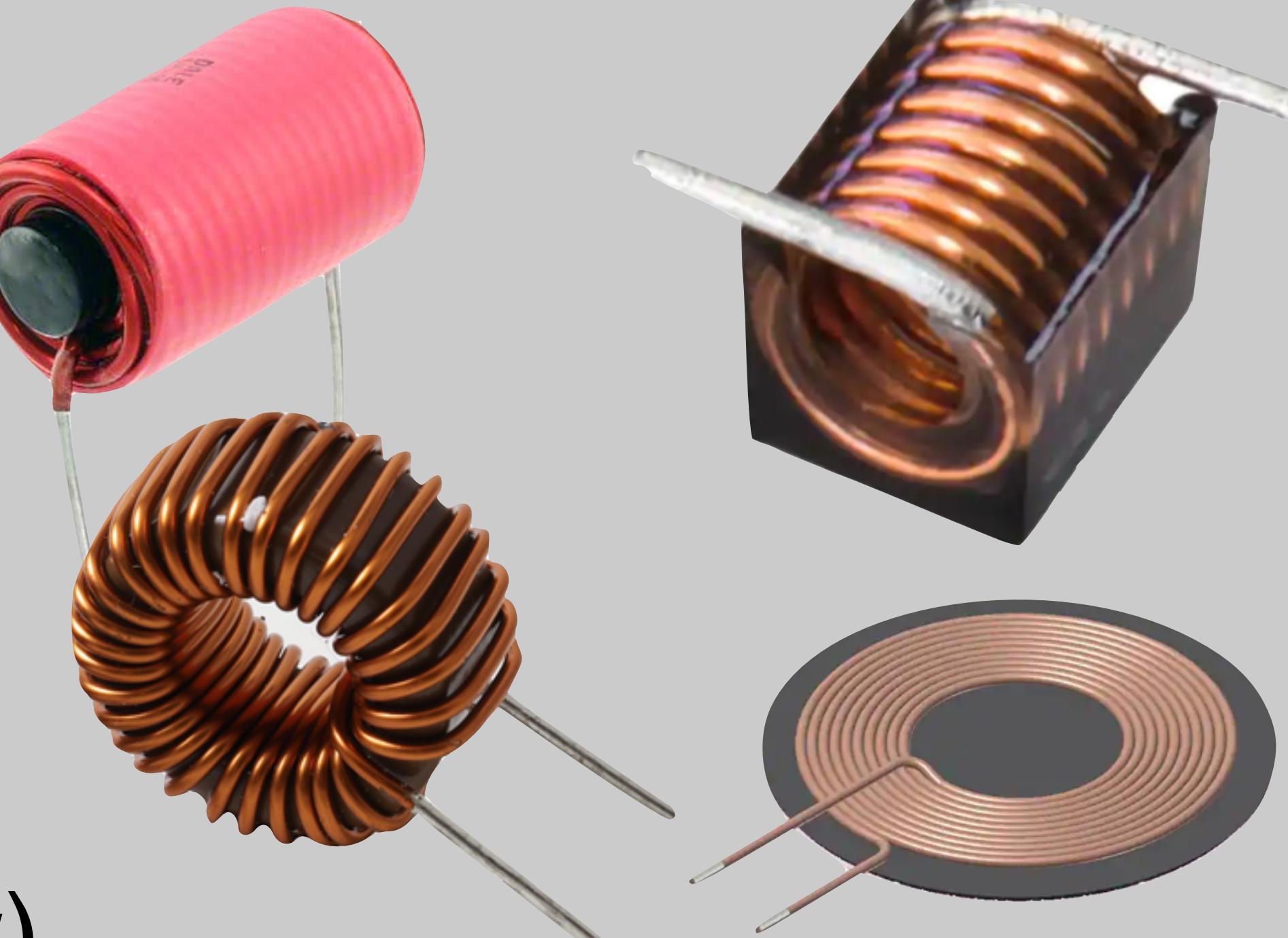
$$v = \frac{d\Phi_B}{dt} \text{ (Faraday's Law)}$$



www.explaininthatstuff.com

Inductors

- For N-turn solenoid, area A and length l


$$L = \frac{\mu N^2 A}{l}$$

magnetic permeability: $\mu = \mu_0 \mu_r$

$$\mu_0 = 4\pi \times 10^{-7}$$


$$\mu_r \approx 1 \quad \text{air}$$
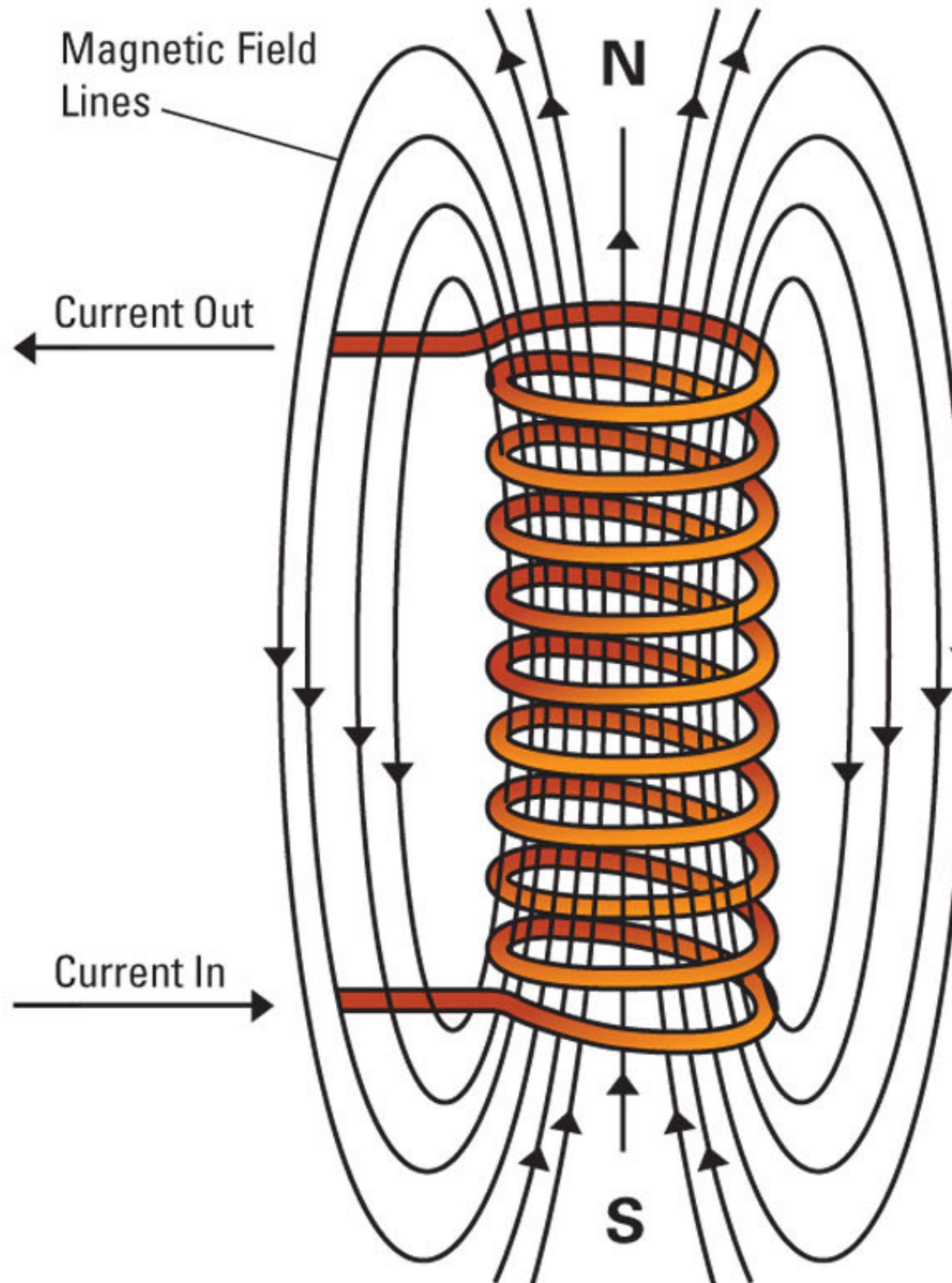
$$\mu_r \approx 350 - 20000 \quad \text{Ferrite}$$





Inductors

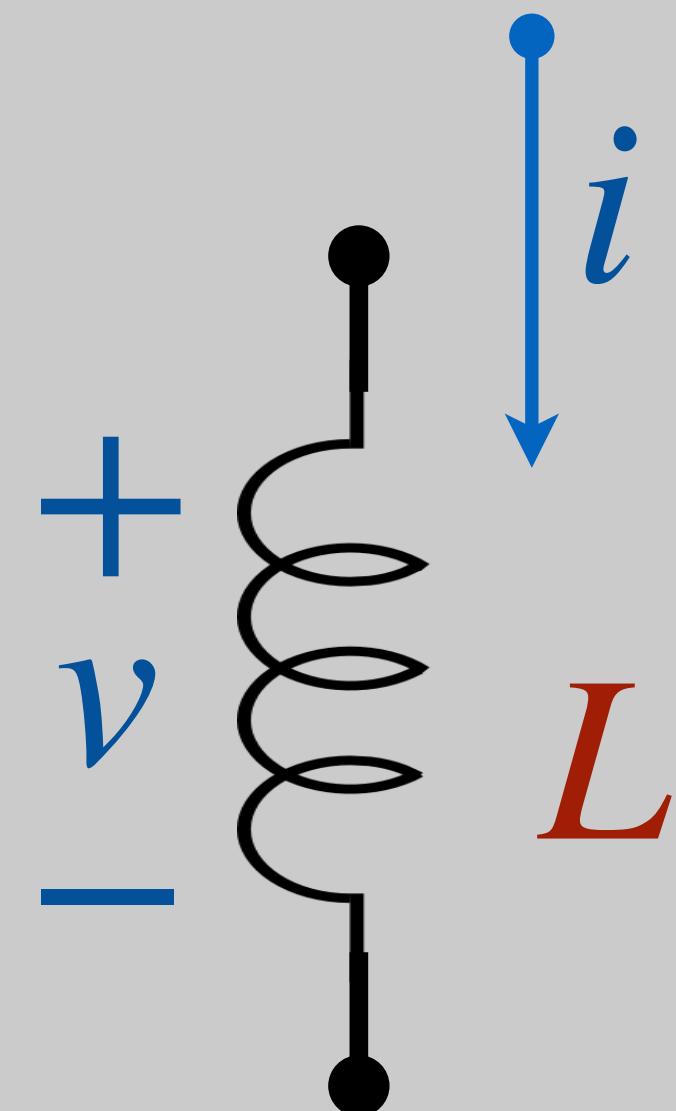


$$\Phi_B = L \cdot i$$

Time varying current:

$$L \frac{di}{dt} = \frac{d\Phi_B}{dt} = v(t)$$

$$i(t) = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

Memory!!!

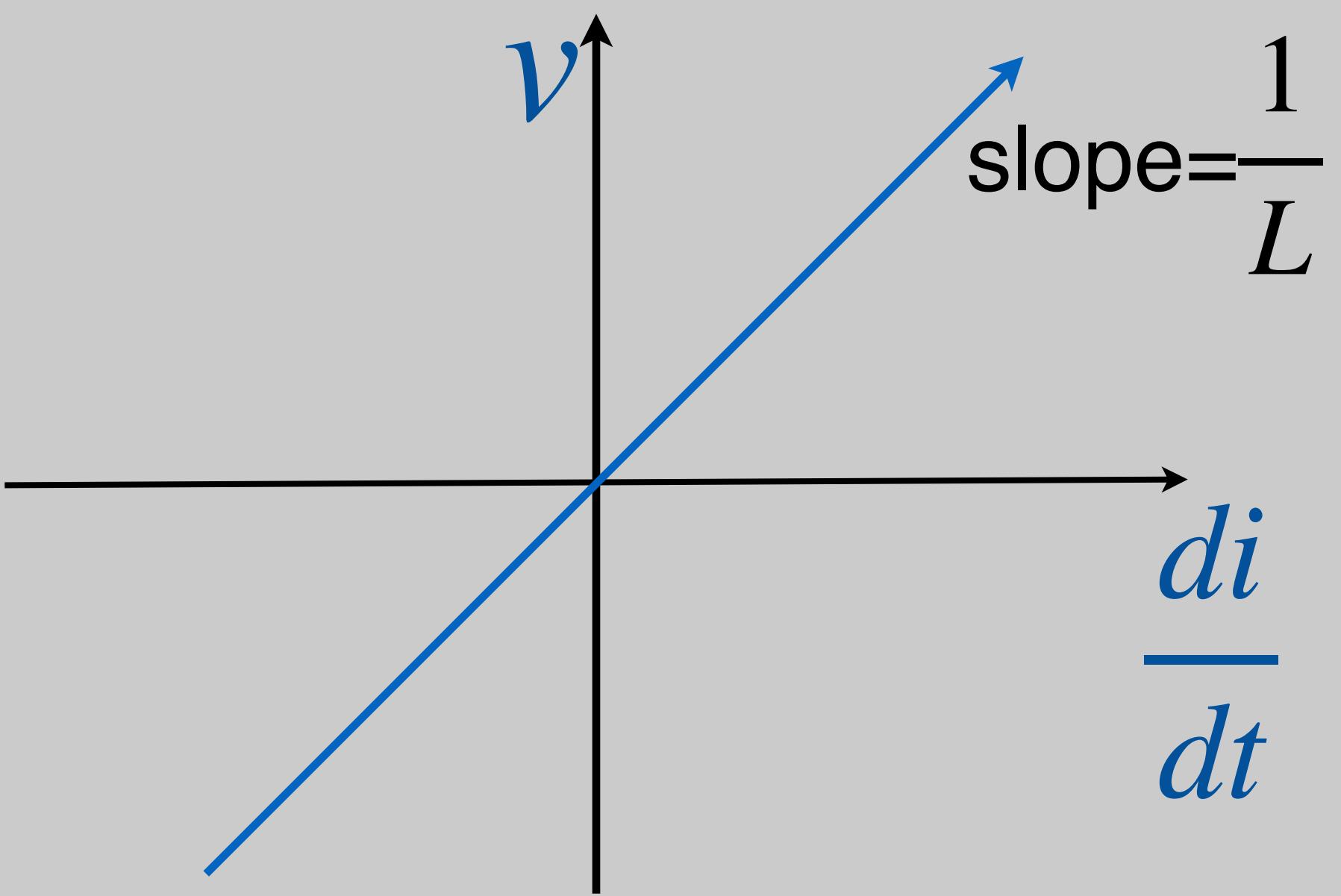

Inductors

- Inductors store energy in the magnetic field


- Power $p(t)$:

$$\begin{aligned} p(t) &= i(t) \cdot v(t) \\ &= L i(t) \frac{di(t)}{dt} \end{aligned}$$

$$p(t)dt = L i(t) di(t)$$


- Energy w is integration of power:
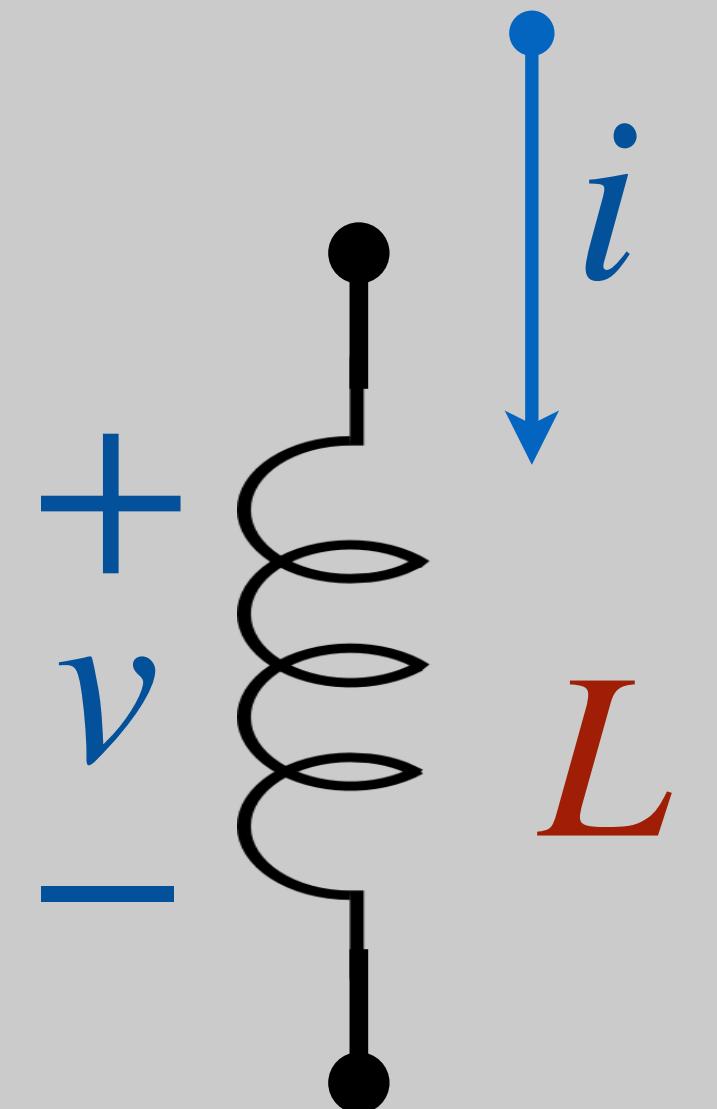
$$w = L \int_0^I i di = L \frac{i^2}{2}$$



Equivalent Inductance

~~Parallel~~
Parallel Inductors:

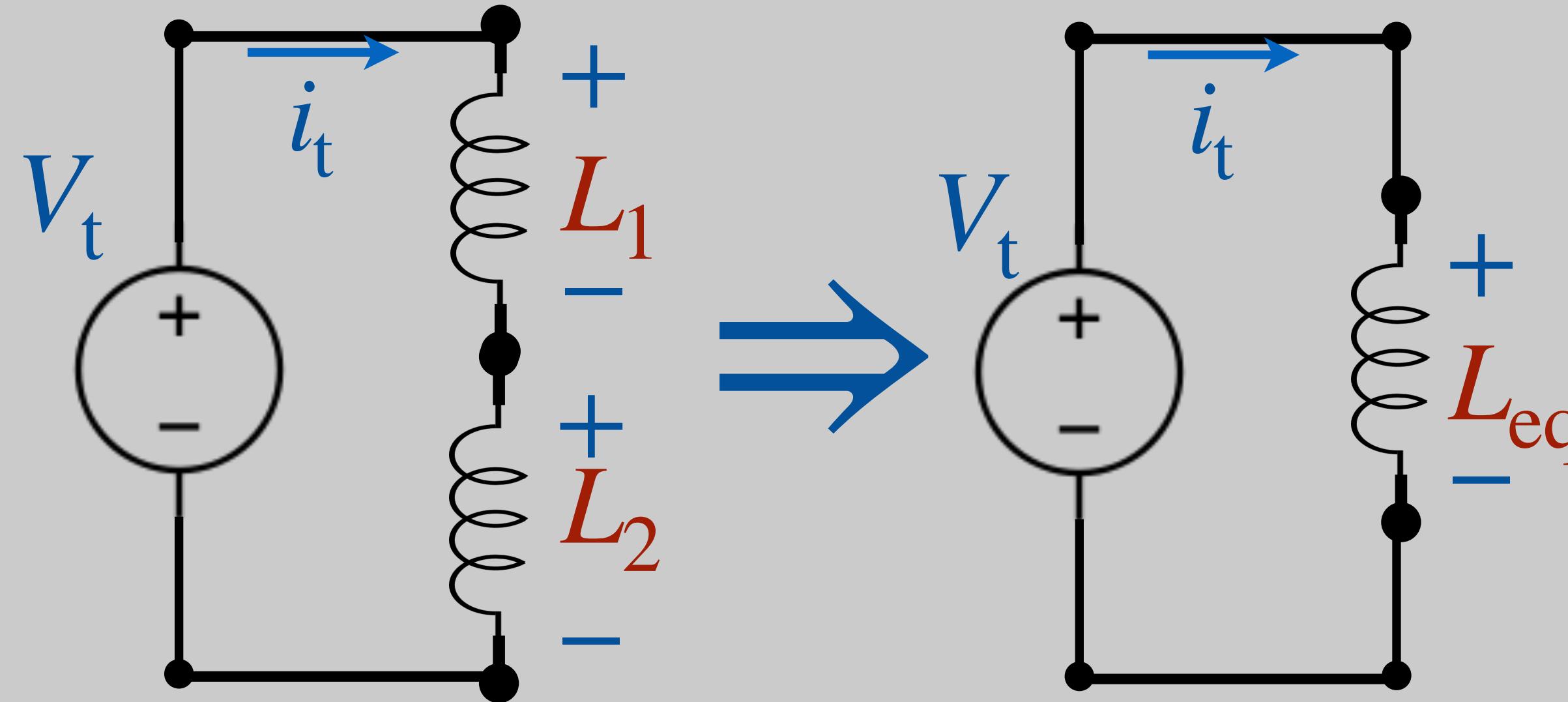


~~Series~~
Parallel Series Inductors:

$$V_t = L_1 \frac{di_t}{dt} + L_2 \frac{di_t}{dt} = (L_1 + L_2) \frac{di_t}{dt}$$

$$L_{eq} = L_1 + L_2$$

Equivalent Inductance

~~Parallel~~ ^{series} Inductors:

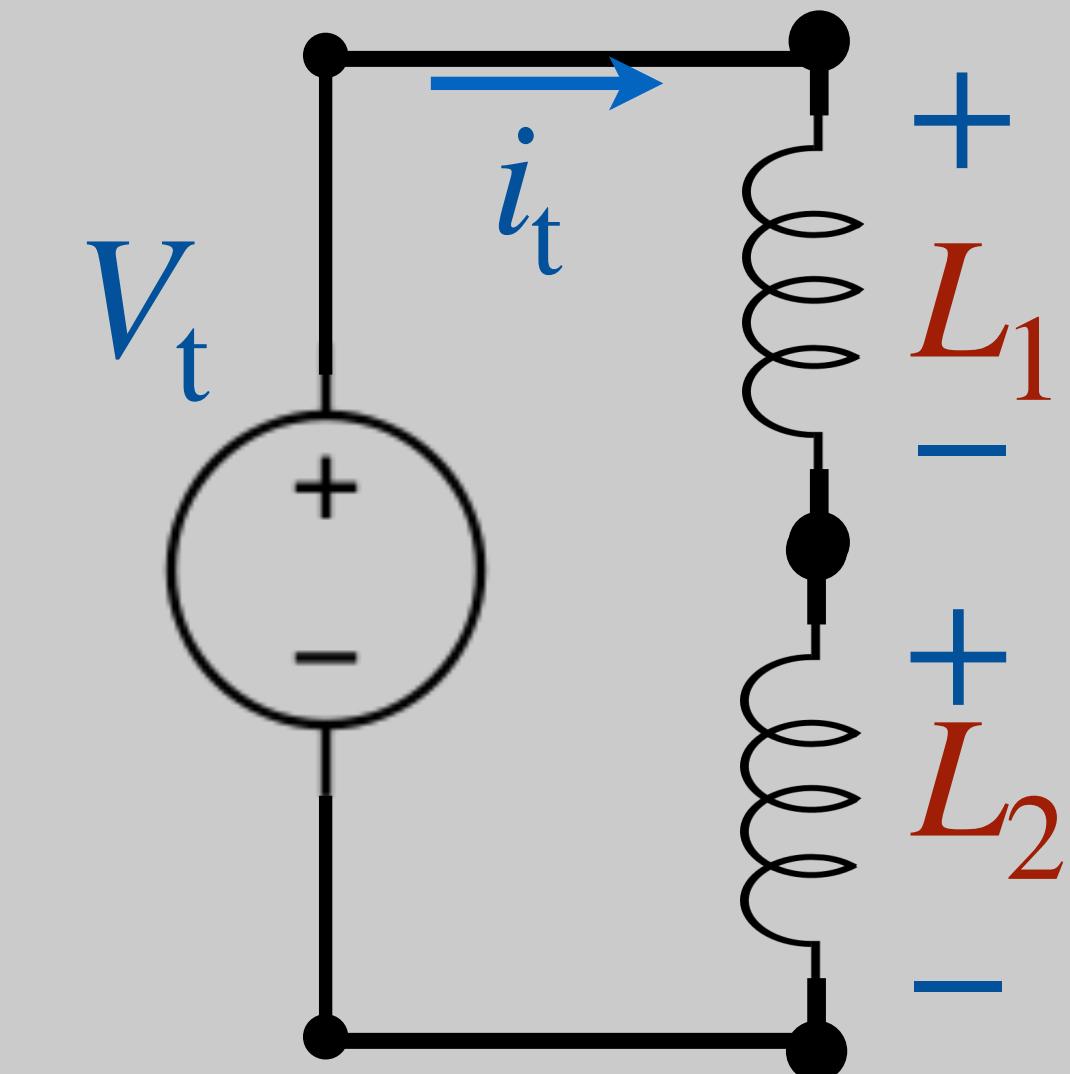


$$V_t = L_1 \frac{di_t}{dt} + L_2 \frac{di_t}{dt} = (L_1 + L_2) \frac{di_t}{dt}$$

$$L_{\text{eq}} = L_1 + L_2$$

Same as resistors!

~~Parallel~~ ^{series} Inductors:

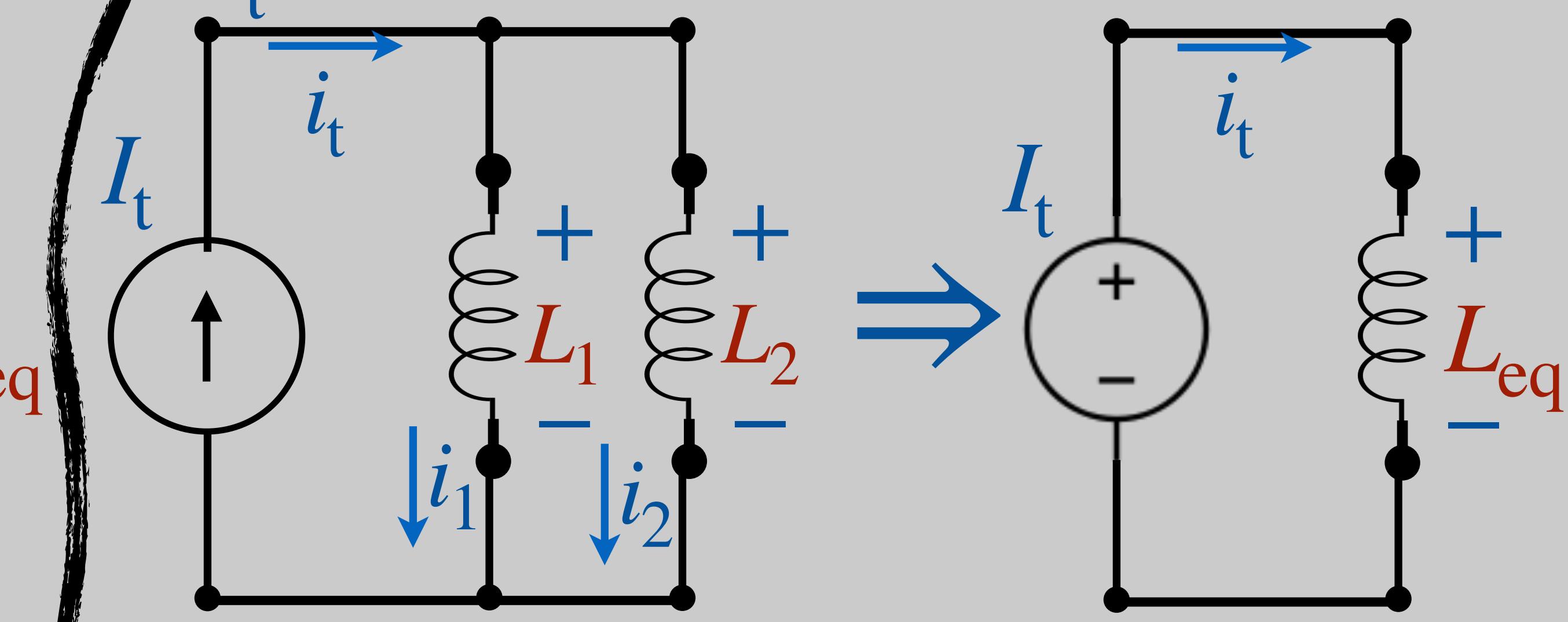

$$L_1 \frac{di_1}{dt} = L_2 \frac{di_2}{dt} = V_t$$

$$i_t = i_1 + i_2 \quad \Rightarrow \quad \frac{di_t}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt}$$

$$\frac{V_t}{L_{\text{eq}}} = \frac{V_t}{L_1} + \frac{V_t}{L_2} \quad \Rightarrow \quad \frac{1}{L_{\text{eq}}} = \frac{1}{L_1} + \frac{1}{L_2}$$

Summary

Capacitors

$$i(t) = C \frac{dv(t)}{dt}$$

$$w = \frac{1}{2} Cv^2$$

- Capacitors resist instantaneous change in voltage
- Current can change instantaneously
- Open circuit in steady-state

$$C_{\text{par}} = C_1 + C_2$$

$$\frac{1}{C_{\text{ser}}} = \frac{1}{C_1} + \frac{1}{C_2}$$

Inductors

$$v(t) = L \frac{di(t)}{dt}$$


$$w = \frac{1}{2} Li^2$$

- Inductors resist instantaneous change in current
- Voltage can change instantaneously
- Short circuit in steady-state

$$\frac{1}{L_{\text{par}}} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$L_{\text{ser}} = L_1 + L_2$$

RL Circuits

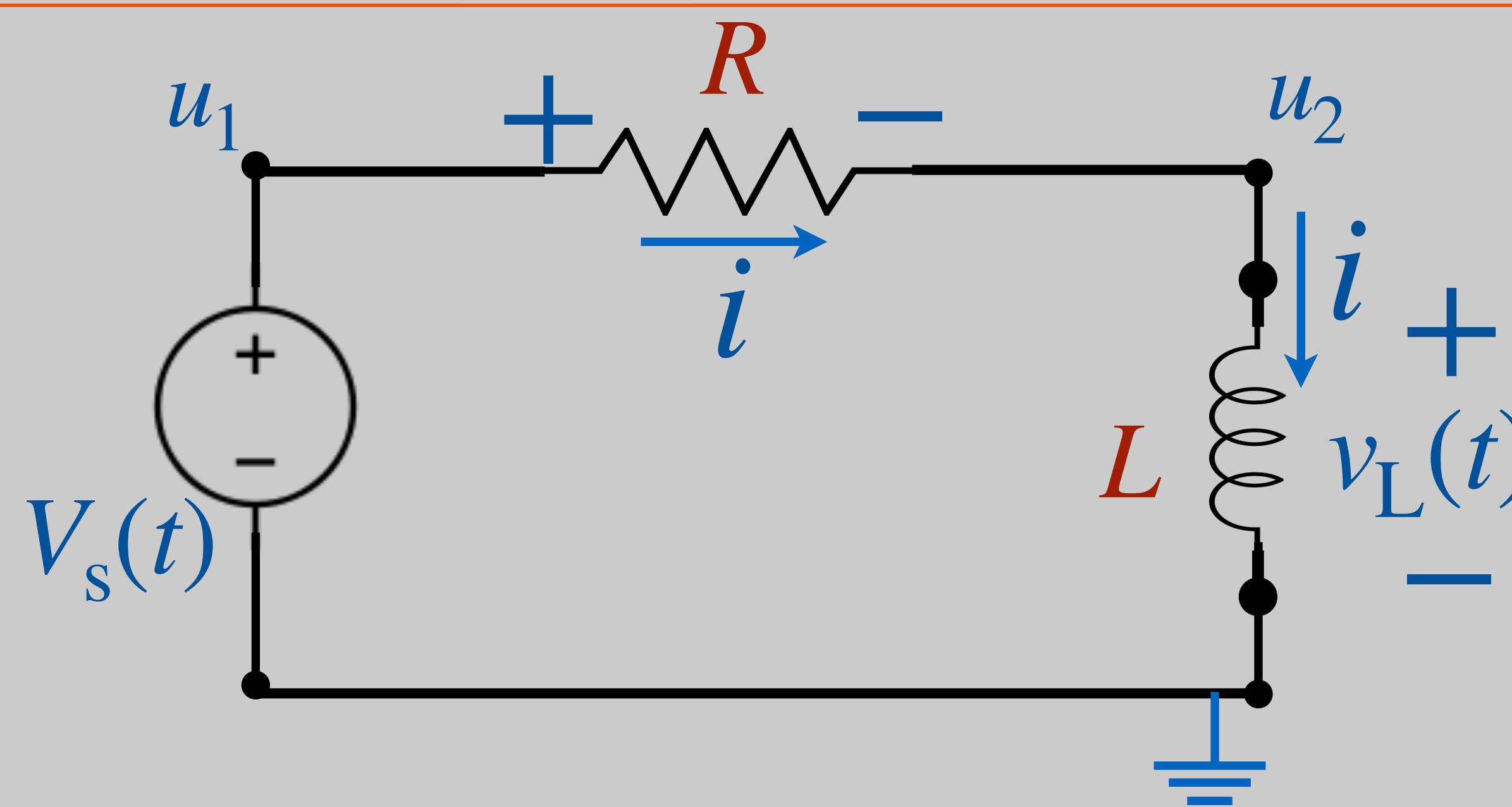

$$V_s - L \frac{di}{dt} = iR$$

$$L \frac{di}{dt} + Ri = V_s$$

$$\Rightarrow \frac{di(t)}{dt} + \frac{R}{L}i(t) = \frac{V_s(t)}{L}$$

$$u_1 = V_s$$



$$u_2 = v_L$$

$$V_s - v_L = iR$$

$$v_L = L \frac{di}{dt}$$

Constant coefficients
1st order diff. Eq.

RL Circuits

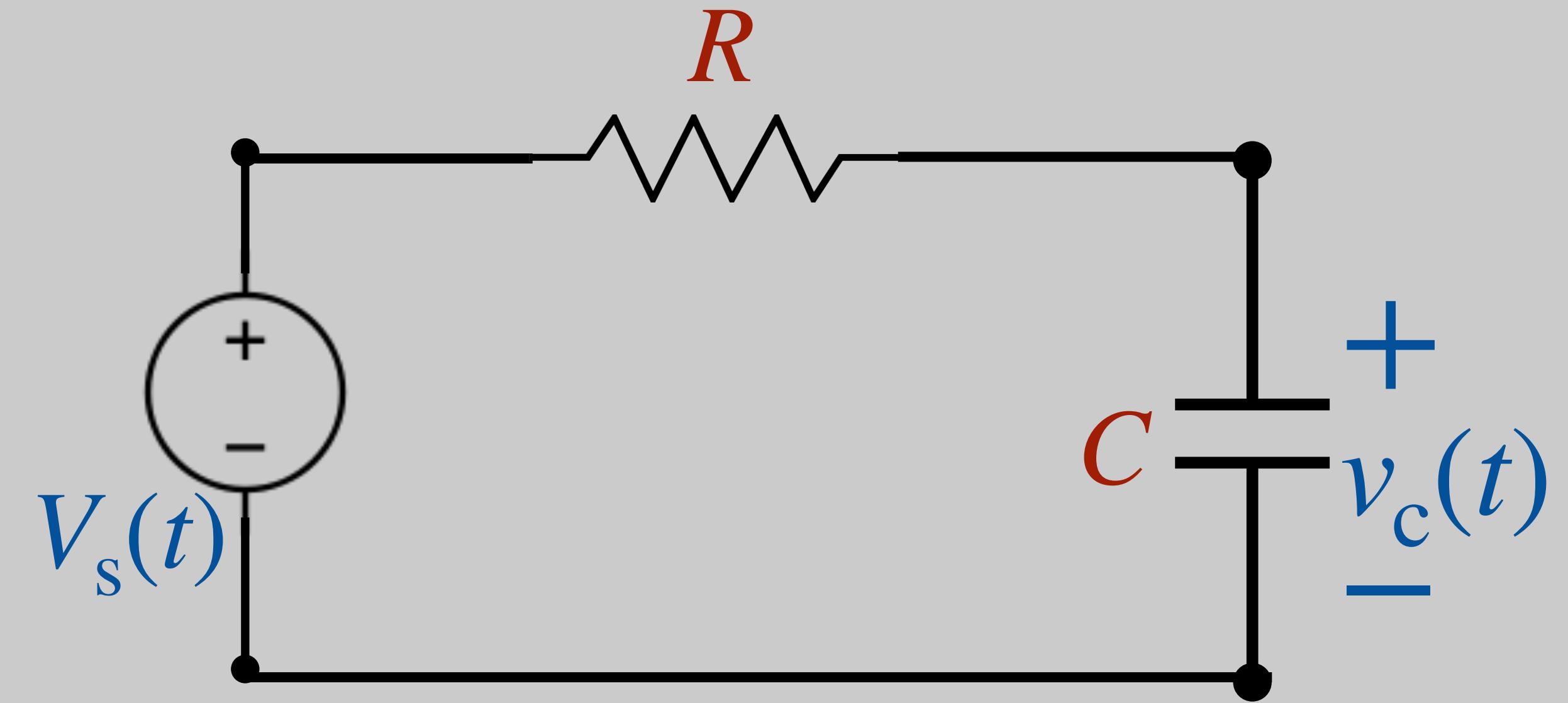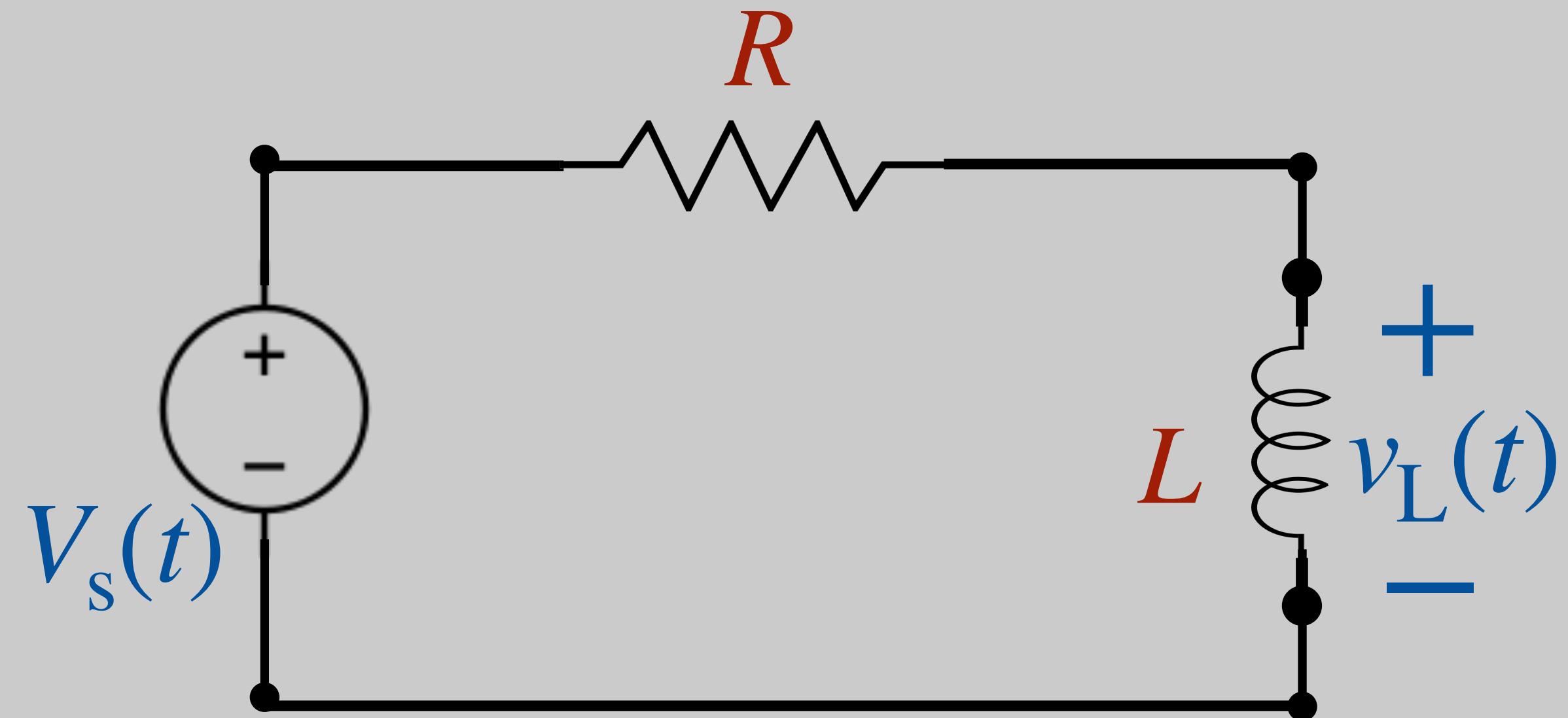



$$\frac{di(t)}{dt} + \frac{R}{L}i(t) = \frac{V_s(t)}{L}$$

$$\frac{di(t)}{dt} + \frac{R}{L}i(t) = \frac{R}{L} \frac{V_s(t)}{R}$$

$$\frac{dv_c(t)}{dt} + \frac{1}{RC}v_c(t) = \frac{1}{RC}V_s(t)$$



RL Circuits

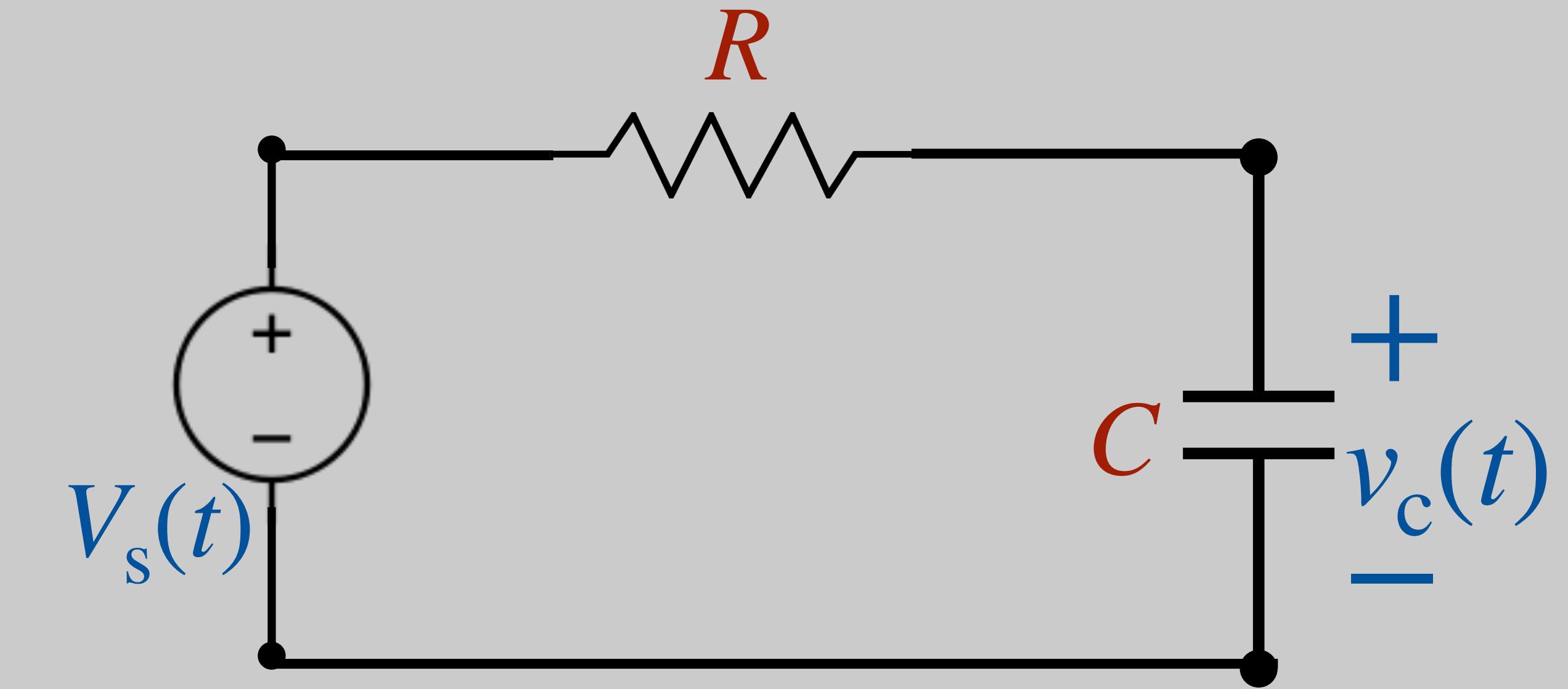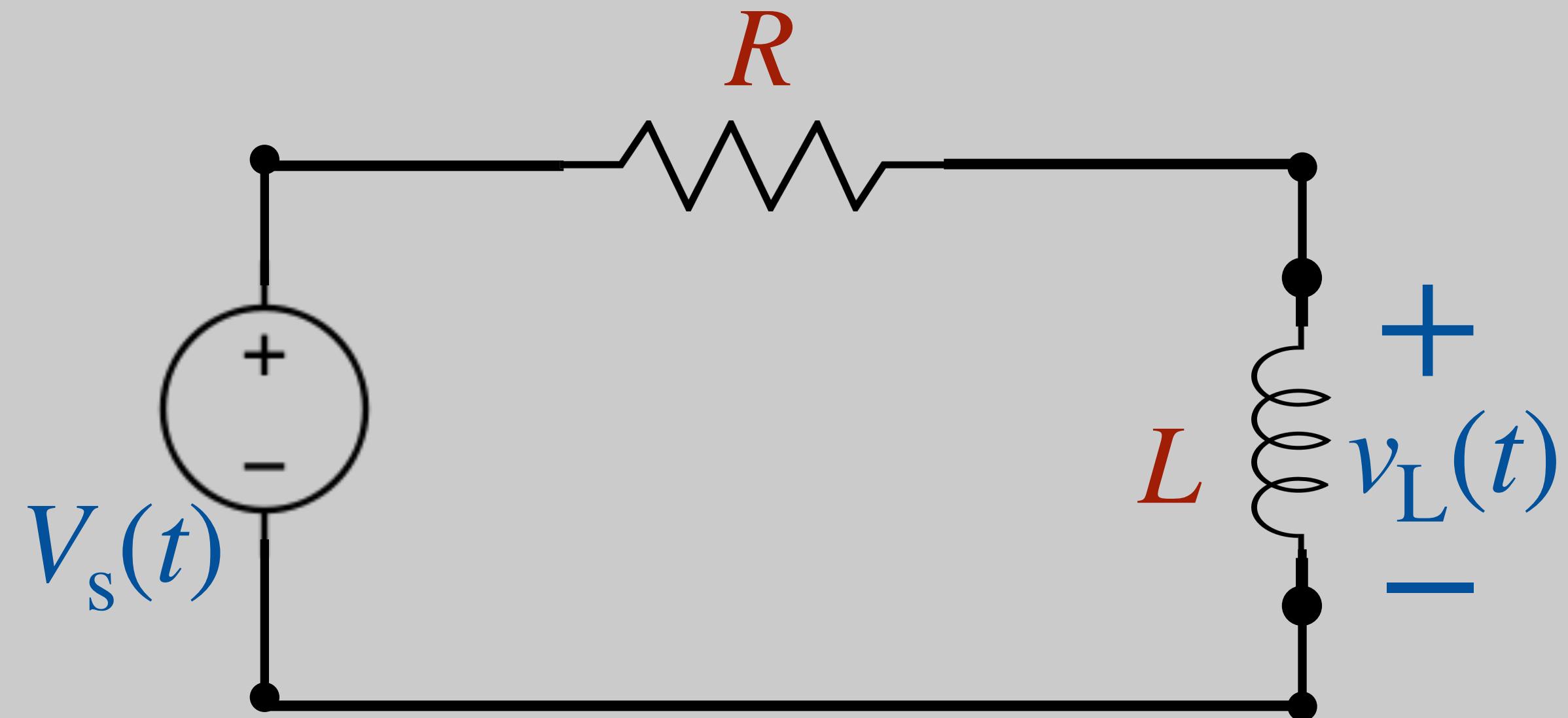

$$\frac{di(t)}{dt} + \frac{R}{L}i(t) = \frac{R}{L}\frac{V_s(t)}{R}$$

$$\frac{dv_c(t)}{dt} + \frac{1}{RC}v_c(t) = \frac{1}{RC}V_s(t)$$

$$\tau = \frac{L}{R}$$


$$\frac{di(t)}{dt} + \tau^{-1}i(t) = \tau^{-1}\frac{V_s(t)}{R}$$

$$\tau = RC$$

$$\frac{dv_c(t)}{dt} + \tau^{-1}v_c(t) = \tau^{-1}V_s(t)$$

Step Response of LC circuits
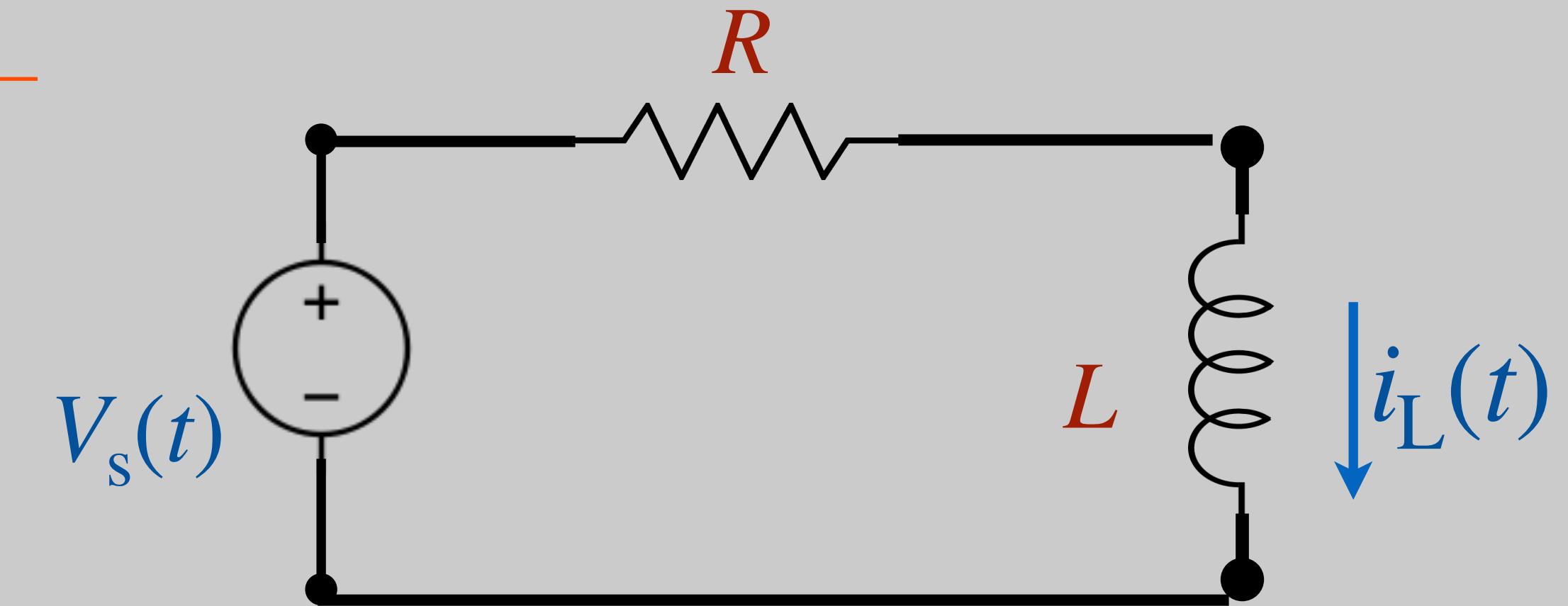
$$\frac{di(t)}{dt} + \frac{R}{L}i(t) = \frac{R}{L}\frac{V_0(t)}{R}$$




Example: Step-Response

$$V_s(t) = V_0 \quad | t > t_0$$

$$i_L(t_0) = 0$$

$$v_L = V_0 - iR$$

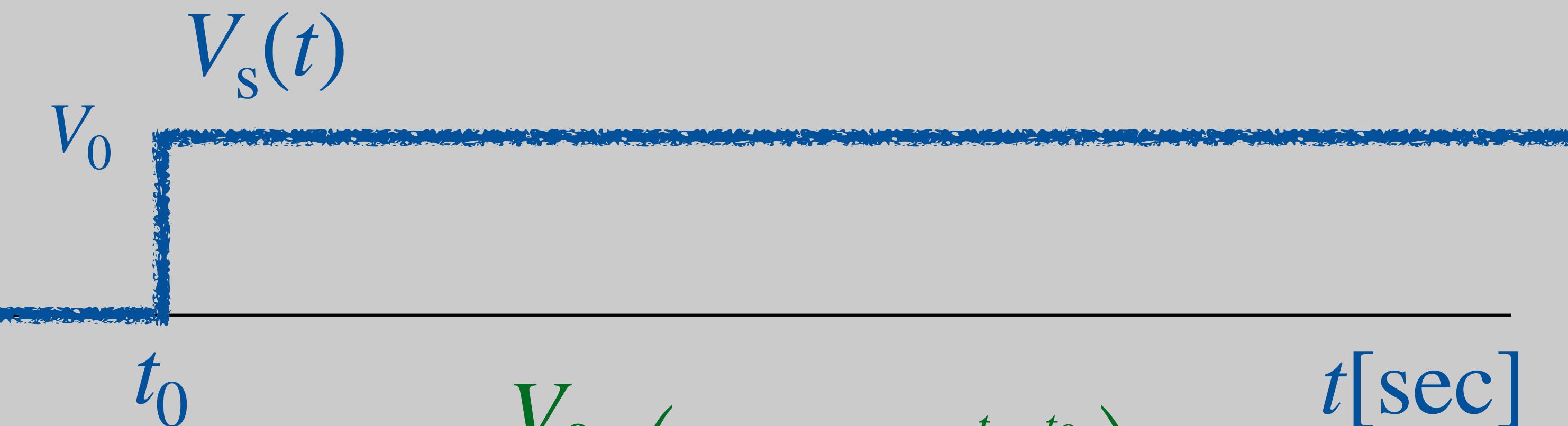


$$i_L = \frac{V_0}{R} \left(1 - e^{-L\frac{t-t_0}{R}} \right)$$

$$v_L = V_0 - V_0 \left(1 - e^{-L\frac{t-t_0}{R}} \right)$$


$$\Rightarrow v_L = V_0 e^{-L\frac{t-t_0}{R}}$$

Step Response of LC circuits
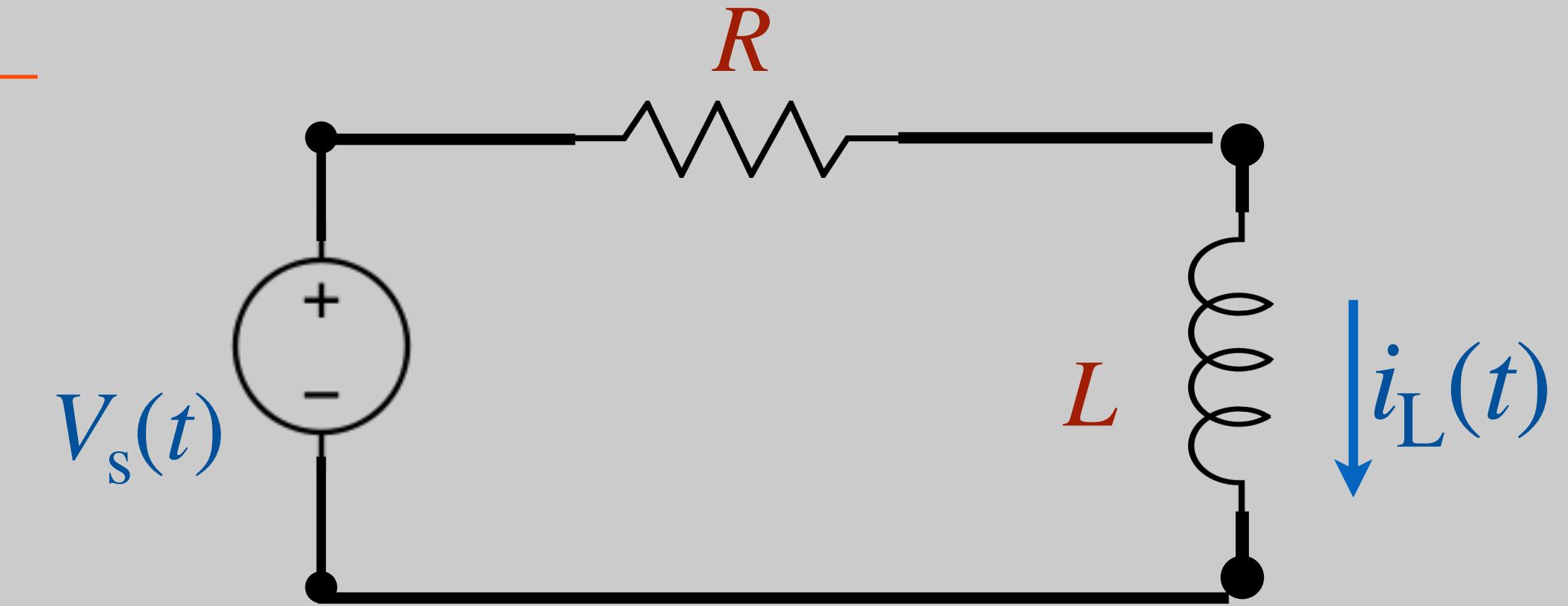
$$\frac{di(t)}{dt} + \frac{R}{L}i(t) = \frac{R}{L}\frac{V_0(t)}{R}$$



Example: Step-Response

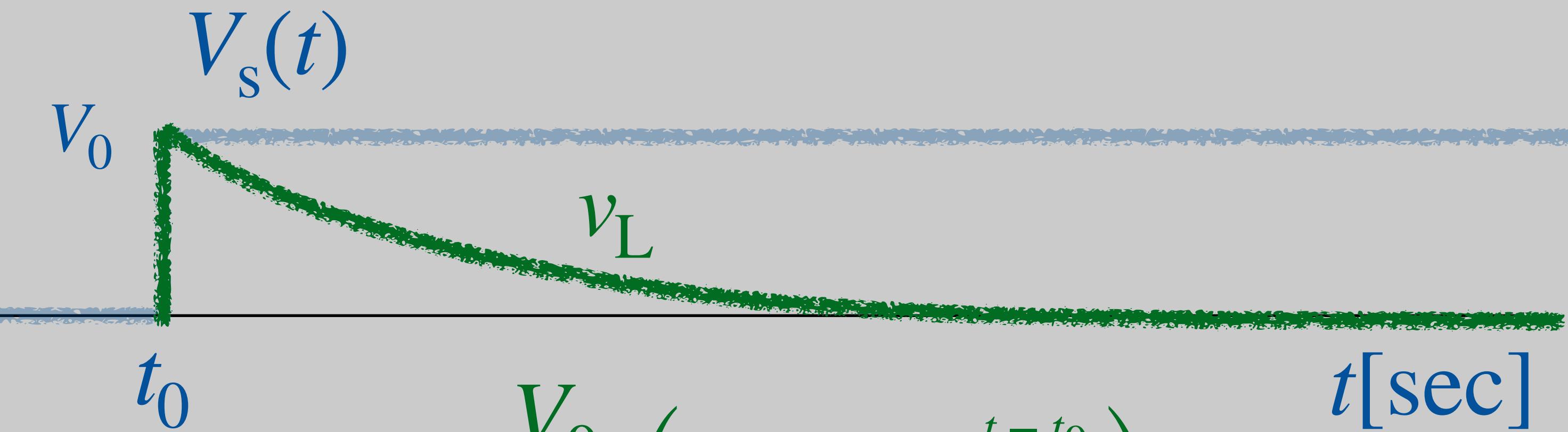

$$V_s(t) = V_0 \quad |t > t_0$$

$$i_L(t_0) = 0$$

$$v_L = V_0 - iR$$


$$i_L = \frac{V_0}{R} \left(1 - e^{-L\frac{t-t_0}{R}} \right)$$

$$v_L = V_0 - V_0 \left(1 - e^{-L\frac{t-t_0}{R}} \right)$$

$$\Rightarrow v_L = V_0 e^{-L\frac{t-t_0}{R}}$$

Mutual Inductance

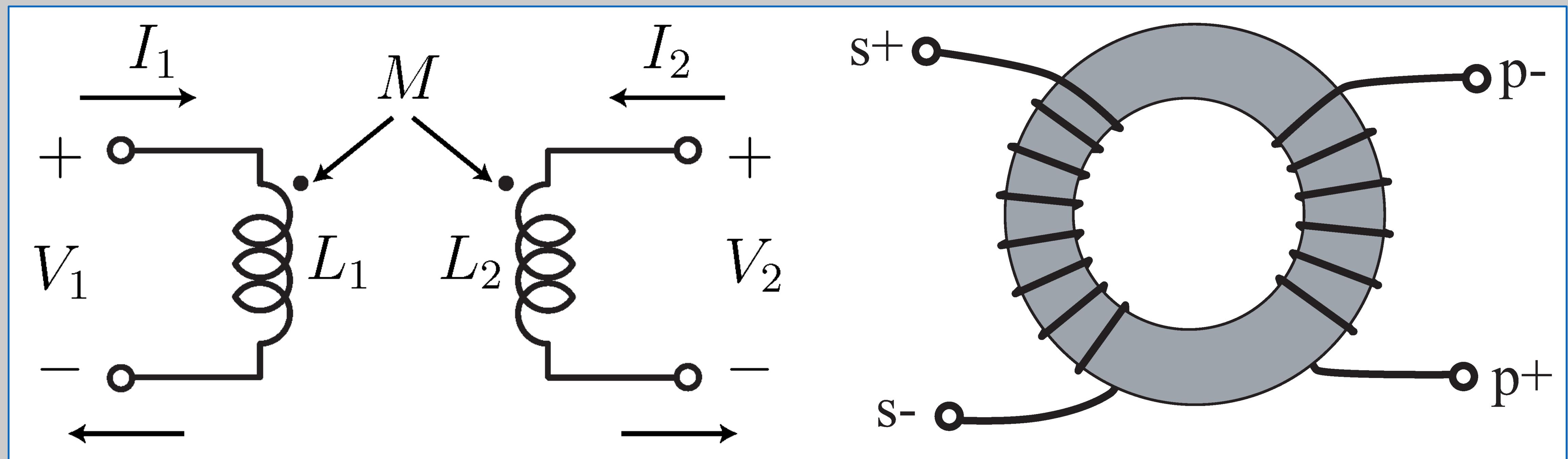
- Occurs when two windings are arranged such flux generated in one runs through the other
- Change in current in one winding, causes voltage in the other



Used in transformers, motors and generators


Dot Convention

- Dot indicates polarity of coupling

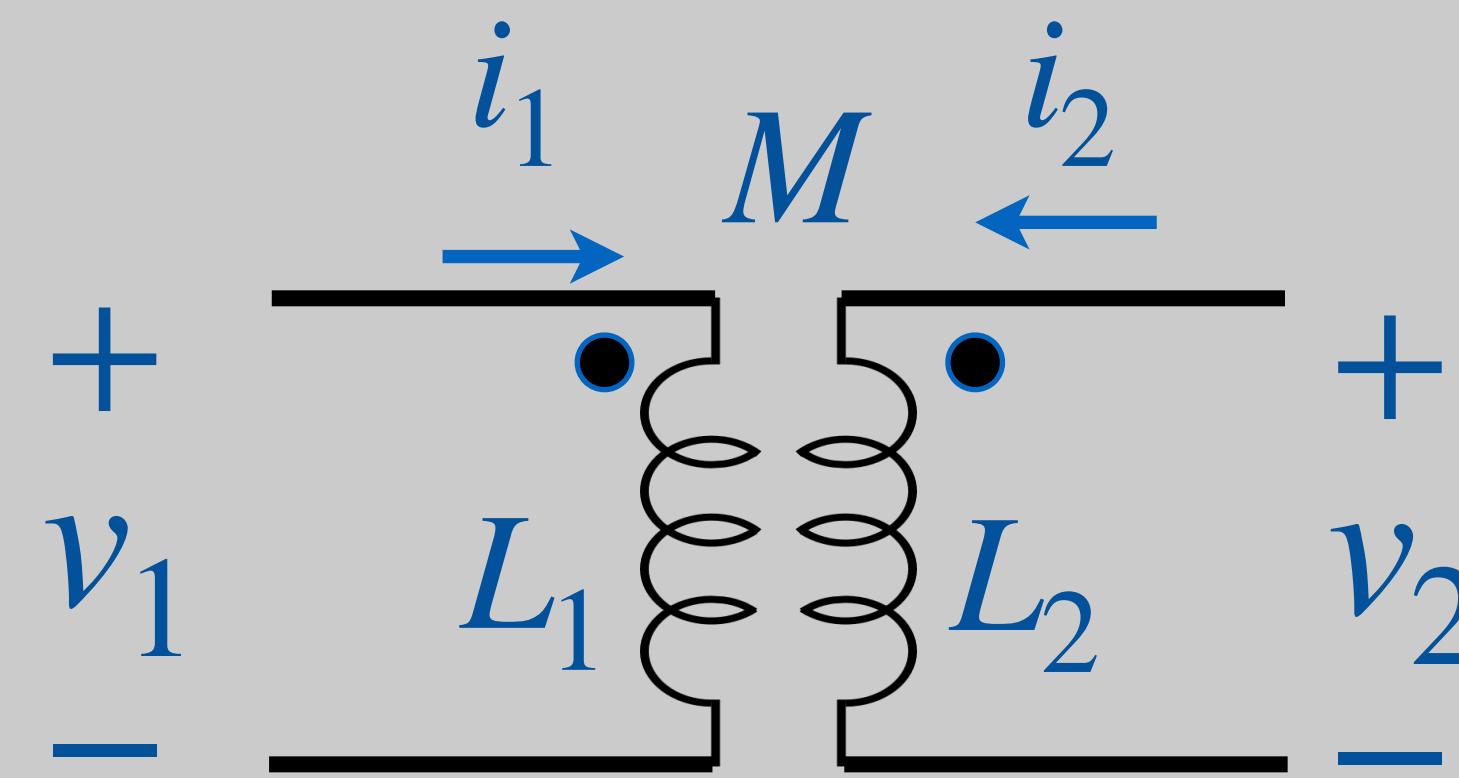

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$


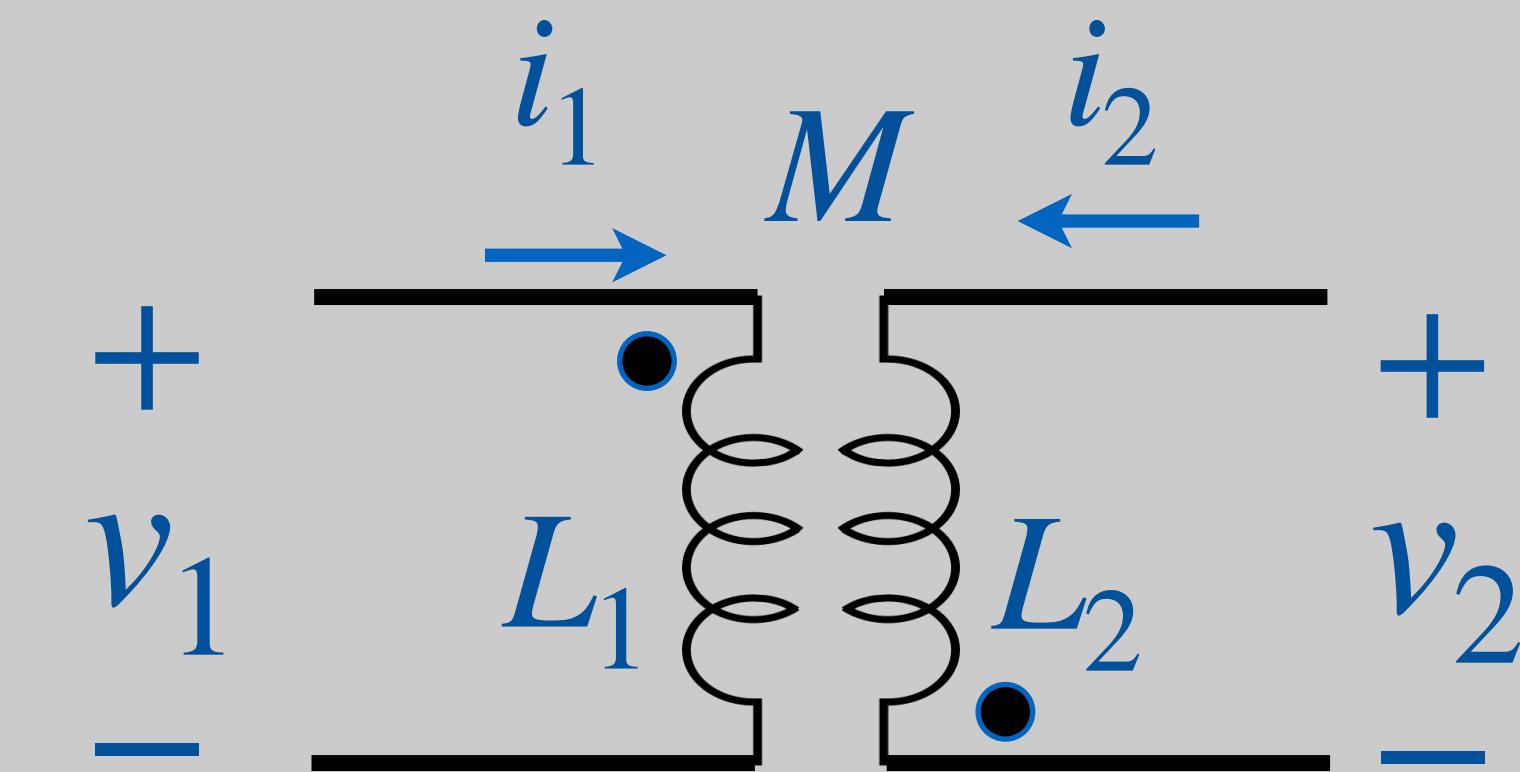
$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$




$$v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$v_2 = -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

RFID: Transformer at a distance!

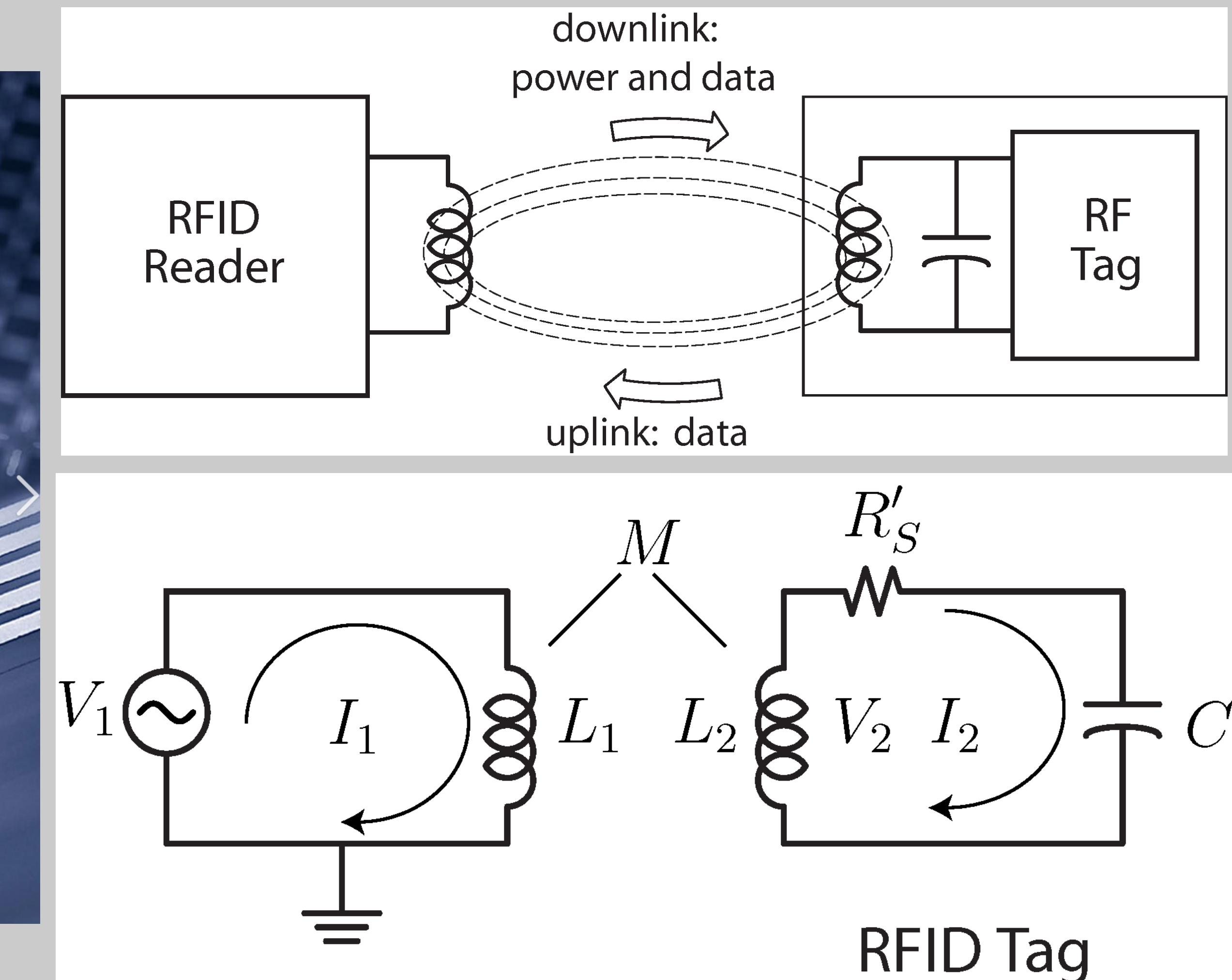
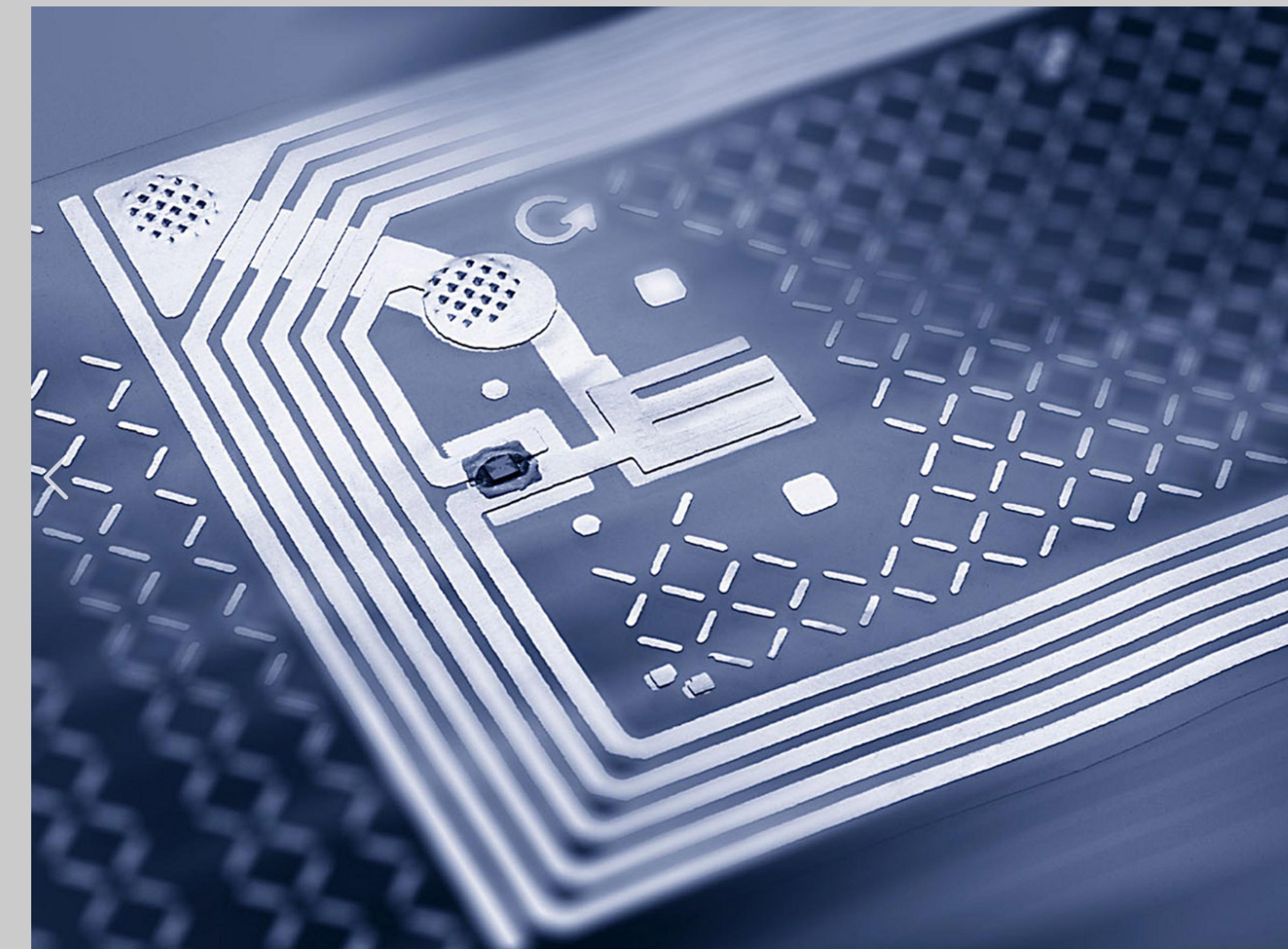


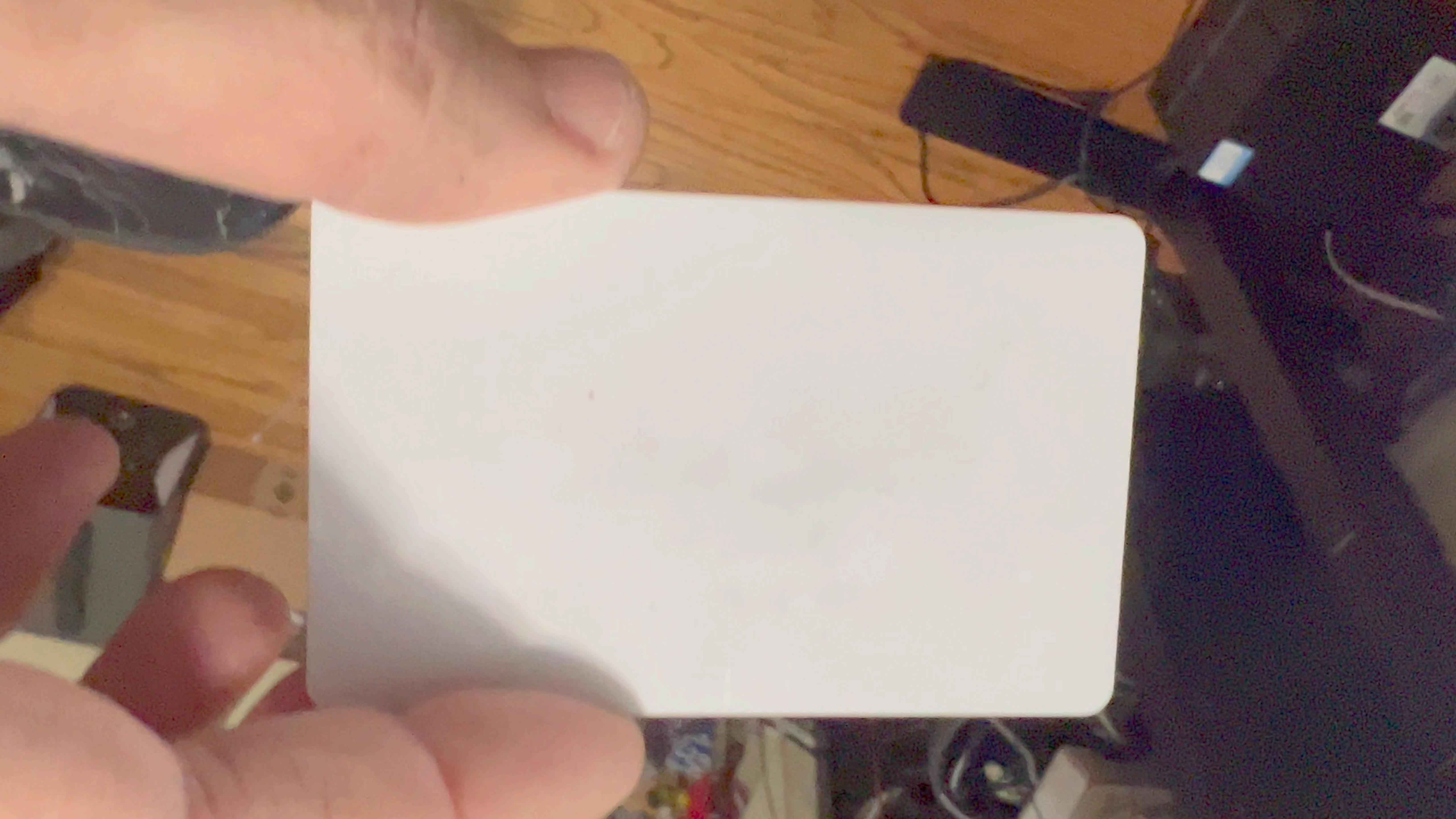- Card Keys, contactless payment, wireless charging




Why twist wires?

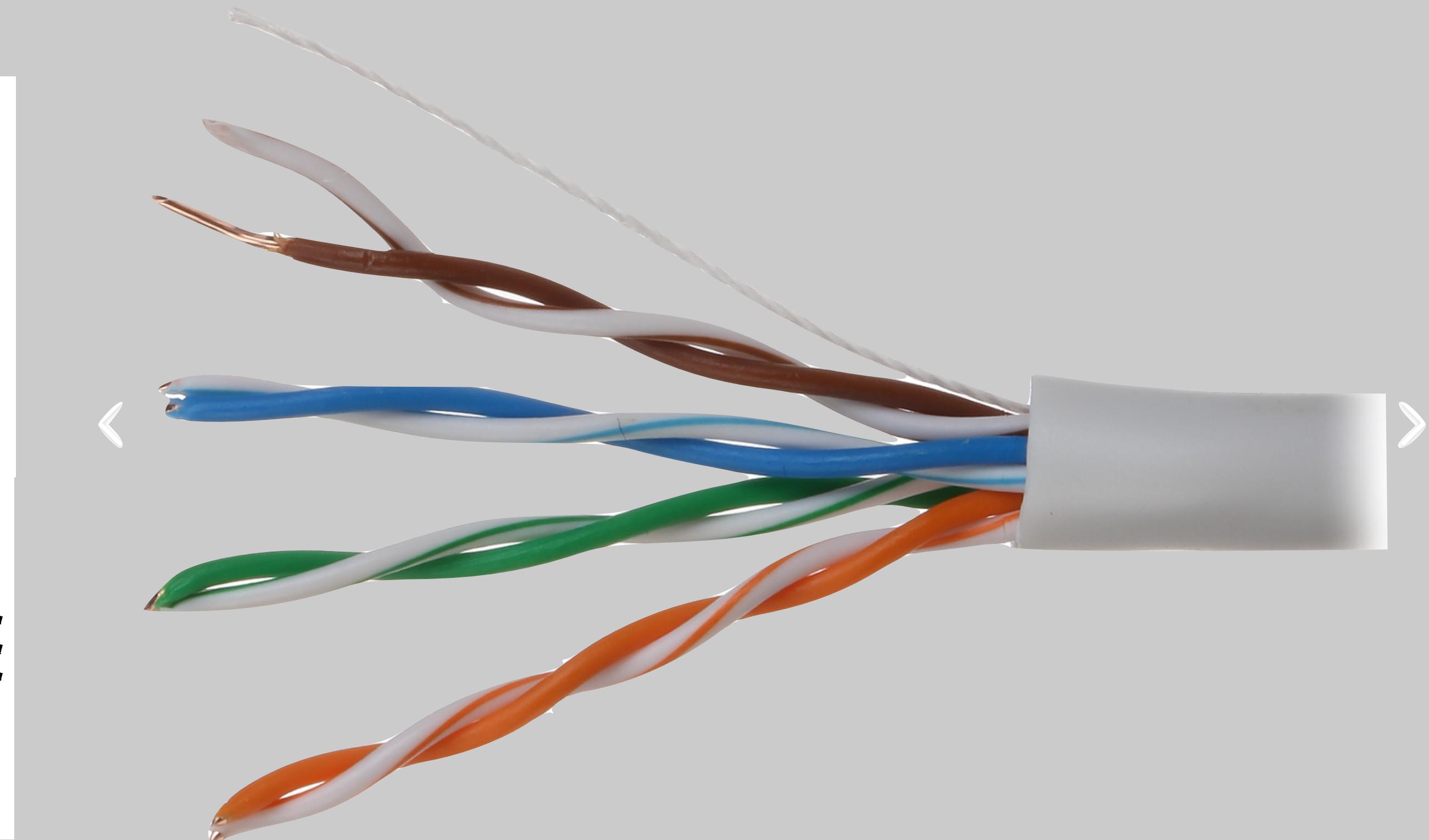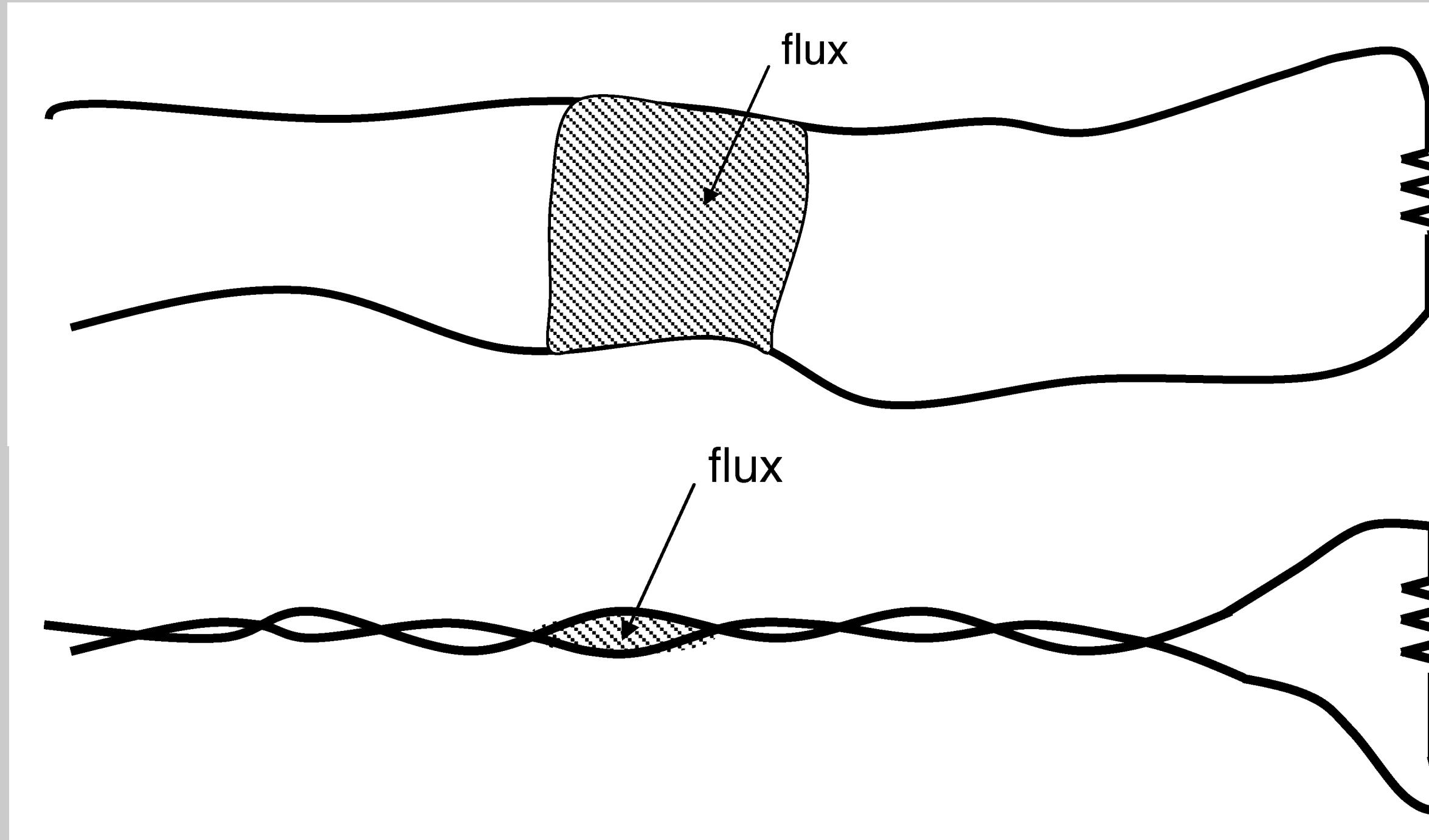- Any loop can capture flux
- Captures interference through mutual inductance



RC Circuits - General Response
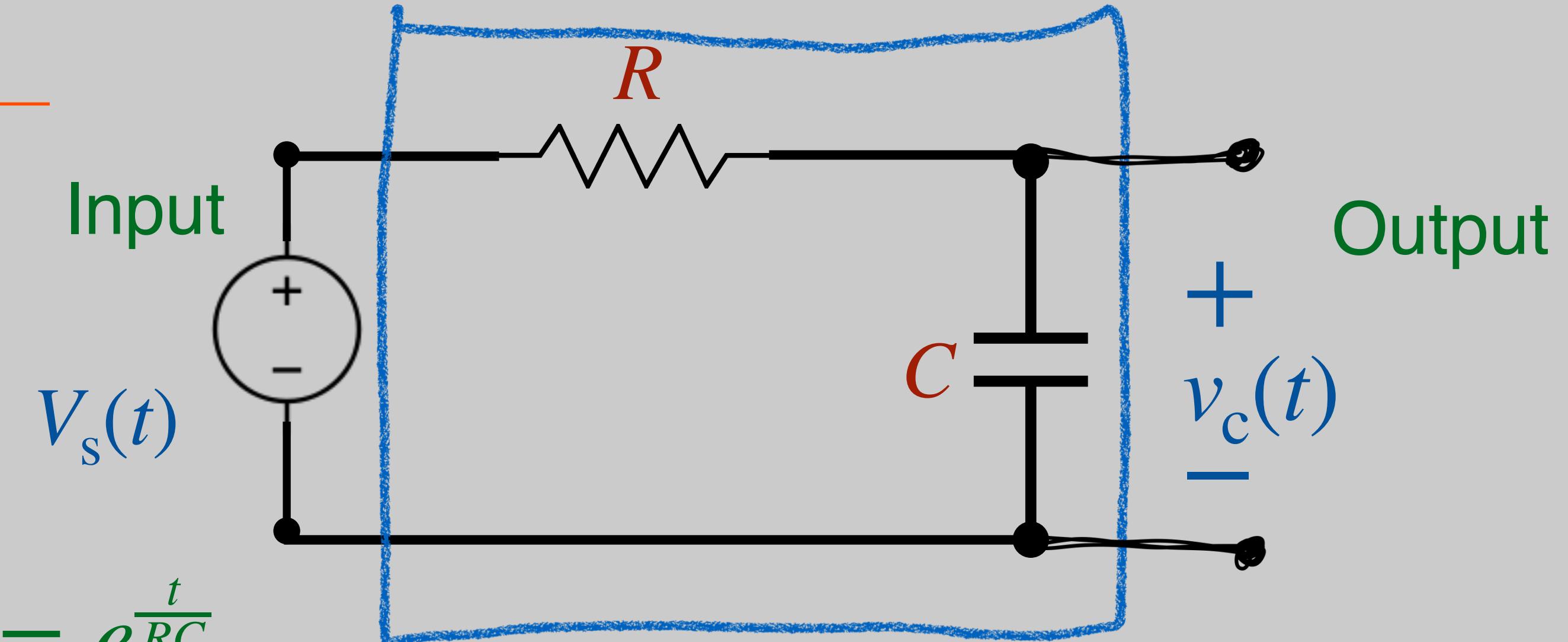
$$\frac{dv_c(t)}{dt} + \frac{1}{RC} v_c(t) = \frac{1}{RC} V_s(t)$$



Method of integrating factor. Use: $m(t) = e^{\frac{t}{RC}}$

$$v'_c m + \frac{1}{RC} v_c m = \frac{1}{RC} V_s m$$


$$(v_c m)' = \frac{1}{RC} V_s m$$

$$v_c(t)m(t) = \frac{1}{RC} \int_{-\infty}^t V_s(\tau)m(\tau)d\tau + K$$

$$\begin{aligned} \text{Since: } m(t) &= e^{\frac{t}{RC}} \\ m' &= \frac{1}{RC} e^{\frac{t}{RC}} = \frac{1}{RC} m \\ \text{Also,} \\ \text{recall: } (v_c m)' &= v'_c m + v_c m' \\ &= v'_c m + \frac{1}{RC} v_c m \end{aligned}$$

RC Circuits - General Response
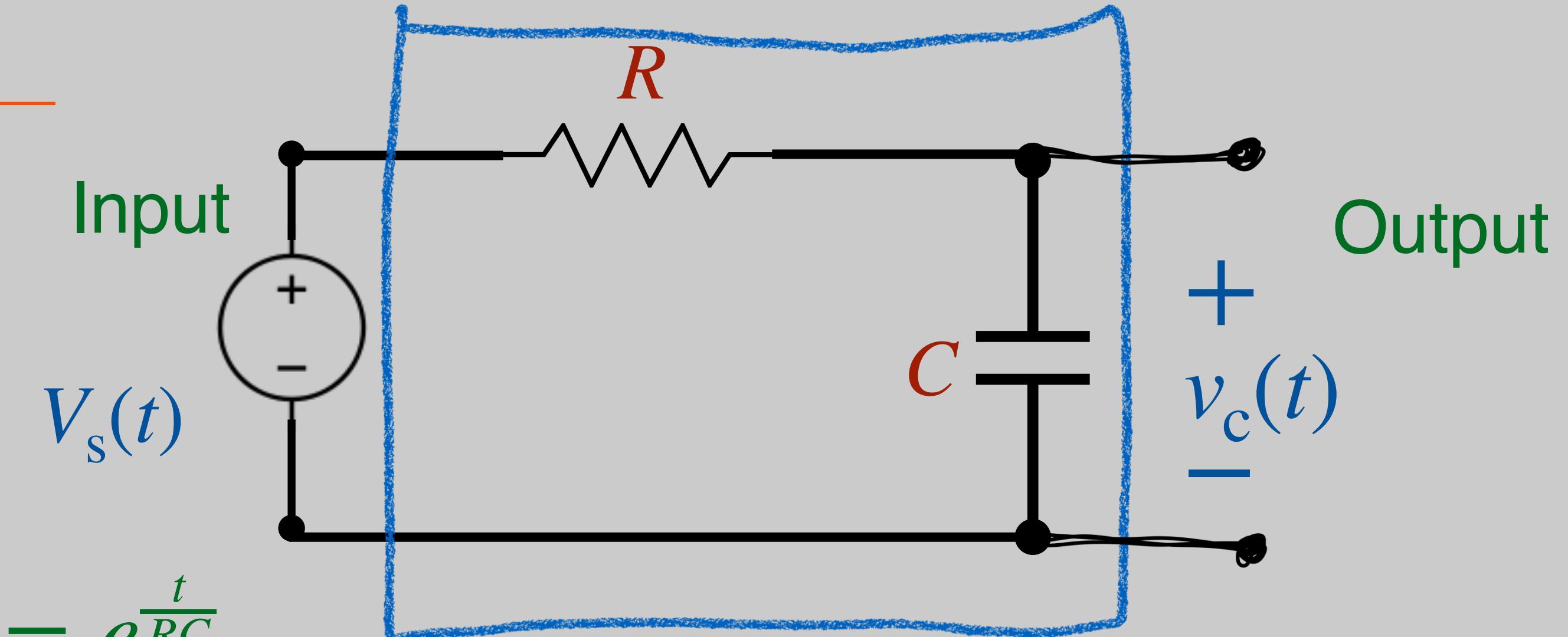
$$\frac{dv_c(t)}{dt} + \frac{1}{RC} v_c(t) = \frac{1}{RC} V_s(t)$$



Method of integrating factor. Use: $m(t) = e^{\frac{t}{RC}}$

$$v'_c m + \frac{1}{RC} v_c m = \frac{1}{RC} V_s m$$

$$(v_c m)' = \frac{1}{RC} V_s m$$

$$v_c(t)m(t) = \frac{1}{RC} \int_{-\infty}^t V_s(\tau)m(\tau)d\tau + K$$

$$v_c(t)e^{\frac{t}{RC}} = K + \frac{1}{RC} \int_{-\infty}^t V_s(\tau)e^{\frac{\tau}{RC}} d\tau$$

$$v_c(t) = K e^{-\frac{t}{RC}} + \frac{e^{-\frac{t}{RC}}}{RC} \int_{-\infty}^t V_s(\tau)e^{\frac{\tau}{RC}} d\tau$$

Homogeneous

Particular