


EE16B
Designing Information
Devices and Systems II

Lecture 2B
Transistors I


Announcements

- Last time:
 - Inductance, inductors, transformers
 - Solving diff. EQ for arbitrary inputs
- Today:
 - Lab 2
 - Transistors


ADCs and DACs

 

R-2R DAC

 


R-2R DAC

 


Solve Via Super Position!


R-2R DAC

 

R-2R DAC

 


R-2R DAC

 


$$V_{out} = \frac{V_{bN}}{2}$$

R-2R DAC

 

$$V_{out} = \frac{V_{b0}}{2^N} + \frac{V_{b1}}{2^{N-1}} + \dots + \frac{V_{bN}}{2}$$

R-2R DAC

 


1	0	0	1
---	---	---	---

 $\rightarrow 9/16$

$$2^3 \quad 2^2 \quad 2^1 \quad 2^0$$

Lab 2: SAR ADC

 - Successive Approximation Resistor
- Use DAC to guess bit by bit
- Iterate ($\log(N)$) times



Devices as part of a system



Resistor




Capacitor



Inductor





Diode

 


Transistor


elemains.com

  




Transistor

 

First transistor - Dec 1947

 


First integrated circuit 1958

   

Computational advances due to fabrication advances


 
Moore's law is the observation that the number of transistors in a dense integrated circuit doubles approximately every two years.



Gordon Moore

Intel Cofounder

B.S. Cal
1950!

  

FinFET

2320 IEEE TRANSACTIONS ON ELECTRON DEVICES, VOL. 47, NO. 12, DECEMBER 2000

FinFET—A Self-Aligned Double-Gate MOSFET Scalable to 20 nm

Digh Hisamoto, *Member, IEEE*, Wen-Chin Lee, Jakub Kedzierski, Hideki Takeuchi, Kazuya Asano, *Member, IEEE*, Charles Kuo, Erik Anderson, Tsu-Jae King, Jeffrey Bokor, *Fellow, IEEE*, and Chenming Hu, *Fellow, IEEE*

Abstract—MOSFETs with gate length down to 17 nm are reported. To suppress the short channel effect, a novel self-aligned double-gate MOSFET, FinFET, is proposed. By using boron-doped $\text{Si}_{0.4}\text{Ge}_{0.6}$ as a gate material, the desired threshold voltage was achieved for the ultrathin body device. The quasiplanar nature of this new variant of the vertical double-gate MOSFETs can be fabricated relatively easily using the conventional planar MOSFET process technologies.

Index Terms—Fully depleted SOI, MOSFET, poly SiGe, short-channel effect.

I. INTRODUCTION

TO DEVELOP sub-50-nm MOSFETs, the double-gate structure has been widely studied. This is because

 


Fig. 1. FinFET typical layout and schematic cross sectional structures.




Prof. Tsu-Jae King Liu



Prof. Jeff Bokor






Prof. Chenming Hu (left)

 

Go Bears!

Sense of Scale

   

Mark
1.66 m


Fly
7 mm

Mite
300 um

Blood Cell
7 um


Virus
100 nm

Silicon Atom
0.24 nm

 


MOS Transistor


 
- MOS: metal-oxide-semiconductor
- MOSFET: MOS field effect Transistor
- Two kinds:
 - NMOS - current carried by electrons
 - PMOS - current carried by “holes” (lack of e)



Simplest Circuit Model of NMOS

 


Or:

  


Simplest Circuit Model of NMOS

$$V_{GS} < V_{t_n}$$


 


Simplest Circuit Model of NMOS



$$V_{GS} < V_{t_n}$$

 


$$V_{GS} \geq V_{t_n}$$

  


Simple NMOS Inverter

  


Simple NMOS Inverter

 


$$V_{GS} < V_{t_n}$$

 



$$V_{GS} \geq V_{t_n}$$

 

Simplest Circuit Model of PMOS

 


Or:

  


$$V_{GS} \leq -|V_{t_p}|$$

CMOS (Complementary MOS)

 - PMOS + NMOS
- Very low power consumption inverter
- Dominant technology



CMOS (Complementary MOS)


 


$$V_{in} = V_{DD} \Rightarrow "1"$$

PMOS: $V_{GS} = 0 > -|V_{t_p}|$
⇒ Off, open circuit

NMOS: $V_{GS} = V_{DD} > V_{t_n}$
⇒ On, short circuit

CMOS (Complementary MOS)

  


$V_{in} = V_{DD} \Rightarrow "1"$

PMOS: $V_{GS} = 0 > -|V_{t_p}|$
 \Rightarrow Off, open circuit

NMOS: $V_{GS} = V_{DD} > V_{t_n}$
 \Rightarrow On, short circuit

$$V_{out} = 0V \Rightarrow "0"$$

CMOS (Complementary MOS)


 


$$V_{\text{in}} = 0 \Rightarrow "0"$$

PMOS: $V_{GS} = -V_{DD} < -|V_{t_p}|$
⇒ On, short circuit

NMOS: $V_{GS} = 0 < V_{t_n}$
⇒ Off, open circuit

CMOS (Complementary MOS)

  


$V_{in} = 0 \Rightarrow "0"$

PMOS: $V_{GS} = -V_{DD} < -|V_{t_p}|$
 \Rightarrow On, short circuit


NMOS: $V_{GS} = 0 < V_{t_n}$
 \Rightarrow Off, open circuit

$$V_{out} = V_{DD} \Rightarrow "1"$$


CMOS (Complementary MOS)

 



CMOS (Complementary MOS)

 


CMOS (Complementary MOS)

 

CMOS (Complementary MOS)

  

CMOS (Complementary MOS)

 

CMOS (Complementary MOS)

