

EE16B
Designing Information
Devices and Systems II

Lecture 4A
Phasors, Freq. Response / Transfer function / AC Power

Announcements

- Last time:
 - Second order systems
 - Intro to VDE
 - RLC circuits
- Today:
 - Resonant Tank
 - AC Response / Phasors

Recap:

$$a = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\zeta = \frac{\alpha}{\omega_0}$$

$$Q = \frac{1}{2\zeta} = \frac{\omega_0 L}{R} = \sqrt{\frac{L}{CR^2}}$$

$\alpha > \omega_0, \zeta > 1 \Rightarrow$ Overdamped

$\alpha = \omega_0, \zeta = 1 \Rightarrow$ Critically damped

$\alpha < \omega_0, \zeta < 1 \Rightarrow$ Underdamped


Damping coefficient (associated with decay)

Resonance frequency

Damping Ratio

Quality factor
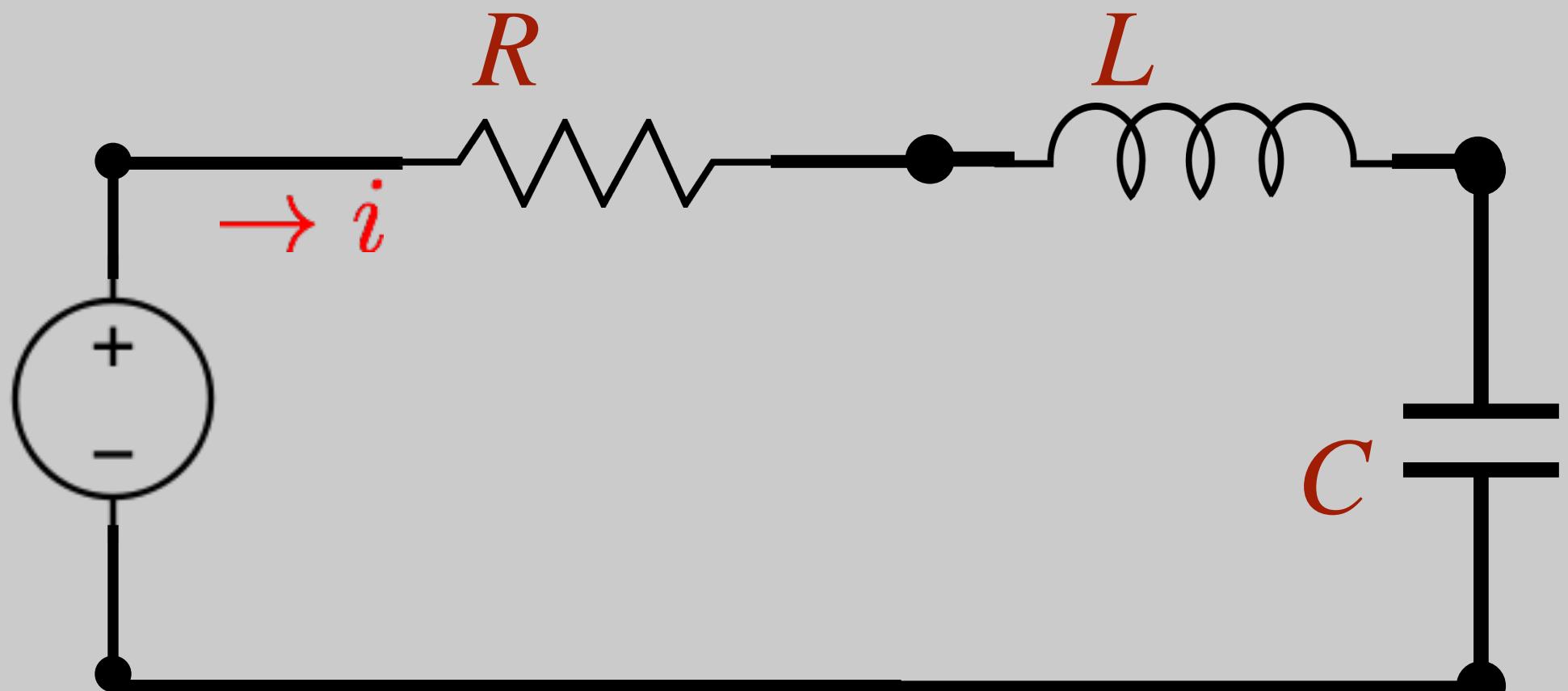
$$\frac{d^2}{dt^2}V_c(t) + 2\alpha\frac{d}{dt}V_c(t) + \omega_0^2V_c(t) = u(t)$$



\Rightarrow Exponential decays

\Rightarrow Fastest decay without oscillations

\Rightarrow decay+oscillations

$\omega_n = \sqrt{\alpha^2 - \omega^2}$ Oscillation frequency

Tank Circuit

RLC with $R \rightarrow 0$


LC “Tank” will store energy

$$V_c(t) = V_{DD} e^{\cancel{-\alpha t}} \left(\cos(\omega_n t) + \frac{\cancel{\alpha}}{\omega_n} \sin(\omega_n t) \right)$$

$$V_c(t) = V_{DD} \cos(\omega_0 t) \quad i(t) = -CV_{DD}\omega_0 \sin(\omega_0 t)$$


Energy in Cap:
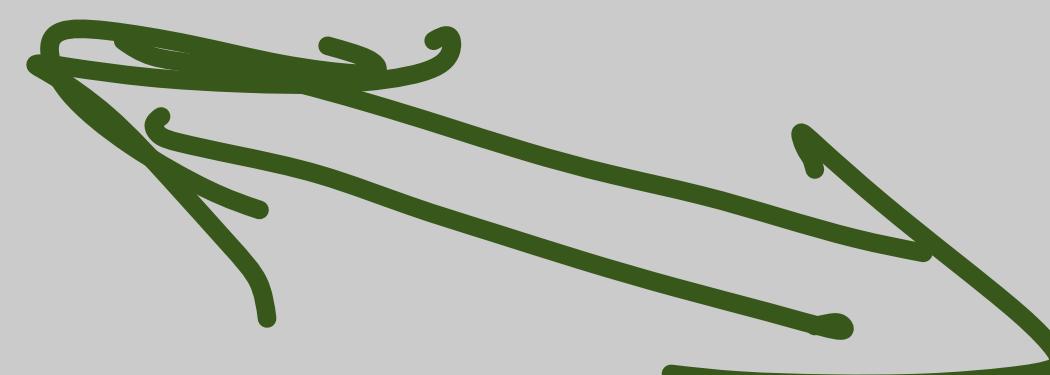
$$W_c = \frac{1}{2}CV_c^2 = \frac{1}{2}CV_{DD}^2 \cos^2(\omega_0 t)$$



Energy in Inductor:
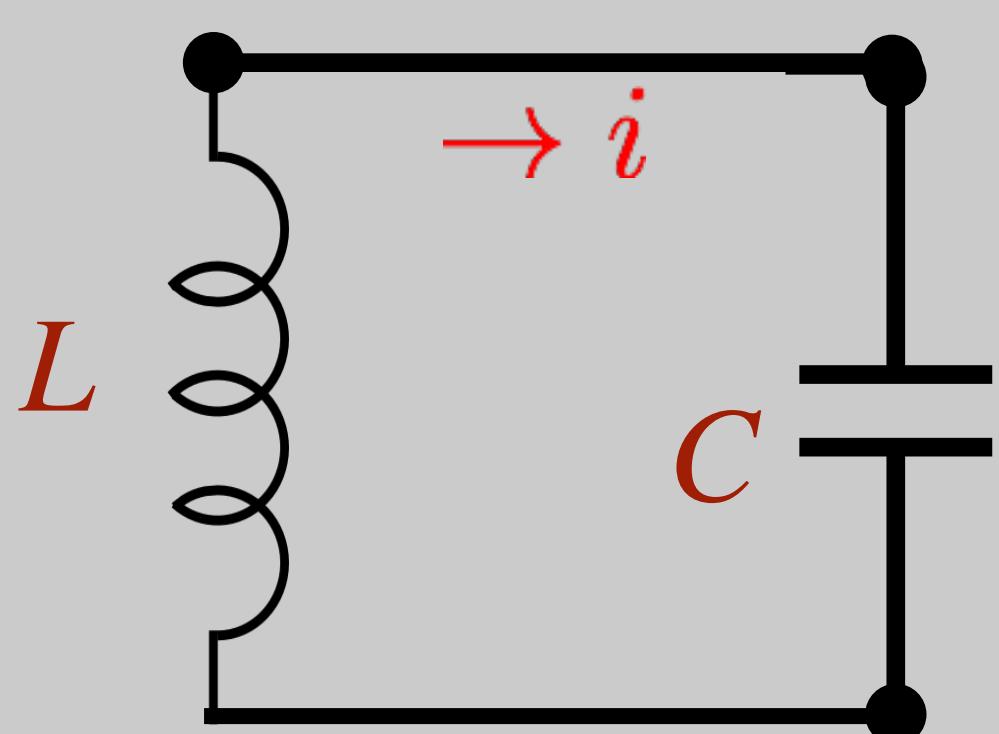
$$\begin{aligned} W_L &= \frac{1}{2}Li^2 = \frac{1}{2}V_{DD}^2 LC^2 \omega_0^2 \sin^2(\omega_0 t) \\ &= \frac{1}{2}CV_{DD}^2 \sin^2(\omega_0 t) \end{aligned}$$





Tank Circuit

Energy in Cap:

$$W_c = \frac{1}{2} C V_{DD}^2 \cos^2(\omega_0 t)$$

Energy in Inductor:
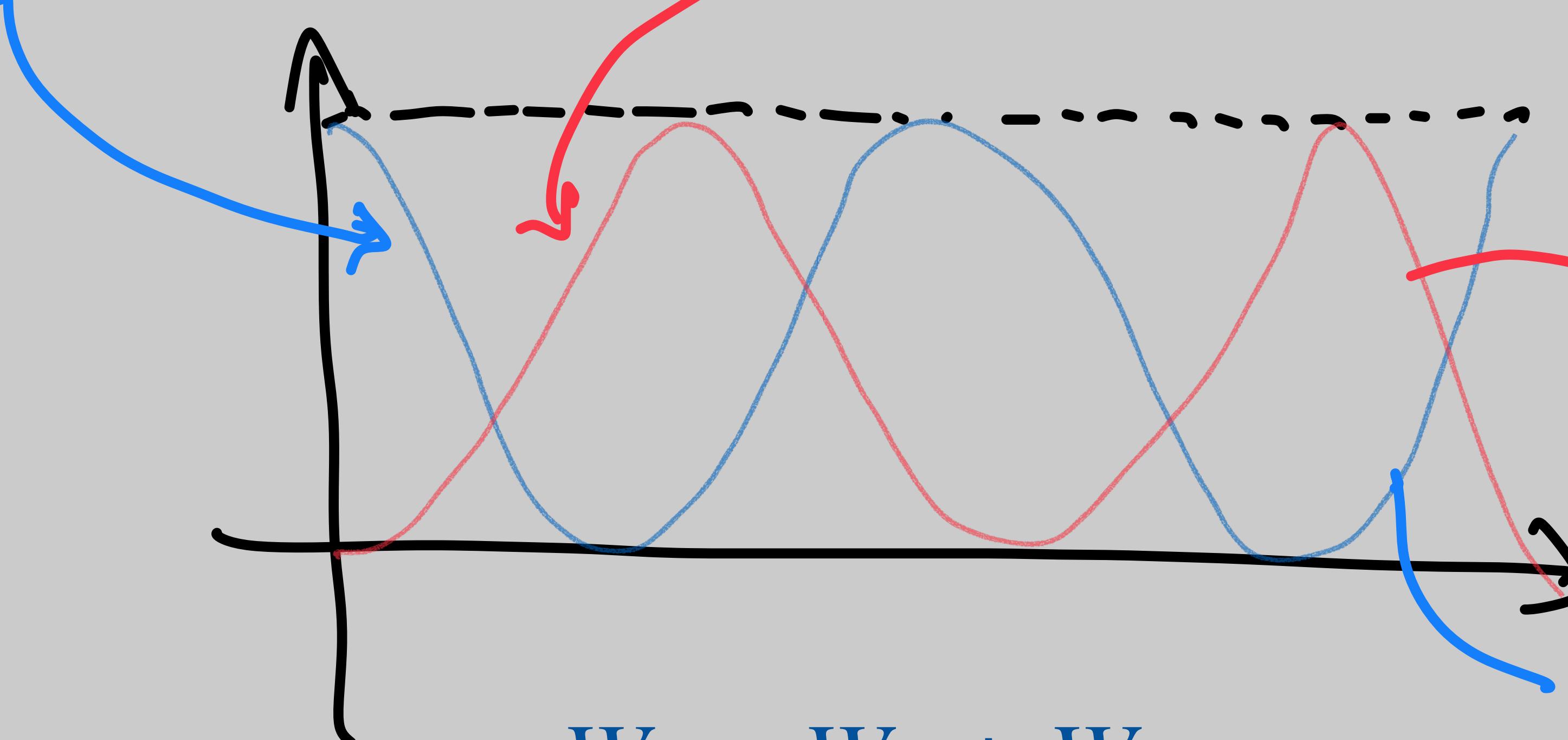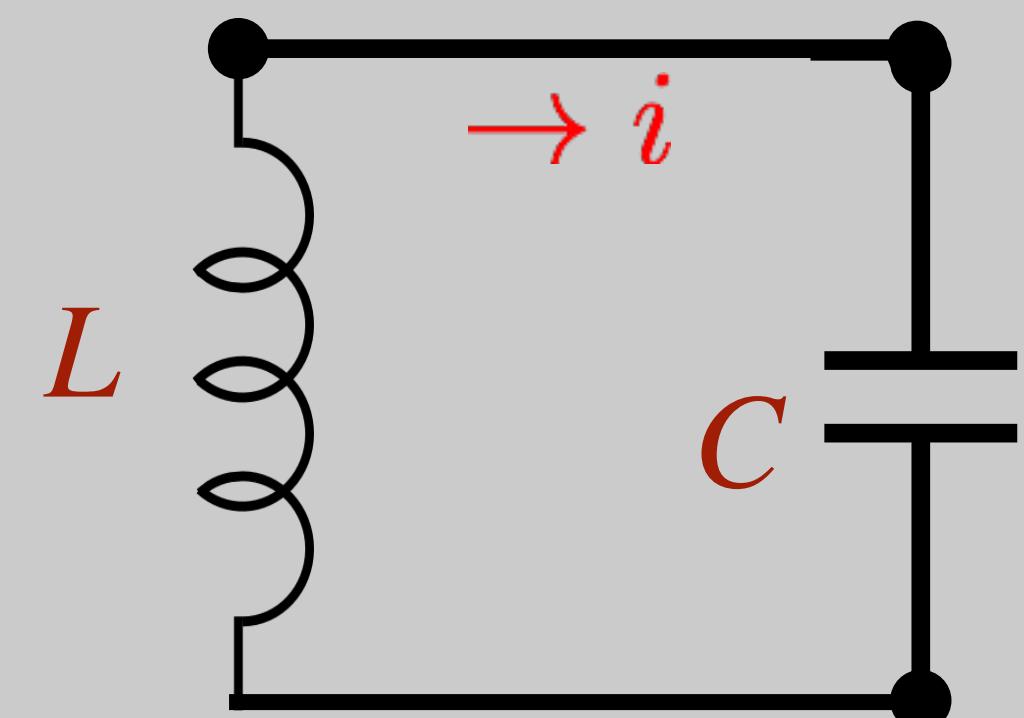
$$W_L = \frac{1}{2} C V_{DD}^2 \sin^2(\omega_0 t)$$




$$W_s = W_L + W_C$$

Magnetic energy
field

Electric energy
field

Pendulum

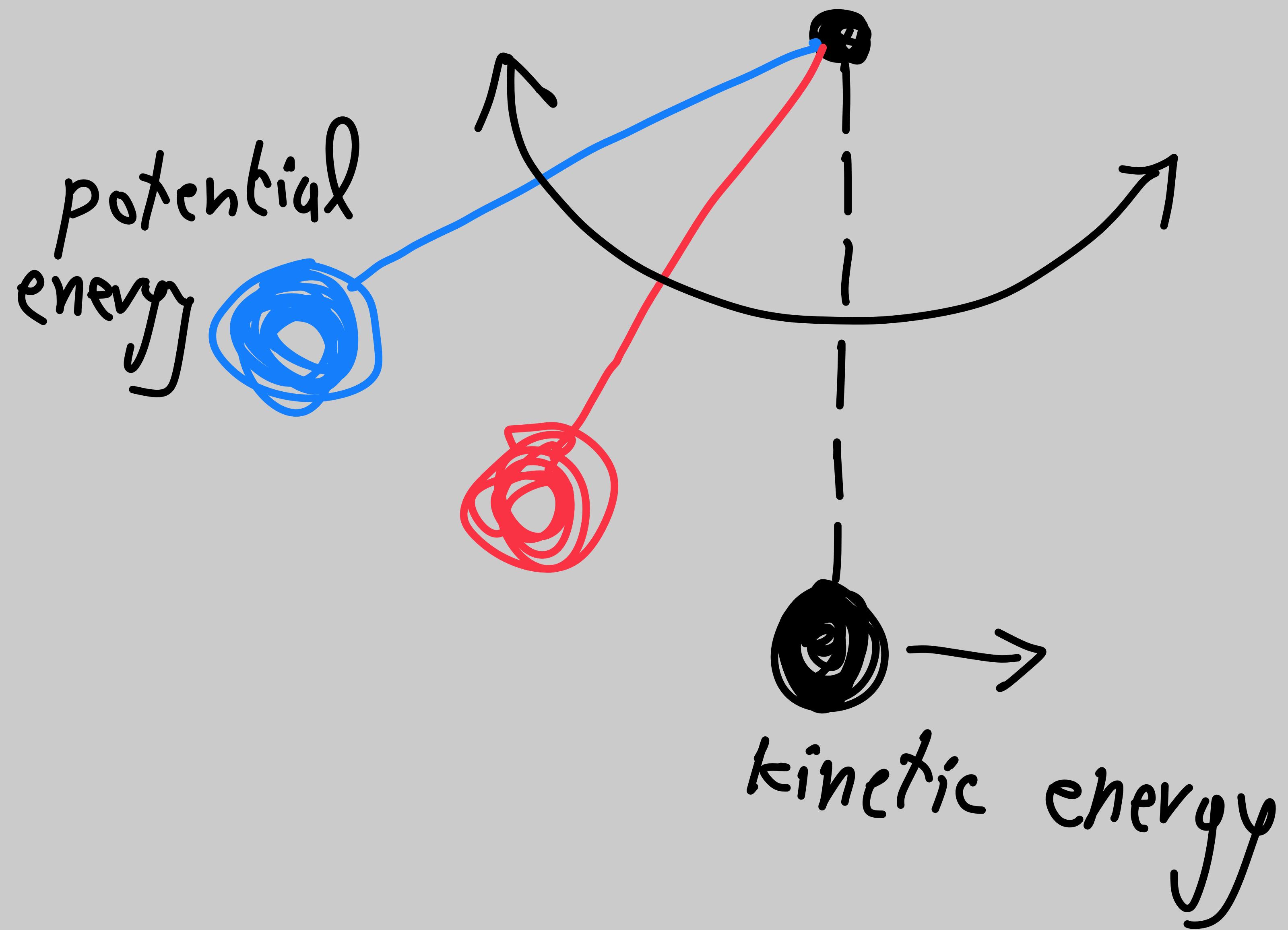


Lossy Tank Circuit

Deal with “small” loss in perturbation

Energy dissipated in resistor per cycle:
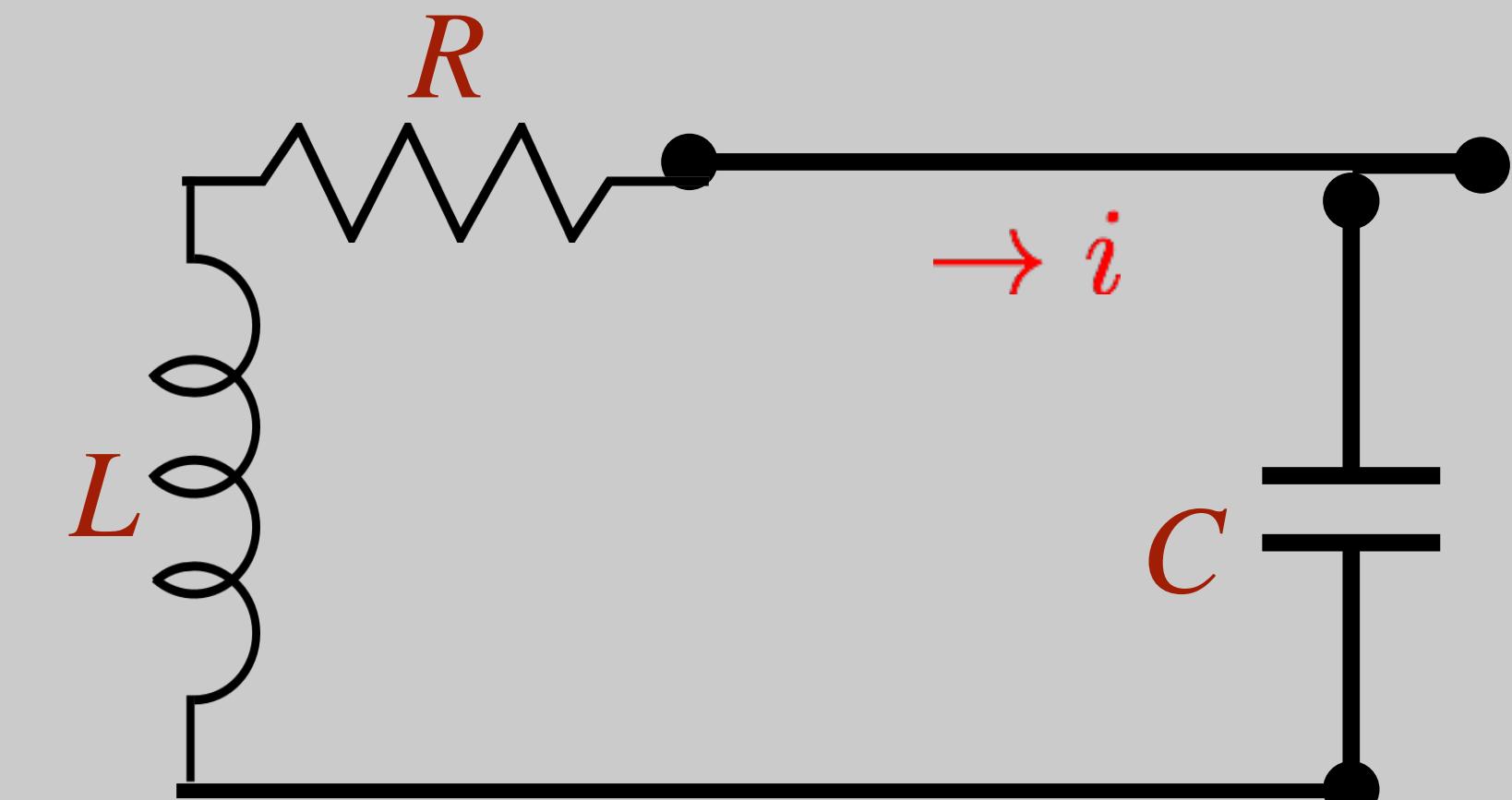
$$W_d = \int_{\text{cycle}} P(t) dt = \int_0^T R i^2(t) dt$$



$$i(t) = I_0 \sin(\omega_0 t)$$

$$= \int_0^T R I_0^2 \sin^2(\omega_0 t) dt = \frac{1}{2} R I_0^2 T = \frac{1}{2} R I_0^2 \frac{2\pi}{\omega_0}$$

$$\frac{W_s}{W_d} = \frac{\frac{1}{2} I_0^2 L}{\frac{1}{2} I_0^2 R \frac{2\pi}{\omega_0}} = \left(\frac{\omega_0 L}{R} \right) \frac{1}{2\pi} \approx \frac{Q}{\mathcal{H}}$$



Non Homogeneous Solution


$$\frac{d^2}{dt^2}V_c(t) + 2\alpha \frac{d}{dt}V_c(t) + \omega_0^2 V_c(t) = u(t)$$

$$V_c(t) = V_h(t) + V_p(t)$$

$$\alpha > \omega_0, \quad \zeta > 1 \Rightarrow V_c(t) = Ae^{s_1 t} + Be^{s_2 t} + V_p(t)$$

$$\alpha = \omega_0, \quad \zeta = 1 \Rightarrow V_c(t) = Ae^{s_1 t} + Bte^{s_1 t} + V_p(t)$$
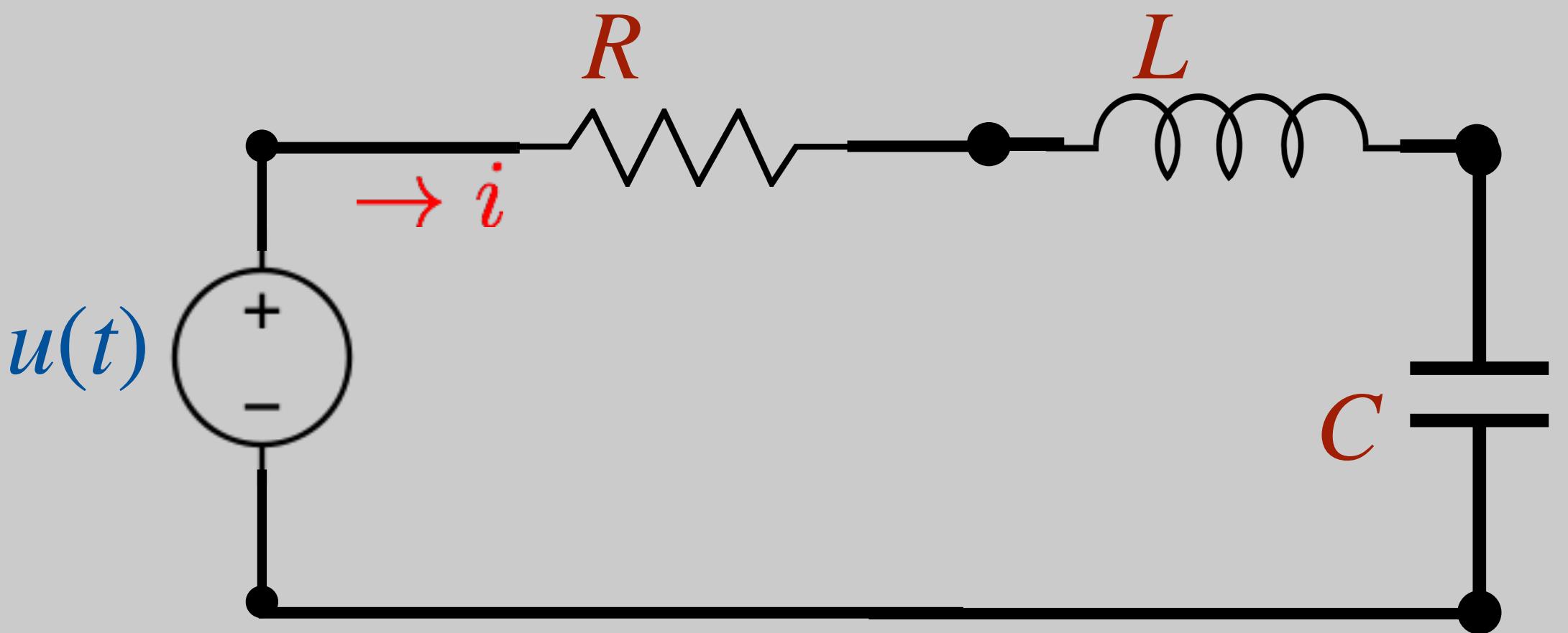
$$\alpha < \omega_0, \quad \zeta < 1 \Rightarrow V_c(t) = e^{s_1 t} (A \cos(\omega_0 t) + B \sin(\omega_0 t)) + V_p(t)$$



Steady-State DC response

$$\frac{d^2}{dt^2}V_c(t) + 2\alpha \frac{d}{dt}V_c(t) + \omega_0^2 V_c(t) = V_{DD}$$

$$V_c(t) = V_h(t) + V_p(t)$$

$$\lim_{t \rightarrow \infty} V_h(t) = 0$$


$$\lim_{t \rightarrow \infty} V_c(t) = V_p(t) = V_{DD}$$

Solve for:


Or $V_c(t) = Ae^{s_1 t} + Be^{s_2 t} + V_{DD}$

Or $V_c(t) = Ae^{s_1 t} + Bte^{s_1 t} + V_{DD}$

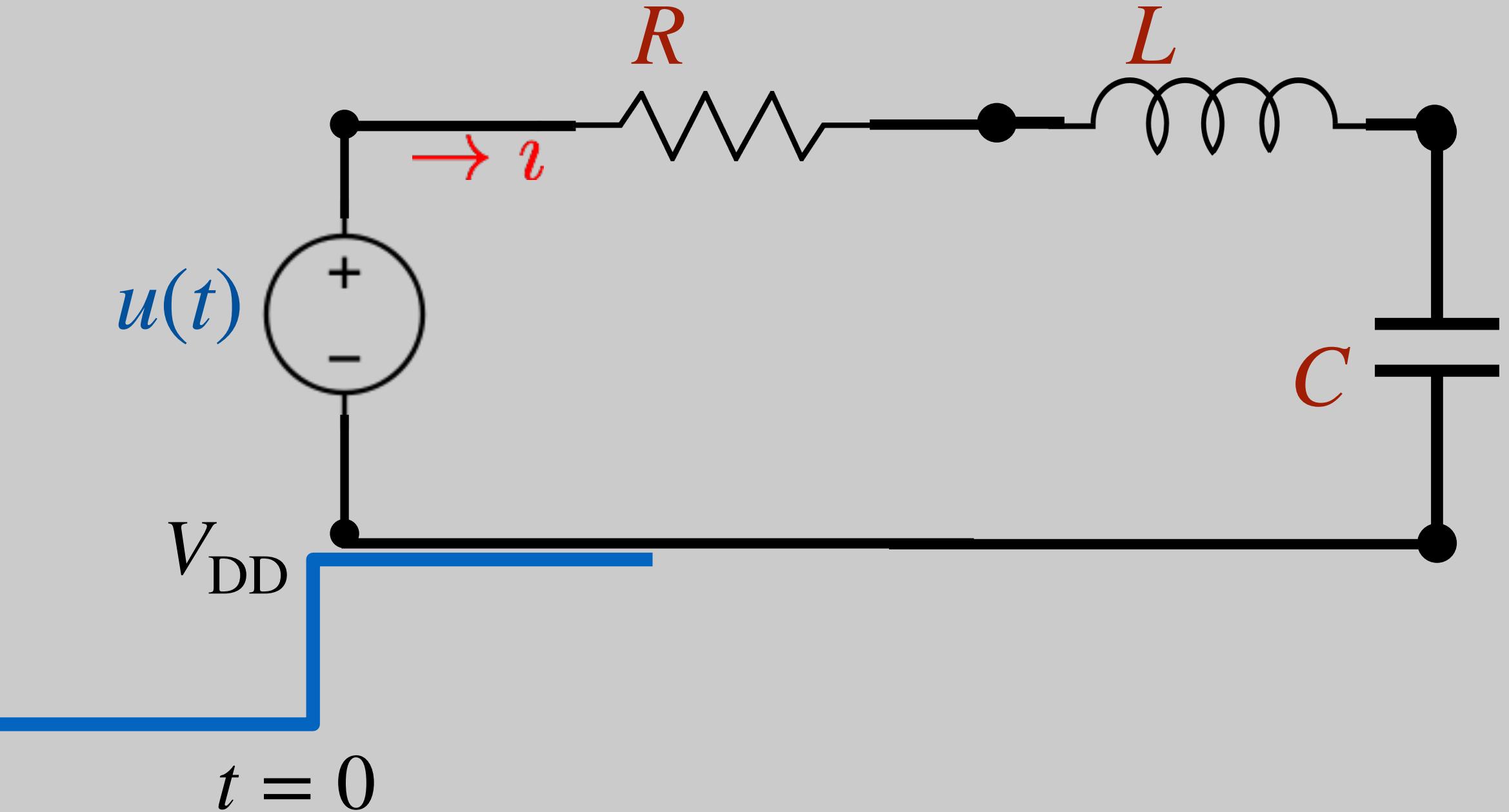
Or $V_c(t) = e^{s_1 t} (A \cos(\omega_0 t) + B \sin(\omega_0 t)) + V_{DD}$



In steady state:

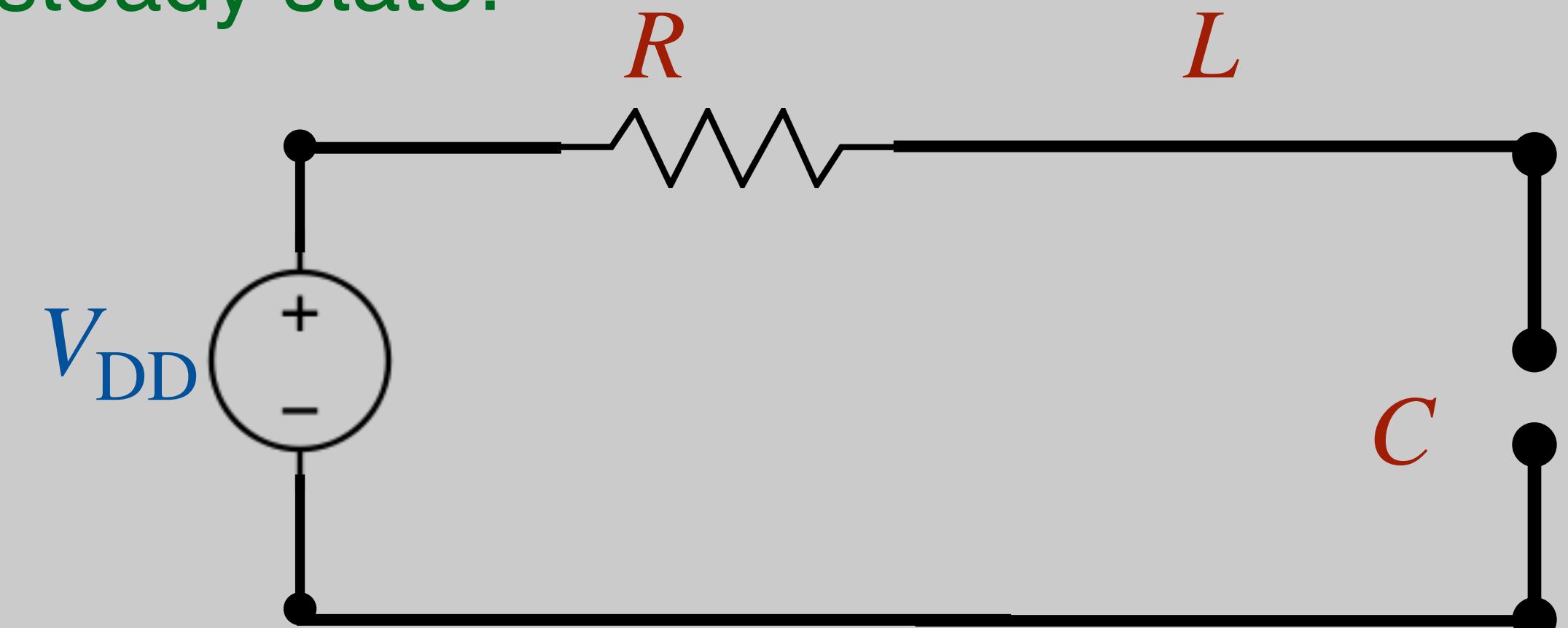


Steady-State DC response

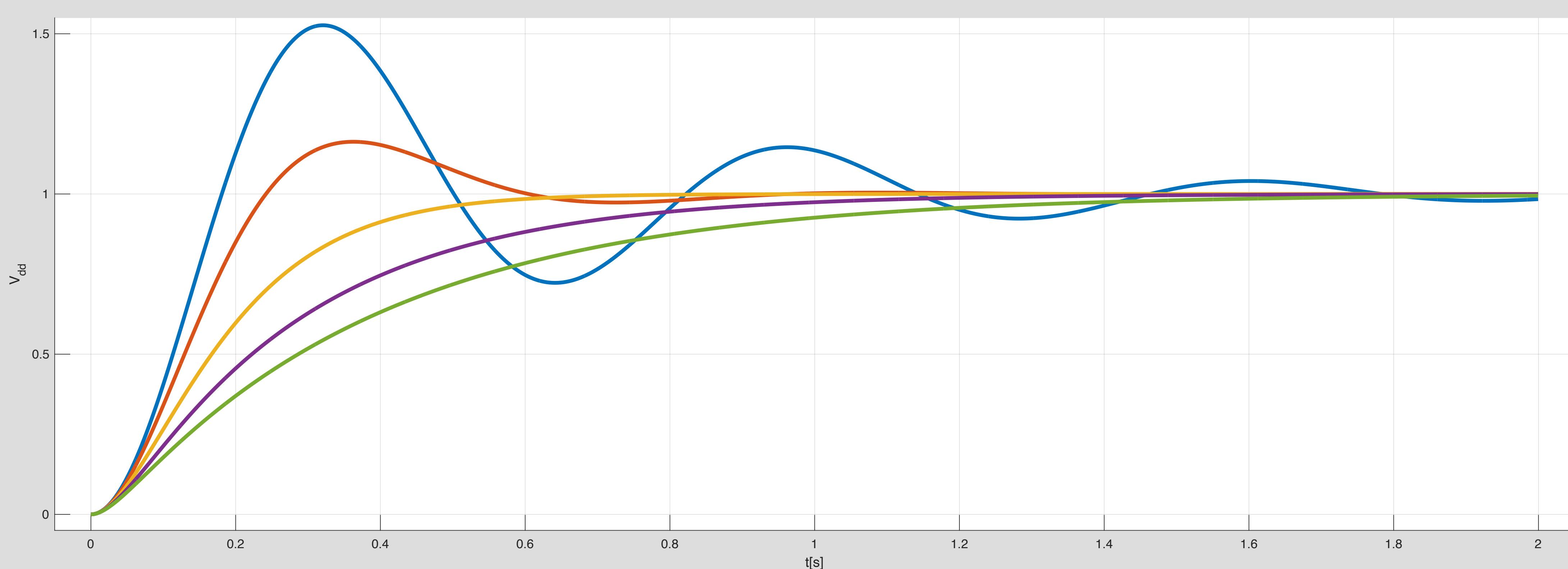

Steady State Sinusoidal Input


Q: What are we going to show?

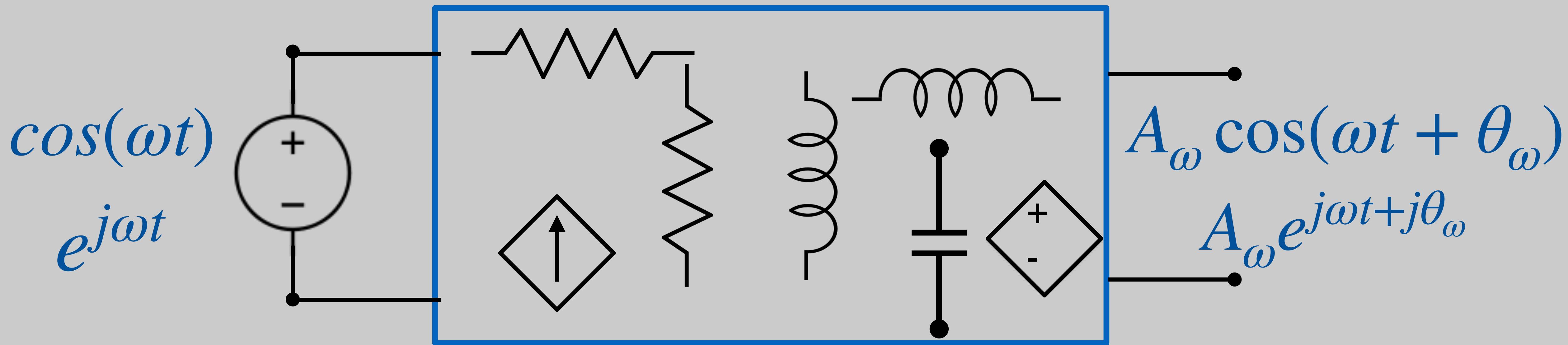


$$H(j\omega) = \frac{A_\omega e^{j\omega t + j\theta_\omega}}{e^{j\omega t}} = A_\omega e^{j\theta_\omega}$$



Back to: VDE / State Space

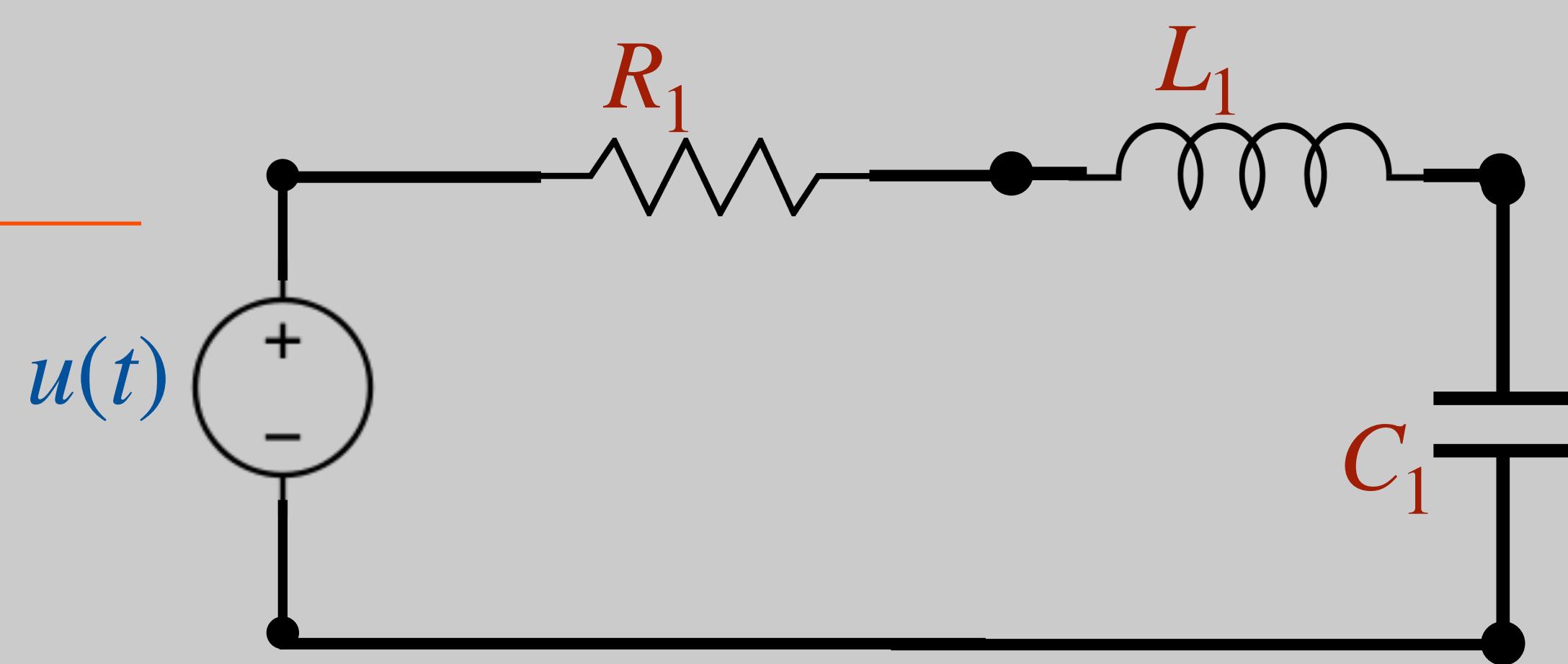

Back to: VDE / State Space

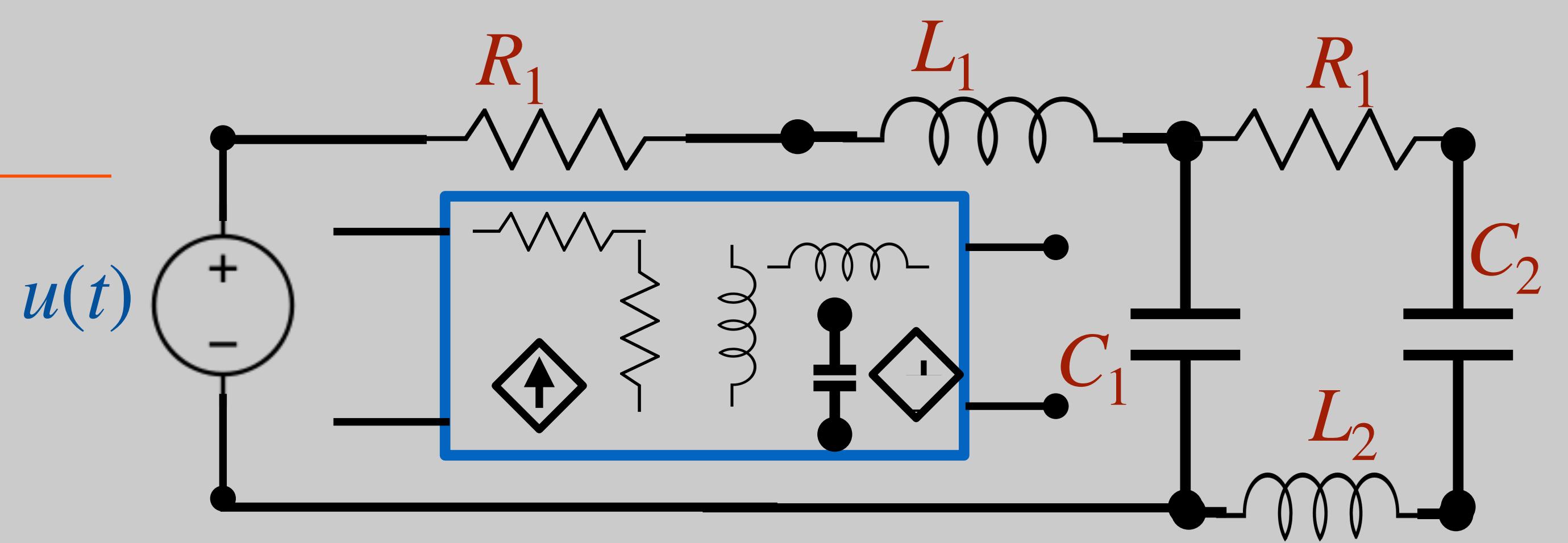

Back to: VDE / State Space

$$\frac{d}{dt} \vec{x}(t) = A\vec{x}(t) + Bu(t)$$


$$\vec{x} = [V_{c_1} \ V_{c_2} \ i_{L_1} \ i_{L_2}]^T$$

$$\vec{z}(t) = T\vec{x}(t)$$

$$\frac{d}{dt} \vec{z}(t) = \begin{bmatrix} \lambda_1 & 0 & \cdots & 0 \\ 0 & \lambda_2 & \cdots & 0 \\ & & \ddots & \\ 0 & 0 & \cdots & \lambda_n \end{bmatrix} \vec{z}(t) + B_{\text{new}} u(t)$$


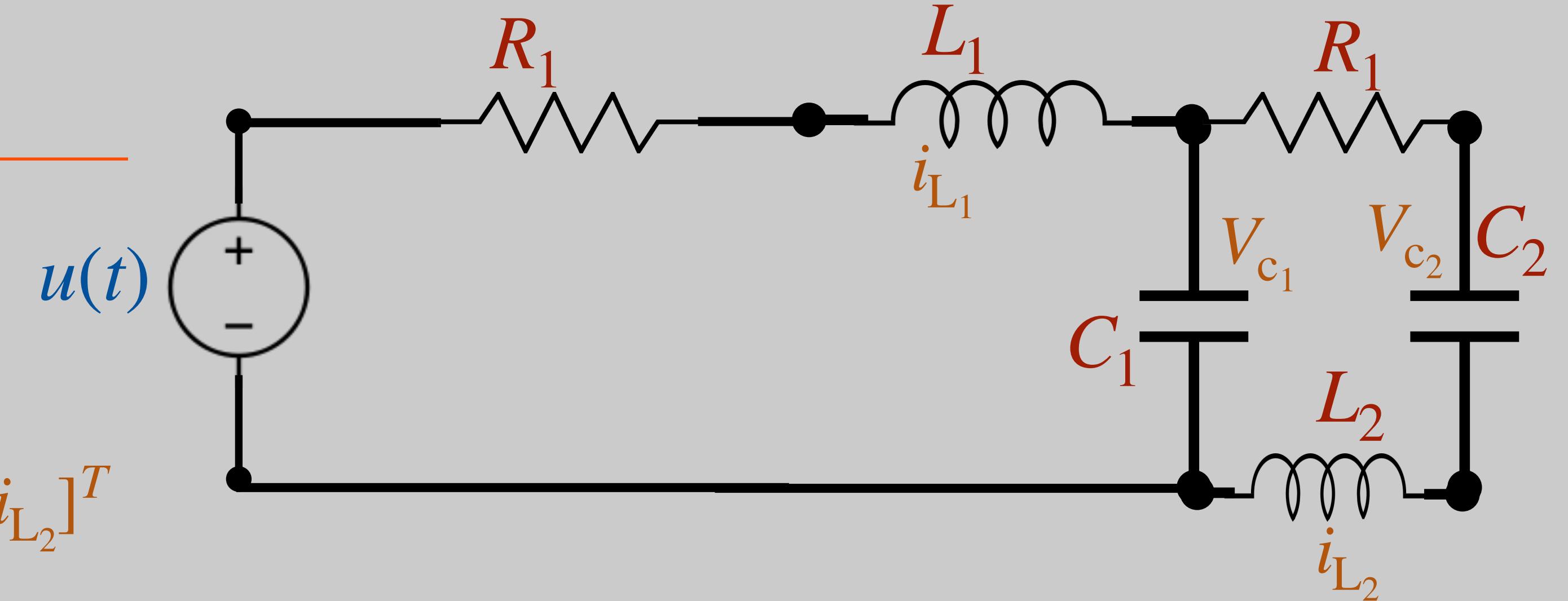
$$\frac{d}{dt} z_1(t) = \lambda_1 z_1(t) + \tilde{b}_1 u(t) \quad \Rightarrow z_1(t) = K e^{\lambda_1 t} + \tilde{b}_1 e^{\lambda_1 t} \int_{-\infty}^t u(\tau) e^{-\lambda_1 \tau} d\tau$$



Back to: VDE / State Space

$$z_1(t) = K e^{\lambda_1 t} + \tilde{b}_1 e^{\lambda_1 t} \int_{-\infty}^t u(\tau) e^{-\lambda_1 \tau} d\tau$$


⋮

$$z_N(t) = K e^{\lambda_N t} + \tilde{b}_N e^{\lambda_N t} \int_{-\infty}^t u(\tau) e^{-\lambda_N \tau} d\tau$$

Go back to original variable by: $\vec{x}(t) = T^{-1} \vec{z}(t)$

So, solution for $x_n(t) = \sum_{k=1}^N T_{nk}^{-1} z_k(t)$ is a linear combination of the “Eigen” responses

nth row elements of T^{-1}

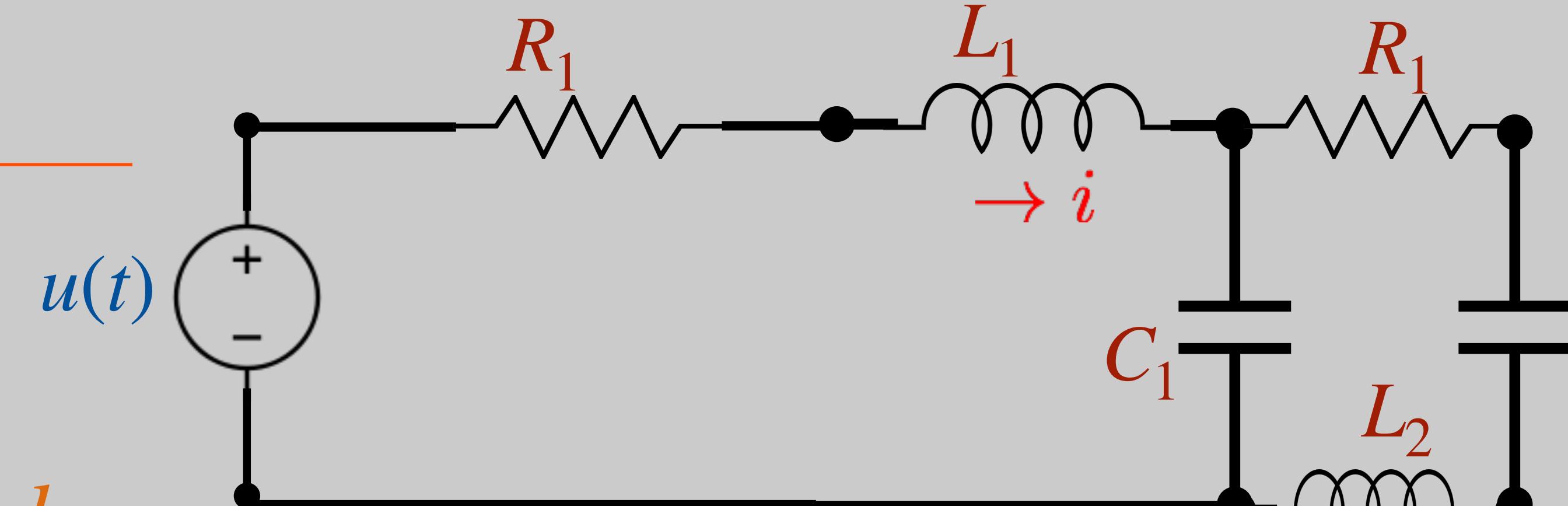


If there is a complex λ , there's also λ^* !

Q: Why? A: Keep it real!


Sinusoidal input

$$z(t) = K e^{\lambda t} + \tilde{b} e^{\lambda t} \int_{-\infty}^t u(\tau) e^{-\lambda \tau} d\tau$$

$$\lambda = -\alpha + j\omega_0$$

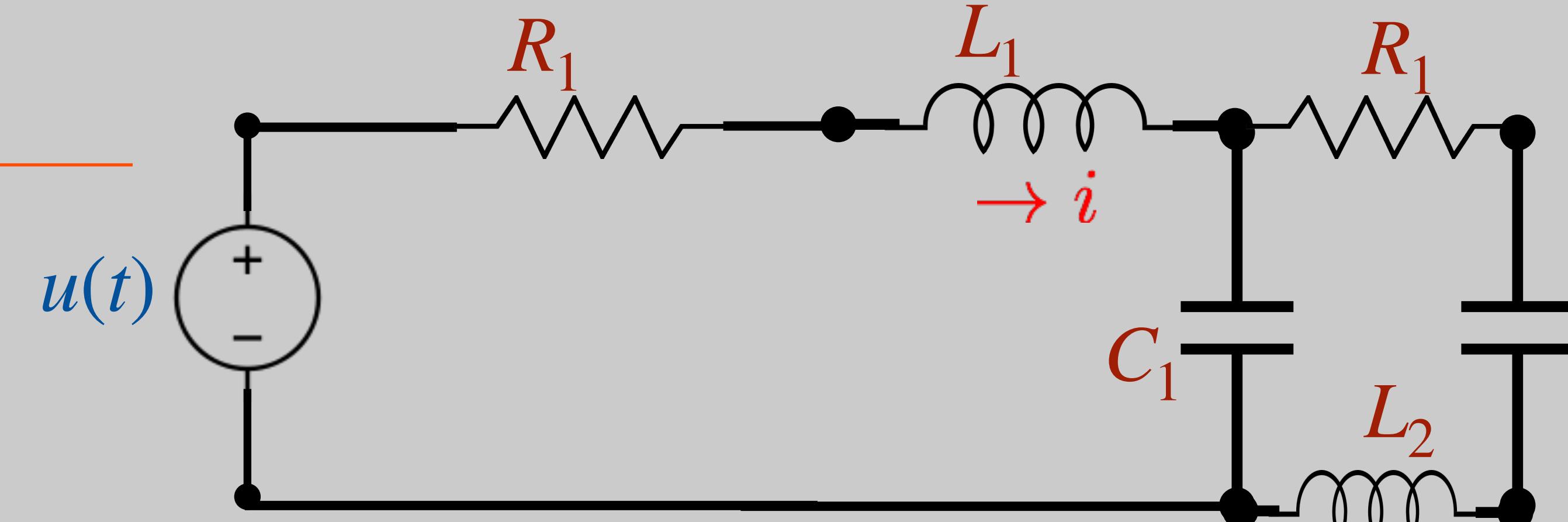
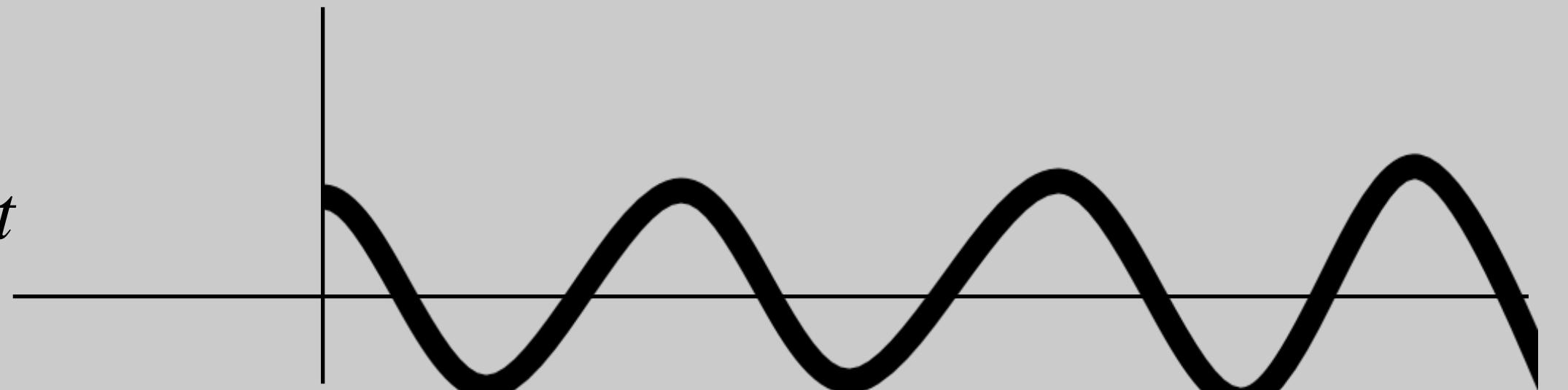
$$u(t > 0) = 2 \cos(\omega t) \Rightarrow u(t) = e^{j\omega t} + e^{-j\omega t}$$



$$z(t) = K \cdot e^{\lambda t} + \tilde{b} e^{\lambda t} \int_0^t e^{(j\omega - \lambda)\tau} d\tau$$

Transient if $\text{real}(\lambda) < 0$

$$= \frac{\tilde{b} e^{\lambda t}}{j\omega - \lambda} [e^{(j\omega - \lambda)t} - 1] = \frac{\tilde{b} e^{j\omega t}}{j\omega - \lambda} - \frac{\tilde{b} e^{\lambda t}}{j\omega - \lambda} \underset{t \rightarrow \infty}{=} \frac{\tilde{b} e^{j\omega t}}{j\omega - \lambda}$$

Transient if $\text{real}(\lambda) < 0$



Sinusoidal input in steady state

$$u(t) = e^{j\omega t}$$

$$z_k(t) = \frac{\tilde{b}_k}{j\omega - \lambda_k} e^{j\omega t}$$


$$x_n(t) = \sum_k \frac{T_{nk}^{-1} \tilde{b}_k}{j\omega - \lambda_k} e^{j\omega t} \Rightarrow x_n(t) = H(j\omega) e^{j\omega t}$$

$$H(j\omega)$$

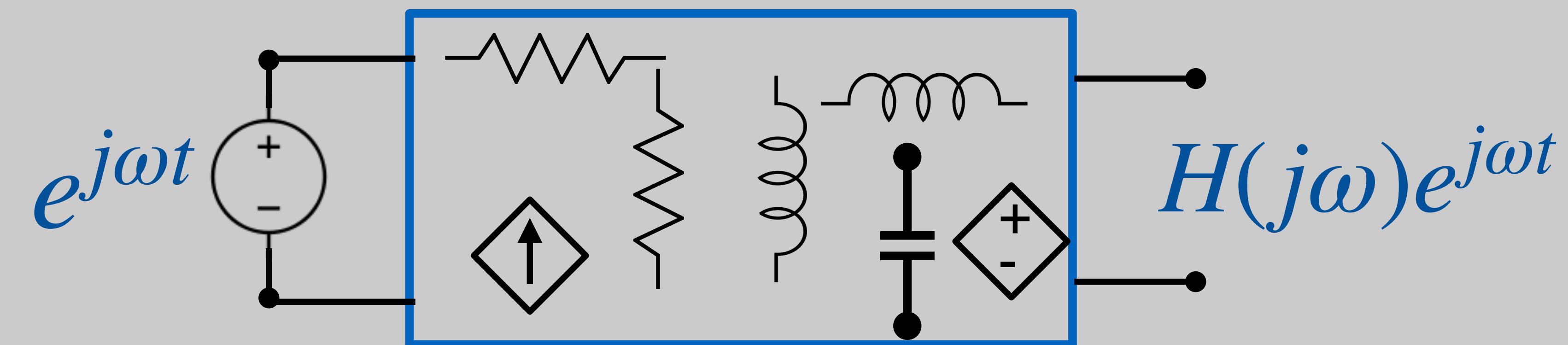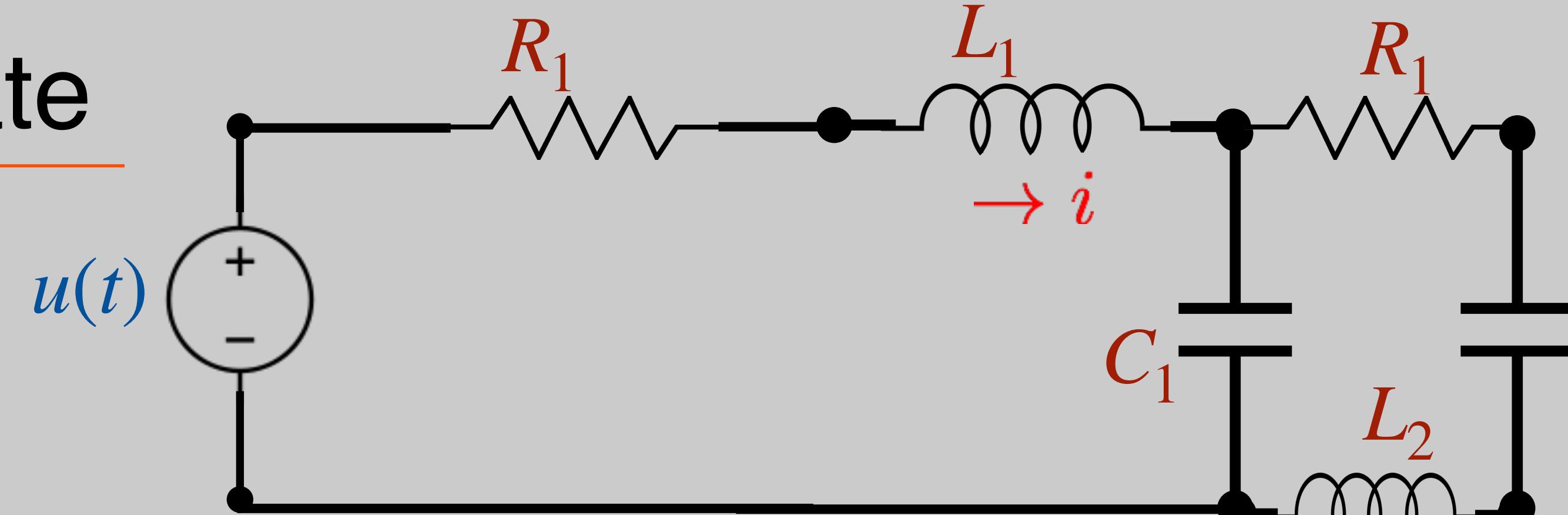


Frequency Response/ Transfer function

Frequency response:

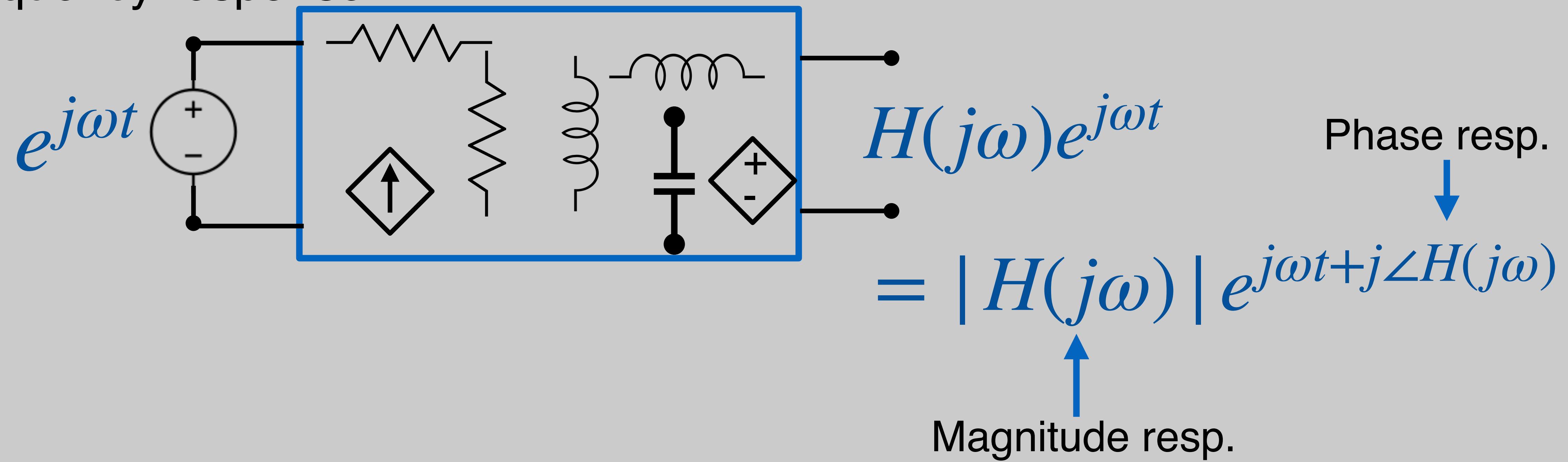


Transfer function:

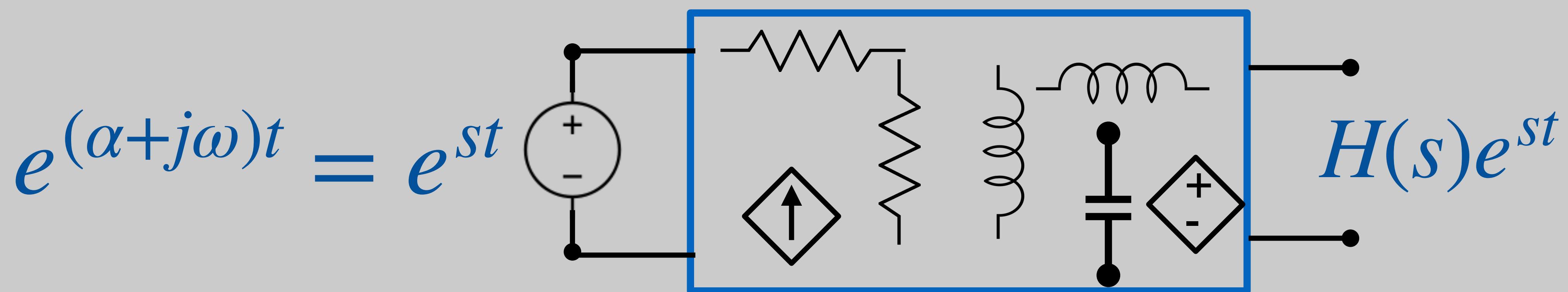

AC Analysis in steady state

Want to avoid solving VDE
every time!

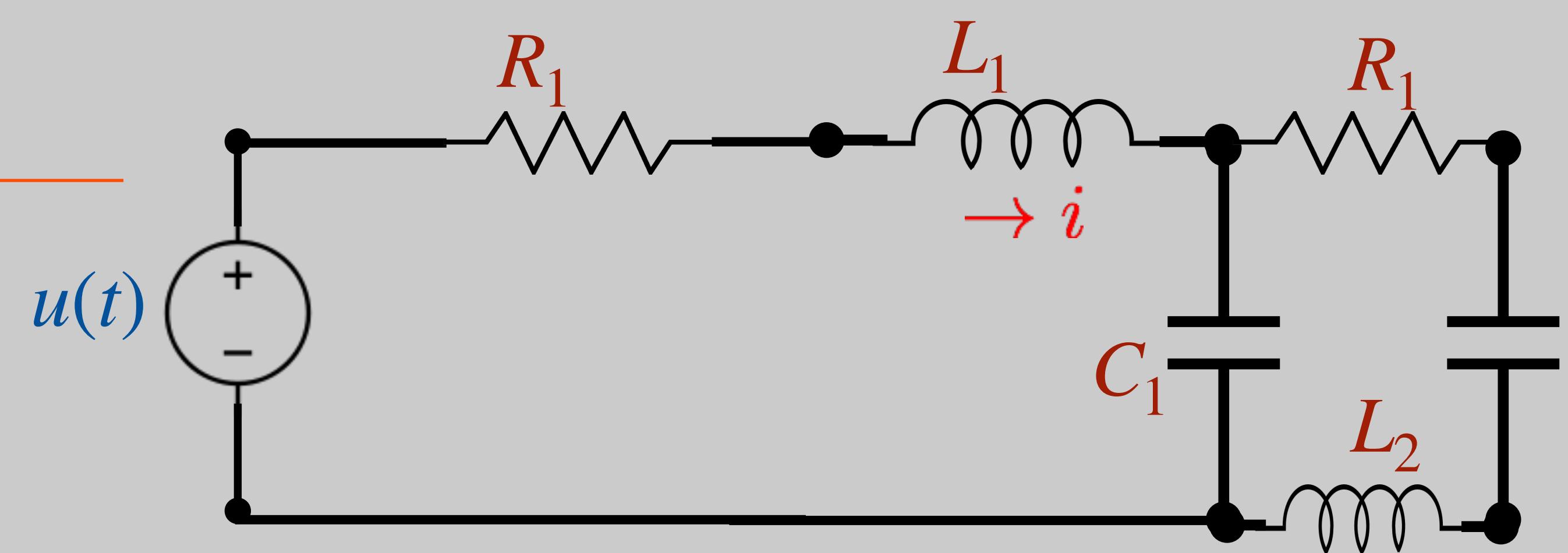

But, we know for sinusoidal input,
we get a sinusoidal output (in steady state)

So, simplify analysis by looking at individual components

Capacitors in AC circuits


$$V_c(t) = V_0 \cos(\omega t + \theta) \quad \text{Use, complex exponentials instead!}$$

$$V_c(t) = V_0 e^{j\omega t + \theta} = V_0 e^{j\theta} e^{j\omega t} = \tilde{V}_c e^{j\omega t}$$

$$i_c(t) = C \frac{d}{dt} V_c(t) = j\omega C \tilde{V}_c e^{j\omega t} = \tilde{I}_c e^{j\omega t}$$
$$\Rightarrow i_c(t) = \omega C V_0 \cos(\omega t + \theta + \pi/2)$$

$$\tilde{I}_c = j\omega C \tilde{V}_c$$
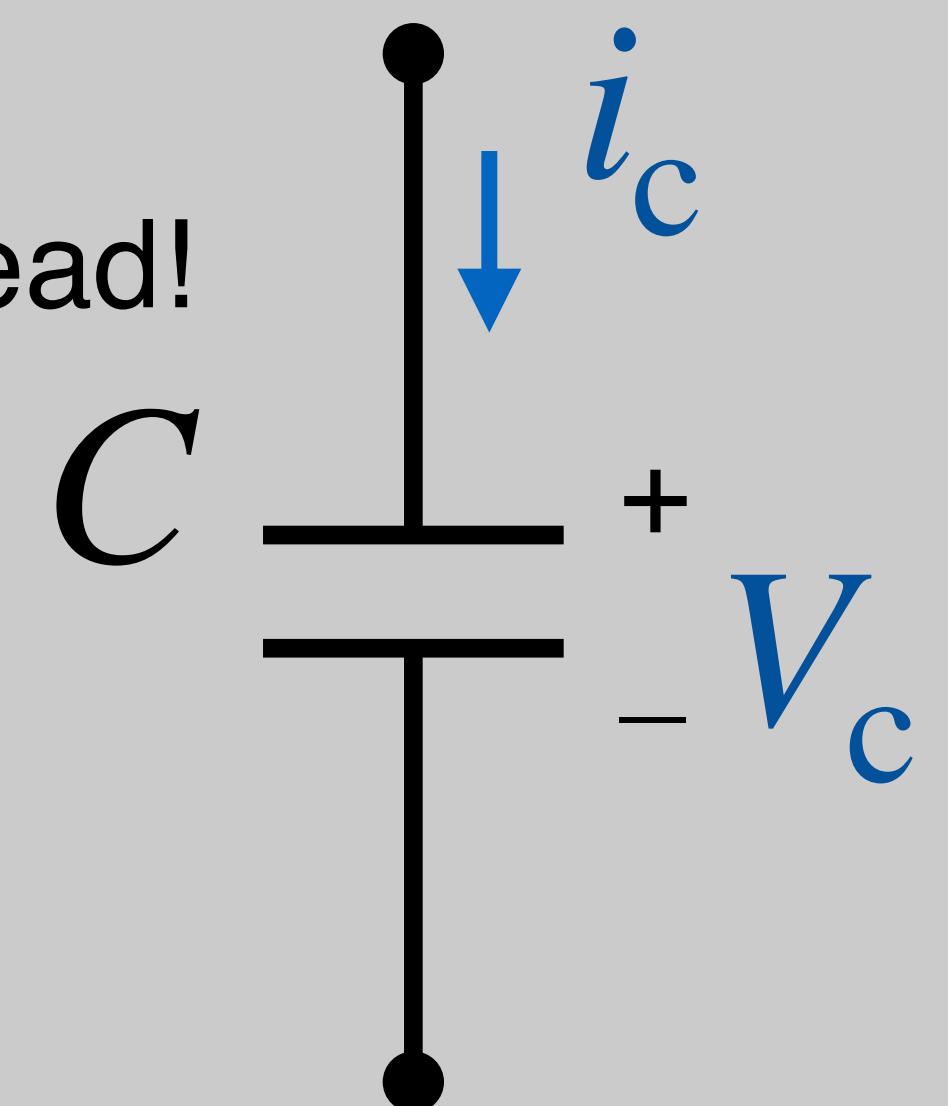
$$\frac{V_c(t)}{i_c(t)} = \frac{\tilde{V}_c}{\tilde{I}_c} = \frac{1}{j\omega C}$$



In steady state, a capacitor IV relationship looks like a “imaginary valued” resistor!


Inductors in AC circuits

$$i_L(t) = I_0 e^{j\omega t + \theta} = \tilde{I}_L e^{j\omega t}$$

$$V_L(t) = L \frac{d}{dt} i_L(t) = j\omega L \tilde{I}_L e^{j\omega t}$$

$$\tilde{V}_L = j\omega L \tilde{I}_L$$
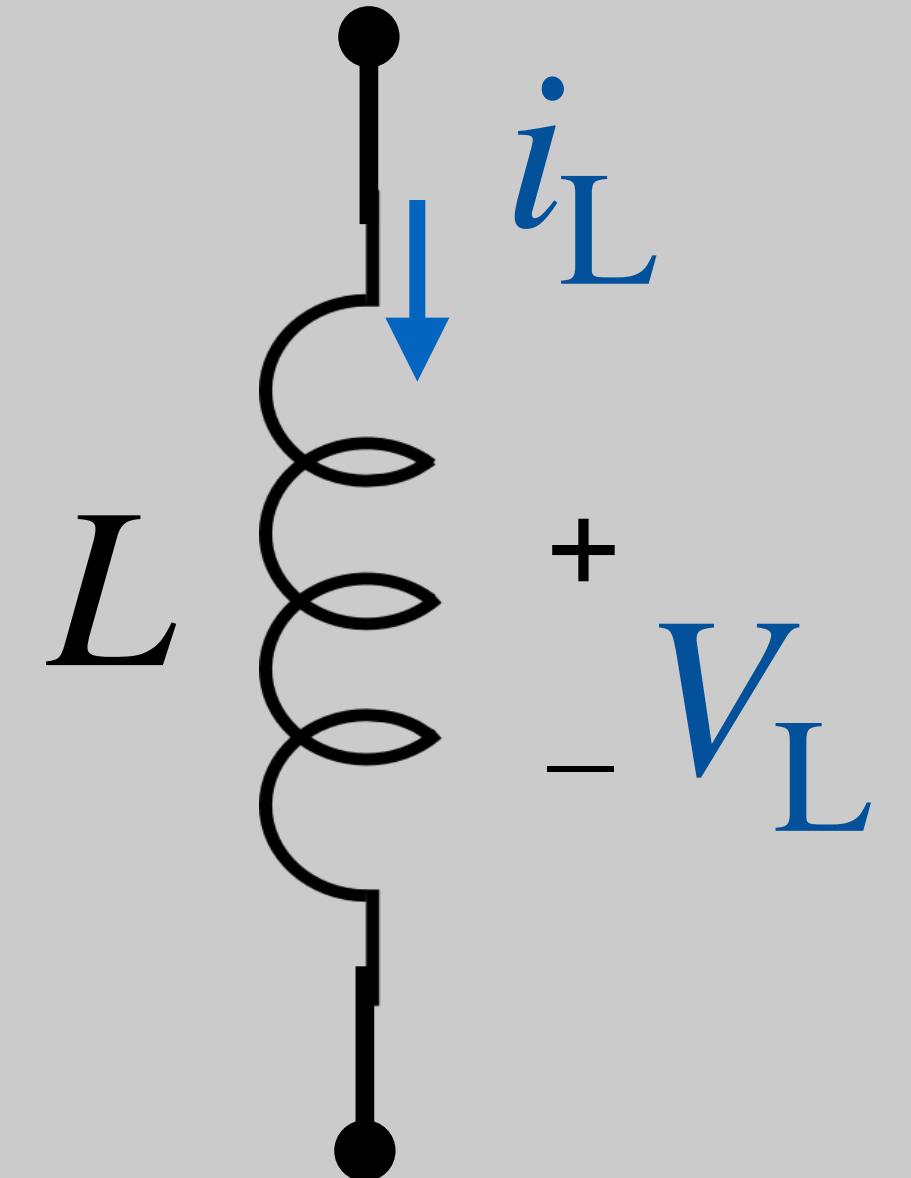
$$\frac{V_L(t)}{i_L(t)} = \frac{\tilde{V}_L}{\tilde{I}_L} = j\omega L$$



In steady state, a Inductor IV relationship looks like a “imaginary valued” resistor!

Phasors



$$i_L(t) = I_0 e^{j\omega t + j\theta} = \tilde{I}_L e^{j\omega t}$$

$$V_c(t) = V_0 e^{j\omega t + j\theta} = \tilde{V}_c e^{j\omega t}$$

\tilde{I}_L and \tilde{V}_c are called “phasors”, complex numbers

representing amplitude and phase of a sinusoidal time signal


In real time domain, $V_c(t) = |\tilde{V}_c| \cos(\omega t + \angle \tilde{V}_c) = V_0 \cos(\omega t + \theta)$

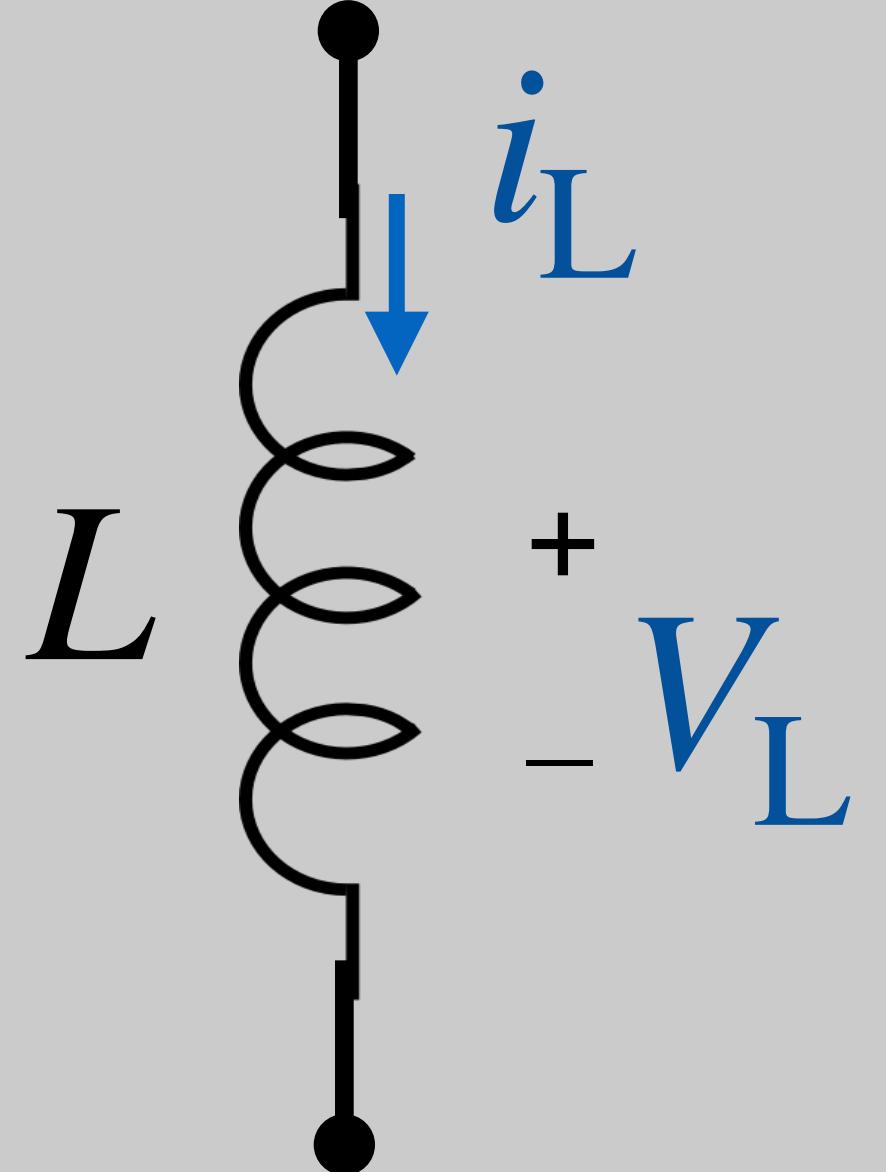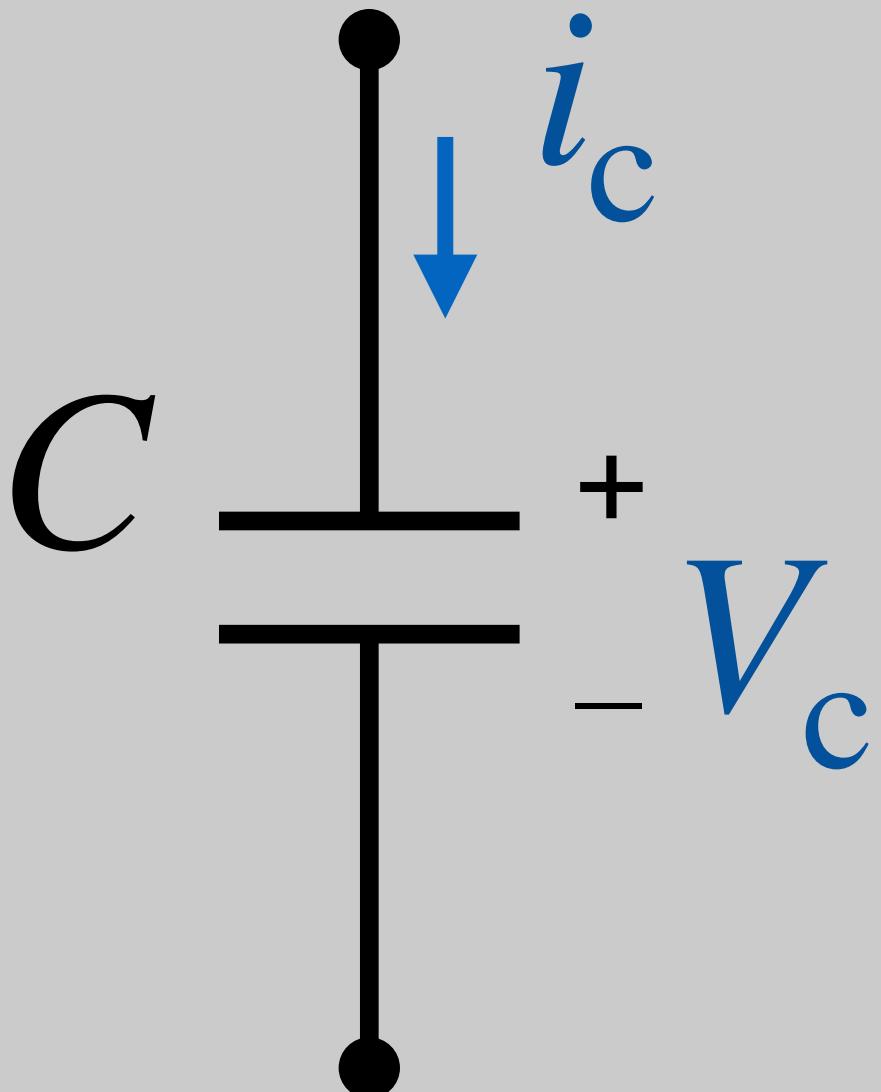

Phasor Arithmetic

$$\tilde{V} = |V| e^{j\theta}$$
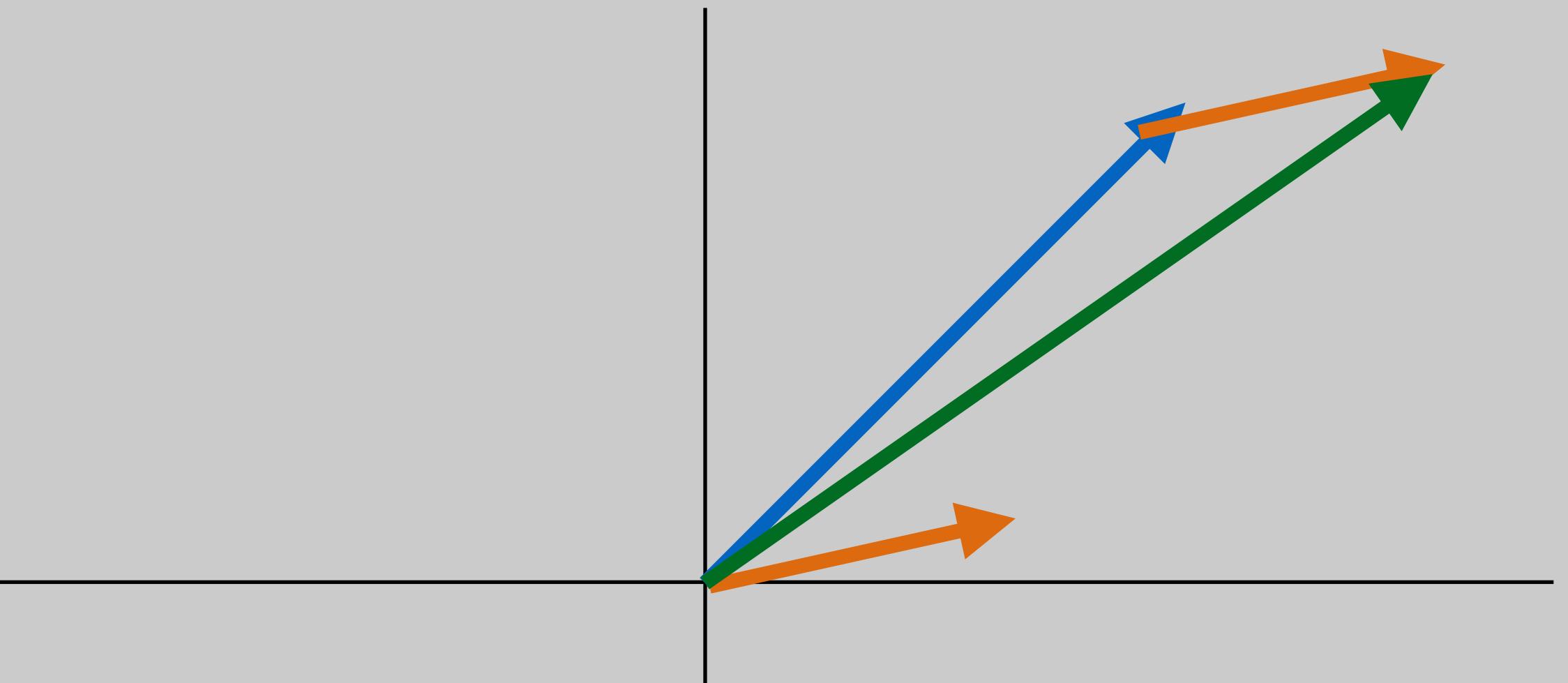
$$\tilde{V}_1 + \tilde{V}_2 = \tilde{V}_1 + \tilde{V}_2 =$$



Phasor Arithmetic

$$\tilde{V} = |V| e^{j\theta}$$

$$\tilde{V}_1 + \tilde{V}_2 = \tilde{V}_1 + \tilde{V}_2 =$$


$$|V_1|\cos(\theta_1) + |V_2|\cos(\theta_2) + j(|V_1|\sin(\theta_1) + |V_2|\sin(\theta_2))$$

$$\tilde{V}_1 \tilde{V}_2 = |V_1| |V_2| e^{j(\theta_1 + \theta_2)}$$

$$j\tilde{V} = \tilde{V} e^{j\frac{\pi}{2}}$$

$$\frac{\tilde{V}_1}{\tilde{V}_2} = \frac{|V_1|}{|V_2|} e^{j(\theta_1 - \theta_2)}$$
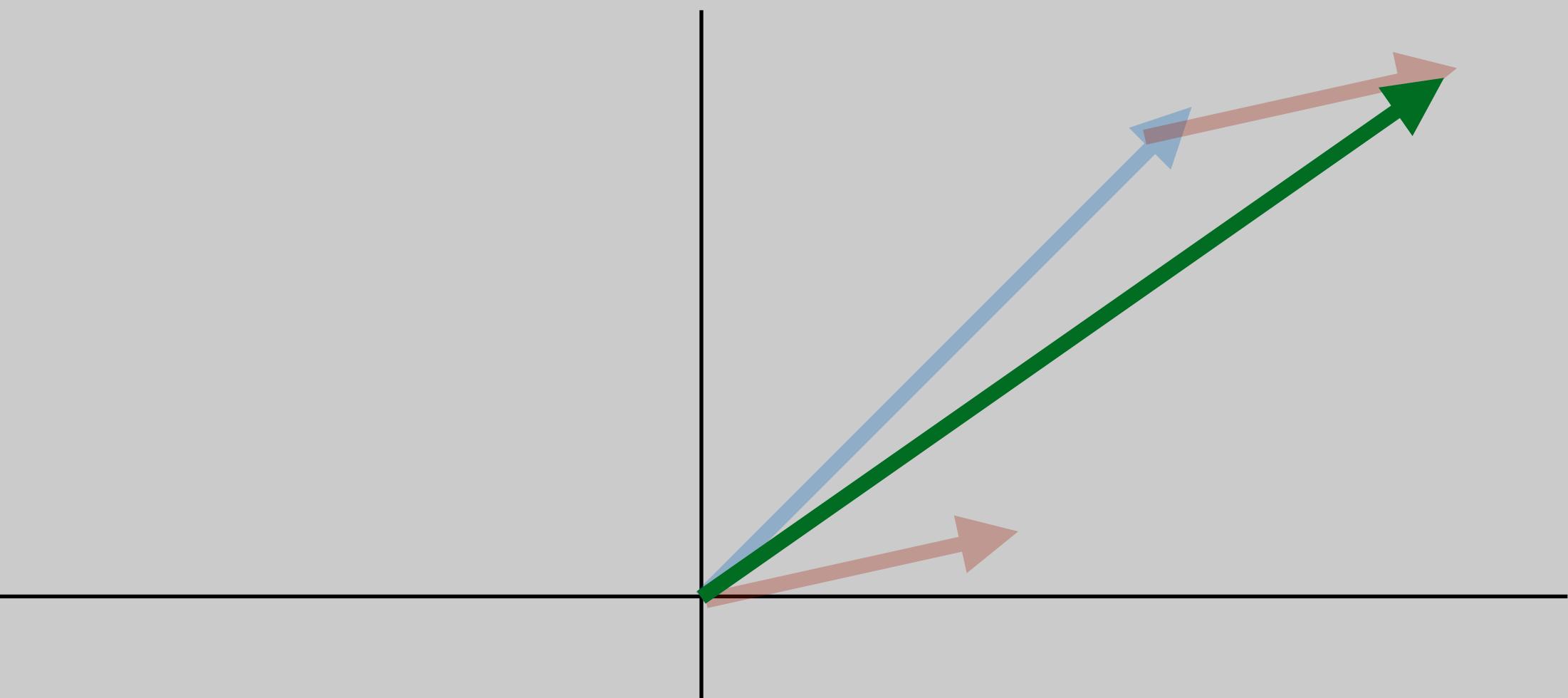
$$\frac{\tilde{V}}{j} = \tilde{V} e^{-j\frac{\pi}{2}}$$



Impedance in AC circuits

Complex valued “resistance”



$$Z = R + jX$$

Impedance Resistance Reactance

$$Z^{-1} = Y = G + jB$$


Conductance Susceptance

New Ohm's law: $\tilde{V} = \tilde{I}Z$

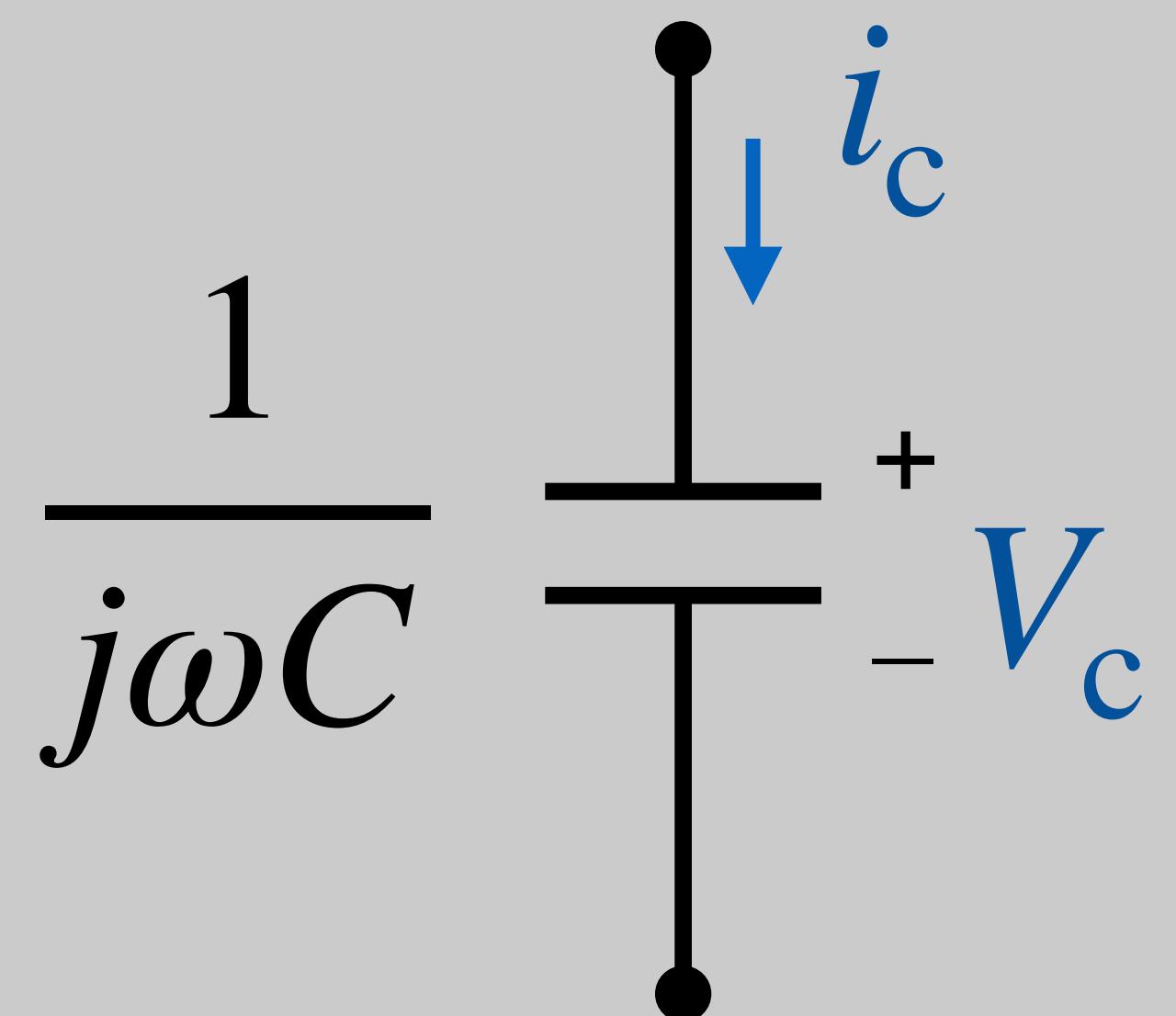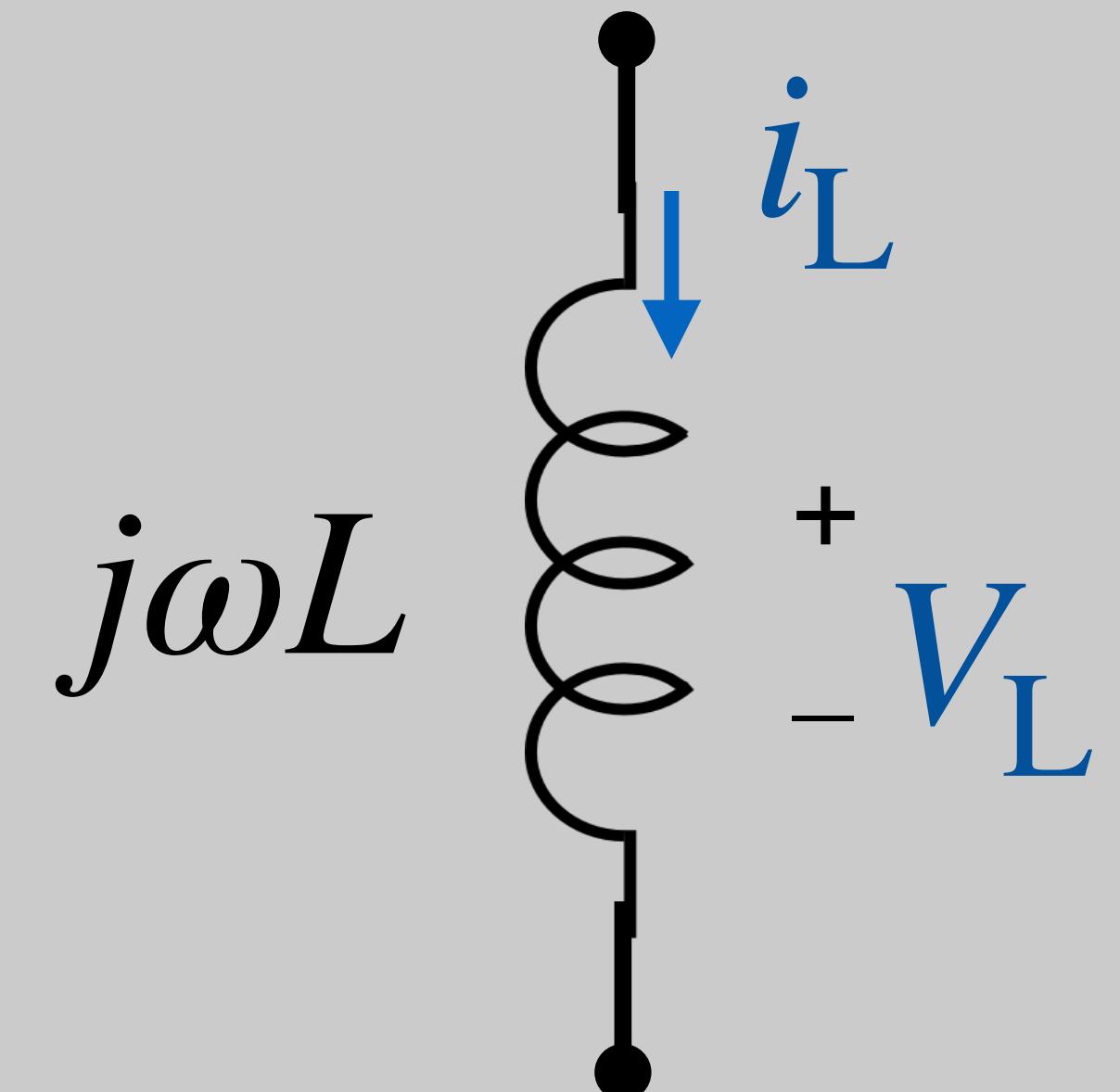

Example 1: AC Response of an RC



$$V_s(t) = V_{DD} \cos(\omega t)$$

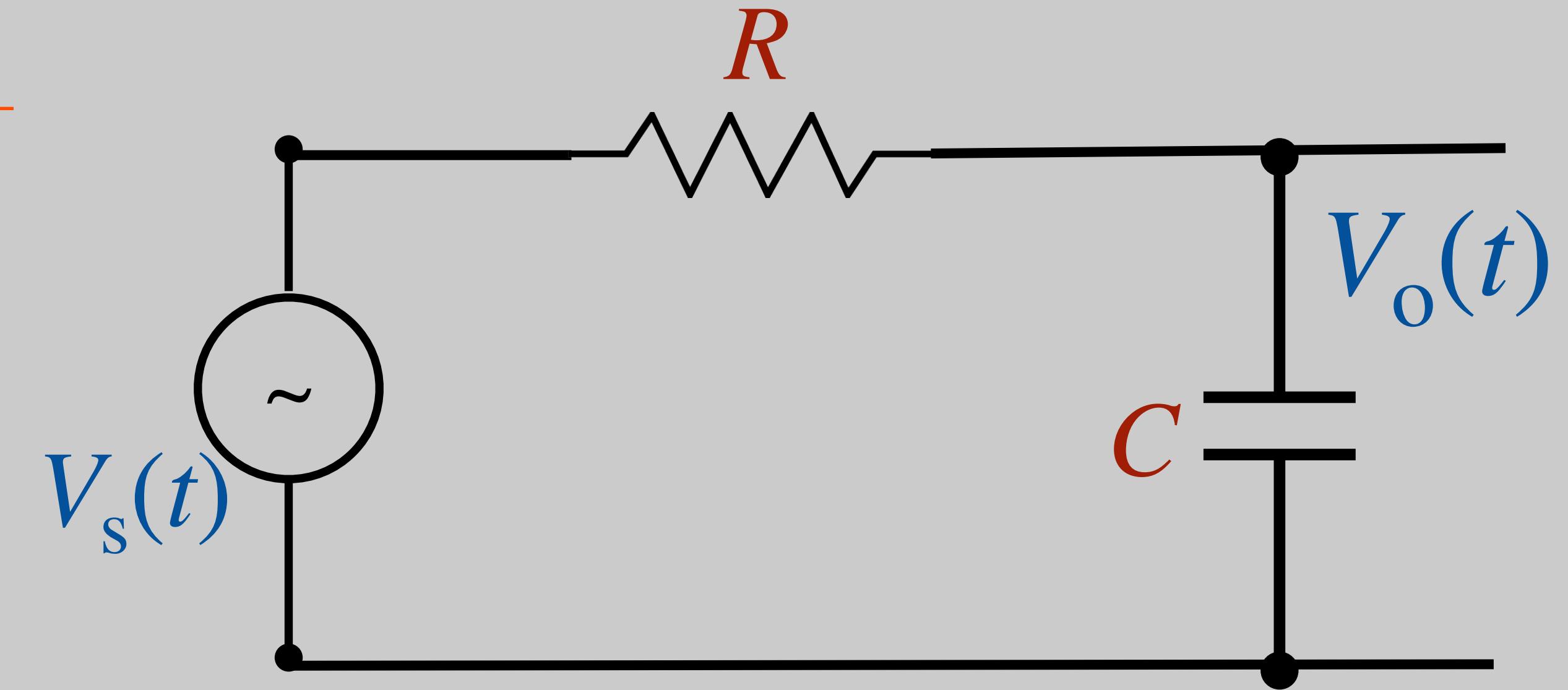

Example 1: AC Response of an RC

$$V_s(t) = V_{DD} \cos(\omega t)$$

AC responses using phasors:

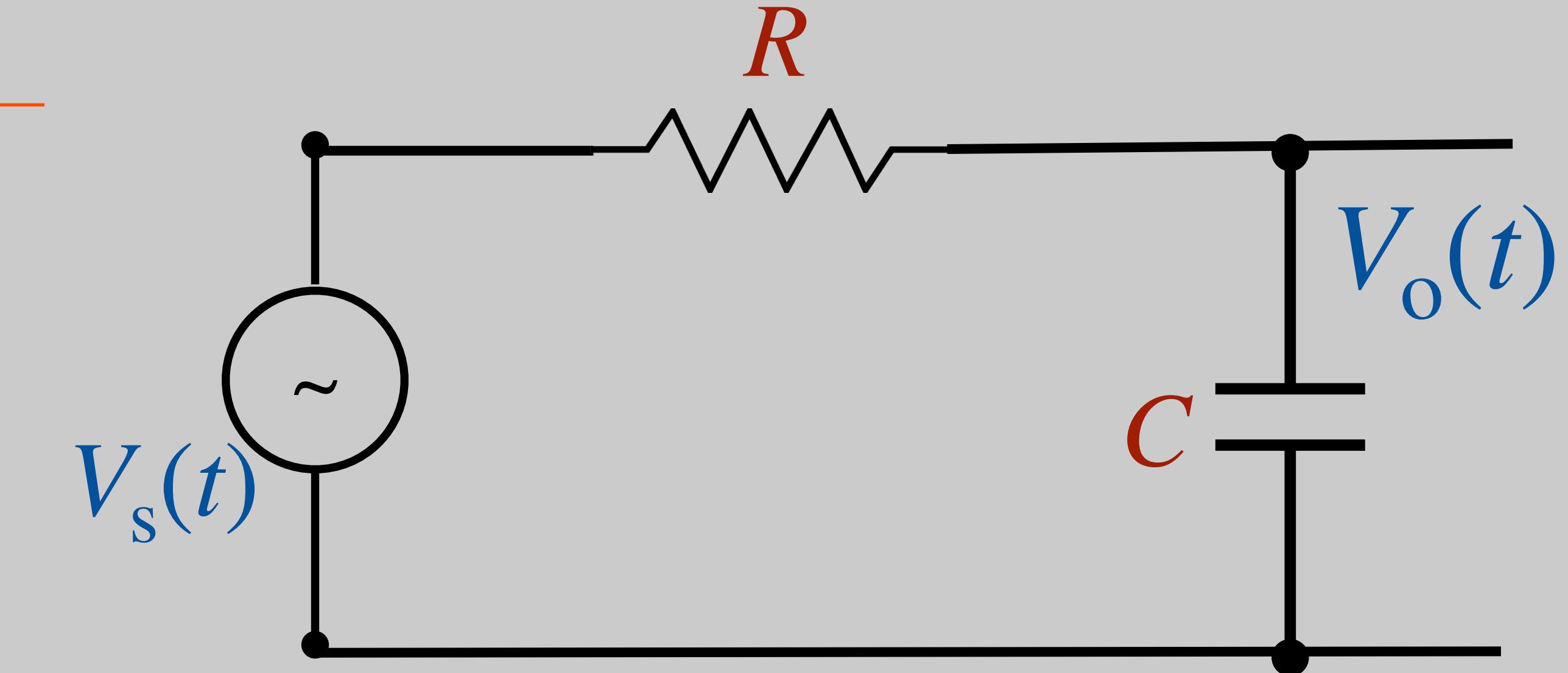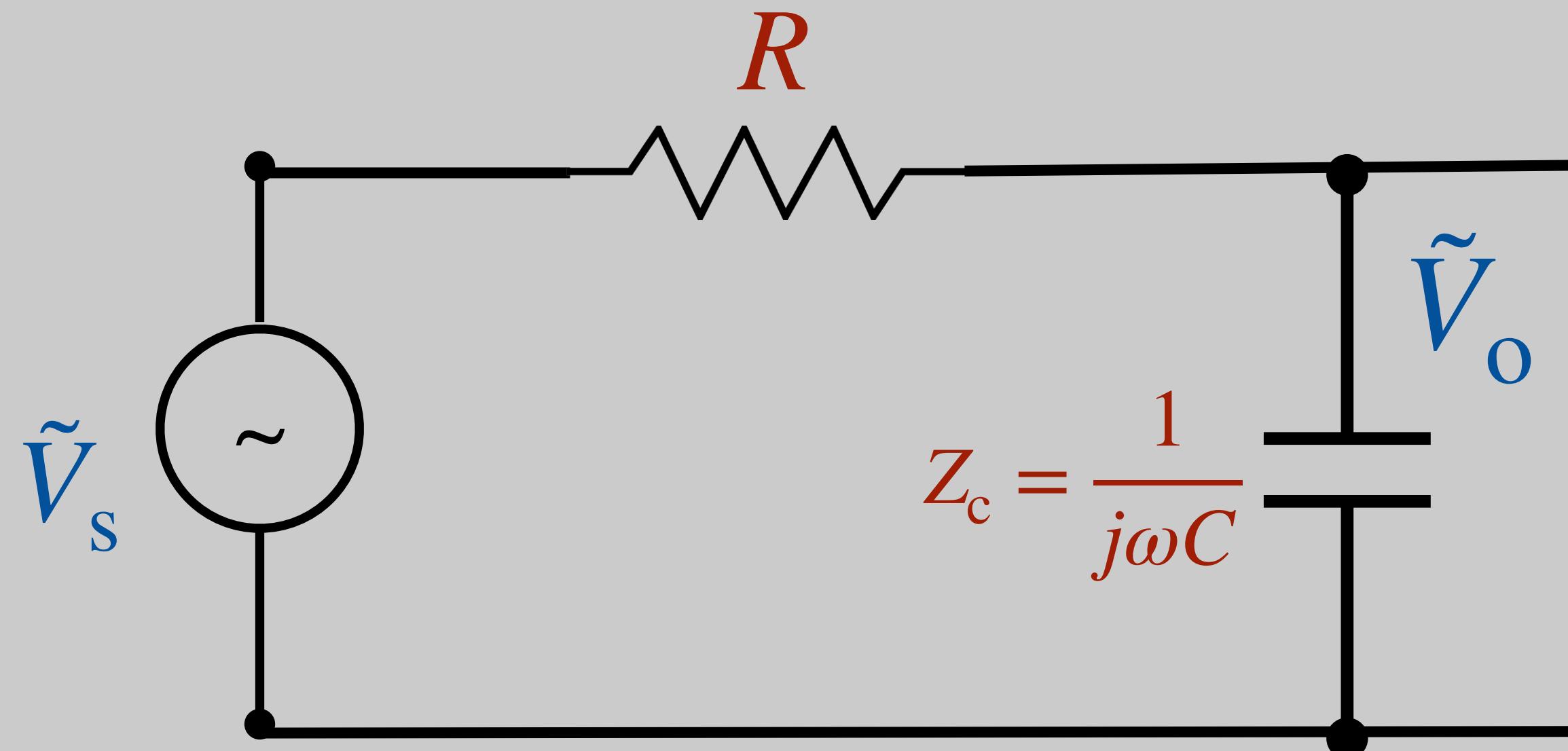

Voltage divider:

$$\tilde{V}_o = \frac{Z_c}{R + Z_c} \tilde{V}_s$$

$$\tilde{V}_o = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \tilde{V}_s$$

$$\tilde{V}_o = \frac{1}{j\omega RC + 1} \tilde{V}_s$$

Example 1: AC Response of an RC

$$\tilde{V}_o = \frac{1}{j\omega RC + 1} \tilde{V}_s$$



$$H(j\omega) = \frac{\tilde{V}_o}{\tilde{V}_s} = \frac{1}{j\omega RC + 1}$$

magnitude Resp:

$$|H(j\omega)| = \frac{1}{\sqrt{\omega^2(RC)^2 + 1}}$$

phase Resp:

$$\angle H(j\omega) = -\text{atan}(\omega RC)$$

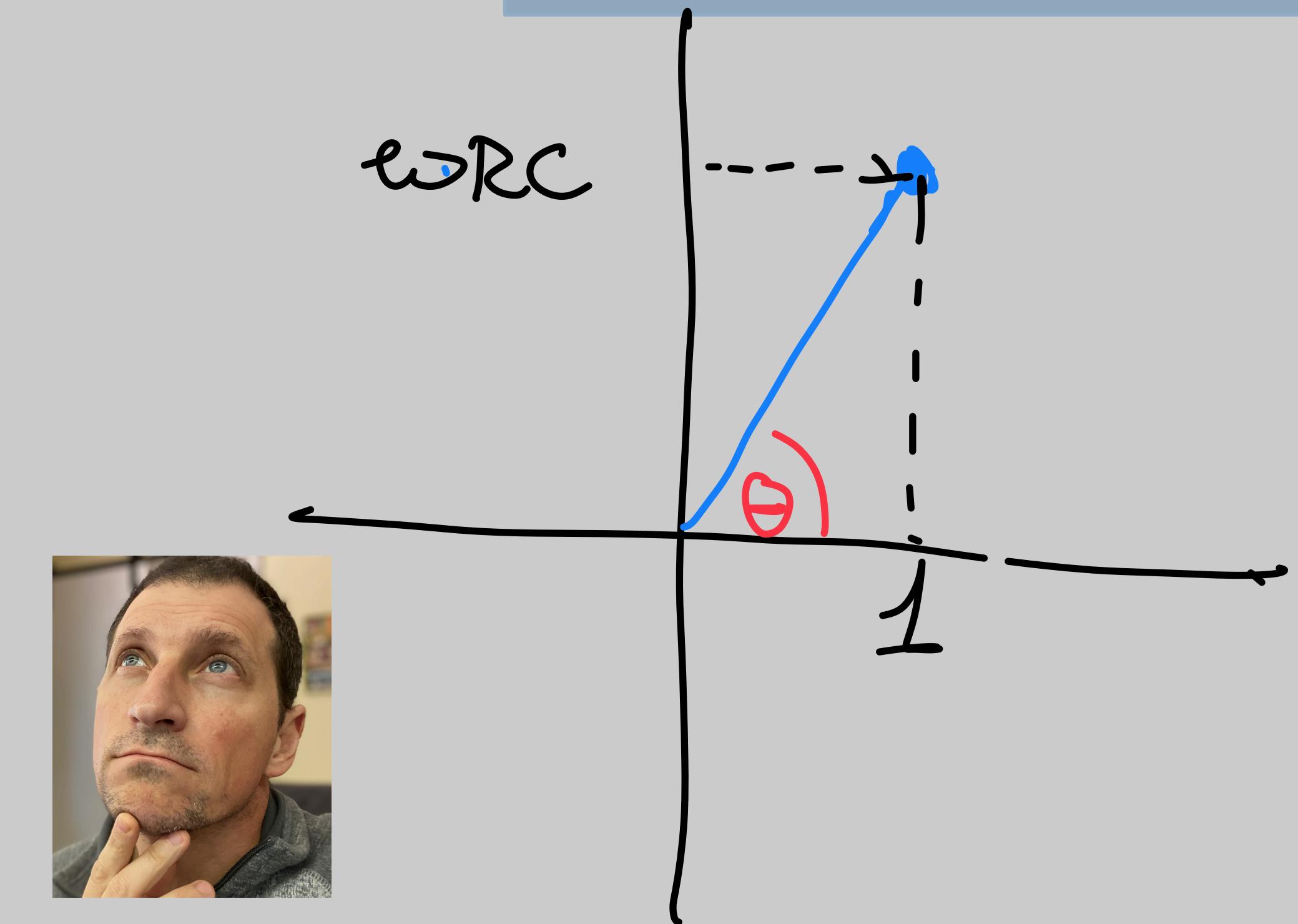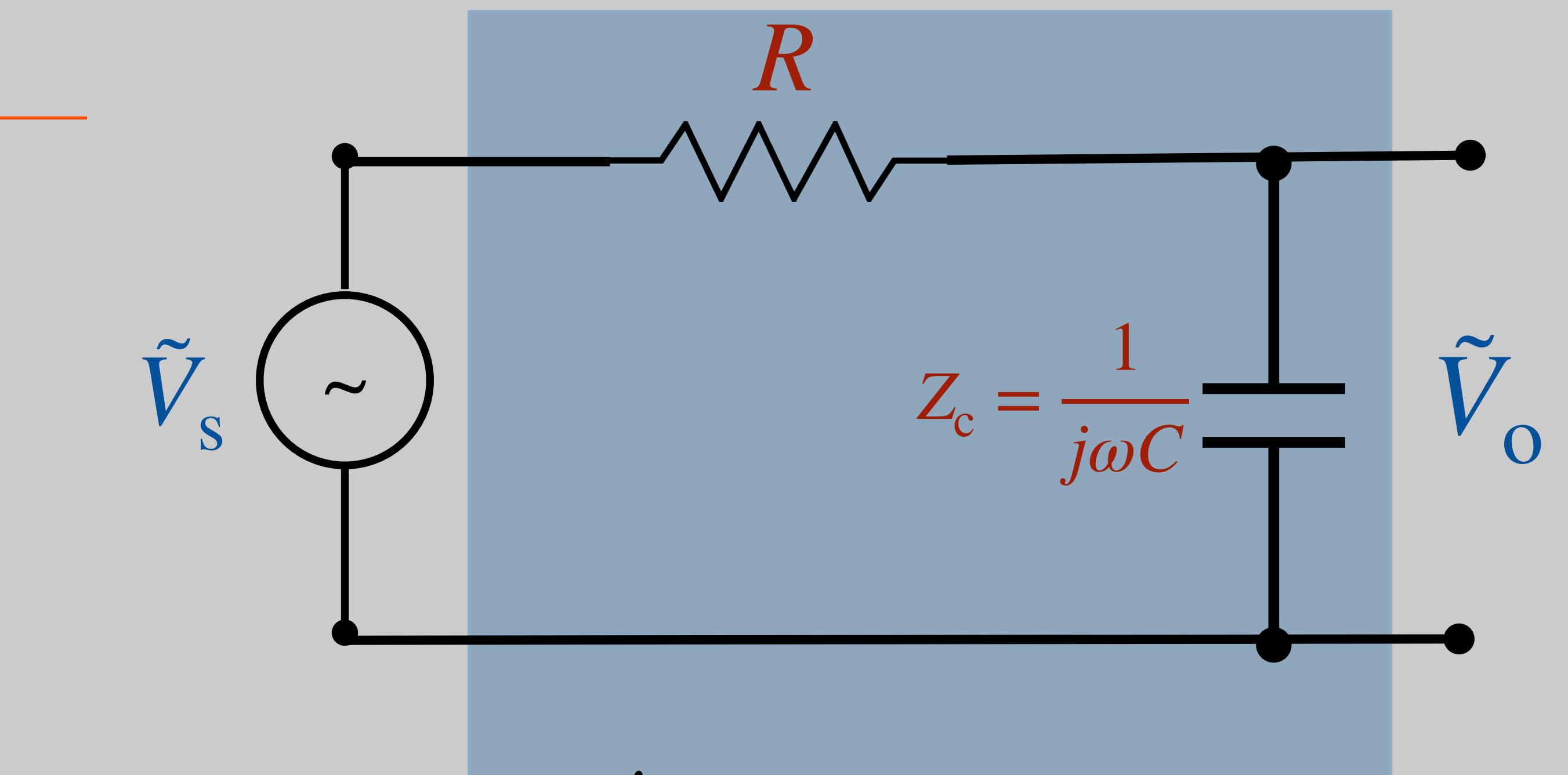

Example 1: AC Response of an RC

$$|H(j\omega)| = \frac{1}{\sqrt{\omega^2(RC)^2 + 1}}$$

$$\angle H(j\omega) = -\text{atan}(\omega RC)$$

$$\omega = 0$$

$$|H(j\omega)| = 1$$

$$\angle H(j\omega) = 0$$

$$\omega = \frac{1}{RC}$$

$$|H(j\omega)| = \frac{1}{\sqrt{2}}$$

$$\angle H(j\omega) = -\frac{\pi}{4} = -45^\circ$$



$$\omega \gg \frac{1}{RC}$$

$$|H(j\omega)| \approx \frac{1}{\omega(RC)}$$

$$\omega \rightarrow \infty$$

$$|H(j\omega)| \rightarrow 0$$

$$\angle H(j\omega) = -\frac{\pi}{2} = -90^\circ$$

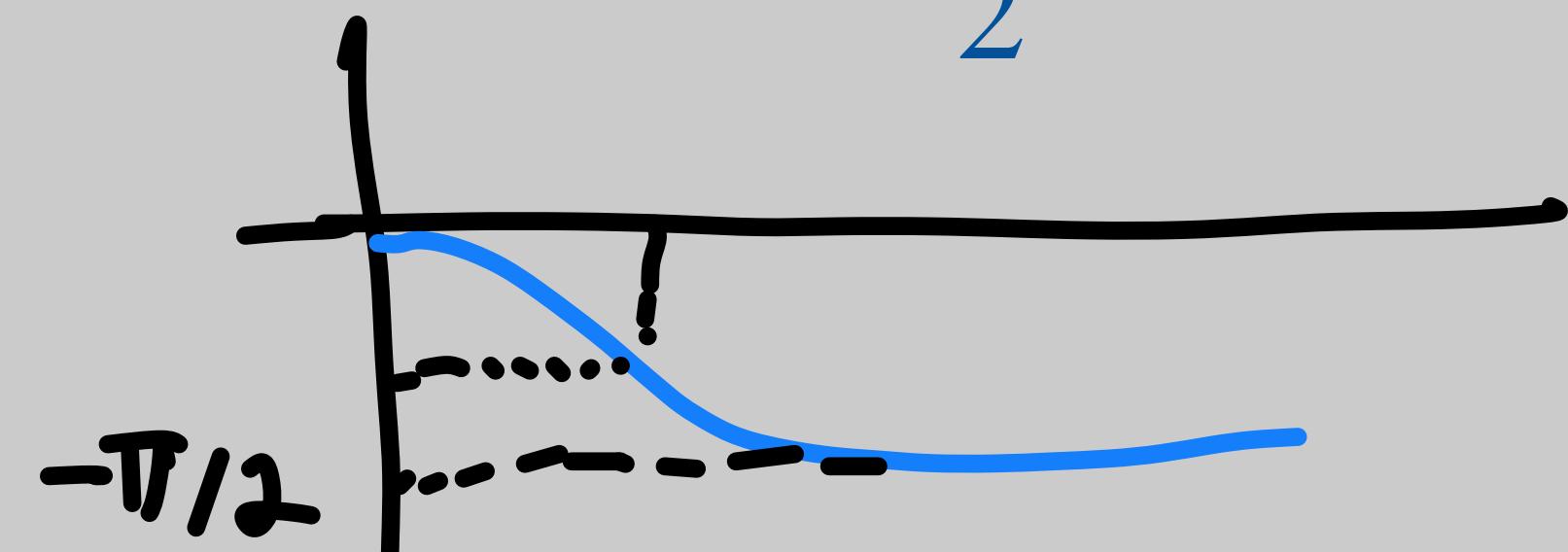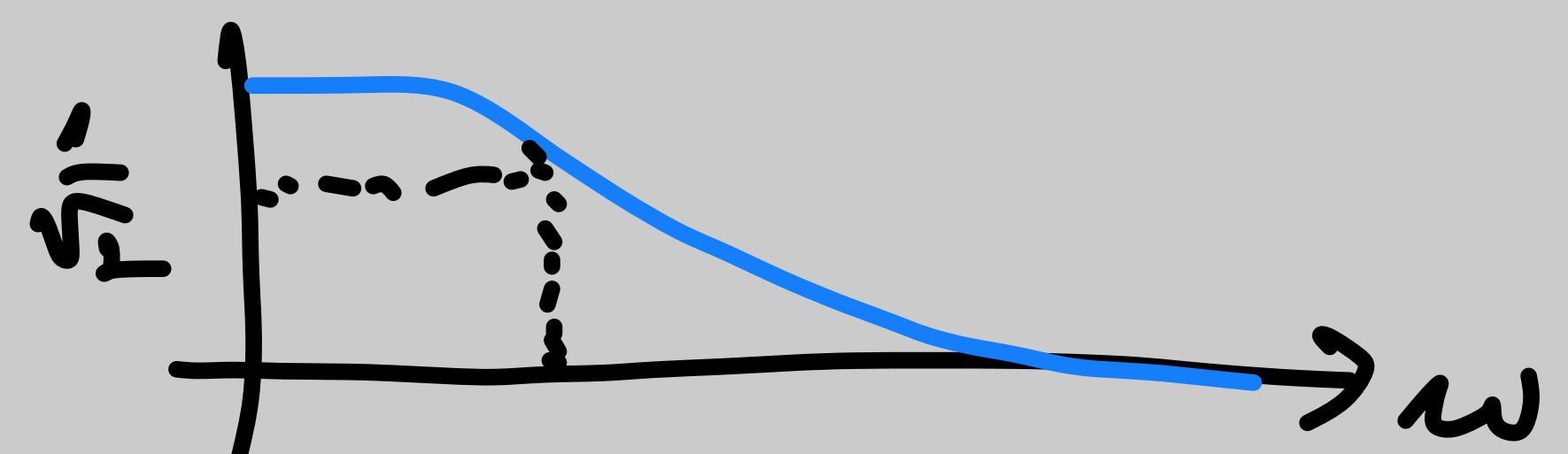


Example 1: AC Response of an RC

$$|H(j\omega)| = \frac{1}{\sqrt{\omega^2(RC)^2 + 1}}$$


$$\angle H(j\omega) = -\text{atan}(\omega RC)$$

$$\omega = \frac{1}{RC} = 2\pi 100$$

$$|H(j\omega)| = \frac{1}{\sqrt{2}}$$

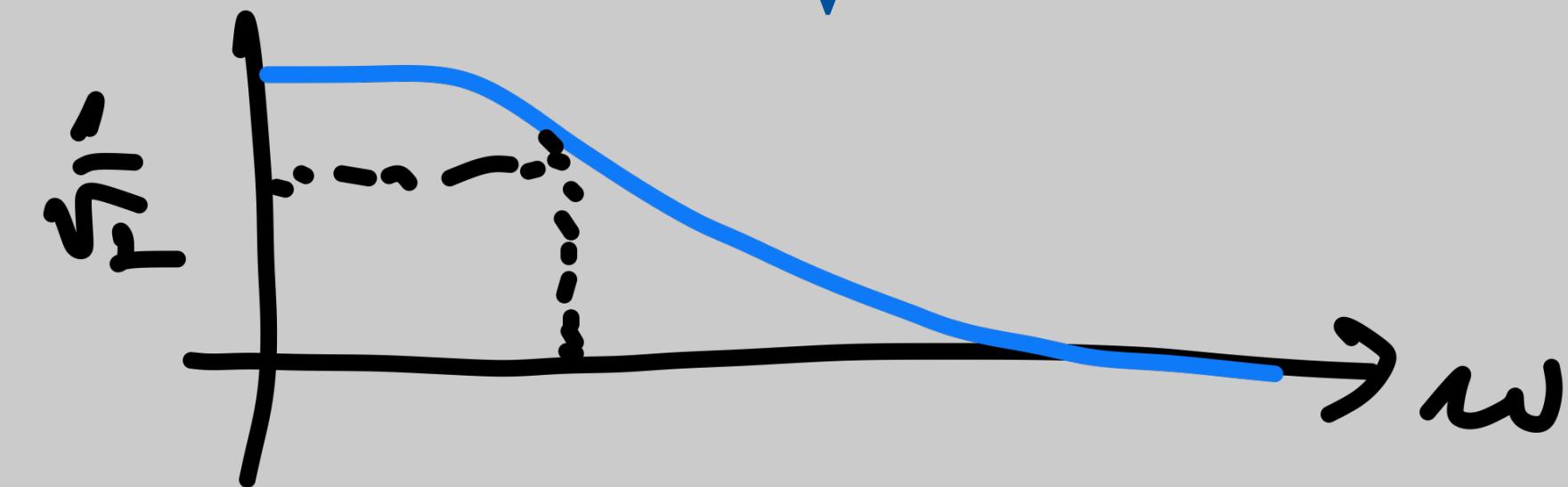
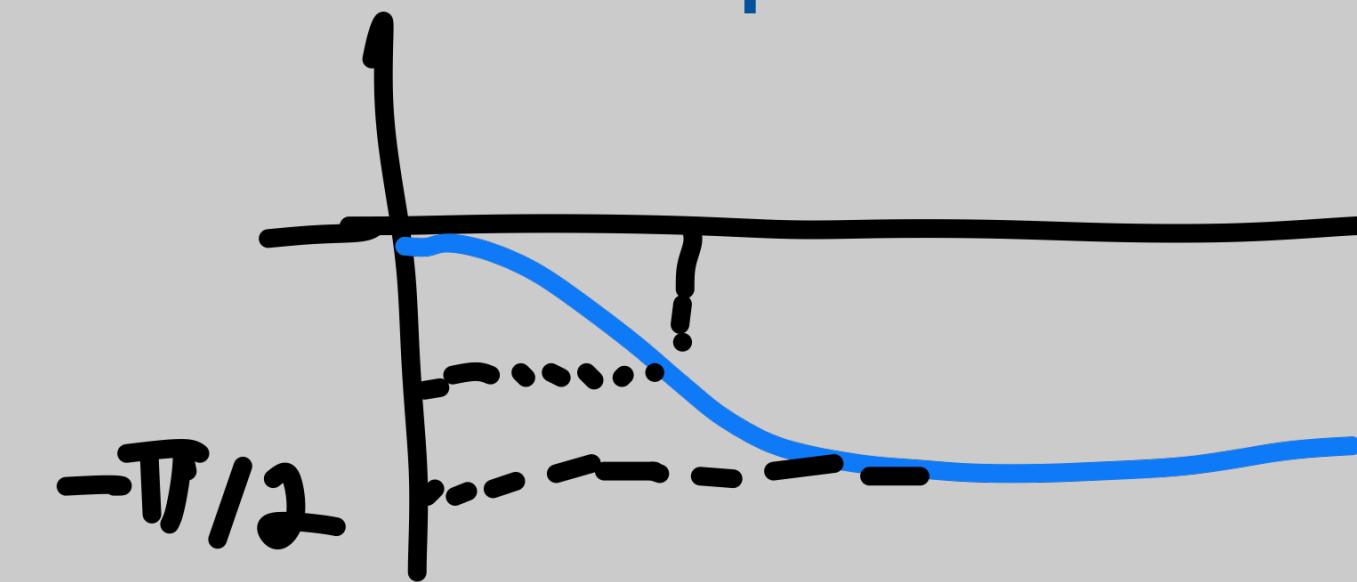
$$\angle H(j\omega) = -\frac{\pi}{4} = -45^\circ$$



Input:

$$V_s(t) = V_{DD} \cos(2\pi \cdot 100t)$$


Output:

$$V_o(t) = \frac{1}{\sqrt{2}} V_{DD} \cos \left(2\pi \cdot 100t - \frac{\pi}{4} \right)$$

Example 1: AC Response of an RC

1

$$|H(i\omega)| = \frac{1}{\sqrt{1 + (\tan(\omega RC))^2}}$$

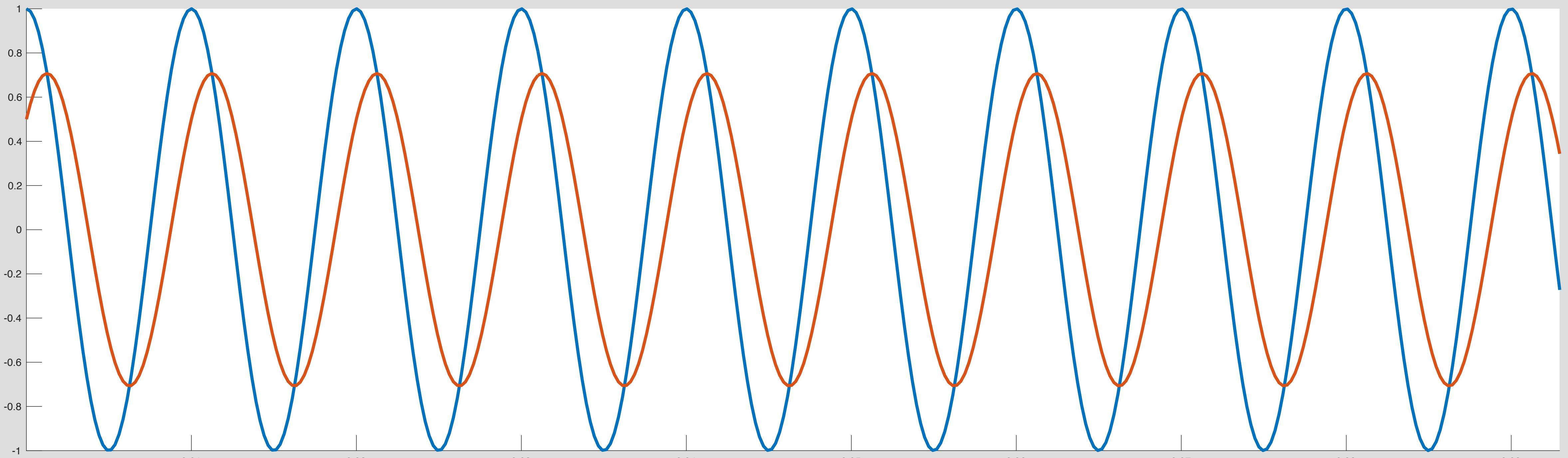

Input:

$$V_s(t) = V_{DD} \cos(2\pi \cdot 100t)$$


Output:

$$V_o(t) = \frac{1}{\sqrt{2}} V_{DD} \cos \left(2\pi \cdot 100t - \frac{\pi}{4} \right)$$

Example 1: AC Response of an RC

1

$$|H(i\omega)| = \frac{1}{\sqrt{1 + (\omega/\omega_{RC})^2}}$$

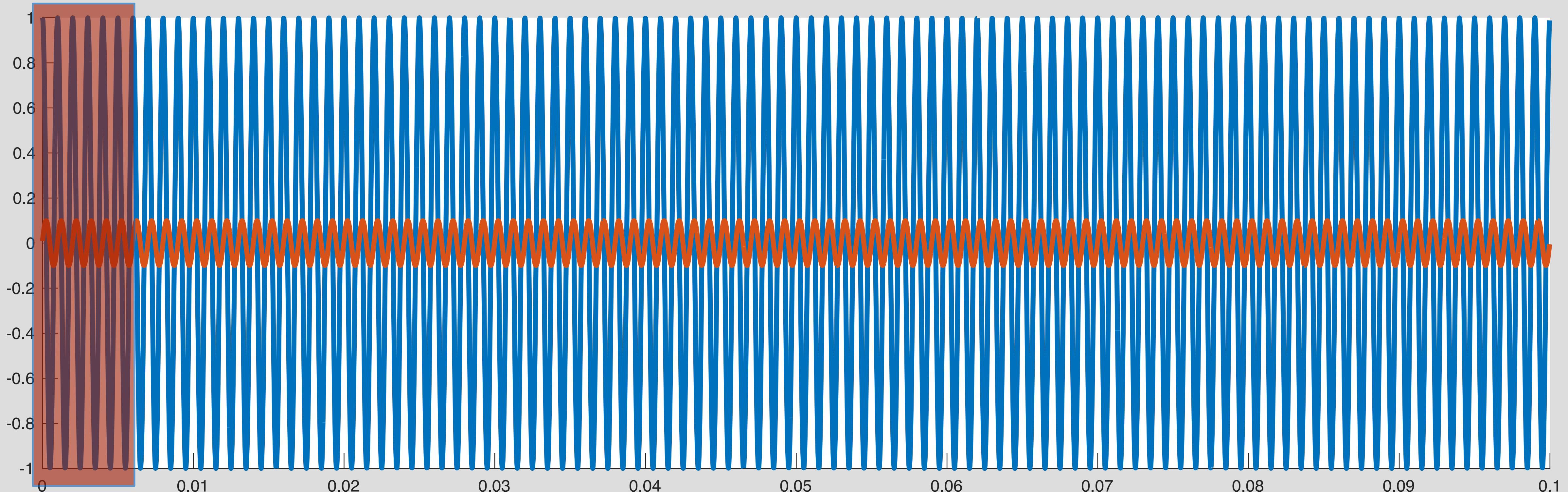


Input:

$$V_s(t) = V_{DD} \cos(2\pi \cdot 1000t)$$

Output:

$$V_o(t) \approx 0.1 V_{DD} \cos(2\pi \cdot 1000t - 0.46\pi)$$

Example 1: AC Response of an RC

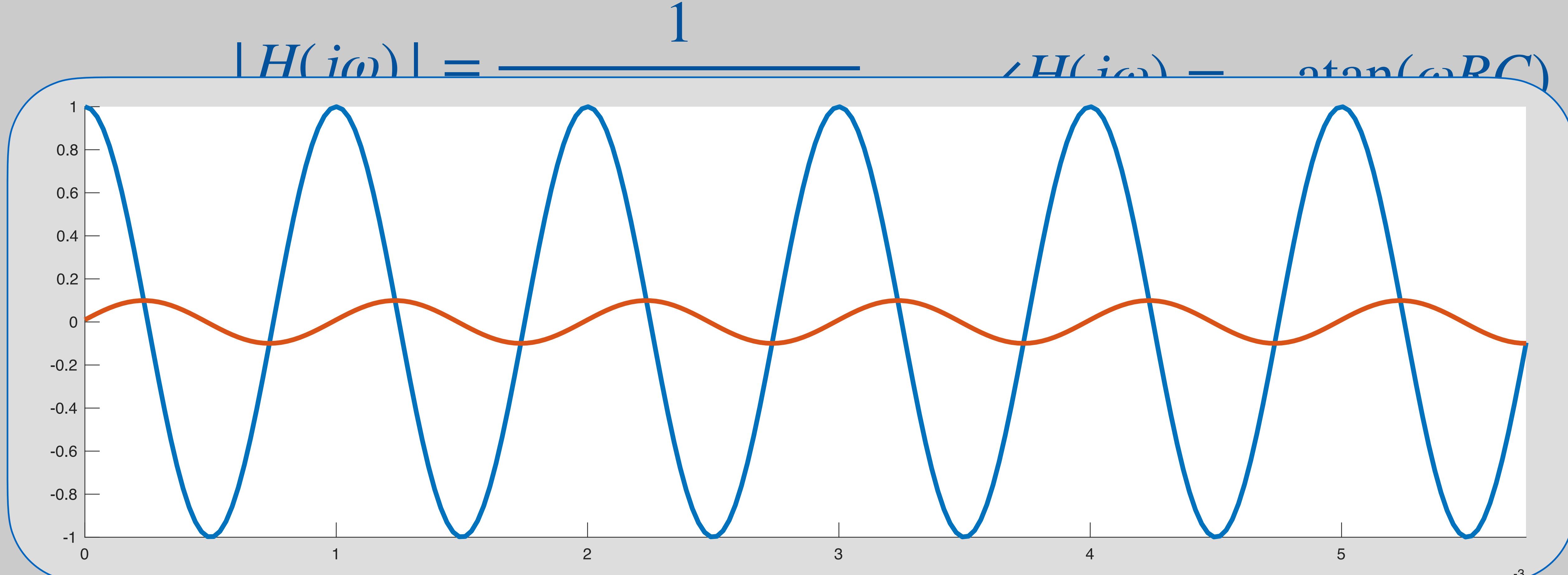

Input:

$$V_s(t) = V_{DD} \cos(2\pi \cdot 100t)$$

Output:

$$V_o(t) \approx 0.1V_{DD} \cos(2\pi \cdot 1000t - 0.46\pi)$$