# EE16BDesigning Information **Devices and Systems II** Lecture 4B More Phasors, Freq. Response / Transfer function / AC Power And MRI Coils

# Announcements

- Last time:
  - Resonant Tank
  - AC Response / Phasors
- Today:
  - Cont. AC response
  - AC Power



# Complex valued "resistance"

# $\sum_{\text{Impedance}} Z = R + jX$ Reactance Resistance







## AC responses using phasors:



EECS16B Tennant & Lustig, EECS UC Berkeley

Voltage divider:



$$\begin{split} \tilde{V}_{o} &= \frac{1}{j\omega RC + 1} \tilde{V}_{s} \\ H(j\omega) &= \frac{\tilde{V}_{o}}{\tilde{V}_{s}} = \frac{1}{j\omega RC + 1} \\ magnitude \ Resp: \\ |H(j\omega)| &= \frac{1}{\sqrt{\omega^{2}(RC)^{2} + 1}} \\ phase \ Resp: \\ \angle H(j\omega) &= -\operatorname{atan}(\omega RC) \end{split}$$







# $\omega \to \infty \quad |H(j\omega)| \to 0 \qquad \qquad \angle H(j\omega) = -\frac{\pi}{2} = -90^{\circ}$





# $\angle H(j\omega) = -\operatorname{atan}(\omega RC)$







# Input: $V_{\rm s}(t) = V_{\rm DD} \cos(2\pi \cdot 100t)$

EECS16B Tennant & Lustig, EECS UC Berkeley

Output:  $V_{\rm s}(t) = \frac{1}{\sqrt{2}} V_{\rm DD} \cos\left(2\pi \cdot 100t - \frac{\pi}{4}\right)$ 

			٦	0
			-	-0
			_	-0
				-0
				-0
				-0
				-1
				-1
				-1
				-1







Input:

Output:

 $V_{\rm s}(t) = V_{\rm DD} \cos(2\pi \cdot 1000t)$ 

EECS16B Tennant & Lustig, EECS UC Berkeley

 $V_{\rm s}(t) \approx 0.1 V_{\rm DD} \cos \left( 2\pi \cdot 1000t - 0.46\pi \right)$ 





$$V_{\rm s}(t) = V_{\rm DD} \cos(2\pi \cdot 100t)$$

- Network theorems that apply:
  - Voltage / current dividers
  - Source superposition
  - Thevenin/Norton





Rules of  $\downarrow$  for L and C:

For DC:

$$\lim_{\omega \to 0} Z_{\rm c} = \frac{1}{j\omega C} = \infty$$

$$\lim_{\omega \to 0} Z_{\rm L} = j\omega L = 0$$





Rules of  $\downarrow$  for L and C:

For DC:

$$\lim_{\omega \to 0} Z_{\rm c} = \frac{1}{j\omega C} = \infty$$

$$\lim_{\omega \to 0} Z_{\rm L} = j\omega L = 0$$





Rules of  $\downarrow$  for L and C:

For DC:

$$\lim_{\omega \to 0} Z_{\rm c} = \frac{1}{j\omega C} = \infty$$

$$\lim_{\omega \to 0} Z_{\rm L} = j\omega L = 0$$

For very high frequency:

$$\lim_{\omega \to \infty} Z_{\rm c} = \frac{1}{j\omega C} = 0$$

$$\lim_{\omega \to \infty} Z_{\rm L} = j\omega L = \infty$$

$\tilde{V}_{s}$	Ĩ	

 $ilde{V}_{
m s}$ 





Rules of  $\downarrow$  for L and C:

For DC:

$$\lim_{\omega \to 0} Z_{\rm c} = \frac{1}{j\omega C} = \infty$$

$$\lim_{\omega \to 0} Z_{\rm L} = j\omega L = 0$$

For very high frequency:

$$\lim_{\omega \to \infty} Z_{\rm c} = \frac{1}{j\omega C} = 0$$

$$\lim_{\omega \to \infty} Z_{\rm L} = j\omega L = \infty$$



# Series RLC AC analysis

 $R+Z_{L}+Z_{c}$   $R+jul+'_{ii}$  $\tilde{V}_{\rm s}$ Q: When Is is maximized A: when jul= Res j20C Q: what is V?? A: = () / ` ` ' Vic



# Series RLC AC analysis

 $R+Z_L+Z_c$   $R+jUL+_jUL+_jUC$ S Q: When Is is maximized A: when jul? E Resu j62C Q: what is V?? A:  $\tilde{V}_{r} = \tilde{I}$ Vic



## Series RLC Resonance

At: 
$$\omega = \frac{1}{\sqrt{LC}} \Rightarrow Z_c + Z_L = 0$$
  
But....  $\tilde{V}_c = -j\tilde{V}_sQ$   
If  $Q = 400 |\tilde{V}_c| = 400 |\tilde{V}_s|$    
Passive voltage gain!

 $ilde{V}_{
m s}$ 

Circuit at DC ( $\omega = 0$ ):



EECS16B Tennant & Lustig, EECS UC Berkeley



## Circuit at high-freq ( $\omega \rightarrow \infty$ ):





# Parallel RLC Resonance

 $Z_{\rm Ld} = Z_{\rm C} || Z_{\rm L}$  $Z_{\text{Ld}} = \frac{1}{j\omega C + \frac{1}{j\omega L}} = \frac{1}{1 - \omega^2 LC}$  $\Rightarrow \tilde{i} \rightarrow 0$  $\lim_{\omega \to \frac{1}{\sqrt{LC}}} Z_{\text{LD}} = \infty$  $\Rightarrow \tilde{V}_{Z_{\rm Ld}} \rightarrow \tilde{V}_{\rm th}$ 



# MRI Receiver Coils

- Near-field antennas
- Receive the MRI signal
- Designed to maximize signal at the MRI frequency
  - Arrays are key for SNR & acceleration



## courtesy Boris Keil, Larry Wald, MGH



# Proximity is the Key



\*Corea et al, Nat Commun. 2016;7:10839



# Coil Arrays

 Use multiple small elements to - Gain SNR and coverage - Gain Speed (parallel imaging)







# **Receive Coil Components**



# **Receive Coil Components: Capacitors**





# **Receive Coil Components: Capacitors**





# **Receive Coil Components: Detuning**



# Pediatric Coil Arrays

- Array density, coverage and fit are key
  Often adult coils are used

  Limits SNR
  Limits acceleration
  - Limits patients management





# Origin Story (2011).



AC Arias



# The Dream







# A Corea, AC Arias et al. Nature comm. 2016;7:10839. UC Berkeley

0



C

# 1st Volunteer Imaging 2013





8 Channel Printed Array

12 Channel Coil



# Baby Hope – preparing for patient imaging 2014









# 1st Baby – 3kg, 10 weeks old patient





# "The Berkeley 12" - 2016

# • 12ch

- Printed Antennas
- Remote Detuning
- Unique Packaging
- Weight 360gr

J. Corea, Lustig, Arias, et al. Nature comm. 2016;7:10839. UC Berkeley J. Corea, Lustig, Arias, et al. MRM. 2017;78(2):775. UC Berkeley







# The Berkeley 12ch Array 5 years old

> Radiology. 2019 Apr;291(1):186-187. doi: 10.1148/radiol.2019190209. Comment Epub 2019 Feb 26.

# Can We Convert a Comfort Blanket to an MRI Coil?

## Hildo J Lamb<sup>1</sup>









# Founded InkSpace Imaging 2017



# INKSPACE IMAGING



## M. Lustig



AC Arias



B. Lechêne



J. Corea





# Pediatric 24ch printed array

- FDA 510K Approved as of 12/2021













# 15-Channel Twisted Wire Head Array



tၞ

![](_page_38_Picture_2.jpeg)

richardedden @richardedden · Jun 4 For when you absolutely need to get an MRI immediately before robbing a bank...

3

![](_page_38_Picture_4.jpeg)

## ıl<sub>ı</sub>ı 155

し

ality

# Multiple Positions, compatible with EEG

![](_page_39_Picture_1.jpeg)

# What now?

![](_page_40_Picture_2.jpeg)

AC Voltage/Current of a Resistive Load

 $V_{\rm R}(t) = V_0 \cos(\omega t)$ 

Phasor form:  $V_{\rm R}(t) = \tilde{V}_{\rm R} e^{j\omega t}$ Amplitude:  $|\tilde{V}_{R}| = V_{0}$ Phase:  $\angle \tilde{V}_{R} = 0$ Frequency:  $\omega = \frac{2\pi}{T_{x}} = 2\pi f^{\text{[Hz]}} \text{[rad/s]}$ > Load: **Resistive Load:**  $i_{\rm R}(t) = \frac{V_{\rm R}(t)}{R} = \frac{\tilde{V}_{\rm R}e^{j\omega t}}{R}$  $\tilde{I}_{\rm R} = \frac{\tilde{V}_{\rm R}}{R} \implies i_{\rm R}(t) = \frac{V_0}{R}\cos(\omega t)$ 

![](_page_41_Figure_4.jpeg)

AC Voltage/Current of a Resistive Load

 $V_{\rm R}(t) = V_0 \cos(\omega t)$ 

Phasor form:  $V_{\rm R}(t) = \tilde{V}_{\rm R} e^{j\omega t}$ Amplitude:  $|\tilde{V}_{R}| = V_{0}$ Phase:  $\angle \tilde{V}_{R} = 0$ Frequency:  $\omega = \frac{2\pi}{T_{x}} = 2\pi f'[rad/s]$ > Load: **Resistive Load:**  $i_{\rm R}(t) = \frac{V_{\rm R}(t)}{R} = \frac{\tilde{V}_{\rm R}e^{j\omega t}}{R}$  $\tilde{I}_{\rm R} = \frac{\tilde{V}_{\rm R}}{R} \quad \Rightarrow i_{\rm R}(t) = \frac{V_0}{R}\cos(\omega t)$ 

![](_page_42_Figure_4.jpeg)

## AC Power of a Resistive Load

![](_page_43_Figure_1.jpeg)

![](_page_43_Figure_3.jpeg)

![](_page_43_Picture_4.jpeg)

## AC Power of a Resistive Load

$$V_{\rm R}(t) = V_0 \cos(\omega t) \qquad i_{\rm R}(t) = \frac{V_0}{R} \cos(\omega t)$$

$$p(t) = V_{\rm R}(t)i_{\rm R}(t) = \frac{V_0^2}{R} \cos^2(\omega_t)$$
Power consumed on positive and negative cycles!
$$p_{\rm avg} = \frac{1}{T} \int_0^T p(\tau)d\tau = \frac{V_0^2}{R} \frac{1}{T} \int_0^T \cos^2(\omega \tau)d\tau = \frac{1}{2}$$
Phasor form:
$$\tilde{V}_{\rm R} \qquad \tilde{I}_{\rm R} = \frac{\tilde{V}_{\rm R}}{R}$$

$$p_{\rm avg} = \frac{1}{2} \tilde{V}_{\rm R} \tilde{I}_{\rm R}^* = \frac{1}{2} \frac{|\tilde{V}_{\rm R}|^2}{R} = \frac{1}{2} \frac{V_0^2}{R}$$

EECS16B Tennant & Lustig, EECS UC Berkeley

![](_page_44_Figure_3.jpeg)

# $\frac{V_0^2}{R}$

![](_page_44_Picture_5.jpeg)

## AC Voltage/Current of a Capacitive Load

 $V_{\rm c}(t) = V_0 \cos(\omega t)$ 

Phasor form:  $V_{\rm c}(t) = \tilde{V}_{\rm c} e^{j\omega t}$ 

Capacitive Load:

![](_page_45_Figure_4.jpeg)

## AC Voltage/Current of a Capacitive Load

 $V_{\rm c}(t) = V_0 \cos(\omega t)$ 

Phasor form:  $V_{\rm c}(t) = \tilde{V}_{\rm c} e^{j\omega t}$ 

![](_page_46_Figure_4.jpeg)

![](_page_46_Figure_16.jpeg)

# AC Power of a Capacitive Load

 $V_{\rm C}(t) = V_0 \cos(\omega t)$   $i_{\rm C}(t) = -\omega C V_0 \sin(\omega t)$ 

 $p(t) = V_{\rm R}(t)i_{\rm R}(t) = -\omega CV_0^2 \cos(\omega t)\sin(\omega t)$ 

![](_page_47_Figure_4.jpeg)

![](_page_47_Figure_5.jpeg)

![](_page_47_Figure_6.jpeg)

## AC Power of a Capacitive Load

 $V_{\rm C}(t) = V_0 \cos(\omega t)$   $i_{\rm C}(t) = -\omega C V_0 \sin(\omega t)$ 

$$p(t) = V_{\rm R}(t)i_{\rm R}(t) = -\omega CV_0^2\cos(\omega t)\sin(\omega t)$$

Power oscillates between positive and negative twice a cycles! Power goes back and forth!

$$p_{\text{avg}} = \frac{1}{T} \int_{0}^{T} p(\tau) d\tau = 0$$
  
Phasor form:  $\tilde{V}_{\text{c}}$   $\tilde{I}_{\text{c}} = j\omega C \tilde{V}_{\text{c}}$ 

$$p_{\text{avg}} = \frac{1}{2} \tilde{V}_{\text{c}} \tilde{I}_{\text{c}}^* = \frac{1}{2} j \omega C V_0^2$$

Pure imaginary average power! Also called reactive power — a

## EECS16B Tennant & Lustig, EECS UC Berkeley

## Also called reactive power — average power stored in a cycle

![](_page_48_Figure_9.jpeg)

![](_page_48_Figure_10.jpeg)

# AC Power

Resistor:  $\tilde{I}_{\rm R} = \frac{\tilde{V}_{\rm R}}{R}$ Resistor: $\tilde{I}_{\rm R} = \frac{\tilde{V}_{\rm R}}{R}$  $p_{\rm avg} = \frac{1}{2} \frac{V_0^2}{R}$ Capacitor $\tilde{I}_{\rm c} = j\omega C \tilde{V}_{\rm c}$  $p_{\rm avg} = jC \frac{1}{2} V_0^2$  $\tilde{I}_{\rm L} = \frac{\tilde{V}_{\rm L}}{j\omega L} \qquad p_{\rm avg} = \frac{1}{2} \frac{V_0^2}{j\omega L}$ Inductor

Pure real resistive/ dissipating power

Pure imaginary **Reactive power** 

Pure imaginary **Reactive power** 

 $\tilde{I} = I_0 e^{j\theta_1}$   $\tilde{V} = V_0 e^{j\theta_2}$ General complex valued power:

$$p_{\text{avg}} = \frac{1}{2} \tilde{V} \tilde{I}^* = V_0 I_0 e^{j(\theta_2 - \theta_1)}$$

# AC Power

 $\begin{array}{ll} \text{Resistor:} & \tilde{I}_{\text{R}} = \frac{\tilde{V}_{\text{R}}}{R} & p_{\text{avg}} = \frac{1}{2} \frac{V_0^2}{R} & \underset{\text{dis}}{\text{dis}} \\ \text{Capacitor} & \tilde{I}_{\text{c}} = j\omega C \tilde{V}_{\text{c}} & p_{\text{avg}} = jC \frac{1}{2} V_0^2 & \underset{\text{Re}}{\text{Pu}} \\ \text{Inductor} & \tilde{I}_{\text{L}} = \frac{\tilde{V}_{\text{L}}}{j\omega L} & p_{\text{avg}} = \frac{1}{2} \frac{V_0^2}{j\omega L} & \underset{\text{Re}}{\text{Pu}} \end{array}$ 

General complex valued power:  $\tilde{I} = I_0 e^{j\theta_1}$   $\tilde{V} =$ 

$$p_{\text{avg}} = \frac{1}{2} \tilde{V}\tilde{I}^* = V_0 I_0 e^{j(\theta_2 - \theta_1)}$$

Resistive dissipating average power: Re

Reactive (storage) average power: Imag

EECS16B Tennant & Lustig, EECS UC Berkeley

Pure real resistive/ dissipating power Pure imaginary Reactive power

Pure imaginary Reactive power

![](_page_50_Figure_9.jpeg)

$$V_0 e^{j\theta_2}$$

$$\operatorname{eal}\{\frac{1}{2}\tilde{V}\tilde{I}^*\} = \frac{1}{2}V_0I_0\cos(\theta_2 - \theta_1)$$
$$\operatorname{g}\{\frac{1}{2}\tilde{V}\tilde{I}^*\} = \frac{1}{2}V_0I_0\sin(\theta_2 - \theta_1)$$

# Grid AC Voltage and Power

$$V_{\rm RMS} = \frac{1}{\sqrt{2}} V_{\rm magn}$$

$$V_{\rm magn}$$
=155V

 $V_{\rm RMS}$ =110V  $\rightarrow$ 

$$V_{\rm pp} = 2V_{\rm magn}$$

$$p_{\text{avg}} = \frac{1}{2} \tilde{V}\tilde{I}^* = \tilde{V}_{\text{RMS}}\tilde{I}_{\text{RMS}}^*$$

![](_page_51_Figure_7.jpeg)

![](_page_51_Figure_8.jpeg)