

EECS 16B

Designing Information Devices and Systems II

Profs. Miki Lustig and JP Tennant

Department of Electrical Engineering and Computer Science

Announcements:

- Midterm #1
 - Monday, February 26, 8-10pm
 - Scope is through material covered on today's lecture (end of circuits module)
- Systems and Controls starts next week (lots of linear algebra)

Today:

- Review/context
- Bode Plots
- Quality Factor (aka Q) for resonant circuits







Why sine waves?

Why sine waves?




Joseph Fourier

Why sine waves?

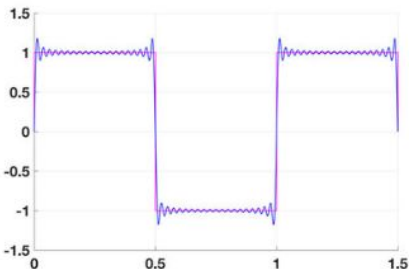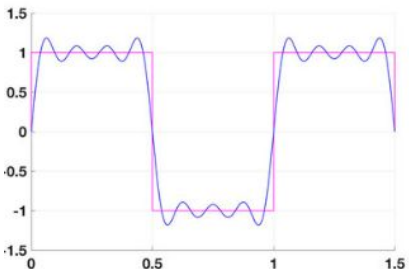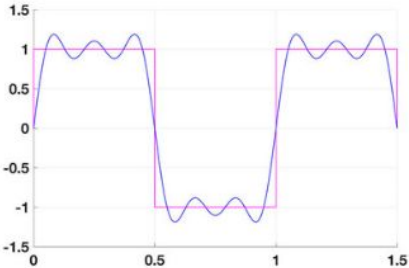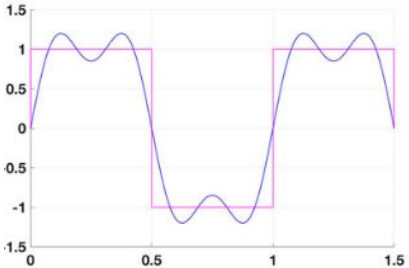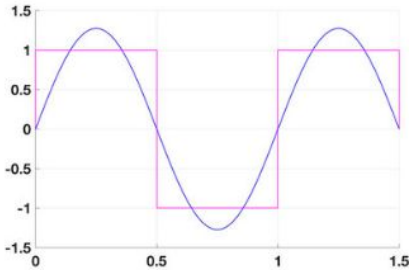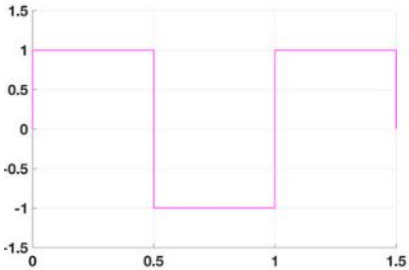

Joseph Fourier


Fourier Series (periodic signals):

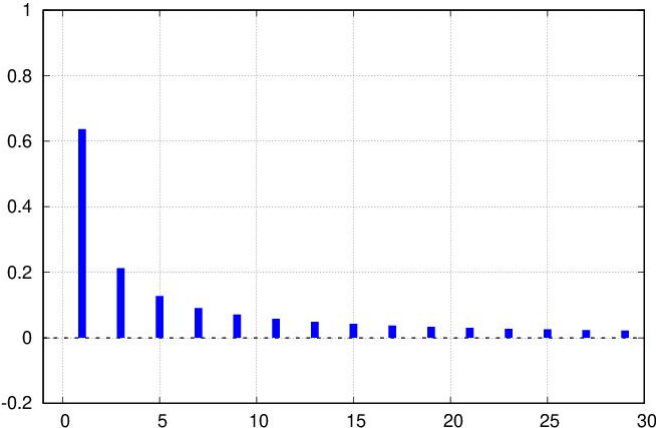


What do filters do?




Joseph Fourier

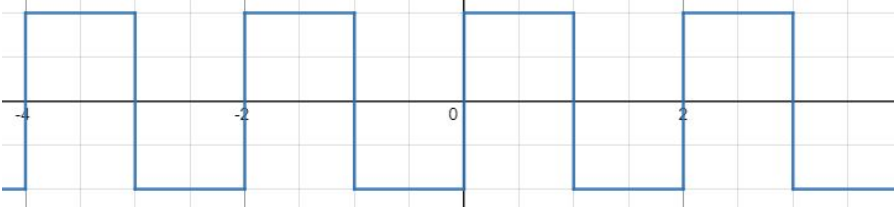


LPF:

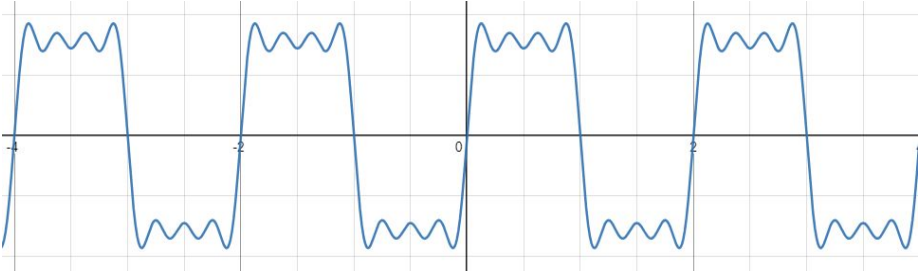

HPF:

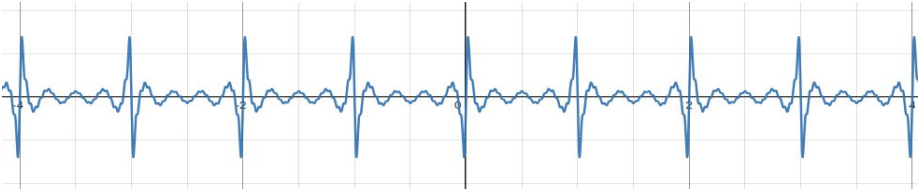

What about aperiodic signals?


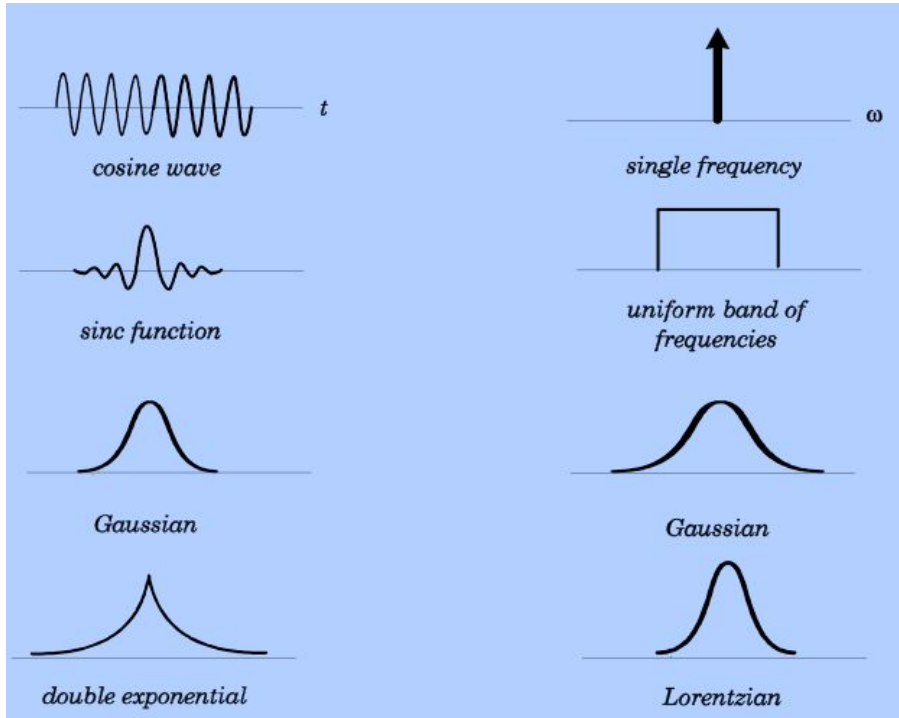



Joseph Fourier

Fourier Transform



What type of filter was used to process the below signal?

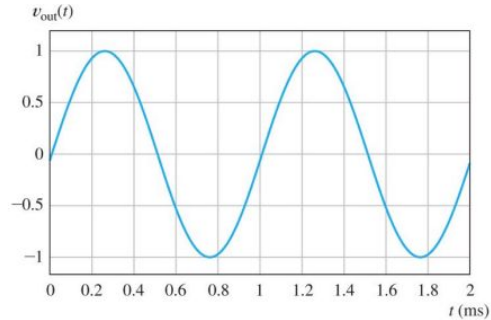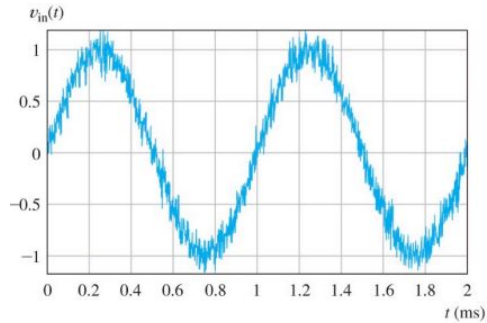1. Low Pass Filter
2. High Pass Filter
3. Band Pass Filter
4. Either 2 or 3
5. None of the above




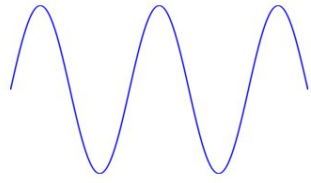


$$A \cos(\omega t + \alpha)$$

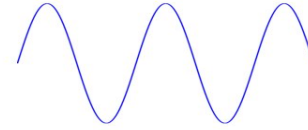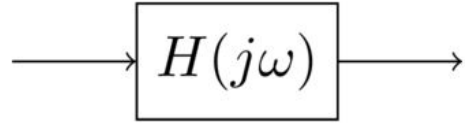


$$B \cos(\omega t + \beta)$$

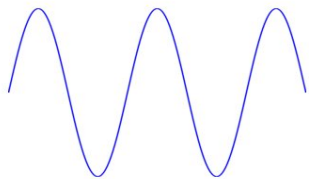



$$A \cos(\omega t + \alpha)$$

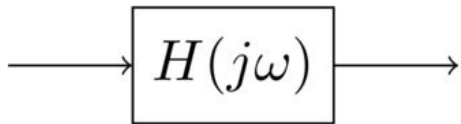



$$B \cos(\omega t + \beta)$$

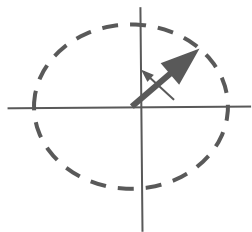

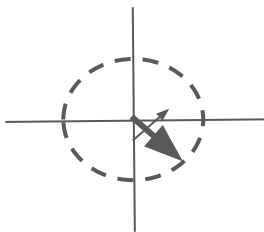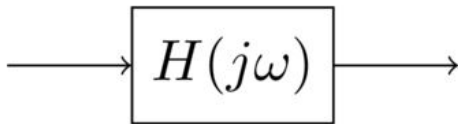
$$\text{Re} [Ae^{j\alpha} e^{j\omega t}]$$



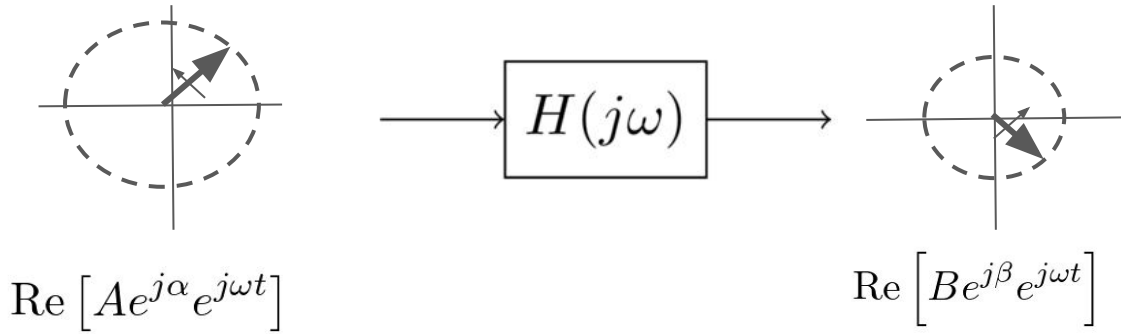
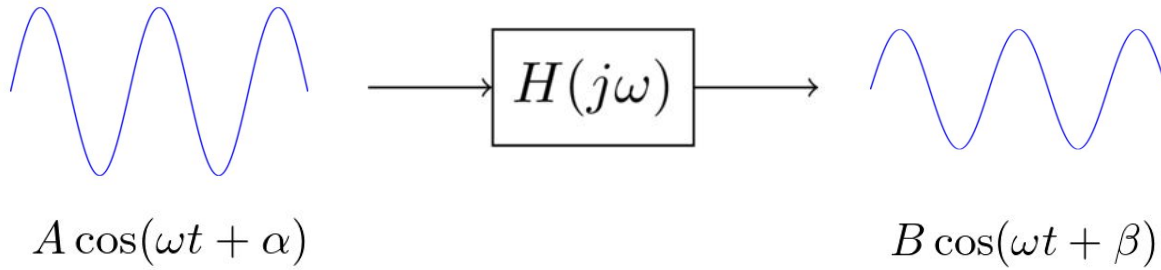
$$\text{Re} [Be^{j\beta} e^{j\omega t}]$$



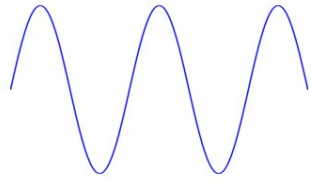
But... by definition, $Be^{j\beta} = H(j\omega)Ae^{j\alpha}$





$$A \cos(\omega t + \alpha)$$

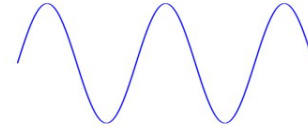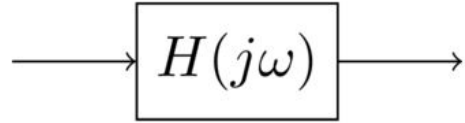

$$B \cos(\omega t + \beta)$$

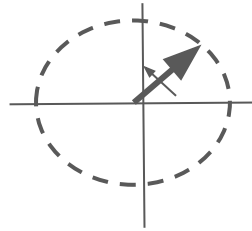
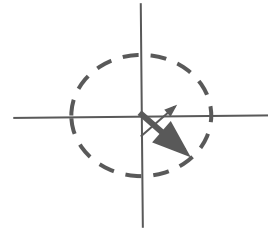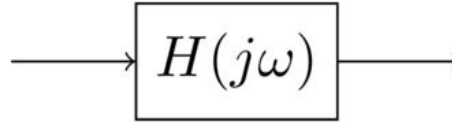
$$\text{Re} [Ae^{j\alpha} e^{j\omega t}]$$



$$\text{Re} [Be^{j\beta} e^{j\omega t}] = \text{Re} [H(j\omega) Ae^{j\alpha} e^{j\omega t}]$$

But... by definition, $Be^{j\beta} = H(j\omega)Ae^{j\alpha}$

True or False: A phasor is a rotating vector on the complex plane.

1. True
2. False


Cascaded systems => transfer functions multiply



Cascaded systems => transfer functions multiply



This is equivalent to:

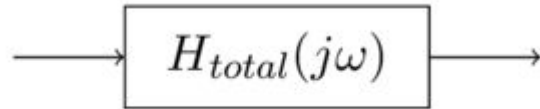

$$H_{total}(j\omega) = H_1(j\omega)H_2(j\omega)$$


Why $H(j\omega)$? Why not just $H(\omega)$?

Why $H(j\omega)$? Why not just $H(\omega)$?



Pierre-Simon Laplace

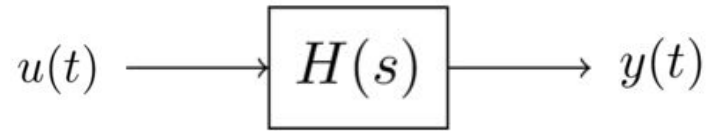Why $H(j\omega)$? Why not just $H(\omega)$?




$$s = \sigma + j\omega$$



Pierre-Simon Laplace

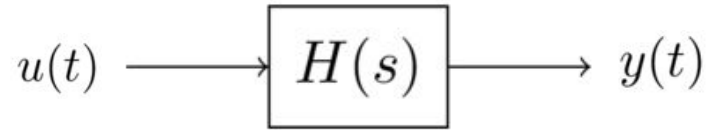Why $H(j\omega)$? Why not just $H(\omega)$?




$$s = \sigma + j\omega$$

$$e^{st} = e^{(\sigma+j\omega)t} = e^{\sigma t} e^{j\omega t}$$



Pierre-Simon Laplace

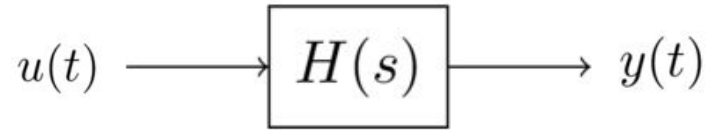Why $H(j\omega)$? Why not just $H(\omega)$?



$$s = \sigma + j\omega$$

$$e^{st} = e^{(\sigma+j\omega)t} = e^{\sigma t} e^{j\omega t}$$

$$H(s) = \frac{N(s)}{D(s)}$$


Zeros are values of s such that $N(s) = 0$

Poles are values of s such that $D(s) = 0$



Pierre-Simon Laplace

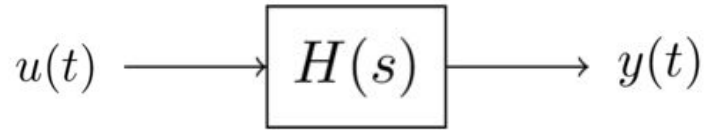Why $H(j\omega)$? Why not just $H(\omega)$?



$$s = \sigma + j\omega$$

$$e^{st} = e^{(\sigma+j\omega)t} = e^{\sigma t} e^{j\omega t}$$


$$H(s) = \frac{N(s)}{D(s)}$$

Zeros are values of s such that $N(s) = 0$


Poles are values of s such that $D(s) = 0$



Pierre-Simon Laplace

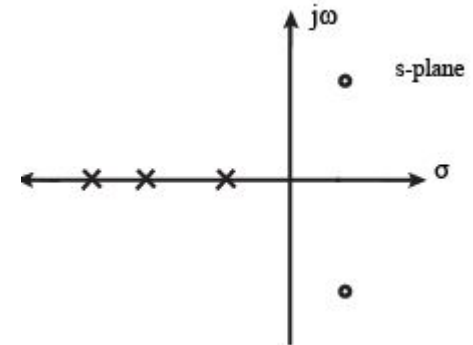

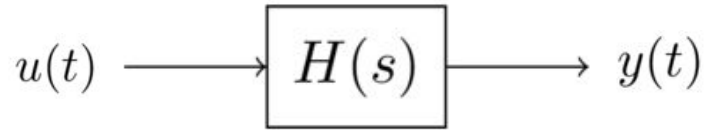Why $H(j\omega)$? Why not just $H(\omega)$?



$$s = \sigma + j\omega$$

$$e^{st} = e^{(\sigma+j\omega)t} = e^{\sigma t} e^{j\omega t}$$

$$H(s) = \frac{N(s)}{D(s)}$$

Zeros are values of s such that $N(s) = 0$


Poles are values of s such that $D(s) = 0$

$H(\cdot)$ is the **transfer function**.


$H(j\omega)$ is the **frequency response**.



Pierre-Simon Laplace

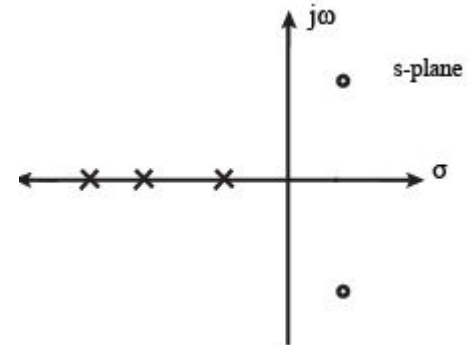

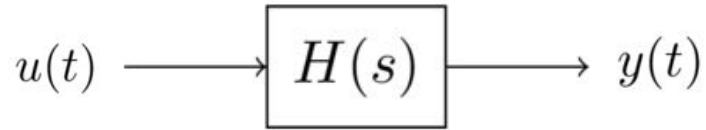Why $H(j\omega)$? Why not just $H(\omega)$?



$$s = \sigma + j\omega$$

$$e^{st} = e^{(\sigma+j\omega)t} = e^{\sigma t} e^{j\omega t}$$

$$H(s) = \frac{N(s)}{D(s)}$$

Zeros are values of s such that $N(s) = 0$


Poles are values of s such that $D(s) = 0$

$H(\cdot)$ is the **transfer function**.

$H(j\omega)$ is the **frequency response**.





Pierre-Simon Laplace

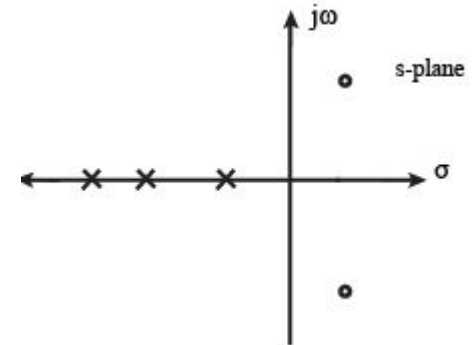



Laplace and s-domain will not be covered on the exam.

Bode Plots - Key Points

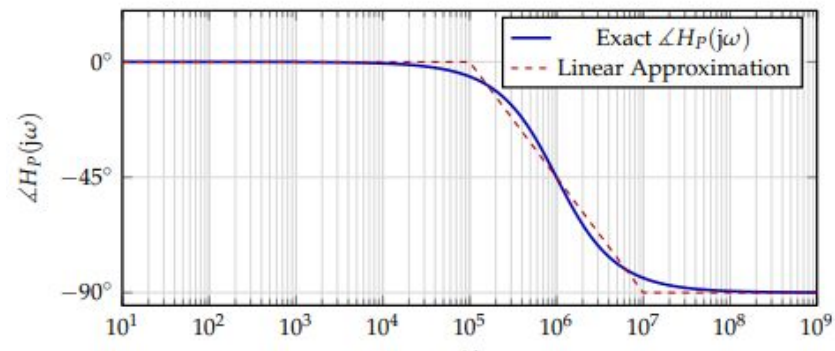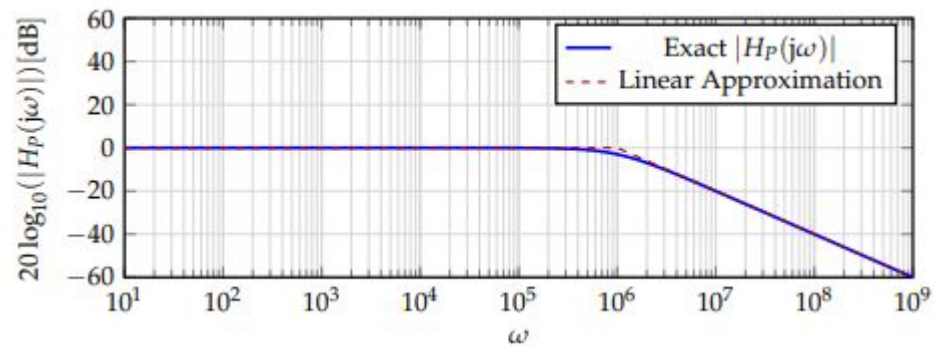



Bode Plots - Key Points

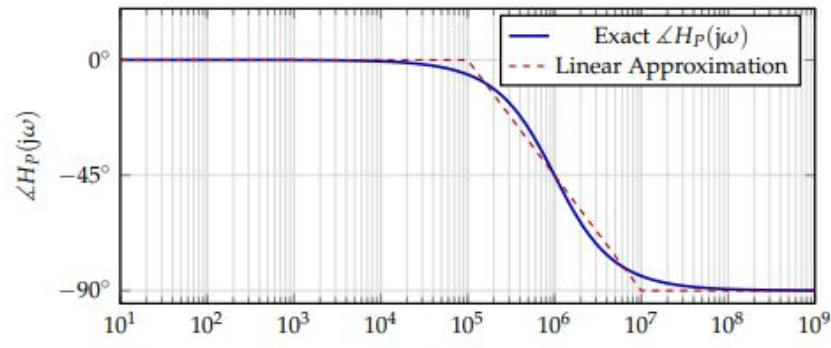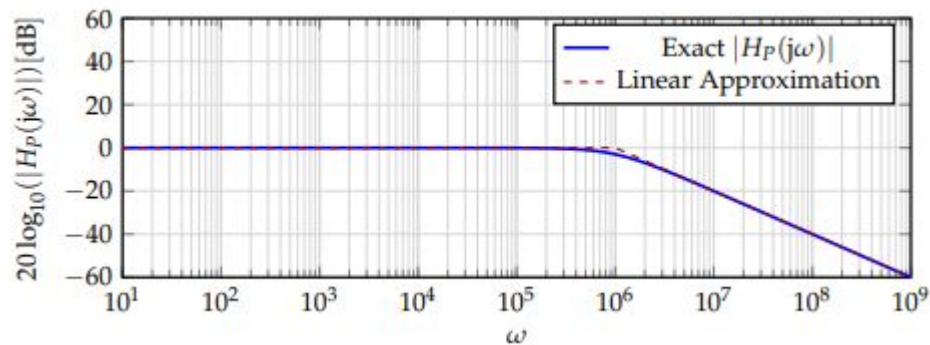- Piecewise linear approximations of frequency response





Bode Plots - Key Points

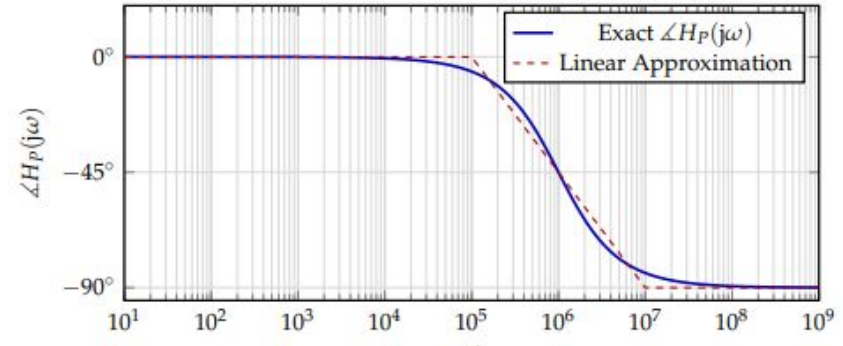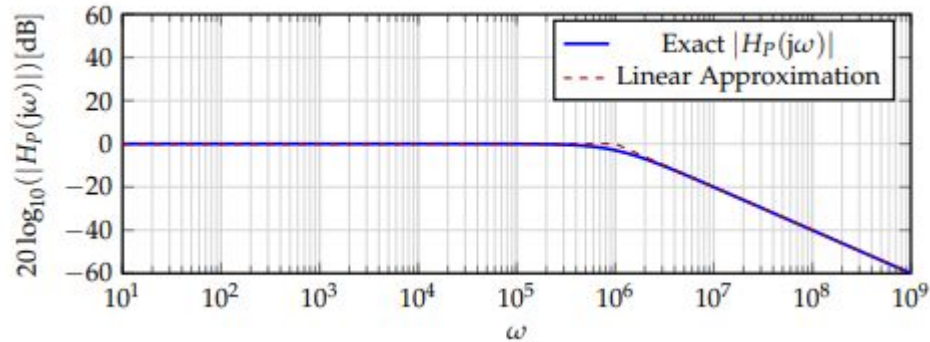- Piecewise linear approximations of frequency response
- Two graphs (magnitude and phase)





Bode Plots - Key Points

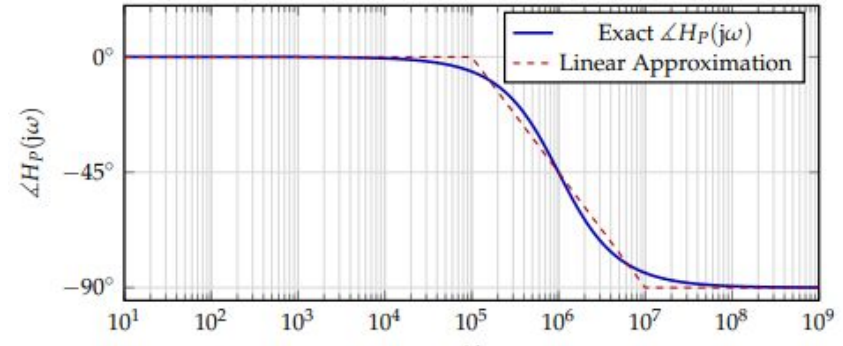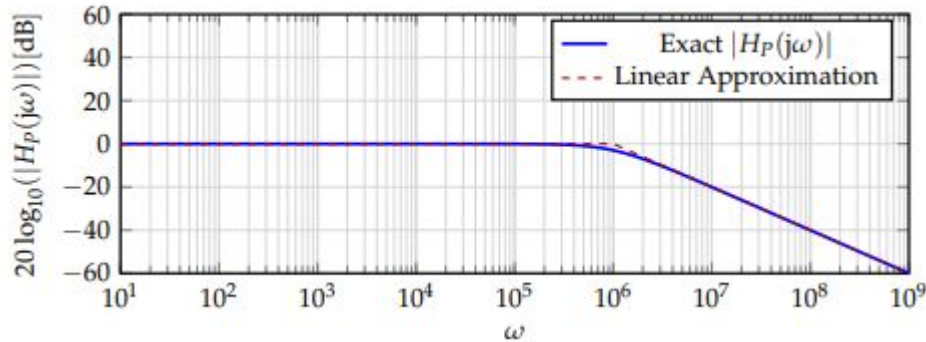- Piecewise linear approximations of frequency response
- Two graphs (magnitude and phase)
- Horizontal axis (ω) is always logarithmic





Bode Plots - Key Points

- Piecewise linear approximations of frequency response
- Two graphs (magnitude and phase)
- Horizontal axis (ω) is always logarithmic
- Magnitude is in dB = $20 \log (|H|)$

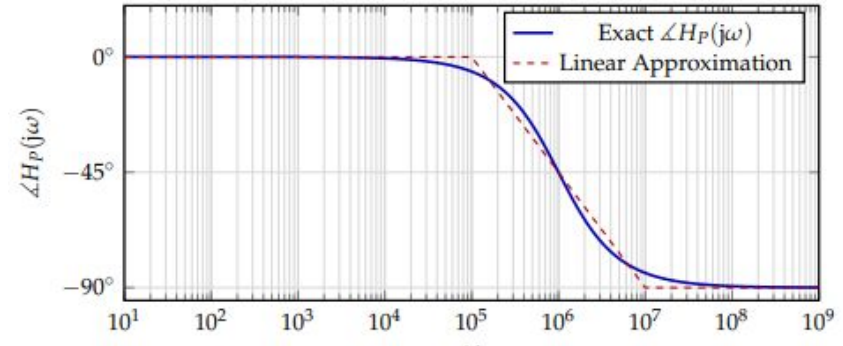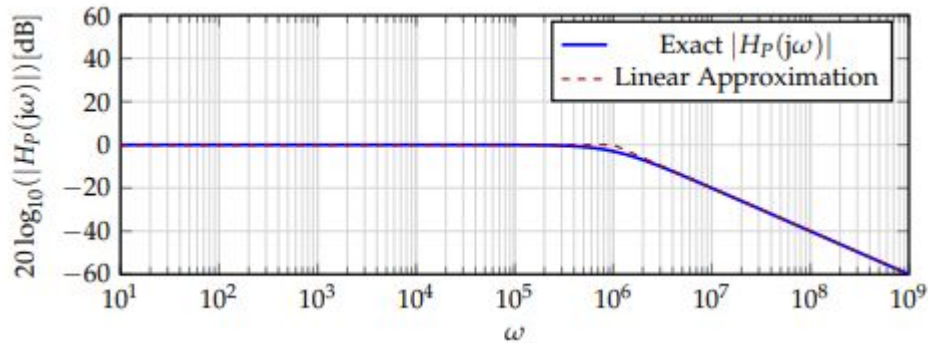



Bode Plots - Key Points

- Piecewise linear approximations of frequency response
- Two graphs (magnitude and phase)
- Horizontal axis (ω) is always logarithmic
- Magnitude is in dB = $20 \log(|H|)$
- Phase is in normal linear scale

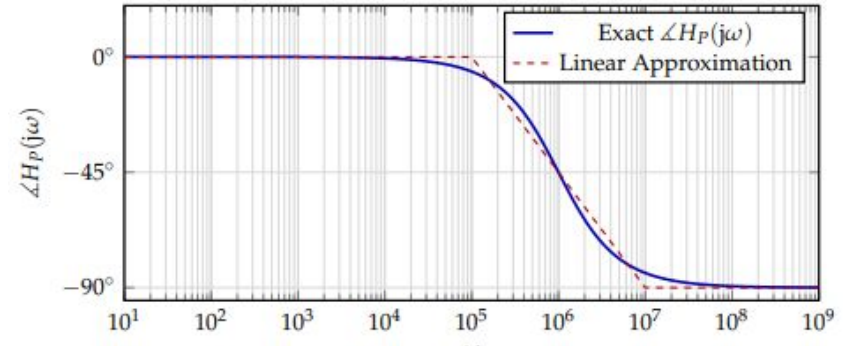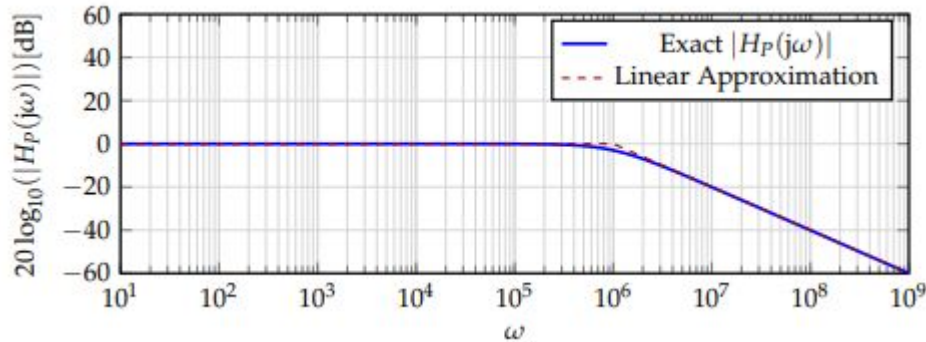



Bode Plots - Key Points

- Piecewise linear approximations of frequency response
- Two graphs (magnitude and phase)
- Horizontal axis (ω) is always logarithmic
- Magnitude is in dB = $20 \log (|H|)$
- Phase is in normal linear scale
- Slope is +/- 20 db/decade per pole or zero, corner at ω_c (magnitude)

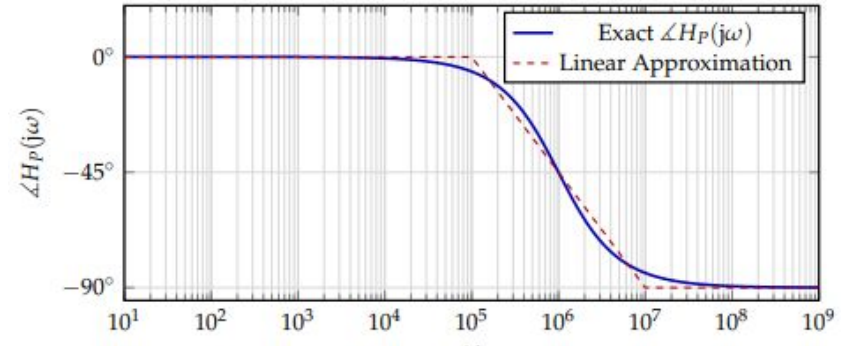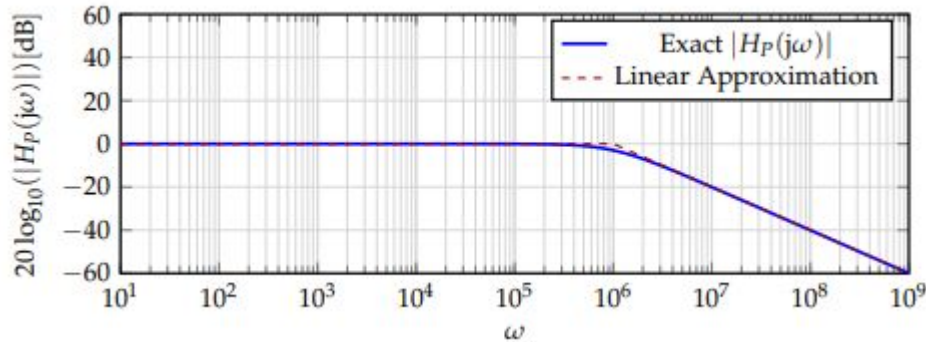



Bode Plots - Key Points

- Piecewise linear approximations of frequency response
- Two graphs (magnitude and phase)
- Horizontal axis (ω) is always logarithmic
- Magnitude is in dB = $20 \log (|H|)$
- Phase is in normal linear scale
- Slope is +/- 20 db/decade per pole or zero, corner at ω_c (magnitude)
- Slope is +/- 45°/decade per pole or zero, corners at $\omega_c/10, 10\omega_c$ (phase)

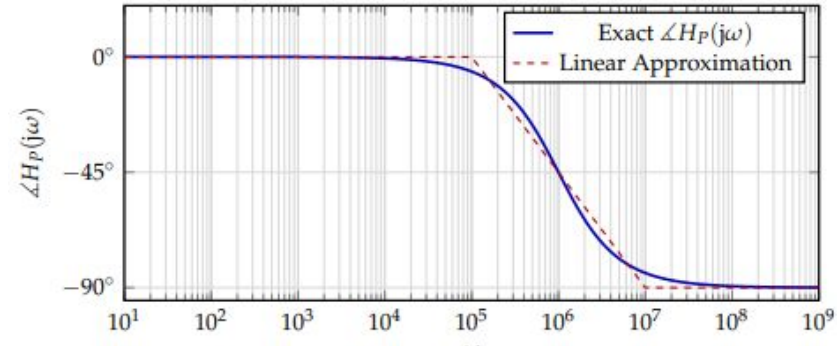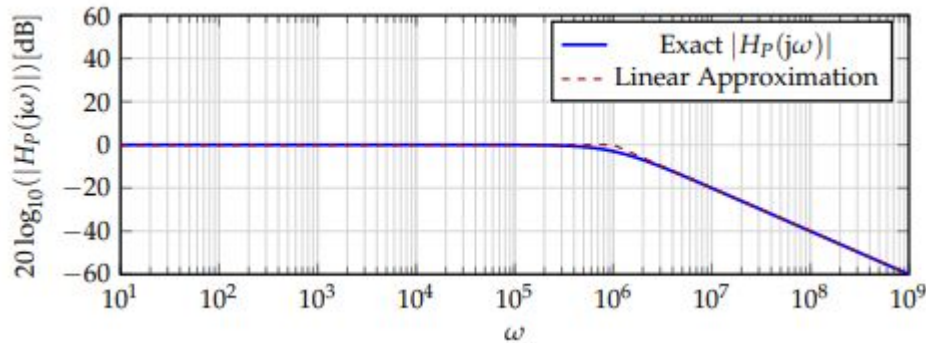

Bode Plots - Key Points

- Piecewise linear approximations of frequency response
- Two graphs (magnitude and phase)
- Horizontal axis (ω) is always logarithmic
- Magnitude is in dB = $20 \log (|H|)$
- Phase is in normal linear scale
- Slope is +/- 20 db/decade per pole or zero, corner at ω_c (magnitude)
- Slope is +/- 45°/decade per pole or zero, corners at $\omega_c/10$, $10\omega_c$ (phase)
- Cascaded system => components add rather than multiply

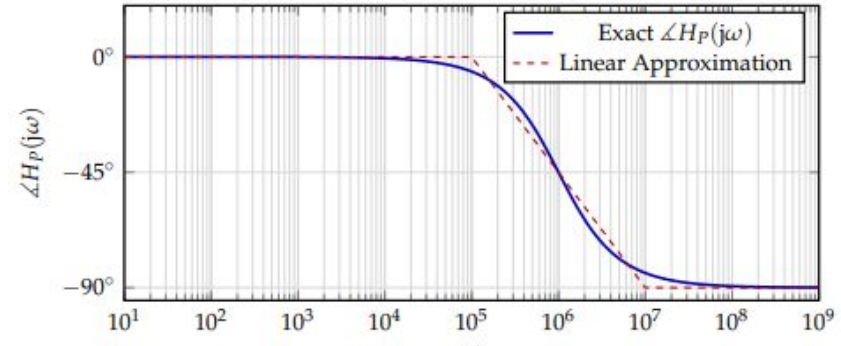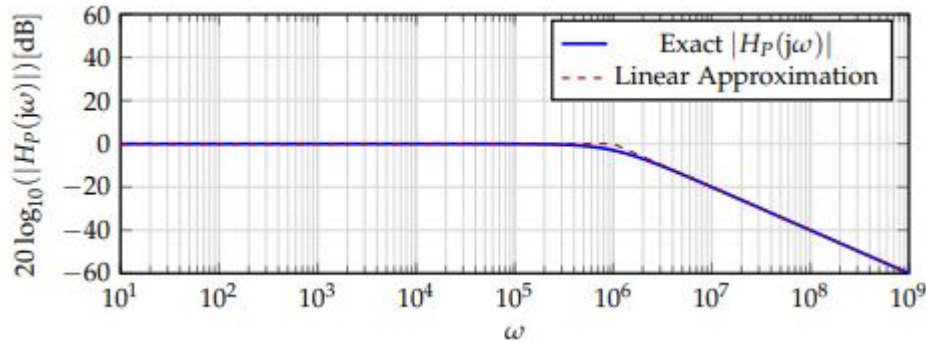

Generic Form for Frequency Response

$$H(j\omega) = K \cdot \frac{N(j\omega)}{D(j\omega)} = K \frac{(j\omega)^{N_{z0}} \left(1 \pm j \frac{\omega}{\omega_{z1}}\right) \left(1 \pm j \frac{\omega}{\omega_{z2}}\right) \cdots \left(1 \pm j \frac{\omega}{\omega_{zn}}\right)}{(j\omega)^{N_{p0}} \left(1 \pm j \frac{\omega}{\omega_{p1}}\right) \left(1 \pm j \frac{\omega}{\omega_{p2}}\right) \cdots \left(1 \pm j \frac{\omega}{\omega_{pm}}\right)}$$

Generic Form for Frequency Response

$$H(j\omega) = K \cdot \frac{N(j\omega)}{D(j\omega)} = K \frac{(j\omega)^{N_{z0}} \left(1 \pm j \frac{\omega}{\omega_{z1}}\right) \left(1 \pm j \frac{\omega}{\omega_{z2}}\right) \cdots \left(1 \pm j \frac{\omega}{\omega_{zn}}\right)}{(j\omega)^{N_{p0}} \left(1 \pm j \frac{\omega}{\omega_{p1}}\right) \left(1 \pm j \frac{\omega}{\omega_{p2}}\right) \cdots \left(1 \pm j \frac{\omega}{\omega_{pm}}\right)}$$

What happens when ω is small?

Generic Form for Frequency Response

$$H(j\omega) = K \cdot \frac{N(j\omega)}{D(j\omega)} = K \frac{(j\omega)^{N_{z0}} \left(1 \pm j \frac{\omega}{\omega_{z1}}\right) \left(1 \pm j \frac{\omega}{\omega_{z2}}\right) \cdots \left(1 \pm j \frac{\omega}{\omega_{zn}}\right)}{(j\omega)^{N_{p0}} \left(1 \pm j \frac{\omega}{\omega_{p1}}\right) \left(1 \pm j \frac{\omega}{\omega_{p2}}\right) \cdots \left(1 \pm j \frac{\omega}{\omega_{pm}}\right)}$$

What happens when ω is small?

What happens when ω is large?

Generic Form for Frequency Response

$$H(j\omega) = K \cdot \frac{N(j\omega)}{D(j\omega)} = K \frac{(j\omega)^{N_{z0}} \left(1 \pm j \frac{\omega}{\omega_{z1}}\right) \left(1 \pm j \frac{\omega}{\omega_{z2}}\right) \cdots \left(1 \pm j \frac{\omega}{\omega_{zn}}\right)}{(j\omega)^{N_{p0}} \left(1 \pm j \frac{\omega}{\omega_{p1}}\right) \left(1 \pm j \frac{\omega}{\omega_{p2}}\right) \cdots \left(1 \pm j \frac{\omega}{\omega_{pm}}\right)}$$

What happens when ω is small?

What happens when ω is large?

Can zeros and poles at the origin coexist?

Generic Form for Frequency Response

$$H(j\omega) = K \cdot \frac{N(j\omega)}{D(j\omega)} = K \frac{(j\omega)^{N_{z0}} \left(1 \pm j \frac{\omega}{\omega_{z1}}\right) \left(1 \pm j \frac{\omega}{\omega_{z2}}\right) \cdots \left(1 \pm j \frac{\omega}{\omega_{zn}}\right)}{(j\omega)^{N_{p0}} \left(1 \pm j \frac{\omega}{\omega_{p1}}\right) \left(1 \pm j \frac{\omega}{\omega_{p2}}\right) \cdots \left(1 \pm j \frac{\omega}{\omega_{pm}}\right)}$$

What happens when ω is small?

What happens when ω is large?

Can zeros and poles at the origin coexist?

Why are there no cutoff frequencies for the zeros/poles at the origin?

Generic Form for Frequency Response

$$H(j\omega) = K \cdot \frac{N(j\omega)}{D(j\omega)} = K \frac{(j\omega)^{N_{z0}} \left(1 \pm j \frac{\omega}{\omega_{z1}}\right) \left(1 \pm j \frac{\omega}{\omega_{z2}}\right) \cdots \left(1 \pm j \frac{\omega}{\omega_{zn}}\right)}{(j\omega)^{N_{p0}} \left(1 \pm j \frac{\omega}{\omega_{p1}}\right) \left(1 \pm j \frac{\omega}{\omega_{p2}}\right) \cdots \left(1 \pm j \frac{\omega}{\omega_{pm}}\right)}$$

What happens when ω is small?

What happens when ω is large?

Can zeros and poles at the origin coexist?

Why are there no cutoff frequencies for the zeros/poles at the origin?

What happens when K is negative?

Generic Form for Frequency Response

$$H(j\omega) = K \cdot \frac{N(j\omega)}{D(j\omega)} = K \frac{(j\omega)^{N_{z0}} \left(1 \pm j \frac{\omega}{\omega_{z1}}\right) \left(1 \pm j \frac{\omega}{\omega_{z2}}\right) \cdots \left(1 \pm j \frac{\omega}{\omega_{zn}}\right)}{(j\omega)^{N_{p0}} \left(1 \pm j \frac{\omega}{\omega_{p1}}\right) \left(1 \pm j \frac{\omega}{\omega_{p2}}\right) \cdots \left(1 \pm j \frac{\omega}{\omega_{pm}}\right)}$$

What happens when ω is small?

What happens when ω is large?

Can zeros and poles at the origin coexist?

Why are there no cutoff frequencies for the zeros/poles at the origin?

What happens when K is negative?

What if I am interested in finding $H(s)$? (Just replace $j\omega$ with s .)